AUGUST 1958

621.384

TWO SHILLINGS

Wireless World

ELECTRONICS

Radio · Television

THE JOHN CRERAR LIBRARY
AUG 4 - 1958

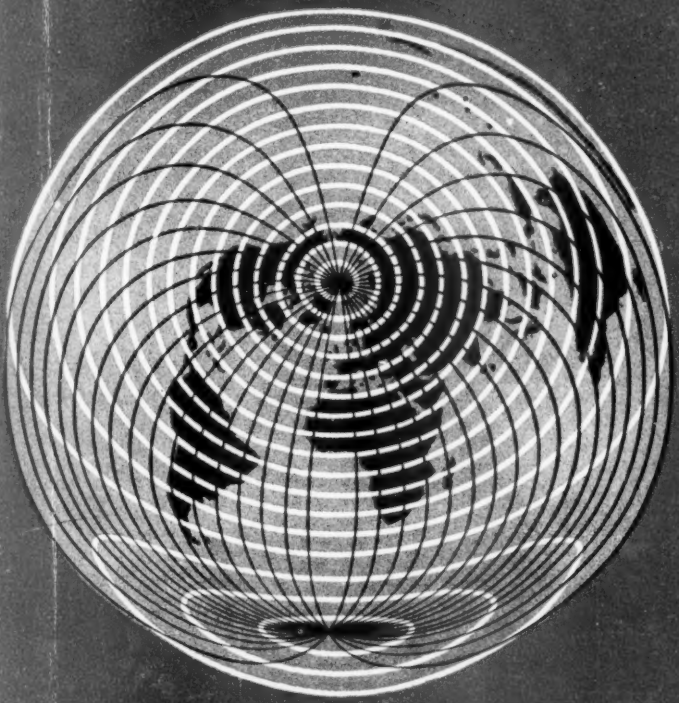

FORTY-EIGHTH YEAR OF PUBLICATION

XUM

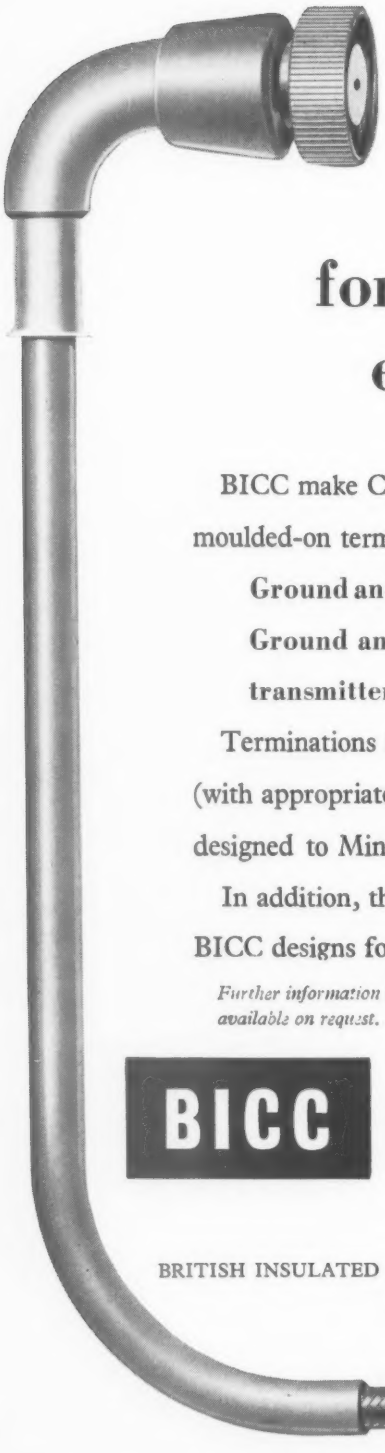

for *interconnecting* electronic equipment

BICC make Coaxial Radio Frequency Connectors with moulded-on terminations for use with—

Ground and airborne radar equipment

Ground and airborne radio transmitters and receivers

Terminations include a standard range (with appropriate panel mounting units) designed to Ministry of Supply requirements.

In addition, there are a number of BICC designs for other applications.

Further information is freely available on request.

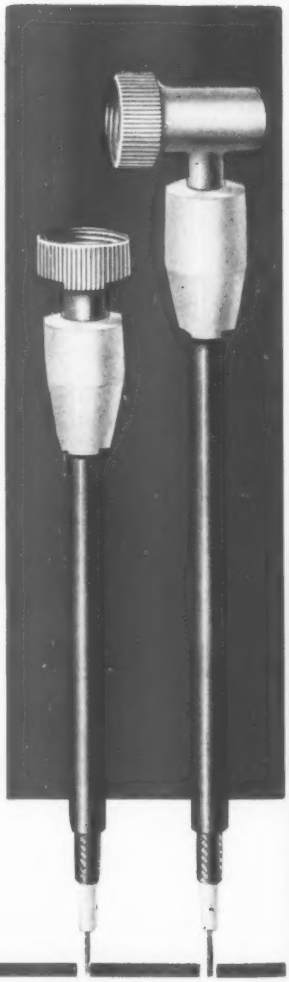

BICC *coaxial* **R. F. CONNECTORS**

BRITISH INSULATED CALLENDER'S CABLES LIMITED,
21 Bloomsbury Street, London, W.C.1

Pocket size... pocket wise!

This sturdy multi-range test meter is remarkable for the wide range of test facilities which have been so neatly incorporated. Full advantage has been taken of printed resistor techniques to produce a compact instrument of low weight.

Printed resistance panel for universal meter shunt.

Composite printed resistors and auxiliary switch.

Meter movement is enclosed to give protection against the infiltration of dust.

Robust range switch similar to that used in the famous Avo-Meter. Eighteen fixed silver-plated contacts embedded in a ring of high-grade moulding material are swept by a double contact rotor arm.

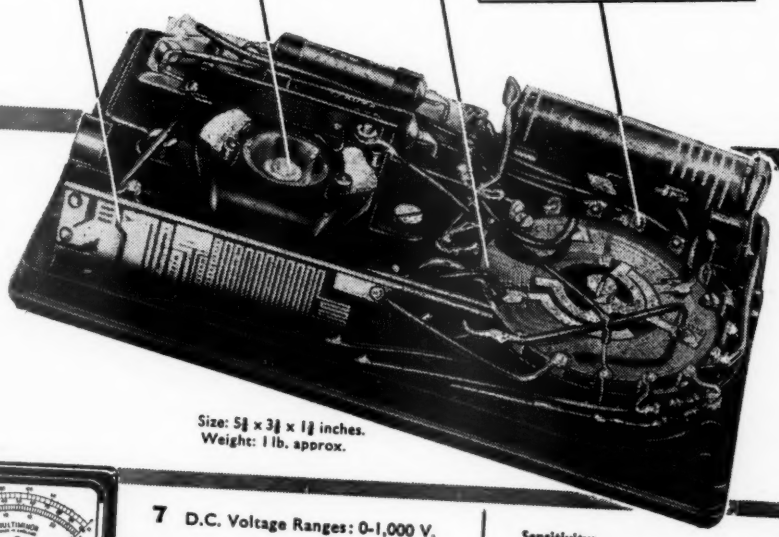

Size: 5¾ x 3¾ x 1¾ inches.
Weight: 1 lb. approx.

Meet us at the
RADIO SHOW
Stand No. **60**

AVO
Regd. Trade Mark.

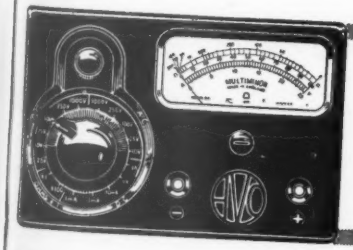

7 D.C. Voltage Ranges: 0-1,000 V.
5 A.C. Voltage Ranges: 0-1,000 V.
5 D.C. Current Ranges: 0-1A.
2 Resistance Ranges: 0-20,000Ω. 0-2MΩ.

Sensitivity:
10,000Ω/V on D.C. voltage ranges.
1,000Ω/V on A.C. voltage ranges.

Accuracy:
3% of full scale value on D.C.
4% of full scale value on A.C.

For a small additional charge, instruments can be supplied to a higher degree of accuracy.

THE **MULTIMINOR**

19 Ranges · Single Knob Control · List Price: £9:10s.

Complete with test leads and clips. Leather case if required 32/6.

• Write for fully descriptive leaflet.

AVO Ltd. AVOCET HOUSE · 92-96 VAUXHALL BRIDGE ROAD · LONDON · S.W.1.
VICtoria 3404 (9 lines)

A

IF YOU ARE USING TRANSISTORS YOU NEED

SOLARTRON

TRANSISTOR POWER SUPPLIES

The new series of Solartron Transistor Power Supplies covers all voltage and current ranges necessary for transistor circuit development work. Types AS 757 and 758 are for bench mounting and AS 759 is the first in a new family of compact sub-units.

Bench mounting units have 3-dial decade switching, with its inherent simple resetting facilities; also automatic overload protection and load current metering. Continuous operation at temperatures up to 35°C (95°F) is assured even under maximum load conditions and with supply 7% above normal.

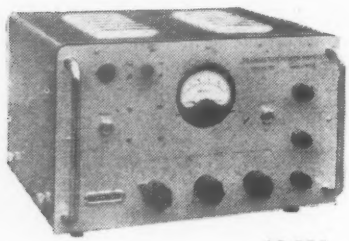

AS.757

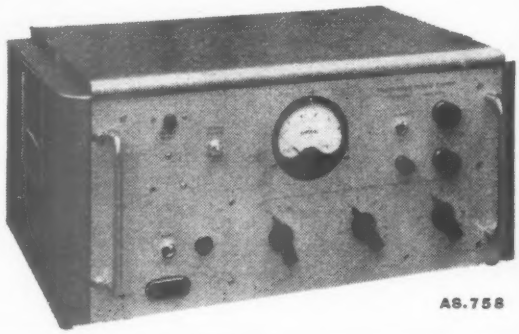

AS.758

Brief Specifications:

AS.757: 1A @ 0-50V, in 0.1 volt steps; Weight 25 lb; Price £95

AS.758: 10A @ 0-30V, in 0.1 volt steps; Weight 55 lb; Price £195

AS.759: 1A @ 1.5V-13.5V, continuously variable; Weight 7½ lb. Price £55

Output resistance: 0.01Ω
Output Z to 100 Kc/s: 0.2Ω
Ripple and noise: less than 1 mV peak to peak
Stability factor: 200 : 1 (AS.758 150 : 1)
Mains input: 90/130—200/240V, 40/60 c/s Permissible deviation ± 7%

THE SOLARTRON ELECTRONIC GROUP LTD · THAMES DITTON · SURREY TELEPHONE: EMBERBROOK 5522 · CABLES: SOLARTRON, THAMES DITTON

transistors

a series of authoritative films by Mullard

Mullard has produced for designers of equipment, and engineers engaged in its maintenance, a unique series of instructional and informative films on the transistor.

Each or all of these films are available on free loan. Just send your request to the address below, stating the films you require, alternative preferred dates, and some indication of the type of audience to which they will be shown.

No. 1 The Principles of the Transistor

Intended mainly as an aid to teaching, the film commences with a review of the early use of crystals and describes how these were soon replaced by thermionic valves, which themselves were subsequently found to have disadvantages in certain applications.

The middle and largest section of the film describes the working principles of the germanium diode and the transistor by use of both diagram and experiment. The film ends with details of the applications and advantages of these devices.

Black and white
16mm. Sound.
20 minutes duration

No. 2 The Transistor— Its Principles and Equivalent Circuit

Intended for those with a good background knowledge of thermionic valve techniques, this film provides a detailed explanation of the complex physics involved in the workings of the junction transistor. The film goes on to describe the derivation of the equivalent circuit and its simplification. The subject is clarified by colour, animation and commentary.

Colour
16mm. Sound.
20 minutes duration

No. 3 The Junction Transistor in Radio Receivers Part I Design of an I.F. Amplifier Part II The Complete Receiver

This two-part film follows on from the simplified circuit which ends "The Transistor—its Principles and Equivalent Circuit" and deals, in like manner, with the special circuitry required in a transistor I.F. amplifier and complete receiver.

Black and white
16mm. Sound.
15 minutes and
10 minutes duration

No. 4 The Manufacture of Junction Transistors

In this film the preparation of the germanium crystal from the raw material is shown in some detail. Following sequences show the cutting of the "p" type wafers, the alloying of the indium pellets into the wafer to form the "p" type collector and emitter, the assembling of a junction transistor and the testing of the finished product. Many close-ups of the ingenious machinery and intricate processes involved in the manufacture of transistors are shown.

Black and white
16mm. Sound.
21 minutes duration

Mullard **MULLARD LTD · FILM SERVICE · MULLARD HOUSE · TORRINGTON PLACE · LONDON W.C.1**

MIS 1

Loud-speaker manufacturers to the Radio Industry since 1930.

REPRODUCERS AND AMPLIFIERS LTD.

WOLVERHAMPTON · ENGLAND

TELEPHONE: 22241/2/3/4 CABLES: AUDIO

WIDE RANGE CAPACITANCE BRIDGE

Designed for the accurate measurement of capacitance and resistance in the range 0·002pF to 100μF and 1Ω to 10,000MΩ respectively.

All measurements are made in the form of a three terminal network and components can be measured in situ. *Accuracy within ± 1% Frequency 1592 c/s (ω=10,000).*

Full technical information on this and other 'Cintel' Bridges is available on request.

CINEMA TELEVISION LTD

A COMPANY WITHIN THE RANK ORGANISATION LIMITED

WORSLEY BRIDGE ROAD · LONDON · S.E.26
HITHER GREEN 4600

SALES AND SERVICING AGENTS:
Hewnt & Co. Ltd., 59 Moore St., Birmingham, 4
Atkins, Robertson & Whiteford Ltd., Industrial Estate, Thornliebank, Glasgow
McKellen Automation Ltd., 122 Seymour Grove, Old Trafford, Manchester 16

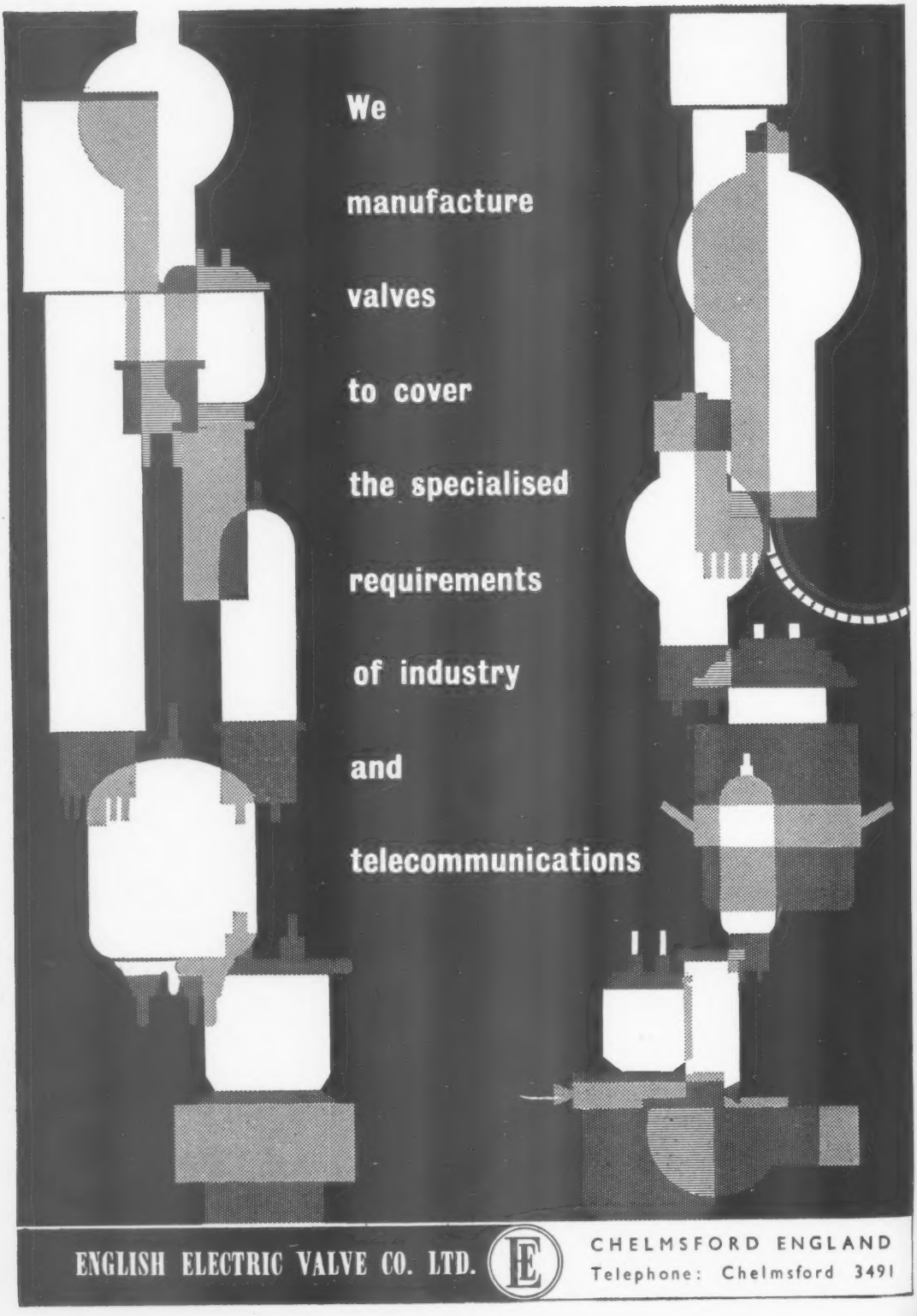
We
manufacture
valves
to cover
the specialised
requirements
of industry
and
telecommunications
ENGLISH ELECTRIC VALVE CO. LTD.
CHELMSFORD ENGLAND
Telephone: Chelmsford 3491

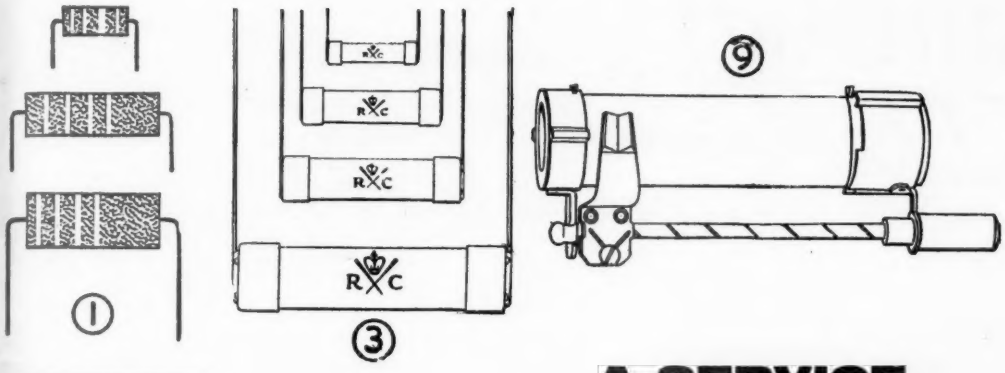

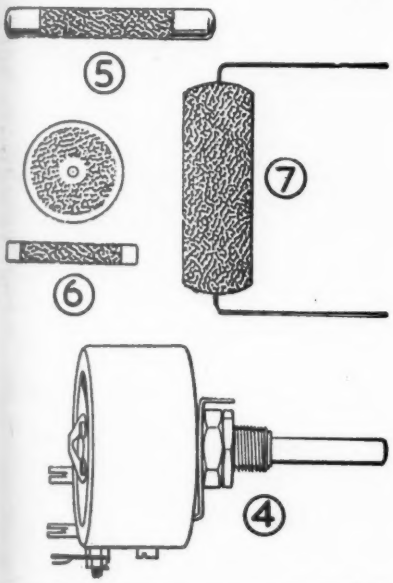

A SERVICE FOR DESIGNERS

The possibility of a component change — due to shortage of supplies, increased costs or failure to meet specific conditions — is a problem facing every designer of electronic equipment. However, one basic component can be 'tailor-made' from the start, for LAB will supply the precise type of Resistor required, ex stock *and* at the right price. Write for full technical data, prototype samples and price schedules to:—

THE RADIO RESISTOR CO. LTD.,
50 ABBEY GARDENS, LONDON, N.W.8.
Telephone: Maida Vale 0888

CARBON	WATTS	OHMIC RANGE	TOLERANCES ±
1. Solid	¼ 1 & 2	10—10M	5% & 10%
2. Cracked	1/30—20	1—500M	5% & 10%
3. * High Stability	1/10—3	1—50M	0.5% 1% 2% 5%
4. Variable	¼	5K—2M	—
5. V. High Resistance	¼—3	50M—10^{13}	5% & 10%
6. V.H.F. (Rods & Discs)	1/10—1	10—1K	1% & 2%
WIREWOUND			
4. Rheostats	4—500	10—80K	—
9. Sliders	3—15	10—16K	—
8. Vitreous	3—500	1—150K	1% 2% 5%
7. Cemented	1—15	1—25K	5% & 10%

* The ubiquitous blue (1%) grey (2%) "HISTABS"

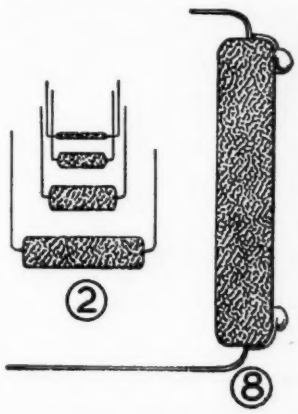

Do you KNOW

THAT Rheostats (4) can be made up in twos and threes on a common spindle.

THAT the whole of the vast range shown under (3) can be delivered ex-stock in all Preferred values.

25 YEARS LAB TESTED
JUBILEE YEAR OF RESISTOR SPECIALISATION

ANTIFERENCE

NEW LOFT AERIALS

for Television and VHF/FM

WILL INCREASE YOUR SALES

HILO COMPOSITE MODEL *FOR*

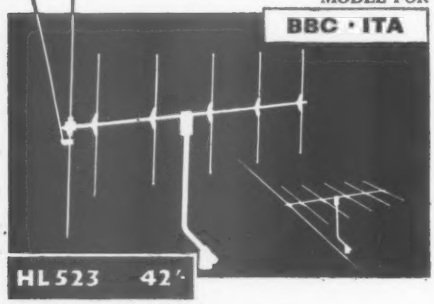

VERTICAL CHANNELS
"Hilo" Band 1 "V" electronically coupled to 5 Band III Elements complete with mounting arm and bracket.
List Price 42/-
(State Band III Channels when ordering).
FOR NEWCASTLE-ON-TYNE AREA
(HORIZONTAL CHANNELS) CAT. NO. H513.
List Price 42/-.

BAND III MODEL *FOR*

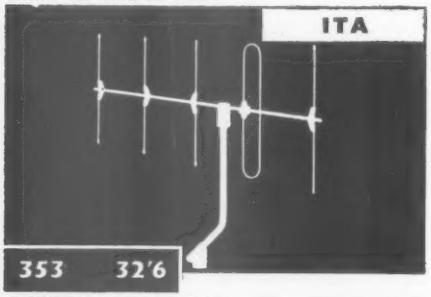

VERTICAL CHANNELS OR HORIZONTAL CHANNELS
5 element folded dipole array complete with mounting arm and bracket. List Price 32/6
(State channel required when ordering).

A completely new range of robust, light-weight loft aerials with equivalent performance to similar outdoor types. Special design features provide exceptional versatility for loft mounting and enable the arrays to be easily adjusted for vertical or horizontal channels and to be tilted, rolled and turned for anti-ghosting.

★CHANNEL OPTIMISED — Outstanding performance on all channels.

★FULLY PREASSEMBLED — Speedy installation with "Automatic" Elements.

★COMPLETE IN ONE ENVELOPE — with mounting arm and bracket.

★Highly COMPETITIVE PRICES.

All Antiference aerials incorporate features which are patented or are the subject of patents applied for.

★★★★★★★★★★★★★★★★
Visit us on
STAND 22
AT THE RADIO SHOW
★★★★★★★★★★★★★★★★

BAND II MODEL *FOR*

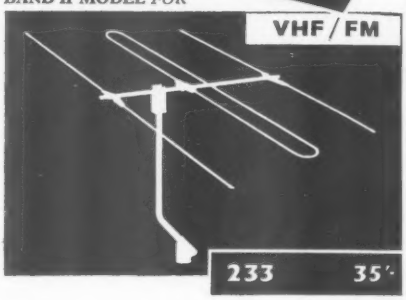

3 element folded dipole array complete with mounting arm and bracket. List Price 35/-

VHF/FM ADAPTORS
For vertically polarised aerials with ¼in. dia. rods. Addex FM/L. List Price 7/6 per kit.

GENERAL CONSTRUCTION

Each model has ¼in. diameter elements, ¼in. diameter boom and ¾in. diameter mounting arm, all of high grade aluminium alloy tubing. The mounting bracket is plated steel. The aerial elements spring easily into position in specially designed clamps (Regd. Design 887.944) with no wing nuts or bolts to tighten. Cable connections are of the "in-line" type, the cable saddle accommodating most sizes of coaxial or twin feeder.

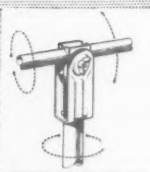

VERTICAL OR HORIZONTAL MOUNTING PLUS tilting, rolling and turning . . .

The new boom clamp fitted to all the new loft aerials provides full adjustment in every direction with the mounting arm and bracket in any position. Single wing nut locks array into position.

NO LOFT MOUNTING DIFFICULTIES

The specially formed arm and angled bracket overcome every mounting difficulty. The four positions illustrated give an indication of their versatility. Single wing nut locks arm into position.

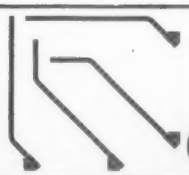

ANTIFERENCE FREE AERIAL INSURANCE
12 months **FULL COVER** *including*
LABOUR CHARGES
WHATEVER THE DAMAGE
WHATEVER THE CAUSE

ANTIFERENCE LIMITED

Aylesbury, Bucks.
Telephone: AYLESBURY 2511 (6 lines)

Mr. Monarch writes about

PROOF BY PERFORMANCE!

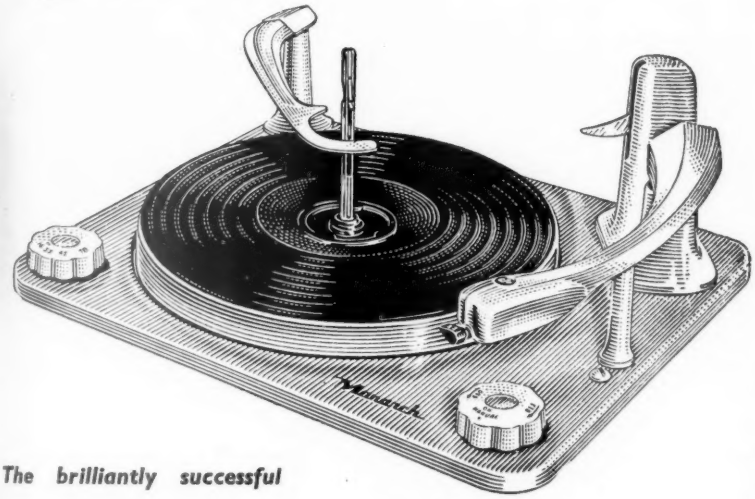

The brilliantly successful

Monarch UA8

World's Finest 4-Speed Autochanger!

Every time the Monarch plays it proves its brilliance. Even those who listen for faults are convinced by its performance. There's no player to touch the Monarch for tonal quality, mechanical precision or styling—*and* you can fit stereo cartridges for stereophonic equipment.

ful-fi

Every Monarch is fitted with Ful-Fi crystal cartridges and sapphire needles —they'll give new life to *any* changer. T.C.8M for high fidelity equipment. T.C.8H low gain amplifiers. Insist on genuine B.S.R. replacements. Look for the red and green display packs at your dealers.

BSR

Makes Music for Millions

BIRMINGHAM SOUND REPRODUCERS LIMITED

THAT ELUSIVE WORKS MANAGER . . .

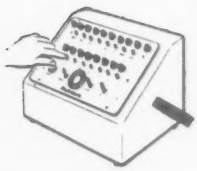

found in 10 seconds

NO LOUDSPEAKERS, BELLS or FLASHING LIGHTS
only the man who's wanted knows and replies.

Selective Induction is saving time, money and worry in Offices, Factories, Hospitals, Hotels, Departmental Stores etc., all over the Country. All key personnel carry small transistorised receivers bearing a number. When they are wanted their numbered key is pressed on a small transmitter. Immediately they must respond to the URGENT 'PEEP PEEP' in their pockets which summons them and them alone to ACTION! A verbal message can be transmitted if desired.

- Covers areas indoors or out, up to 10,000,000 sq. ft.
- Designed for the man who cannot afford to be tied to his office.
- Equally suitable for large or small concerns.
- Low purchase price—virtually no indoor wiring—low rental terms.

Write or 'phone for further particulars — WE CAN BE FOUND IN TEN SECONDS

personal call

(the 'Peep Peep' in the Pocket)

THE ONLY STAFF LOCATION SYSTEM WORTH INSTALLING

MULTITONE ELECTRIC COMPANY LIMITED
12/20 UNDERWOOD STREET LONDON N.1. TELEPHONE: CLERKENWELL 8022

Now A VALVE VOLTMETER FROM Advance

With these
OUTSTANDING FEATURES

EXTREME SENSITIVITY
accurate measurements are possible down to 100μV.

WIDE VOLTAGE RANGES
1mV. to 300 volts F.S.D.

WIDE FREQUENCY RANGE
15c/s to 4.5Mc/s accuracy ± 2dB

METER SCALE CALIBRATED IN VOLTS AND dB

CAN BE USED AS A NULL DETECTOR AND INDICATOR
from 10c/s to 10Mc/s

CAN BE USED AS AN AMPLIFIER FROM 10c/s to 10Mc/s

INCORPORATES ITS OWN H.T. STABILIZER

SMALL COMPACT SIZE & ROBUST CONSTRUCTION

at this price . . .

£50 nett in U.K.

(including very low capacity screened lead and probe)

with this backing . . .

Behind this, the most modern instrument in its sphere, is that specialist instrumentation skill and experience which has earned for all "Advance" products a reputation second to none throughout the industry. From our up-to-the-minute factory at Hainault comes this latest addition to the world-famous "Advance" range of inxtruments.

Full Technical details in Leaflet W 50.

GD 64

THE Advac

Size 4¾" x 7½" x 6¾"
Weight 7lb.

Advance COMPONENTS LIMITED

ROEBUCK ROAD · HAINAULT · ILFORD · ESSEX · TELEPHONE: HAINAULT 4444

G.E.C.

Series Stabilisers

The M-O Valve Company Limited—the specialists in the development and manufacture of valves and cathode ray tubes for industry—supplies a wide range of valves, suitable for use as series stabilisers.

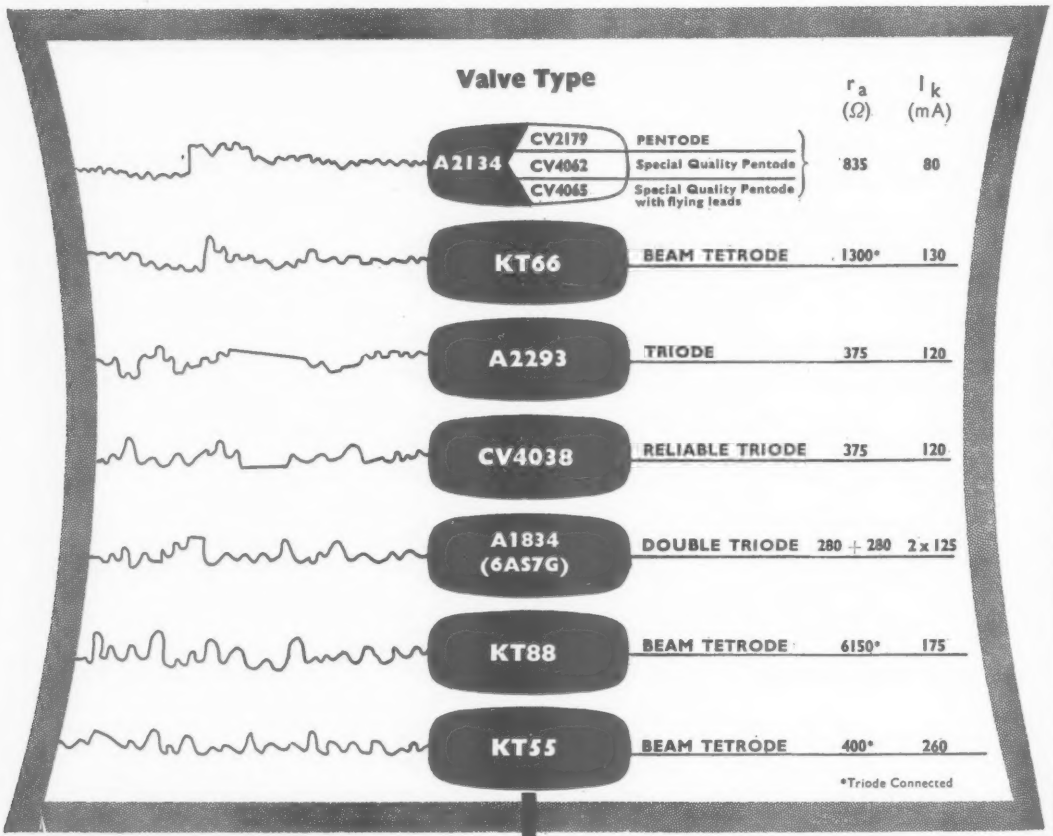

Details of the wide range of the Company's products, including valves and CRTS, are given in a new catalogue which will gladly be sent on request.

GENERAL SHEET 4
An informative data sheet which describes the design and operation of series valve stabiliser circuits.
Write now for your copy.

M-O VALVE COMPANY LIMITED, Brook Green, Hammersmith, London, W.6.
MAKERS OF G.E.C. HIGH GRADE RADIO VALVES AND CATHODE RAY TUBES
a subsidiary of The General Electric Company Limited.

MARKINGS IN WHITE TO CUSTOMERS' REQUIREMENTS

McMURDO
Multi-Way Voltage Selectors

14 WAY
Type B279001
BLACK P.F. MOULDING

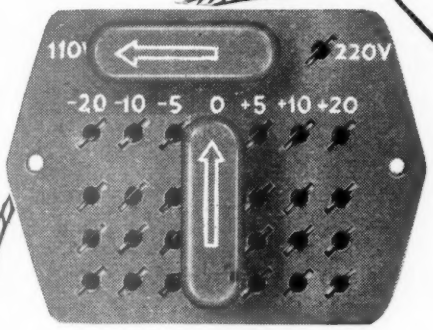

4 Pin Shorting Plugs

6 WAY
Type XVS/6
NYLON LOADED P.F. MOULDING

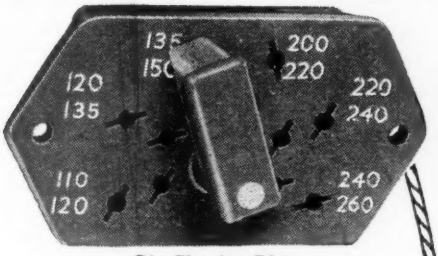

3 Pin Shorting Plug

4 WAY
Type BVS/4
BLACK P.F. MOULDING

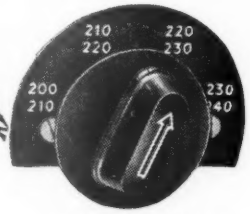

3 Pin Shorting Plug

6 WAY
MINIATURE
Type BMVS/6
BLACK P.F. MOULDING

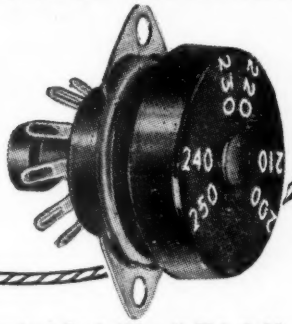

Standard B9A (Noval) Valveholder with 2 Pin Captive Shorting Plug

Send for full details to :—

THE McMURDO INSTRUMENT CO. LTD., ASHTEAD, SURREY. Tel: ASHTEAD 3401

MVS15

LINEAR

For *HIGH SENSITIVITY!*
HIGHEST FIDELITY!
MAXIMUM RELIABILITY!
REASONABLE COST!

THE 'CONCHORD'

A HIGH FIDELITY 30 WATT AMPLIFIER INCORPORATING PRE-AMPLIFIER AND TONE CONTROLS

EMPLOYING THE LATEST MULLARD EL34 OUTPUT VALVES IN ULTRA LINEAR OPERATION AND HIGH GRADE SECTIONALIZED OUTPUT TRANSFORMER

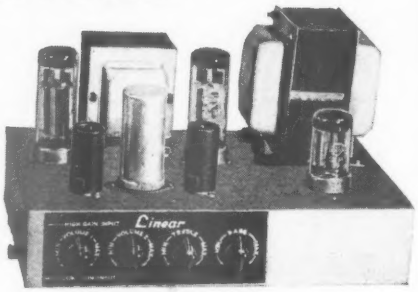

Size approx. 13 x 8½ x 7in. Stoved gold hammered finish. Weight 14lb. For operation on 200-250 v. 50 c.p.s. A.C. mains. Or other voltages to order. A chrome-handled cover is available at 25/-.

15 Retail Price GNS.

The Following Outstanding Test Figures Include Pre-amplifier and Tone Control Stages

FREQUENCY RESPONSE
(Exc. Rumble Filter.) ± 1 d.b. 20-20,000 c.p.s.

RUMBLE FILTER.
12 d.b. per octave below 50 c.p.s.

BASS CONTROL.
Continuously variable + 12 d.b. to — 12 d.b. at 50 c.p.s.

TREBLE CONTROL.
Continuously variable + 12 d.b. to —6 d.b. at 12,000 c.p.s.

HUM LEVEL.
Referred to full output —73 d.b.

MAXIMUM POWER OUTPUT.
In excess of 33 watts.

MAINS POWER CONSUMPTION.
110 watts.

STABILITY.
Entirely stable with capacity of .08 mfd. in parallel with loudspeaker load.

EFFECTIVE OUTPUT IMPEDANCE.
0.9 ohms across 15 ohm terminals.

INPUT IMPEDANCE.
Both inputs 500k plus 10 pfd.

NEGATIVE FEEDBACK.
Total 28 d.b.

SENSITIVITY.
Input (1) 20 millivolts for rated output.
Input (2) 200 millivolts for rated output.

HARMONIC DISTORTION.
0.05% at 10 watts. 0.1% at 20 watts.

OUTPUT SOCKETS.
Provide matchings for 3 ohm and 15 ohm loudspeakers.

EXTERNAL POWER SUPPLY.
300 v. 30 m/a. 6.3 v. 1.5 a. for radio tuner.

VALVES.
B.V.A. EF86, EF86, ECC83, EL34, EL34, GZ34.
Due to use of Mullard EF86 valves microphony is virtually nil.
As in our extremely successful 'Diatonic' two individually controlled inputs provide mixing facilities for microphone and gram, etc., etc.

The 'DIATONIC' HIGH FIDELITY 10-14 WATT ULTRA LINEAR AMPLIFIER

WITH INTEGRAL PRE-AMP AND TONE CONTROLS

H.T. and L.T. Supply Point is included for a radio tuner

ALL TEST FIGURES INCLUDE PRE-AMP FREQUENCY RESPONSE.
±2 d.b. 30-20,000 c.p.s.

MAXIMUM POWER OUTPUT. In excess of 14 watts.

RATED OUTPUT 10 WATTS.

SENSITIVITY.
Vol. (1) 22 millivolts for rated output. Vol. (2) 220 millivolts for rated output.

TREBLE LIFT CONTROL. Continuously variable +6 d.b. to —13 d.b. at 12,000 c.p.s.

BASS CONTROL.
Continuously variable +13 d.b. to —18 d.b. at 50 c.p.s.

HARMONIC DISTORTION, 0.19% measured at 6 watts.

HUM LEVEL. Referred to maximum output—60 d.b.

NEGATIVE FEEDBACK.
Total 32 d.b.

Size only 9-7-6½in. Weight 12½lb. Power consumption 120 watts. Outputs for 3 and 15 ohm loudspeaker.

12 Retail Price GNS.

For A.C. mains 200-250 v. 50 c.p.s. Or other voltages to order. Chassis finish stoved hammered gold, or grey blue. Attractive cover with chromium carrying handles now available at **17/6.**

Full advantage has been taken of the latest component miniaturization developments to reduce unit size to a minimum. Two high impedance input sockets are provided for microphone and gram., etc. Each input has its associated vol. control. B.V.A. valves are employed, ECC83, ECC83, EL84, EL84, EZ81.

ALSO AVAILABLE:

The L45. A compact High Quality 4-5 watt amplifier.

Size approx. 6-5-5½in. high. Sensitivity is 28 millivolts so that the input socket can be used for either microphone or gram., tape, radio tuner, etc. B.V.A. valves used are ECC83, EL84, EZ90. Controls are: Vol., Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker.
Retail price **£5/19/6.**

THE LT45 TAPE DECK AMPLIFIER. A complete unit (power pack and oscillator incorporated) ready for connection to A.C. mains. 3 ohm loudspeaker and practically any make of deck. Negative feedback equalization adjustment by multi-position switch for 3¾, 7½ and 15in. per sec.
Retail price **12 gns.**

THE LG3 GRAM AMPLIFIER. Overall size 6½ x 4½ x 2½in. Controls: Vol. and Tone (with mains switch). Output for 2-3 ohm loudspeaker. All above for 200-250 v. 50 c.p.s. A.C. mains.
Retail price **55/9.**

Send S.A.E. for Leaflets. **TRADE AND EXPORT ENQUIRIES TO—**

LINEAR PRODUCTS LTD. **ELECTRON WORKS,** Tel.: Leeds 630-126 (3 lines), Armley, Leeds

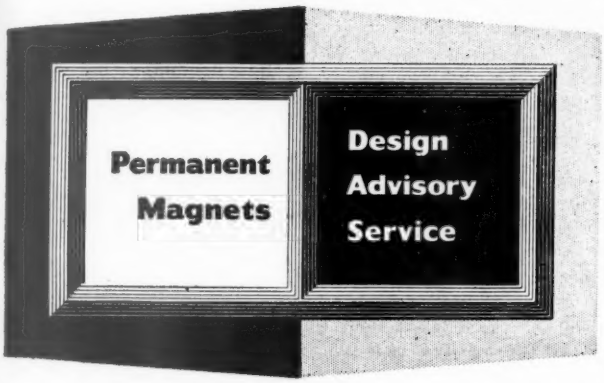

No 5

Symbols and Definitions

Advertisements in this series deal with general design considerations. If you require more specific information on the use of permanent magnets, please send your enquiry to the address below, mentioning the Design Advisory Service.

A_g Cross sectional area of air gap.

A_m Cross sectional area of magnet.

B Magnetic Flux Density; the number of lines of flux per unit area in a section normal to the direction of flux. The c.g.s. unit is the maxwell or line. The M.K.S. unit is the weber.

B_d Value of B on the major hysteresis loop, or demagnetisation curve, corresponding to a given value of −H (denoted H_d), usually at $(BH)_{max}$.

B_g The flux density in the air gap.

B_r Remanence or residual induction; the flux density which remains in the material (a closed or short-circuited specimen) after being magnetised to saturation.

B_{sat} Saturation flux density.

F or **M.M.F.** Magnetomotive force. That force which produces or tends to produce a magnetic flux.

The c.g.s. unit is the gilbert.

$$1 \text{ gilbert} = \frac{10}{4\pi} \text{ ampere turns.}$$

The M.K.S. unit is the ampere turn (the product of turns and amperes in a magnetising coil).

$$1 \text{ ampere turn} = \frac{4\pi}{10} \text{ gilberts.}$$

H Magnetising force.

The c.g.s. unit is the oersted.

$$\text{Magnetising force} = \frac{\text{M.M.F. (in gilberts)}}{\text{length (in cms)}}$$

The M.K.S. unit force is the ampere-turn per metre.

$$\text{Magnetising force} = \frac{\text{M.M.F. (ampere turns)}}{\text{length (in metres)}}$$

H_c Coercive force; the magnetising force applied to a fully magnetised magnet to reduce the residual induction (B_r) to zero.

H_d Value of −H on the major hysteresis loop or demagnetisation curve corresponding to a given value of B (denoted B_d) usually at $(BH)_{max}$.

H_{sat} The value of H corresponding to B_{sat}.

L_g Length of air gap.

L_m Effective magnetic length of magnet.

μ Permeability; the ratio of the magnetic flux density induced in a given medium to that which would be produced in vacuum by the same magnetising force.

Φ Total flux over a cross section, i.e. the integral of B over the cross-section.

CONVERSION TABLE c.g.s. TO M.K.S. UNITS

		c.g.s.		M.K.S.
Magnetomotive force	F	1 gilbert	=	Ampere-turns $\times \frac{4\pi}{10}$
Magnetising force	H	1 oersted	=	Ampere-turn/metre $\times \frac{10^3}{4\pi}$
Total Flux	Φ	1 maxwell or 1 line	=	Webers $\times 10^{-8}$
Flux Density	B	1 gauss	=	Webers/m^2 $\times 10^{-4}$

Reprints of advertisements in this series will be gladly sent on application to the address below.

Advertisements that have appeared to date are:—

Modern Theory of Permanent Magnets
Magnetic Circuits
Circuit Design Recommendations
The Choice of Magnet Materials

Mullard

'TICONAL' PERMANENT MAGNETS
'MAGNADUR' CERAMIC MAGNETS
'FERROXCUBE' MAGNETIC CORES

MULLARD LIMITED, COMPONENT DIVISION, MULLARD HOUSE, TORRINGTON PLACE, W.C.1. Tel: LANgham 6633
MC267A

NEW Industrial Cathode Ray Tubes

12" RADAR TUBE
Electrostatic Focus, High Brightness with helical acceleration to 25 kV screen potential.

5" OSCILLOSCOPE TUBE
Very high plate sensitivity—2·5 v/cm with 10kV screen potential.

8" RECTANGULAR DISPLAY TUBE
Electrostatic Focus Neck reduced to 23 mm dia. Less weight, more compact, easier scanning.

The Electronics Dept. of Ferranti Ltd., manufactures a wide range of cathode ray tubes and valves for many industrial applications.

FERRANTI

FERRANTI LTD · GEM MILL · CHADDERTON · OLDHAM LANCS
London Office: KERN HOUSE, 36 KINGSWAY, W.C.2

FERRANTI

FE.183

Way Ahead!

A few miles from the Equator at 16,000 ft. on the Lewis Glacier, meteorologists of the I.G.Y. Mount Kenya Expedition had direct communications with Nyeri (5,800 ft.) 30 miles away, with the B.C.C. Type 46 lightweight pack set (12 lbs.).

" We supplied the Expedition with three Type 46 sets, all of which functioned perfectly, for communication direct to our headquarters. Transmission often lasted 20 minutes or more, exchanging long messages—no difficulty at all, twice daily, and between themselves at various points on the mountain at frequent intervals."

" The batteries were never changed and no faults at all occurred."

Extract from report by Kenya Police Signals Branch at Nyeri.

W E

An Impressive performance for a small VHF Pack Set.

B.C.C. Type 46 lightweight pack set is well known throughout the world for its outstanding performance and rugged dependability under all conditions. Simple to operate, it requires little maintenance and can be used by personnel with no radio training.

BRITISH COMMUNICATIONS CORPORATION LIMITED

Wembley
Telephone : Wembley 1212

England
Cables : BeeCeeCee

5BUP1
5" Diameter Tube

High quality p.d.a. tube with flat screen and side plate connections. A wide range of operating voltages suit this tube for a variety of applications.

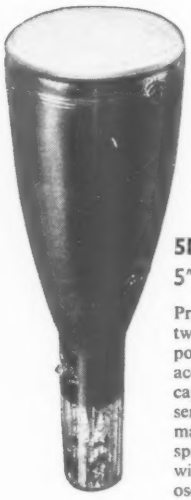

5BKP1
5" Diameter Tube

Precision tube with a two-stage, distributed post deflection accelerator. Low input capacitances and high sensitivity combine to make the 5BKP1 specially suited for wide-bandwidth oscillography.

5BVP1
5" Diameter Tube

Aluminized tube with the same features as the 5BUP1. Higher operating voltages suit this tube for recording faster phenomena.

ETEL range of instrument tubes

serves industry and research

ETEL CATHODE RAY TUBES

4EP1
4" Diameter Tube

High quality general purpose tube. High sensitivities may be obtained at accelerations of the order of 2kV. Alternatively, high writing speeds may be obtained at 10kV operation.

For Transistorized Instruments

Specially designed for transistorized instruments, this 2¾" diameter tube has a low consumption heater and a low focus voltage. The sensitivity is such that deflection voltages may be derived from transistor amplifiers.

Alternative screens are available for all tubes

3AFP1
2¾" Diameter Tube

Low cost general purpose tube. A drive of only 50 volts on the Y-plates will give full screen deflection. This sensitivity materially simplifies deflection amplifier design.

1CP1
1" Diameter Tube

Small, inexpensive monitor tube. The operating voltage is so low that in most equipment suitable connection to existing H.T. lines is all that is required.

ELECTRONIC TUBES LIMITED

Kingsmead Works, High Wycombe, Bucks • Tel: High Wycombe 2020

ETL6a

A NEW RANGE OF
"Miniature" Instruments

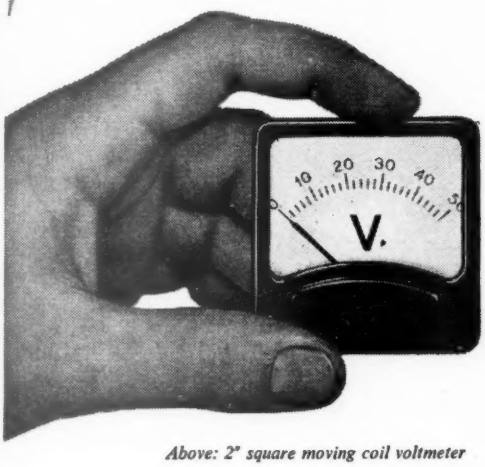

Above: 2" square moving coil voltmeter

★ **DESIGNED TO HARMONISE WITH ALL MODERN ELECTRONIC EQUIPMENT**

★ **FIXINGS CONFORM TO ACCEPTED PRACTICE**

★ **PRICES ARE HIGHLY COMPETITIVE**

For utmost reliability all 'ENGLISH ELECTRIC' miniature instruments have been designed with a higher-than-normal torque/weight ratio in combination with lower power consumption. All types have been successfully subjected to the following tests:
RESISTANCE TO IMPACT SHOCK OF 200g in any plane.
VIBRATION FATIGUE TEST—two million cycles at peak resonant frequency.
OSCILLATORY TEST—up to one million operations.

SPECIFICATIONS B.S. 89–1954 and other International Specifications.

TYPES
Moving coil for D.C. applications.
Rectifier moving coil for A.F. applications.
Thermo-couple operated moving coil for R.F. applications.

SIZES
Square: 2", 2½" and 3½" nominal scale length.
Round: 2½" and 3½" nominal scale length.
Rectangular: 5" x 6" or 3" x 4" nominal case size.

Design registrations pending.

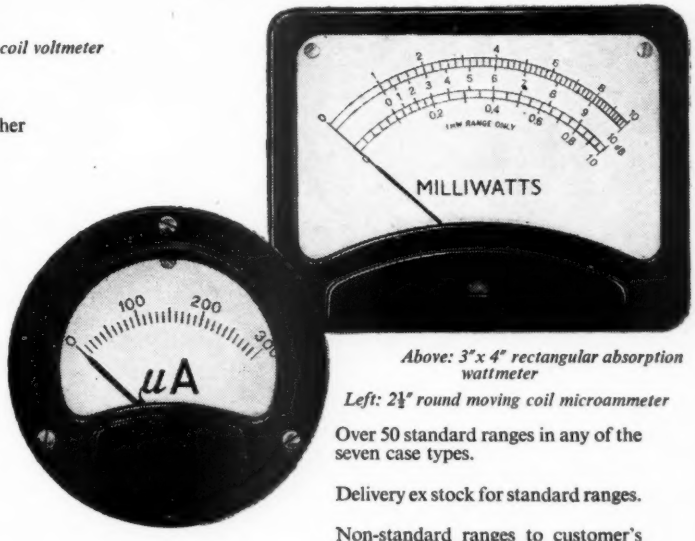

Above: 3"x 4" rectangular absorption wattmeter

Left: 2½" round moving coil microammeter

Over 50 standard ranges in any of the seven case types.

Delivery ex stock for standard ranges.

Non-standard ranges to customer's specification within 21 days.

Literature available on request to The ENGLISH ELECTRIC Co. Ltd., Instrument Department, Stafford.

'ENGLISH ELECTRIC'

THE ENGLISH ELECTRIC COMPANY LIMITED, MARCONI HOUSE, STRAND, LONDON, W.C.2
Meter, Relay and Instrument Division, Stafford
WORKS: STAFFORD · PRESTON · RUGBY · BRADFORD · LIVERPOOL · ACCRINGTON
RES.43C8

no rungs missing in the ladder of our range

of **QUARTZ CRYSTALS**

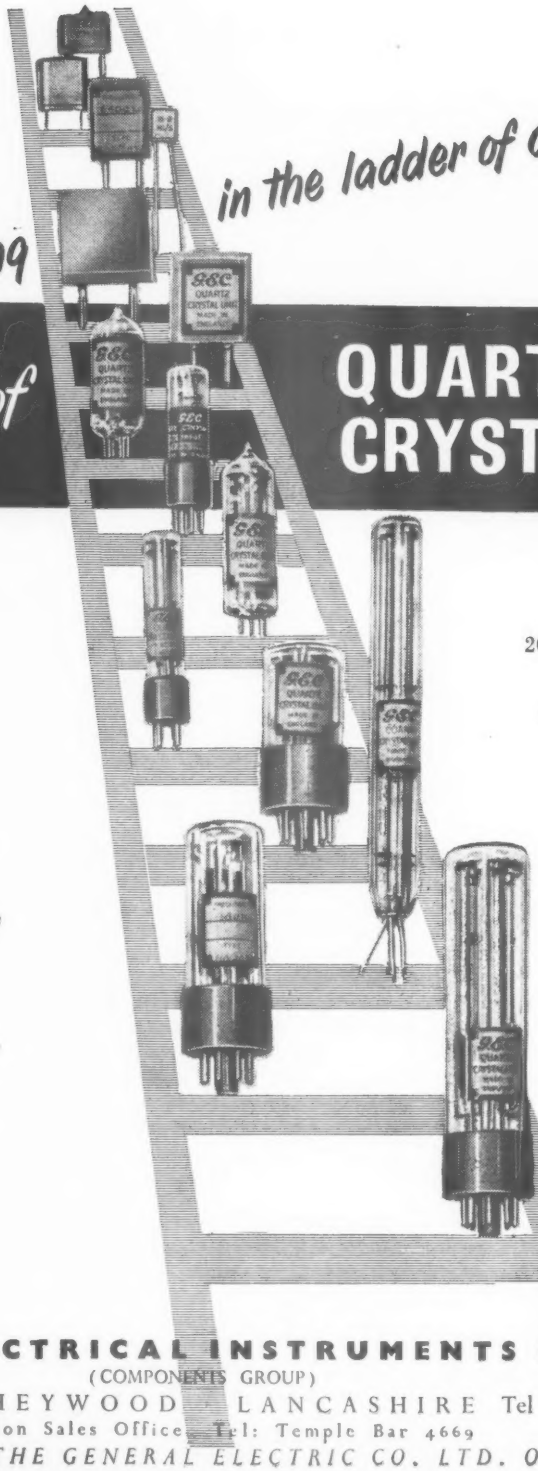

G.E.C.

From
200 cycles/sec.
to
90 Mc/sec.

For long term stability and unfailing activity, G.E.C. Quartz Crystal Units provide the basis for reliable communications systems.

A complete range of units to meet D.E.F. 5271 and R.C.L. 271 Inter Services styles can be supplied.

SALFORD ELECTRICAL INSTRUMENTS LIMITED
(COMPONENTS GROUP)
TIMES MILL · HEYWOOD · LANCASHIRE Tel: Heywood 6868
London Sales Office Tel: Temple Bar 4669
A SUBSIDIARY OF THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

Aero Research Ltd

ANNOUNCE

that from June 30th 1958 the Company will be known as

CIBA (A.R.L.) LTD

Makers of synthetic resins for industry

REDUX	RESOLITE
AERODUX	ARALDITE
AEROLITE	AEROWEB

(registered trade names)

CIBA (A.R.L.) LTD

Duxford, Cambridge

AP 4313

Designed made and rated ...

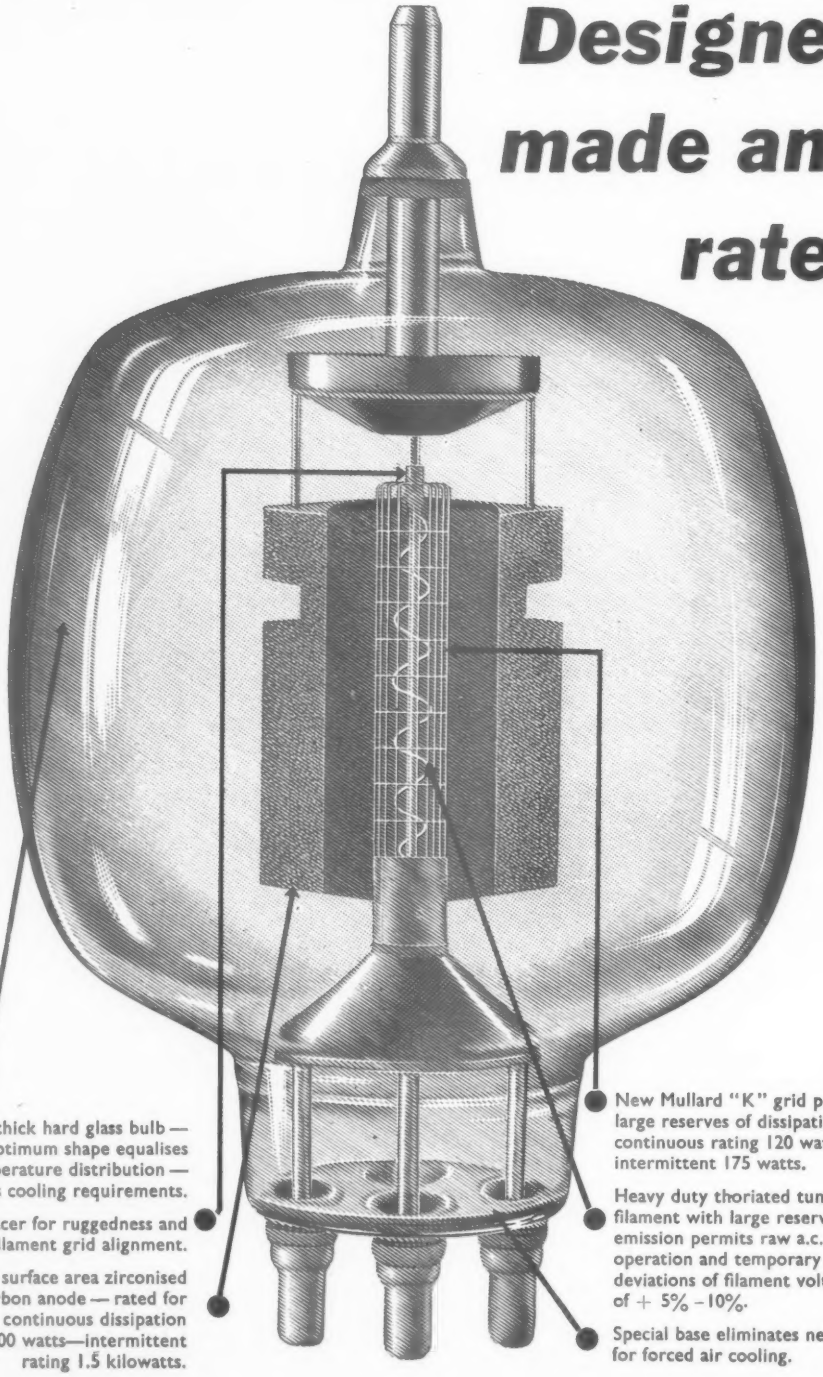

Extra thick hard glass bulb — optimum shape equalises temperature distribution — cuts cooling requirements.

Silica spacer for ruggedness and accurate filament grid alignment.

Large surface area zirconised carbon anode — rated for continuous dissipation of 800 watts—intermittent rating 1.5 kilowatts.

New Mullard "K" grid provides large reserves of dissipation— continuous rating 120 watts, intermittent 175 watts.

Heavy duty thoriated tungsten filament with large reserves of emission permits raw a.c. operation and temporary deviations of filament voltage of + 5% -10%.

Special base eliminates need for forced air cooling.

FROM THEIR VERY FIRST CONCEPTION these two new Mullard triodes, the TY6-800 and TY5-500, have been specifically designed for use in industrial R.F. heaters. They are rated with generous reserves of anode dissipation, grid dissipation and filament emission to accommodate the variations encountered in industrial R.F. heater operation. Their construction is fundamentally rugged and they are designed for easy and simple cooling. Write to the address below for full details of Mullard industrial valves for R.F. heating.

... for industrial R.F. heaters

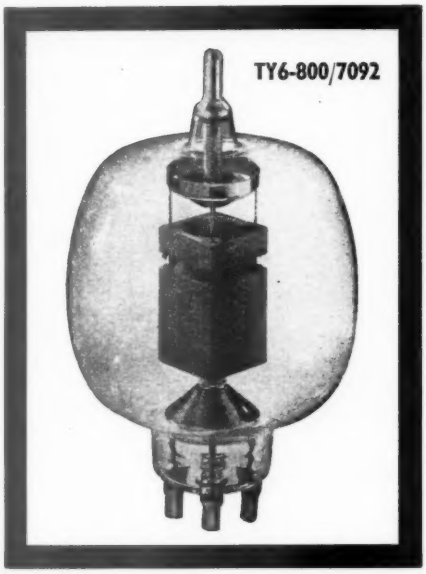

For 2kW equipment. Features of this new valve are described on the opposite page.

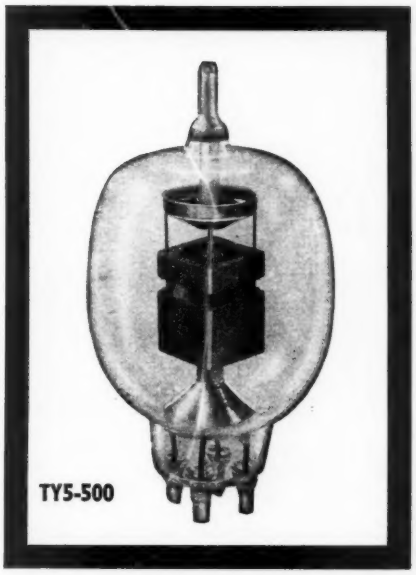

For 1kW equipment. Same new type of construction as the TY6-800. Supersedes communications types such as 833A.

Typical Industrial Oscillator Operation

Type No.	Vf(V)	If (A)	Va (kV)	Ia (mA)	P load (kW)	f (Mc/s)
TY6-800/ 7092	6.3 +5-10%	32	5.0	700	2.3	50
TY5-500	5.0 +5-10%	32.5	4.0	535	1.4	50

MVT349c

Mullard

GOVERNMENT AND INDUSTRIAL VALVE DIVISION

MULLARD LIMITED
MULLARD HOUSE
TORRINGTON PLACE
LONDON · W.C.1
TEL: LANGHAM 6633

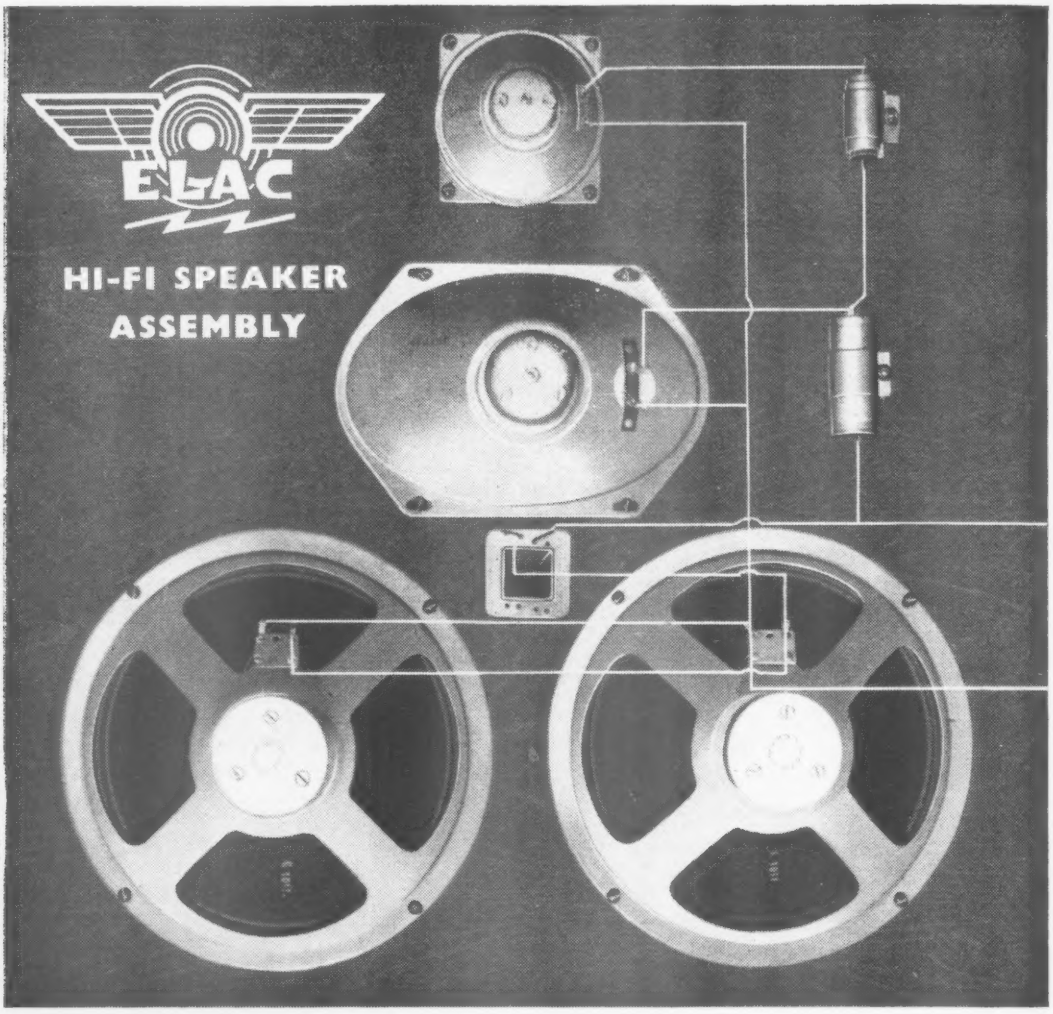

Now ELAC *bring* QUALITY HI-FI *within the reach of everyone*

This new Elac combination comprises four acoustically matched high fidelity loudspeakers.
An outstanding feature is its high sensitivity which is of considerable value when used with low power amplifiers.
Full descriptive details of a suitable enclosure together with a point-to-point wiring diagram are included with each pack.
Two packs are available—types HFP/1 and HFP/2 for 7.5 ohm and 15 ohm systems respectively.
True high fidelity reproduction will be experienced with this economically designed combination at a cost considerably less than other systems.
Frequency response : 40 cycles—17,000 cycles. Power handling : 12 watts.

PRICE COMPLETE **£7. 11. 6**
P. Tax £2 13. 10

ELECTRO ACOUSTIC INDUSTRIES LTD., Stamford Works, Broad Lane, Tottenham, N.15. Telephone: TOT 0505/9

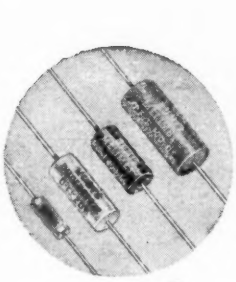
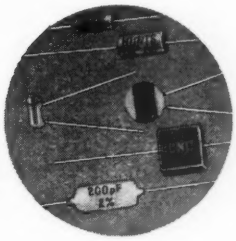
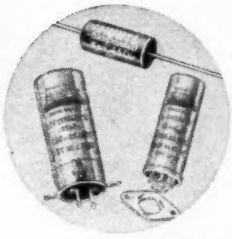

You can bank on

Hunts

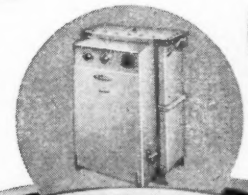

HUNTS
CAPACITORS
THE TRADE MARK OF RELIABILITY

...for all types and applications

ALL TYPES	ALL APPLICATIONS
DRY ELECTROLYTIC	RADIO & TELEVISION EQUIPMENT
METALLISED PAPER (HUNTS PATENTS)	ELECTRONIC EQUIPMENT
METALLISED PLASTIC FILM (HUNTS PATENTS)	POWER FACTOR IMPROVEMENT
PLASTIC FILM · FOIL & PAPER	CAPACITOR MOTORS
SILVERED MICA · STACKED MICA	FLUORESCENT LIGHTING
CERAMIC, POWER CERAMIC	PHASE SPLITTING · H.F. & R.F. HEATING
TRANSMITTING TYPES	IGNITION AND INTERFERENCE SUPPRESSION
SPECIAL R.F. TYPES	TELEPHONE INSTALLATIONS

A. H. HUNT (Capacitors) LTD., WANDSWORTH, LONDON, S.W.18. Tel: BATtersea 1083
Factories also in ESSEX, SURREY and NORTH WALES

A NEW INTERMEDIATE POWER TRANSISTOR

Bridges the gap between audio and power types

GOLTOP **Type V15/20 IP and V30/20 IP**

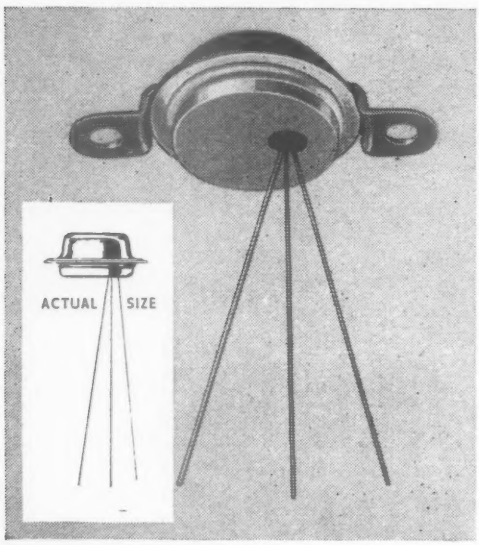

Available now for development purposes

The Newmarket Transistor Company, first to make RF transistors in Britain on a commercial scale and first again with power types, now introduces a new intermediate power transistor which fills the gap between the general purpose audio and 10-Watt power types.

Perfectly sealed by a cold welding process, this new unit has a special clip mounting which eliminates large fixing studs. Maximum power dissipation is obtained with the unit on a heat sink but a useful output is obtainable with the transistor alone, making it ideal for use with printed circuit boards.

Abridged data

MAXIMUM RATINGS

Collector Voltage (Vcb)	DC or Peak, 15V (V15), 30V (V30)
Collector Current (Ic)	DC or Mean, 2A
Junction Temperature	75°C.
Collector Power Dissipation—	
(1) On 9 sq. in. of 16 swg aluminium, 2 Watts.	
(Derating 40 mW/°C. rise above 25°C.)	
(2) transistor only in free air, 0.5 Watt.	
Thermal Resistance (Junction to mounting surface)—10°C./W.	

CHARACTERISTICS

Collector cut-off current		50μA (max.)
Current gain (Beta)	—20mA	40 (typical)
	—150mA	25 ,,
	—500mA	16 ,,
Alpha cut-off frequency	—20mA	250 Kcs (Typical)

Typical applications

R.F. TRANSMITTERS
Output powers up to 3 Watts are possible at frequencies up to 500 Kc/s.

AMPLIFIERS
Class A or B amplifiers operating at audio or radio frequencies.

DRIVER AMPLIFIERS
Characteristics are ideal for driving Goltop V15 and V30 power transistors in push-pull.

SWITCHING CIRCUITS
The maximum mean current rating of 2 Amps permits the use of large pulse currents as required in servo control systems.

OSCILLATORS
Ultra-sonic and low RF power oscillators up to 500 Kc/s.

D.C. CONVERTERS
Outputs up to 6 watts per transistor.

STABILISED POWER SUPPLIES
Can be used for the series elements of supplies delivering up to 2 Amps or as drivers in larger units.

NEWMARKET TRANSISTORS

All enquiries to:

Newmarket Transistor Co Ltd
Exning Road, Newmarket, Suffolk
Telephone: Newmarket 3381-4

ACOUSTICAL

For the closest approach to the Original Sound— that your enjoyment and appreciation of music may be unimpeded

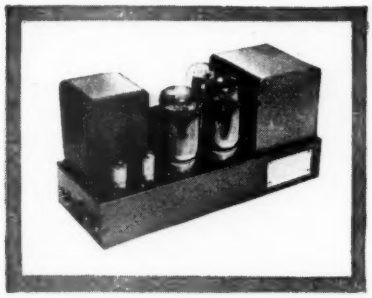

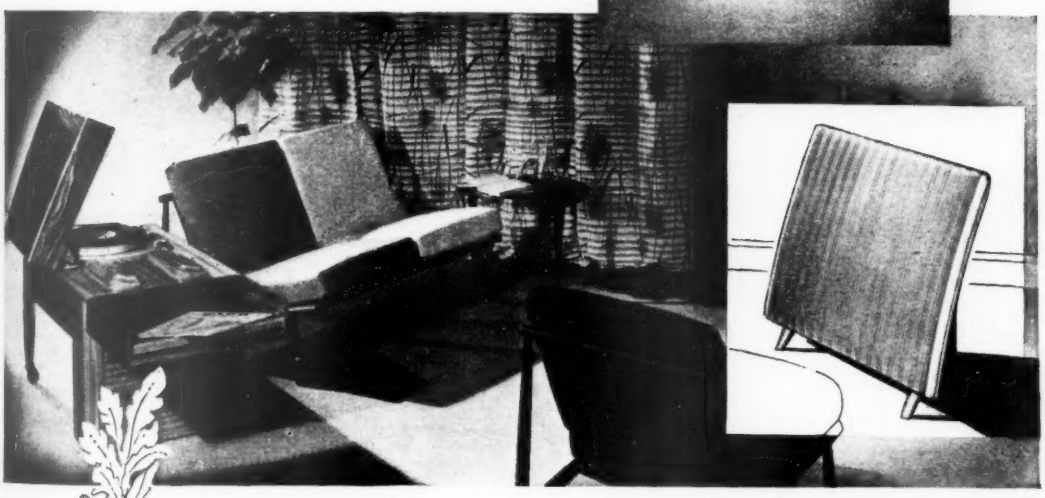

Please ask for illustrated literature describing the QUAD II Amplifier, FM Tuner and Electrostatic Loudspeaker.

ACOUSTICAL MANUFACTURING CO. LTD.
HUNTINGDON, HUNTS.
HUNTINGDON 361.

The Nodistron

A NEW NUMERICAL DISPLAY TUBE

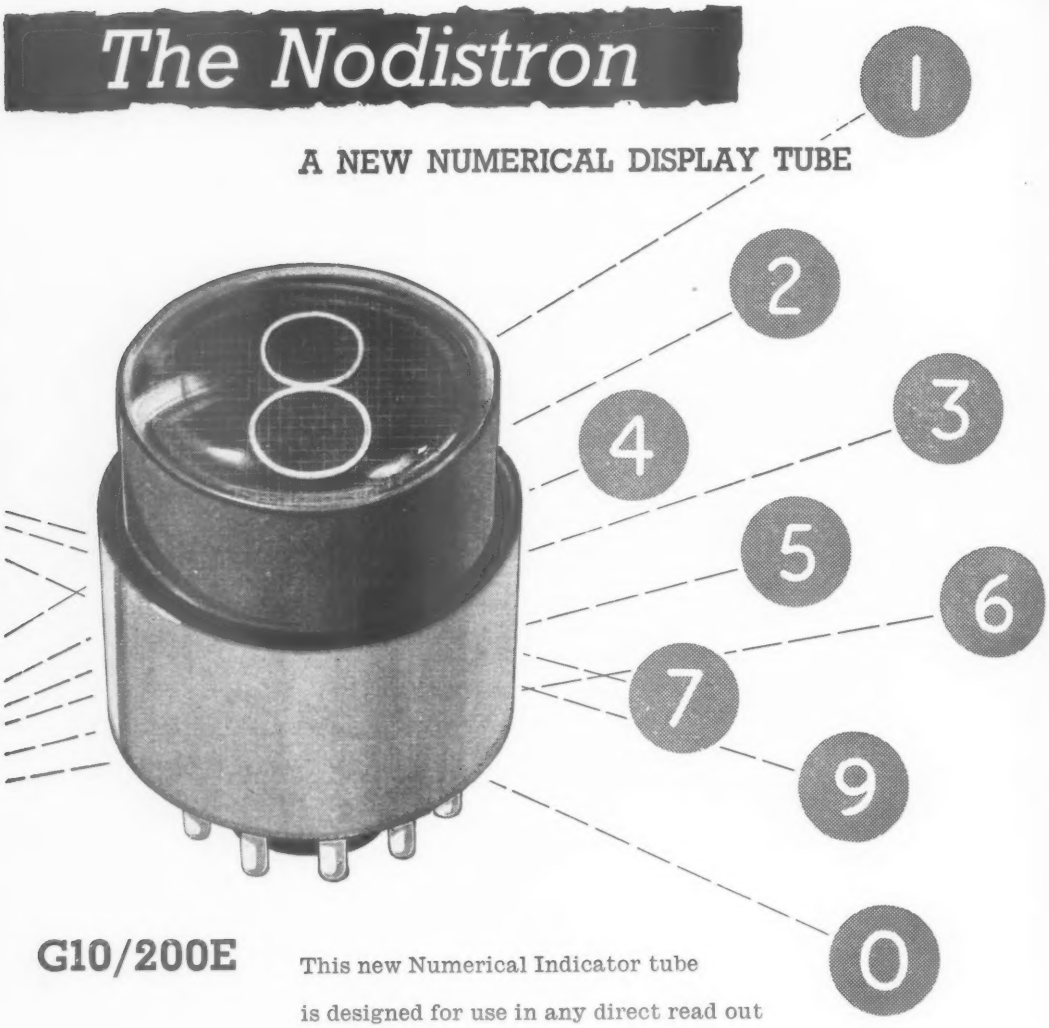

G10/200E

This new Numerical Indicator tube is designed for use in any direct read out equipment. It is a cold cathode device, the cathodes being shaped in the form of numerals and brought out to separate pins on a duodecal base. The application of approximately 200 volts between any specified cathode and the common anode causes a glow discharge in the form of any individual numeral from 0 to 9.

Standard Telephones and Cables Limited

SPECIAL VALVE SALES DEPARTMENT

CONNAUGHT HOUSE · 63 ALDWYCH · LONDON W.C.2

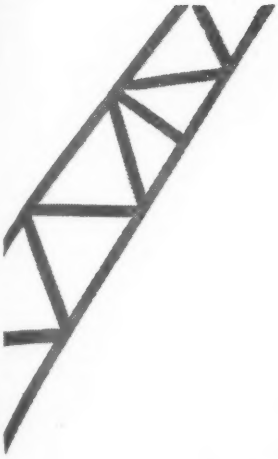

It is gratifying to know that in a world of rising prices our policy of maintaining and, in many instances, reducing prices has resulted over the years, and especially at this period, in ever increasing sales.

We carry a stock of 2,000 types of receiving transmitting and special purpose tubes, and invite your enquiries not only for commercial grade tubes but also for those tested to C.V., JAN and MIL specifications.

Our Organisation is A.R.B. Approved.

If you are not already on our Mailing List, please send for latest Price and Stock List.

HALL ELECTRIC LTD

Haltron House, 49/55 Lisson Grove, London, N.W.1

Telephone:
AMBassador 1041 (5 lines)
Cables:
Hallectric, London
TELEX 2-2573

RADAR NAVIGATION TRAINING by— ELECTRONICS

WITH THE NEW ***ULTRA*** *MARINE RADAR SIMULATOR*

Employing the most advanced electronic techniques, Ultra Electric have developed the Marine Radar Simulator, an equipment which allows the student navigator to perform, entirely within the classroom, tactical and collision-avoidance exercises of a nature impossible or dangerous to simulate at sea. Utmost realism is achieved, and every aspect of navigation can be reproduced quickly and economically. Already acclaimed by both marine and technical worlds, the Marine Radar Simulator is a valuable contribution towards efficiency and safety on the world's sea lanes.

ULTRA ELECTRIC LIMITED

SPECIAL PRODUCTS DIVISION

WESTERN AVENUE · ACTON · LONDON, W.3

THE SERVISCOPE

REGD TRADE MARK

DC TO 6 Mc/s

TIME AND VOLTAGE CALIBRATION

A PORTABLE HIGH PERFORMANCE MEASURING OSCILLOSCOPE

★ INCORPORATES AN ENTIRELY NEW TYPE OF TIME BASE
formerly only available on the most expensive American oscilloscopes.

★ 18 PRE-SET CALIBRATED SWEEP SPEEDS FROM
.5 sec/cm to 1 μ sec/cm

★ AUTOMATIC TRIGGERING OR TRIGGER LEVEL SELECTION

★ DC COUPLED UNBLANKING

★ 9 CALIBRATED Y SENSITIVITIES
FROM 100 mV/cm to 50V/cm ALL DC TO 6 Mc/s

★ SWEEP EXPANSION TO OVER 10 SCREEN DIAMETERS

★ BUILT-IN TV SYNC SEPARATOR

★ ULTRA BRIGHT 3″ FLAT FACE CRT

★ COMPLETELY PORTABLE 8″ x 6″ x 12″

THE FINEST, MOST VERSATILE

portable oscilloscope ever offered to the electronics industry.

Write for fully illustrated leaflet.

TELEQUIPMENT LTD

313 Chase Road, Southgate, London N.14. PALmers Green 7111

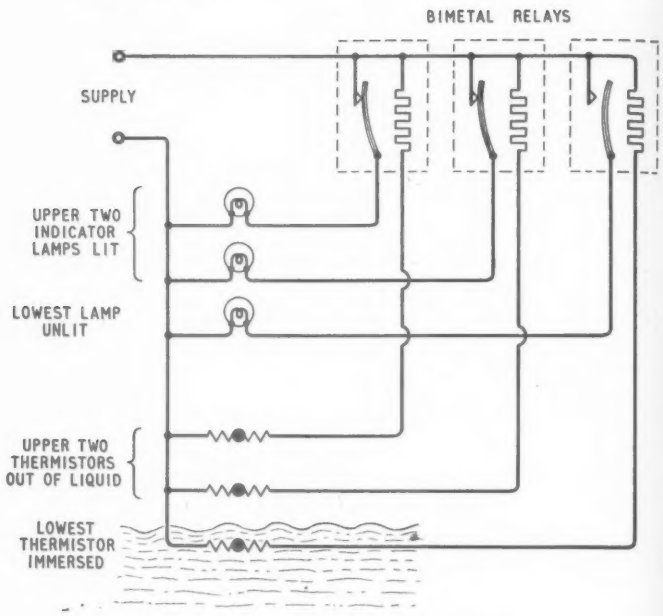

Thermistor properties and applications

The July issue of ELECTRONIC & RADIO ENGINEER contains an article on the properties and general applications of thermistors. The author's approach is practical and largely non-mathematical. Brief descriptions of thermistor manufacture and the physics of negative-temperature coefficient materials are included.

Original articles by leading authorities are a prominent feature of ELECTRONIC & RADIO ENGINEER. *Regular readership will keep you in constant touch with progress in the entire field of electronics, radio and television.*

ARTICLES IN THE AUGUST ISSUE WILL INCLUDE

Coils for Magnetic Fields
The performances of foil-wound and wire-wound solenoids are compared from the viewpoint of internal temperature rise. A further type of coil, in which co-axial power cable is employed, is also discussed.

Low-Power Ferrite Duplexers
Describes two short ferrite duplexers suitable for low-power Doppler navigational systems. Isolations of 25 dB over bandwidths of more than 1.3 per cent at X-band frequencies are obtainable.

ALSO
The unique monthly Abstracts and References feature compiled by the Radio Research Organization of the Department of Scientific and Industrial Research.

POST THIS COUPON TODAY

ELECTRONIC & RADIO ENGINEER

TO: ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1.

Please enter my name as a subscriber to:—
ELECTRONIC & RADIO ENGINEER *for 12 months commencing with the August issue. I enclose remittance £2 9s. (U.S.A. and Canada $7.50).*

ORDERS CAN ALSO BE PLACED THROUGH ANY NEWSAGENT.

NAME .....

ADDRESS .....

.....

DATE .....

DUBILIER

Capacitors for high grade equipment

Dubilier tubular capacitors are produced in a wide range of ratings and have been designed to meet the most arduous conditions including the highest performance classification in government specifications.
The three capacitors shown below are examples from the complete range. Full details are given in Catalogue PT.3 which we shall be pleased to supply upon request.

TYPE 470A

Hermetically sealed in an aluminium tube, this paper capacitor conforms to British Joint Service Standards RCS.131, temperature category —40°C to +100°C and humidity classification to H.2. Capacitance range: 0.001 to 1.0μF ±20%. Voltage range: 350V to 1000V d.c. working. Also available with insulating sleeves.

MINICAP

Hermetically sealed, this sub-miniature paper capacitor conforms to the same B.J.S. Standards as Type 470A. Capacitance range: 0.001 to 0.1μF ±20%. Voltage range: 200V to 500V d.c. working.
Also available with insulating sleeves.

500 H.T.

This capacitor is suitable for use on high voltage d.c. where the a.c. ripple is extremely small, as for example, the E.H.T. supply in television and other cathode ray tube applications. The 500 H.T. is moulded in plastic to improve external insulation resistance for very humid conditions.
Capacitance range: 0.0005 to 0.1μF ±20%.
Voltage range: 2kV to 30kV d.c. working at 70°C.

We shall be pleased to see you on STAND 55 at the Radio Show, Earls Court.

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, NORTH ACTON, LONDON, W.3.

Phone: ACOrn 2241 *Grams: Hivoltcon Wesphone London.*
DN 212A

Aspects of design 2

VISION I.F. AMPLIFIERS (Part 2)

This is the second of a series of special features dealing with advanced problems in television and radio circuit design to be published by Siemens Edison Swan. The Ediswan Mazda Applications Laboratory will be pleased to deal with any questions arising from this, or future articles, the third of which will appear in the September issue.

STABILITY.

In the design of an I.F. amplifier the stability, or freedom from feedback from output to input, over a single stage has to be considered if the response shape and performance are to remain consistent from one receiver to another. For band-pass circuits where Qk = 1 and where the stability is required to be five times better than the conditions that produce oscillation the general equation can be written as:

$$R_{d(in)} \times R_{d(out)} \times gm \times \omega \times C_{a,g_1} = 0.16$$

where R_d = dynamic resistance of the tuned circuits
gm = mutual conductance of the valve
$\omega = 2\pi f$
C_{a,g_1} = interelectrode capacitance g_1 to a

One of the factors controlling stability then is the g_1 to a capacitance of the valve and usually its value is measured at a low frequency and the result used for calculating the stability of the stage.

However, in a valve structure and the associated valveholder there are several alternative paths, other than the g_1 to a capacitance, through which the output voltage at the anode can be transferred back to the input.

These alternative feedback paths are provided by the inductance of the lead-out wires, the mutual inductance between adjacent leads, and interelectrode capacitances other than g_1 to a, such as for example the g_1 to g_2 and the g_2 to a capacitance.

The effects of the feedback resulting from the coupling between lead inductances has been found to follow a given law which when expressed in terms of the g_1 to a admittance can be written as:

$$\text{Effective admittance } g_1 \text{ to a} = \omega C_{a,g_1} - k\omega^2$$

where k is a factor whose value depends upon the disposition of the internal wires in the valve base as well as the interelectrode capacitances and it is therefore a measure of the amount of feedback existing in a particular valve design.

The effective admittance of g_1 to a path being made up of a positive term proportional to ω and a negative term proportional to ω^2 will have a value which is zero at one particular frequency as shown in Fig. 1.

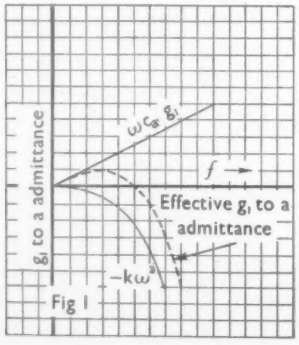

Fig 1

Unless care is taken to keep the grid to anode capacitance as low as possible and to minimise the value of k by low couplings within the valve, the zero admittance frequency can occur within the working band. Although feed-back will be non-existent at this point the variation of the admittance is reaching the steep part of the curve and as it is here changing so rapidly it can lead to unstable operation when normal tolerances are taken into account.

For very many years in the design of the Ediswan Mazda range of R.F. pentodes for television, great care has been taken to achieve a low g_1 to a capacitance and at the same time to keep the value of k as low as possible by using short internal leads arranged to reduce coupling to a minimum. This results in a low value of g_1 to a admittance with only a small change of admittance over the normal working band of television I.F. frequencies.

The effective g_1 to a admittance of a typical 30F5 plotted against frequency is shown in Fig. 2.

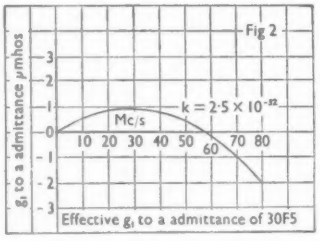

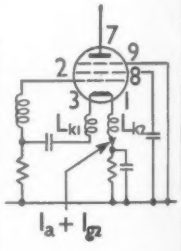

Fig 3

THE EFFECT OF CATHODE CONNECTIONS ON INPUT RESISTANCE.

It is often an advantage to make use of the two cathode connections provided in the R.F. pentodes in the Ediswan Mazda range. This feature enables the grid circuit to be decoupled to one cathode pin while the other cathode pin is taken to chassis via the self-bias network as shown in Fig. 3.

By the use of separate cathode connections the effective input resistance is increased. This is because the arrangement prevents degeneration from occurring in the cathode circuit owing to the fact that the total output current $I_a + Ig_2$ can only pass through Lk_2 which has no common path with the input circuit. By raising the value of input resistance in this manner the required Q of a wideband I.F. transformer can be controlled almost entirely by external damping resistors and so become less dependent upon the valve. Alternatively, the arrangement can be used to give greater selectivity on a narrow-band sound I.F. transformer.

Typical values for input risistance for the 30F5 at 38 Mc/s with strapped or separate cathode connections are:-

$R_{(in)}$ with strapped cathodes = 8,800 ohms
$R_{(in)}$ with separate cathodes = 21,000 ohms

SIEMENS EDISON SWAN LIMITED

An A.E.I. Company, 155 Charing Cross Rd., London, W.C.2. & branches.
Telephone: GERrard 8660. Telegrams: Sieswan, Westcent, London.

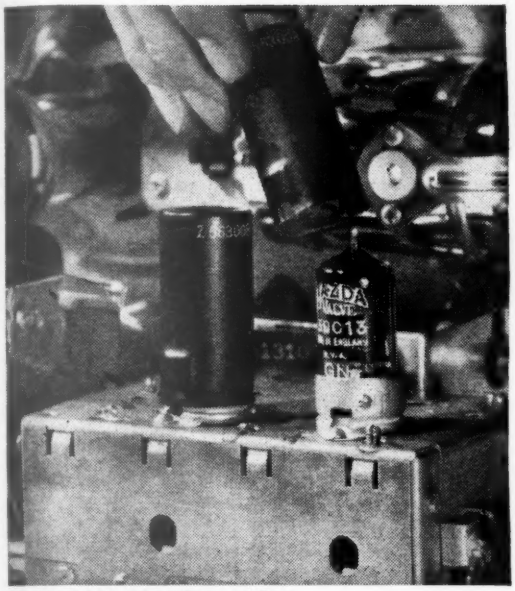

EDISWAN MAZDA 30C13.

V.H.F. Frequency Changer for printed circuit tuners.

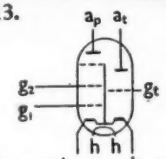

Heater volts ..	9.0
Heater current	0.3 amps
Maximum anode volts	
Pentode ..	250
Triode	250
Maximum screen volts	175

TYPICAL OPERATION.

As frequency changer with oscillator volts applied to g_1.

PENTODE

Anode volts	170
Screen volts	150
g_1 Resistance for grid current bias	100,000 ohms
g_1 current	42 μA
Conversion conductance	2150 μA/V
Heterodyne peak volts	4.5
Anode current	6.3 mA
Screen current	1.9 mA

TRIODE

Anode volts	120
Anode current	6.0 mA (average)

CAPACITANCES.

PENTODE		TRIODE	
g_1 to all	6.3 pF	g to E.....	3.5 pF
ap to all	5.2 pF	a to E	3.3 pF
g_1 to ap	0.016 pF	g to a	1.7 pF

APPLICATION USE OF THE 30C13.

The performance of a television tuner on Band III is often limited by the comparatively low input resistance of the triode pentode mixer that is commonly used. One of the principal causes of low input resistance at these frequencies is the cathode lead inductance, part of which is in the valve and part in the external circuit. This inductance causes degeneration and produces resistive damping of the input circuit.

With the use of printed circuit technique the external cathode lead inductance is very low making it more important than ever to reduce to a minimum the cathode lead inductance in the valve. In the 30C13 this has been done by strapping together the pentode cathode and the triode cathode internally with a low inductance connection thus practically halving the cathode lead inductance in the valve base. In addition the disposition of the pins in the base has been chosen so that with the 30C13 the fullest use can be made of the opportunity of providing the best circuit layout for printed circuit techniques when used in conjunction with a cascode valve like the 30L1.

The use of the 30C13 in a printed circuit will result in a gain increase on Band III of 1½ dB compared to the 30C1 used in a wired tuner.

Characteristic curves of average Ediswan Mazda Valve type 30C13.

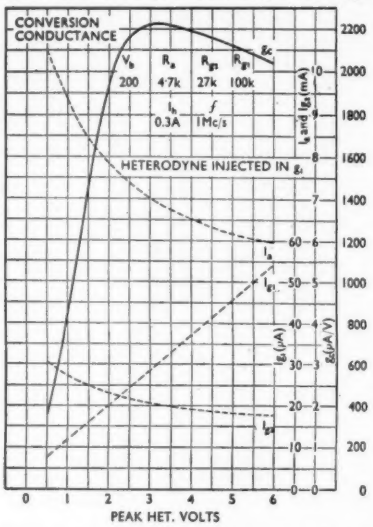
CONVERSION CONDUCTANCE
V_b R_a R_{g2} R_{g1} g_c
200 4·7k 27k 100k
I_h 0.3A
f 1Mc/s
HETERODYNE INJECTED IN g_1
I_a and I_{g2} (mA)
I_a
I_{g2}
I_{g1} (μA)
g_c (μA/V)
I_{g1}
PEAK HET. VOLTS
0 1 2 3 4 5 6
2200 2000 1800 1600 1400 1200 1000 800 600 400 200 0
10 9 8 7 6 5 4 3 2 1 0
60 50 40 30 20 10 0

The base connections of the 30C13 provide the following advantages for printed circuit use:

(a) The pentode g_1 and cathode are brought out on adjacent pins. This enables the grid trimmer to be placed very close to the g_1 to k capacitance thus minimising errors in alignment that can arise at differing frequencies if the trimmer has series inductance.
(b) The g_3 connection is conveniently placed close to the cathode.
(c) The heater pins are easily accessible for series connection in a printed circuit board while still allowing easy decoupling to the strapped cathodes.
(d) The position of the grid and anode pins of the triode oscillator makes it possible to use short connections to the oscillator coil.
(e) The reduction in cathode lead inductance increases the gain on Band III.

These points are illustrated in Fig. 1 which shows part of a printed circuit layout using the 30C13 where the R.F. stage is assumed to be a cascode amplifier using the 30L1.

If the 30C1 were used in place of the 30C13 a much less satisfactory layout would result. This is shown in Fig. 2 where the g_1 circuit has a longer return path to cathode with the added disadvantage that this is shared by the g_2 circuit and for these reasons the 30C1 should not be considered for this application.

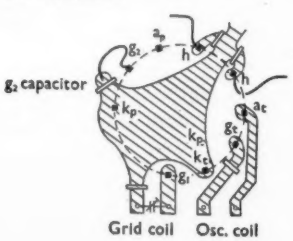

Fig 1 30C13

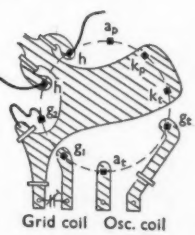

Fig 2 30C1

EDISWAN
MAZDA
SIEMENS EDISON SWAN LIMITED

An A.E.I. Company, 155, Charing Cross Road, London, W.C.2, and branches. Telephone: GERrard 8660. Telegrams: Sieswan, Westcent, London.
CRC 15/20

ADCOLA

(Regd. Trade Mark)

SOLDERING INSTRUMENTS
& ALLIED EQUIPMENT

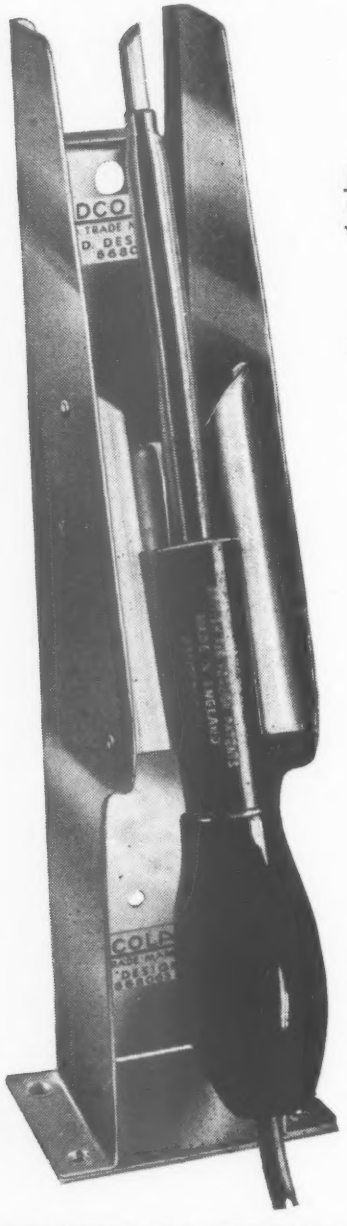

ILLUSTRATED
DETACHABLE
¼" BIT MODEL
LIST NO. 64

Protective
Shield
List No. 68

CATALOGUES HEAD OFFICE SALES & SERVICE

ADCOLA PRODUCTS LTD.,
GAUDEN ROAD,
CLAPHAM HIGH ST.,
LONDON, S.W.4.

TELEPHONES:
MACaulay 3101
& 4272

Connoisseur

SOUND PRODUCTS

We make no extravagant claims for Connoisseur products, all we ask is that you listen to them and judge for yourself. They are not cheap, but then the best never is. Look at the specifications.

Connoisseur Variable Three-speed Gramophone Motor

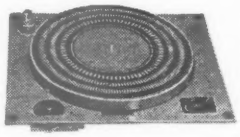

Mechanical speed change without braking provides 4 per cent variation at all speeds. Synchronous motor is virtually vibrationless. Main spindle runs in phosphor bronze bearings. Turntable is full 12in. lathe turned from non-ferrous material.

Connoisseur Pick-up

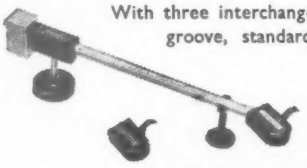

With three interchangeable heads for micro-groove, standard, and older records, available with Diamond or Sapphire Stylus. Frequency range 25-20,000 cps ±2dB's, 400 ohms Model gives 15 M.V. output from the average LP disc; 25 M.V. from a standard 78 r.p.m. recording.

Connoisseur HQ 20 Amplifier and Pre-amplifier

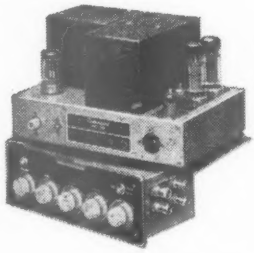

Both units are built to the highest electrical and mechanical standards and incorporate the latest developments in Audio technique. High power output allows the reproduction of peak passages without overload or distortion.

Send for descriptive leaflets

A. R. SUGDEN & CO. (ENGINEERS) LTD.
Well Green Lane, Brighouse, Yorks.
Telephone: BRIGHOUSE 2397

OVERSEAS AGENTS:
U.S.A.: Ercona Corporation, 551, Fifth Street, New York 17, N.Y. CANADA: The Astral Electric Co. Ltd., 44, Danforth Road, Toronto13. Ontario. NEW ZEALAND: Turnbull & Jones Ltd., Head Office 12/14, Courtenay Place, Wellington. HONG KONG: The Radio People Ltd., 31 Nathan Road, Hong Kong.

MAIN DISTRIBUTORS:
AUSTRALIA: British Merchandising Pty. Ltd., 183, Pitt Street, Sydney and J. H. Magrath (Pty.), Ltd., 208 Little Lonsdale Street, Melbourne. EAST AFRICA: International Aeradio (East Africa) Ltd. P.O. Box 3133, Nairobi. MALAYA: Eastland Trading Co., 1 Prince Street, Singapore.

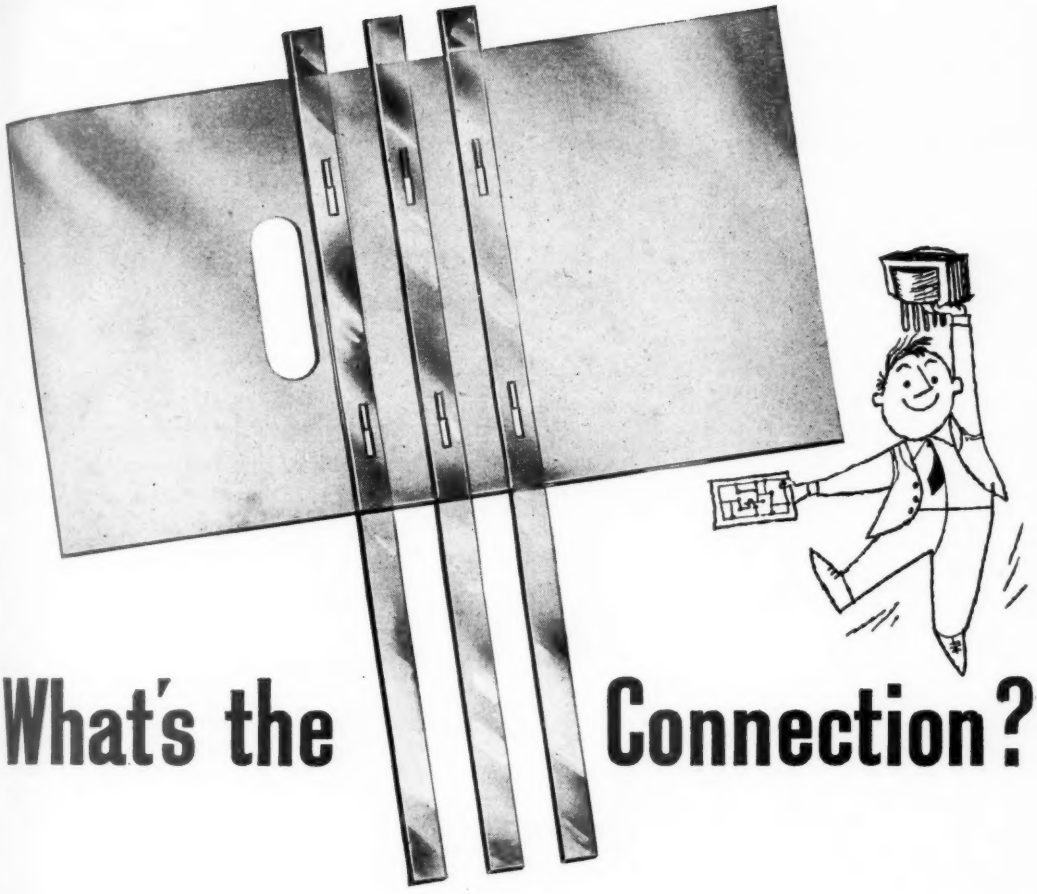

What's the Connection?

It's a very neat one—a special tri-acetate harness assembly of high electrical quality which allows assembly shops to connect Hinchley transformers to the now widely used printed circuits with an absolute minimum of labour. It was made on a special purpose machine designed by Hinchley when printed circuits first came to Britain. It is this kind of foresight, coupled with specialized production techniques, rigid quality control, an unequalled design service, and—vital today—cost consciousness, that has kept Hinchley in the forefront of the industry. Our technical service is immediately at your call. Why not make use of it?

Take a look at the quality of

Hinchley TRANSFORMERS

HINCHLEY ENGINEERING CO. LTD · DEVIZES · WILTSHIRE · Tel: DEVIZES 573/5

Armstrong

AM/FM Radiogram chassis

MODEL PB409 (*Illustrated*) **28 gns**

A High Quality Radiogram replacement unit

• 9 valves • 6 watts Push-Pull output • Negative Feedback • 4 wavebands including VHF • Quick action Piano Key selectors • Separate Bass and Treble controls • Magic Eye

MODEL AFI05 £37

AM and FM Tuners and High Fidelity Amplifier on one compact chassis

• 10 valves • 10 watts Push-Pull output • 20 dB Negative Feedback • 5 wavebands including VHF • Independent wide range Bass and Treble controls with visual indicators • Magic Eye.

Post this coupon for descriptive literature or call at your local High Fidelity dealer, or at our Holloway showrooms, for full demonstration.

BLOCK CAPITALS PLEASE

NAME.....

ADDRESS.....

..... WAU

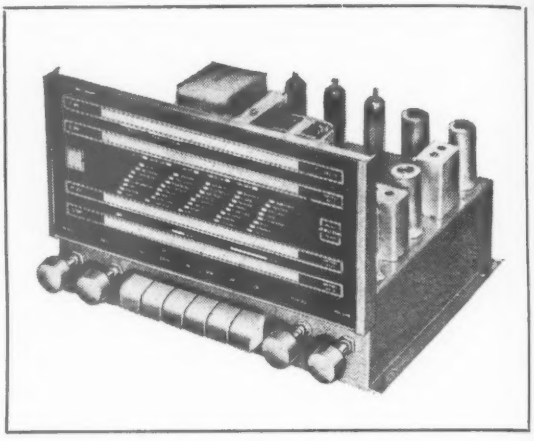

Armstrong have been making radiogram chassis for almost 25 years and have always concentrated on the requirements of those who demand the highest quality. You may wish to modernise your existing radiogram, or build a new and up-to-date reproducing system. In either case . . .

an **Armstrong** *is the answer!*

4 girls now do work of 5

New techniques demand new tools. Transistors, printed circuits, sub-miniature components can now be soldered more accurately, with much less effort, without risk of damage to adjacent components with the feather-weight pencil-thin Oryx. Available in seven models for continuous working up to 470°C. Widely used by instrument makers, electronic equipment makers throughout the world. It will pay you to give the Oryx an extended trial on your own production lines.

from **25/-** subject

For QUICKER . . BETTER Joints at less cost!

EXCLUSIVE ORYX FEATURES

★ Low voltage (6-24 v.), absolutely safe, therefore ideal for female operatives.
★ Heats up in 35 seconds—cannot overheat during extended use
★ Uses renewable, interchangeable, corrosion-resistant bits
★ Patented heating element has no ceramic spacers or mica insulators
★ Ideal for battery-operated mobile service on cars, trucks, aircraft
★ Efficiency equal to mains-operated 80-watt iron at fraction of weight and size
★ Fully guaranteed against breakdown for twelve months

Write now for illustrated Folder and Price List.

ORYX

ORYX ELECTRICAL LABORATORIES LTD.,
DOMINION ROAD, WORTHING, SUSSEX *Tel:* WORTHING 9895

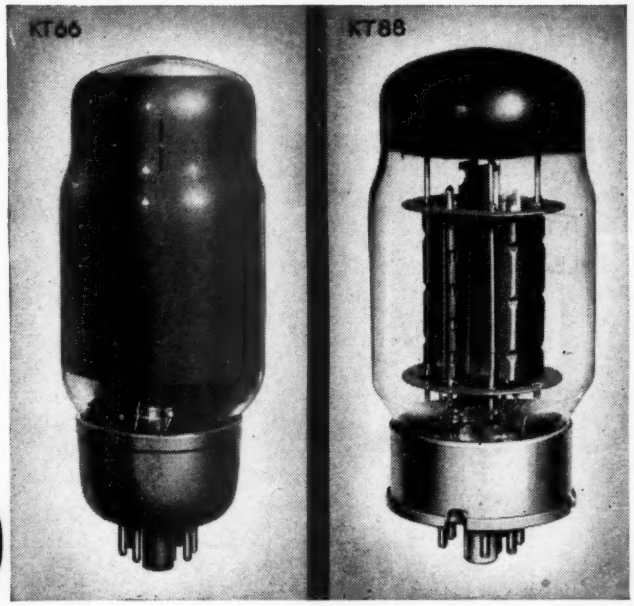

G.E.C.

VALVES

for reliability and power at audio frequencies

The KT 66—still leading the world after 21 years

When the KT 66 was introduced in 1937, it was far ahead of its time. So far ahead that it still leads the world today. Over the years that have passed, many millions of these valves have been manufactured and the excellent design plus the quality of materials used have won a phenomenal reputation for long-lasting reliability. 12 valves, recently installed in multi-channel radio equipment, each completed 32,600 hours without failure. The KT 66 has been used in a number of well-known high quality audio amplifiers including the 'Williamson' and the 'Leak Point 1', designed for outputs of up to 50 watts.

	KT 66	KT 88
V_a (max.)	500	600 volts
V_{g2} (max.)	400	600 volts
P_a (max.)	25	35 watts
g_m	6.3	11 mA/V
Pout (ABI push-pull fixed bias, U.L.)	50	100 watts
V_h	6.3	6.3 volts
I_h	1.27	1.8 amps
Price ... ... P.T.	17s. 6d. 6s. 10d.	£1 2s. 6d. —

The KT 88—for even higher powers

As the need for higher powers of audio frequencies increased, the G.E.C. used the basic design of the KT 66 and experience gained in its manufacture to develop the KT 88. This valve has a maximum anode dissipation of 35 watts as opposed to 25 watts for the KT 66, has a higher g_m and a cathode of larger emissive area. Physically the valve uses a smaller envelope and a pressed glass base and two valves in push-pull can provide 100 watts of audio power. The KT 88 is therefore ideal for high power public address systems in addition to many industrial applications.

For Data Sheets giving full technical descriptions of the KT 66 and KT 88 together with 'circuit supplement' sheets giving typical application details, write to the Valve and Electronics Department.

Come and hear a demonstration of
G.E.C. High Quality Sound Equipment
at STAND 433
(Audio Section of the National Radio Show)

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2

There's nothing new in this relay EXCEPT

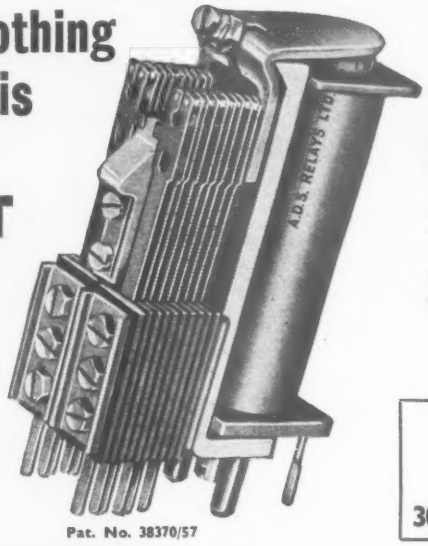

Pat. No. 38370/57

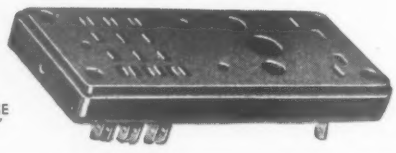

SIZE OF BASE
2¾" x 1⅝" x ½"

The ONLY PLUG-IN 3000 TYPE RELAY

COMPLETE WITH BASE AND TRANSPARENT DUST COVER

A.I.D. A.R.B. ADMIRALTY APPROVED
3000 & 600 TYPE RELAYS

A. D. S. RELAYS LTD.
12, STORE STREET, LONDON, W.C.1

Reduce your press tool costs with the HUNTON UNIVERSAL BOLSTER OUTFIT

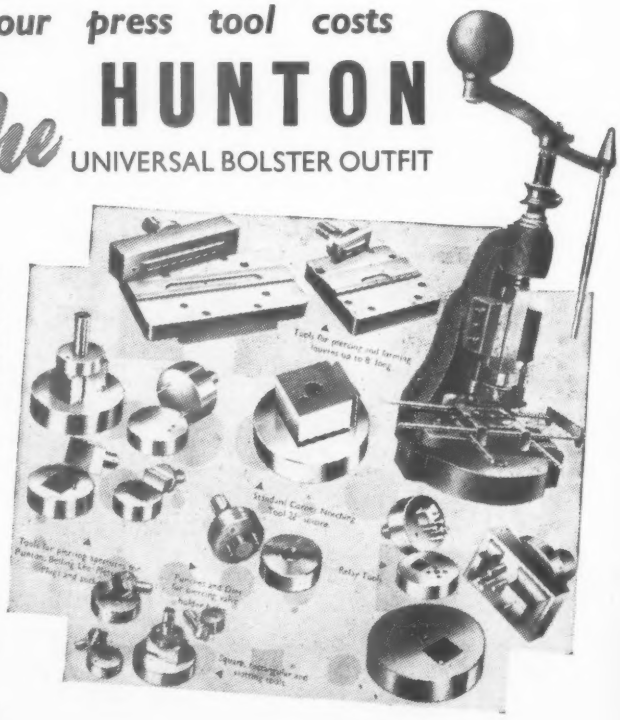

In addition to the range of Punches and Dies ⅛in. to 3½in. dia. available from stock, some of the tools usually required in the Radio and Electronic Industries have been standardised for use with the Hunton Universal Bolster Outfit. Illustrated here are a few which can be supplied quickly or from stock.

In London and Home Counties, ask for a practical demonstration in your own works.

Write for illustrated brochure W.W.1.

HUNTON LTD.
Phoenix Works,
114-116, Euston Road, London, N.W.1

Telephone: EUSton 1477 (3 lines).
Telegrams: Untonexh, London.

Now! For the "uncovered" 10 mw to 10 watt range

NEW hp CALORIMETRIC WATTMETER

no external barretter or plumbing required

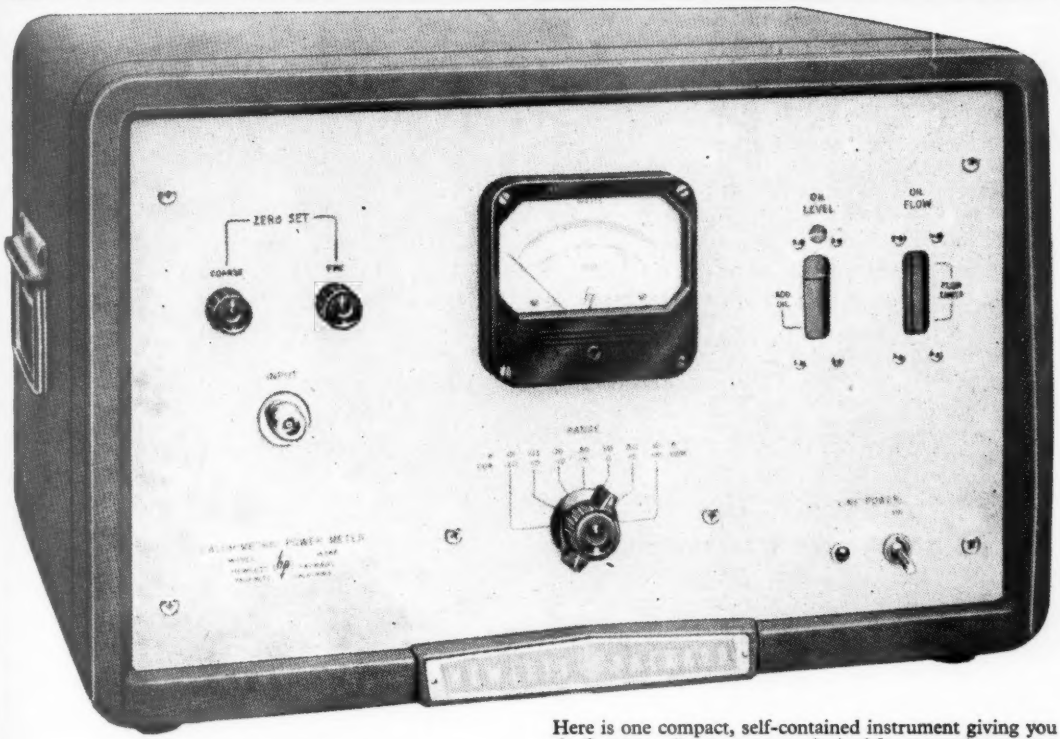

SPECIFICATIONS

-hp- 434A Calorimetric Power Meter

Input Power Range:	7 ranges; full scale readings of 0.01, 0.03, 0.1, 0.3, 1.0, 3.0 and 10 watts. Meter calibrated — 10 to 0 DBW, continuous readings — 30 to + 10 DBW
Frequency Range:	dc to 10 KMC
dc Input Impedance:	50 ohms ± 5 ohms at Type N input jack
Input SWR:	Less than 1.5 full range
Meter Response: (Full Scale)	Approximately 10 seconds on highest range, approximately 2 seconds on lower ranges
Controls:	Zero set and Meter Range
Accuracy:	Within 5% full scale
Power:	115/230 v. ± 10%, 50/60 cps, approximately 155 watts
Sizes:	Cabinet: 20½" wide, 12½" high, 14½" deep. Rack: 19" wide, 10½" high, 13½" deep. Wt. 50 lbs.
Price:	£457 (cabinet) £451 (rack mount)

Delivered in U.K. plus duty if applicable. Data subject to change without notice.

Here is one compact, self-contained instrument giving you the fastest, easiest means ever devised for measuring powers 10 mw to 10 watts between dc and 10 KMC!

With the new *-hp-* 434A measurement is literally as simple as connecting to a 50 ohm Type N front panel terminal and reading power direct. No complex setups, no barretter, thermistor, terminations or external plumbing are needed. The instrument is thus ideal for use by non-technical personnel.

10 second response, high stability

-hp- 434A provides a 10 second response time, permitting even small input changes to be tracked promptly. Fluctuations from oil flow rate or temperature changes are avoided by twin power sensitive elements in either leg of the self-balancing bridge which is the power comparison section of the instrument.

HEWLETT-PACKARD COMPANY
Represented by
LIVINGSTON LABORATORIES LTD.
RETCAR STREET, LONDON, N.19, ENGLAND
Tel.: Archway 6251

hp also offers 430C Power Meter, 0.1 to 10 mw!

REALISTIC REPRODUCTION—REALISTIC PRICE

When you think about converting to Hi-Fi you ask yourself —or your dealer—these questions.

1. **Can I really get concert standards of reproduction?**
2. **What units will I need?**
3. **Can I avoid a big outlay?**
4. **Can I compare systems so that I get the best value for money?**

The Dulci range of Tuners and Amplifiers have been designed not only to give the highest standards of reproduction but also to keep the price within the reach of all. Here is a selection from the Dulci range which will give you all you need.

MODEL DPA 10 AND PRE-AMPLIFIER

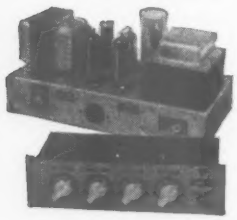

10-14 watts. Ultra linear with choice of control unit or pre-amplifier. A superb laboratory-designed amplifier, modern styled and of precision quality for domestic use. Incorporates every facility for the reproduction of high quality sound, from radio, records, tapes or microphone. **DPA 10 only £12/12/-. DPA 10 with control unit, £15/15/-. DPA 10 with pre-amplifier, £19/19/-.**

MODEL H4T2 SELF-POWERED AM/FM TUNER

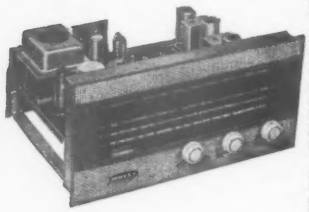

For clear, clean reception of the B.B.C. high fidelity transmissions on the VHF/FM Band and customary Long, Medium and Short wave broadcasts. Magic eye tuning — Audio Stage incorporating negative feedback — dual output for high and low sensitivity amplifiers. Simple "through" cabinet mounting — full automatic volume control and limiting on 2 IF stages. **Price £24/19/- inc. P.T.**

AND HERE'S THE SUPERIOR TAPE UNIT FOR THE SERIOUS ENTHUSIAST

DULCI TAPE UNIT — for superb performance and presentation. It's all ready for addition to a Hi-Fi system. Recording amplifier incorporated with erase and bias oscillator. Playback equaliser and pre-amplifier integrated with deck. 2 speeds—7½in./sec. and 3¾in./sec. **Price 55 gns.**

Write for illustrated literature.

DISTINCTLY **DULCI** QUALITY PRODUCTS

THE DULCI COMPANY LIMITED

97-99 Villiers Road London N.W.2
Telephone: WILlesden 6678/9.

The

Superspeed

Soldering Iron

heats up from cold in 6 seconds

Designed on an entirely new principle, this lightweight, versatile iron is eminently suitable for soldering operations in the radio, television, electronic and telecommunication industries. For test bench and maintenance work it is by far the most efficient and economical soldering iron ever designed.

Length, 10"; weight, 3½ ozs.

For best results with this iron use ENTHOVEN SUPERSPEED CORED SOLDER and ALUMINIUM CORED SOLDER

- **Activated by light thumb pressure on the switch ring. When pressure is released, current is automatically switched off—thus greatly reducing electricity consumption, wear on copper bit and carbon element.**
- **Can be used on 2.5 to 6.3 volt supply (4 volt transformer normally supplied) or from a car battery.**
- **More powerful than conventional 150-watt irons; equally suitable for light wiring work or heavy soldering on chassis.**
- **Simple to operate; ideal for precision work.**
- **Requires minimum maintenance—at negligible cost; shows lowest operating costs over a period.**

LIST PRICES	
IRON	39/6
TRANSFORMER	35/6

All prices and trade discounts subject to revision

ENTHOVEN SOLDERS LTD.
(Industrial Equipment Division)

Sales Office & Works:
Upper Ordnance Wharf, Rotherhithe Street, London, S.E.16. Tel: BERmondsey 2014

Head Office:
Dominion Buildings, South Place London, E.C.2. Tel: MONarch 0391

Printed circuits

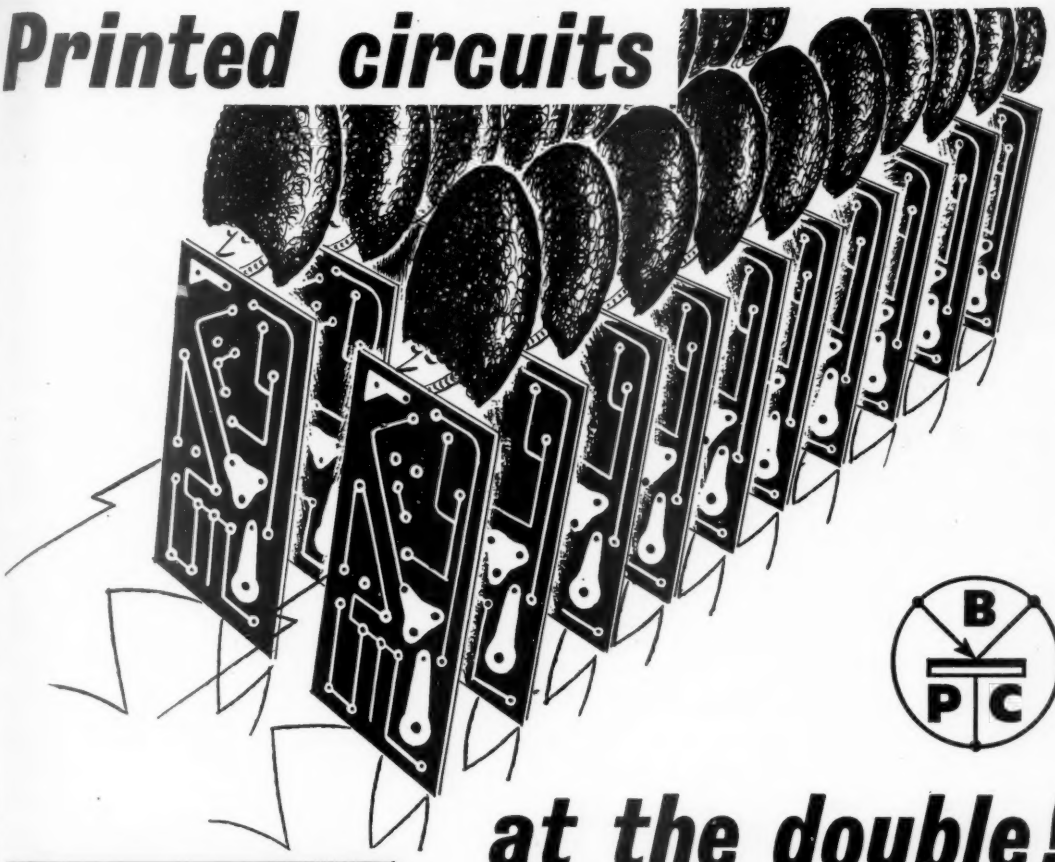

B P C

at the double!

Prototypes in 48 Hours

A special Prototype Service can produce the initial experimental circuit, on which future production can be planned, within 48 hours! All we need is a clean circuit image, 2, 3 or 4 times larger than actual size, from a dimensionally stable drawing material (such as Astrafoil)—the finished overall dimension of the circuit being indicated on the drawing. If desired, and time permits, we can design the circuit from a conventional wired assembly!

From design to production under one roof

You can keep in step with modern assembly methods with the help of Bribond. For the latest Bribond development brings the manufacture of all types of printed Circuit into line with the manufacture of other electrical components.

Organised on the modern line production principle, output up to 3,000 finished circuits an hour is practical. Each individual circuit is subjected to rigid inspection at three vital stages of manufacture, enabling us to offer a completely *reliable* service, both as regards *quality* and *delivery*.

Runs from 1-off upwards can be carried out at a very economical cost.

Enquiries are invited, which will be treated in strict confidence and some of the keenest minds in this field of engineering will be brought to bear on each problem.

BRIBOND LIMITED

PRINT CIRCUITS faster - cheaper

Send your enquiry to

Bribond Ltd., Burgess Hill, Sussex. Telephone: Burgess Hill 85611

AYLING INDUSTRIAL GROUP

TAKE YOUR PICK

Our wide range of capacitors, incorporating all the latest developments, are described fully in these new leaflets...

SEND NOW for COPIES

DALY has succeeded in maintaining full capacity values and working voltages in more compact designs, specially suited to ultra modern equipment :—

PHOTO-FLASH EQUIPMENT • DEAF AIDS
PRIVATE TELEPHONE INSTALLATIONS
AMPLIFIERS • D.C. POWER UNITS
TRANSISTOR EQUIPMENT
MAGNETISATION EQUIPMENT
TEST GEAR

DALY
ELECTROLYTIC CAPACITORS

Condenser Specialists for over 20 years.

DALY (*Condensers*) **LTD.,** WEST LODGE WORKS,
THE GREEN, EALING, LONDON, W.5. Phone: Ealing 3127-8-9. Cables: Dalcyon, London

STEREOPHONIC SOUND

RICHARD ALLAN PRESENT NEW SPEAKER ASSEMBLIES

3 STAR SPEAKERS for 3-D LISTENING

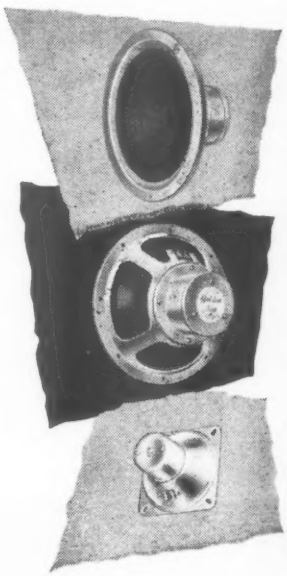

★ **Musically satisfying**
The Golden or Bronze Ten and 410T Tweeter give a steady response from 40 to over 15,000 cps.

★ **Dimensionally Suitable**
They are big enough to give near perfection (remember the Bass units are on a 1½in. centre pole) and are small enough for two assemblies to be used in the average room.

★ **Economically Practical**
They are built to a high standard at down-to-earth prices. Golden Ten Bass unit, Crossover CN104 and 410T Tweeter, £11/2/2 inc. P. Tax.
Bronze Ten Bass unit, Crossover CN104 and 410T Tweeter, £10/1/4 inc. P. Tax.

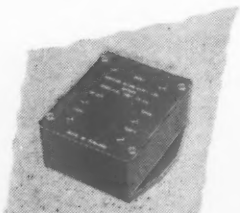

Richard Allan High Fidelity speakers are world renowned.

Send for descriptive leaflets to:

Richard Allan **RADIO LTD.**
Taylor St., Batley, Yorks.
Tel: Batley 1123 and 1308.

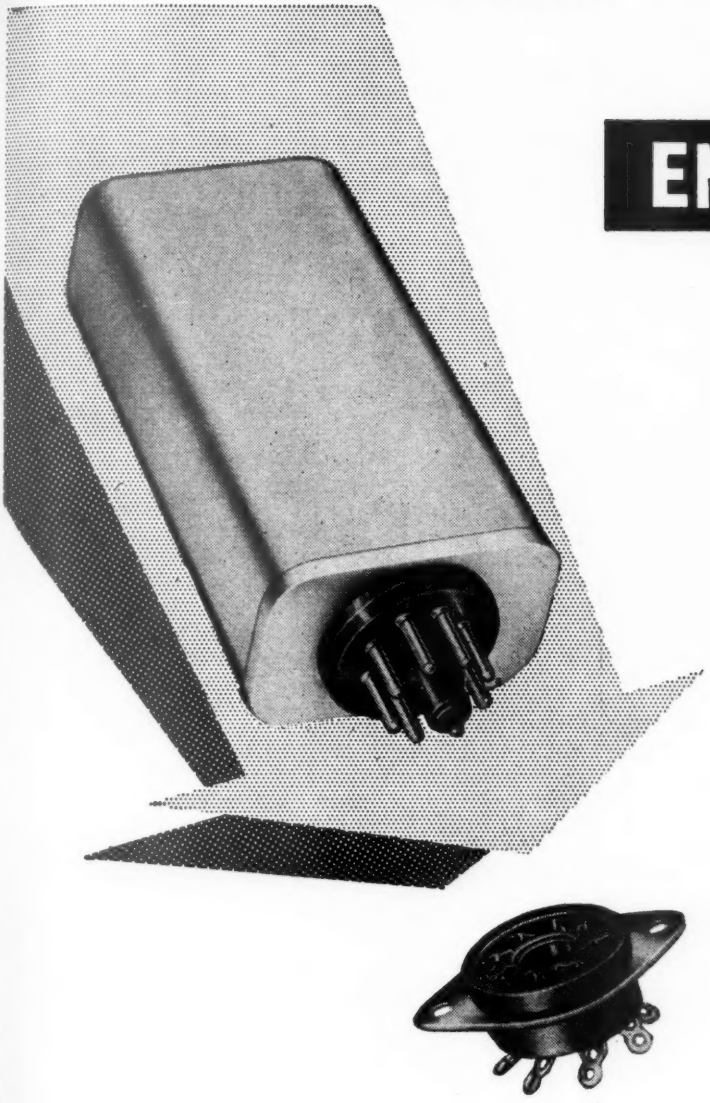

THIS ENCLOSED p.o. 3000 RELAY JUST PLUGS IN!

MAGNETIC DEVICES LIMITED
A.I.D. & A.R.B. Approved

This Series 305 Relay, which is the well-known P.O. type 3000 Relay, is now available with an easily removed dust cover (Type 305E) or hermetically sealed with glass-to-metal seals (Type 305H).
Connection is made by means of an 8 or 9-pin octal-type header. It is as simple as plugging in a valve!

MAGNETIC DEVICES LTD., EXNING RD., NEWMARKET, SUFFOLK

Telephone: Newmarket 3181-4 Telegrams: Magnetic Newmarket

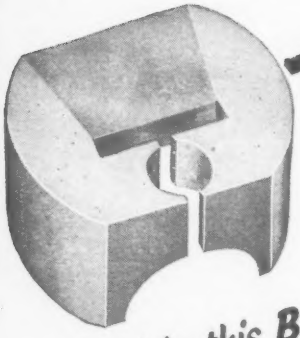

MUREX 'SINCOMAX' MAGNETS

are used in this B.P.L. TRANS RANGER

A typical example of the use of Murex 'Sincomax' Magnets where a high energy product with high magnetic stability is essential. Murex 'Sincomax' Magnets with an alloyed bond between magnet and soft iron, continue to give accurate and reliable service in this and many other applications.

MUREX LTD. *(Powder Metallurgy Division)*
RAINHAM · ESSEX · *Rainham, Essex 3322*
Telex 28632. Telegrams: Murex, Rainham-Dagenham, Essex.
London Sales Office: CENTRAL HOUSE, UPPER WOBURN PLACE, W.C.1. *EUSton 8265*

Photograph by courtesy of British Physical Laboratories Ltd.

AWA Teleradio* 5A

SIMPLE EFFICIENT

Made by AWA, Australia's largest manufacturer of telecommunications equipment of all types. AWA are approved contractors to the Crown Agents.
The 5A is in use by Governments and private networks in many places. Please write for details.

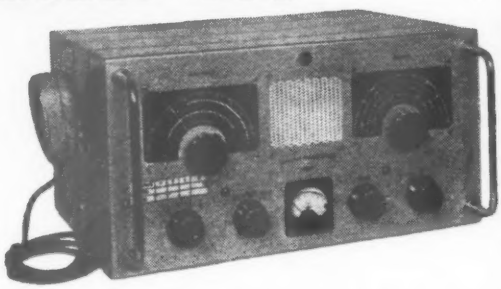

SPEECH COMMUNICATION

The AWA Teleradio 5A is a low-power H.F. transmitter-receiver for distances up to several hundred miles over land or sea.
One to four channels between 2 and 9 mc/s may be pre-tuned in the crystal-controlled transmitter. The receiver also tunes from 550 to 1540 kc/s.
The standard model operates from 12-volt battery.

* *Regd. Trade Mark 34699 (Aust.)*

AMALGAMATED WIRELESS (AUSTRALASIA) LIMITED
47 YORK STREET, SYDNEY, N.S.W. 99 ALDWYCH, LONDON

ES11-56

PYE

Mozart Companion

The creative mind of the scientist... in the hands of the craftsman

Introduced at this years' Audio Fair, the new Pye Mozart Companion 10-watt Speaker has been critically designed to match the outstanding performance and finish of the Pye Mozart Lowboy 10-watt Amplifier. It incorporates an 8" 15-ohm driver and a 4" 15-ohm tweeter mounted in a speaker enclosure of unique design. This is a totally enclosed folded isothermalized duct with the driver near one end, and an acoustic resistance coupling the closed end internally to control resonances. The crossover frequency is 7,000 c.p.s. The crossover network is inductive and capacitive.

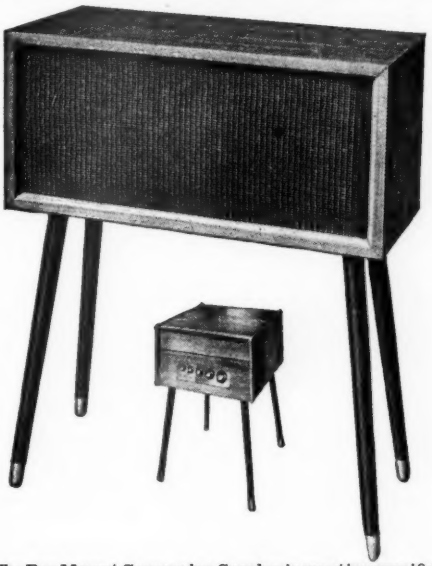

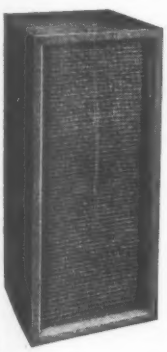

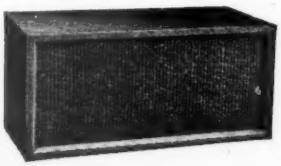

A pair of Mozart Companion Speakers is more than adequate for stereophonic systems. The design ensures any two such units would be perfectly matched.
The frequency response after bass equalisation at the amplifier is level to ± 4 dB. from 60 c.p.s. to 15,000 c.p.s. The response extends smoothly from 45 c.p.s. to 17,000 c.p.s.

The Pye Mozart Companion Speaker's exacting specification has been reached only through good design and hand-finishing by experts. The hand of the craftsman may also be seen in its presentation. All surfaces are attractively veneered in walnut and fitted with interchangeable rubber feet for horizontal or vertical mounting. The clean lines and practical dimensions are in keeping with its character as a high quality electronic instrument.
Dimensions: 25" x 11¼" x 10¼". 18" legs and mounting plates are optional. Weight: 22¼ lbs.

PYE HIGH FIDELITY SYSTEMS

Pye Pty. Ltd., Melbourne, Australia.

Svenska Pye A.B. Strindbergsgatan 32, Stockholm NO.

Deutsche Pye G.m.b.H., Berlin-Zehlendorf-West, Roonstrasse 2, Germany.

Pye Limited, Auckland, C.I. New Zealand.

Pye (Ireland) Ltd., Dublin, Eire.

Pye Limited, Mexico City.

Pye (Canada) Ltd., Northline Road, Toronto.

Pye Corporation of America, 1149 Raritan Avenue, Highland Park, New Jersey, U.S.A.

NEW SPRING LOADED TERMINALS

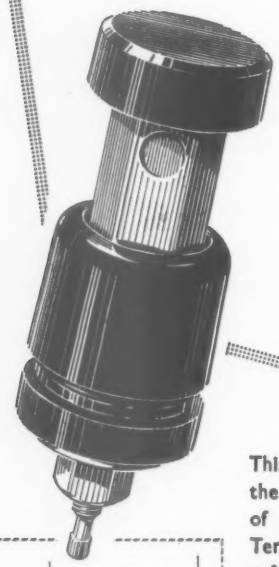

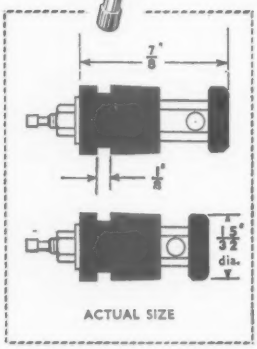

ACTUAL SIZE

This addition to the Painton range of Spring Loaded Terminals employs a form of construction which permits the unit to be very economically priced so as to appeal to the widest possible field of general purpose use.

PAINTON

PRICES

PART NO.	1—99	100—999	1,000 and over
316394 Black	1/4 each	1/3 each	1/2 each
316395 Red	1/4 each	1/3 each	1/2 each
316396 Green	1/4 each	1/3 each	1/2 each

Painton & Co. Ltd.
KINGSTHORPE NORTHAMPTON
Tel: 32354-5-6 Telegrams: 'Ceil, Northampton'

REMOTE CONTROL ?

We cannot emulate the mystics of the East but with

FLEXIBLE SHAFTING

We can operate any element requiring rotation or push-pull movement, or both, no matter if the controlled element is close to or at a distance from the control point.
We can operate from an accessible point, switches, valves and other electrical and mechanical devices located in inaccessible places.
We can, in fact, solve *your* problems.

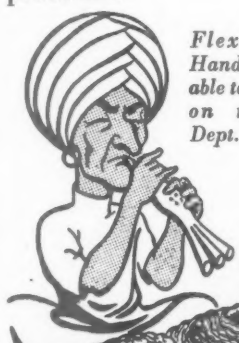

Flexible Shaft Handbook available to technicians on request to Dept. W.

THE S. S. White CO. OF GREAT BRITAIN LTD.
INDUSTRIAL DIVISION
BRITANNIA WORKS,
ST. PANCRAS WAY, LONDON, N.W.1.
Telephone: EUSton 5393 R.C.3

EMITAPE

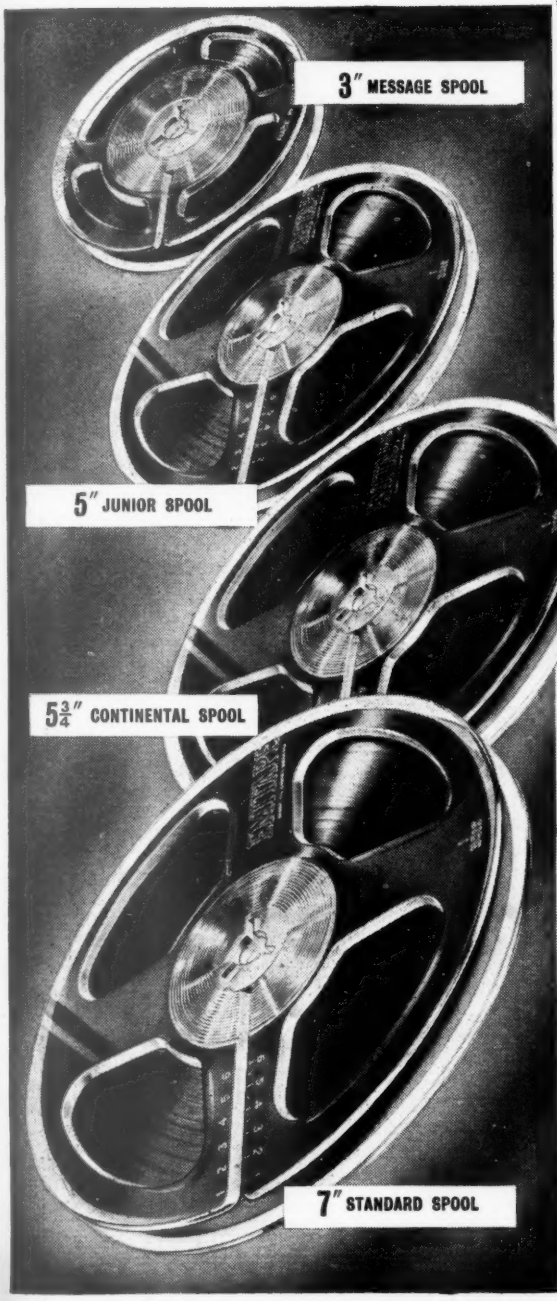

the magnetic recording tape with the highest technical standards

- High sensitivity
- Low noise level
- Low print through factor
- Anti-static
- Freedom from curl and stretch

"88" GENERAL PURPOSE "99" LONG PLAY

Type No.	Title	Size	Length Approx.	Price
88/3	"Message"	3" dia.	175'	7.6
99/3		3" dia.	250'	9.6
88/3N		3½" dia.	175'	7.6
99/3N		3½" dia.	250'	9.6
★88/6	"Junior"	5" dia.	600'	£1. 1.0
★99/9		5" dia.	850'	£1. 8.0
★88/9	"Continental"	5¾" dia.	850'	£1. 8.0
★99/12		5¾" dia.	1200'	£1. 15.0
★88/12	"Standard"	7" dia.	1200'	£1. 15.0
★99/18		7" dia.	1800'	£2. 10.0
88/18	"Professional"	8½" dia.	1750'	£2. 17.6
99/24		8½" dia.	2400'	£3. 12.6

★ *Also available in EMICASE — 2s. 6d. extra*

EMICASE

now available separately!

the polystyrene container that solves tape storage problems, protects spools from dust and allows easy identification of leader tapes.

7" – 4s. 0d; 5¾" – 3s. 6d; 5" – 3s. 6d.

E.M.I. SALES & SERVICE LTD (RECORDING MATERIALS DIVISION)

Hayes · Middlesex · Tel: SOUthall 2468

EB/B/14

Good clean high notes

The Super 3 provides a convenient and economical method of extending the upper frequency range of an existing loudspeaker system. The unusually smooth response is well maintained up to 17 kc/s and the useful output extends to over 20 kc/s.

A powerful Alcomax III magnet assembly and aluminium wire voice coil make the Super 3 sensitive enough for use with the most highly efficient loudspeakers, such as the Super 12/FS/AL.

Other features include foam surround, aluminium centre dome and a unique internal foam plastic centring system which eliminates the resonances associated with conventional spiders.

When mounted on a small open baffle facing upwards, a truly omni-directional treble source is achieved, and the open diecast alloy chassis allows useful rear radiation to be "splashed" into the room.

In the majority of cases a crossover network is unnecessary, and the Super 3 should be connected as shown below.

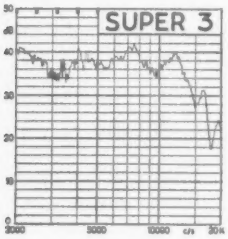

NB.—If the impedance of the mian loudspeaker is 2/3 ohms, the Super 3 should have the same impedance. The filter capacitor and volume control should then be 12 microfarads and 20 ohms respectively. Axial response of Super 3.

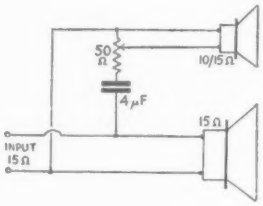

SUPER 3

2/3 ohms or 8/15 ohms. Flux Density 14,000 gauss. Total Flux 58,000 maxwells 1in. dia. Centre pole.

Aluminium Speech Coil Max. peak input 6 watts above 1,000 c/s.

PRICE

139/11

(including P.T.).

WHARFEDALE WIRELESS WORKS LTD
IDLE . BRADFORD . YORKS
Tel: Idle 1235/6. Grams: Wharfdel, Idle, Bradford

Wharfedale

Bullers CERAMICS FOR INDUSTRY

High quality material and dimensional precision are attributes of Bullers die-pressed products.

Prompt delivery at competitive prices.

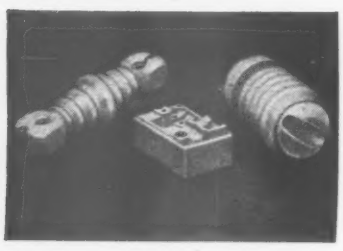

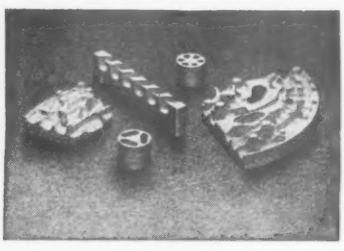

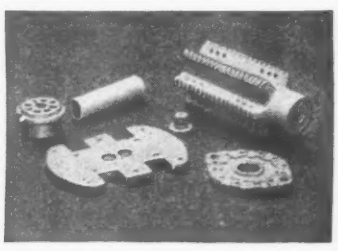

We specialise in the manufacture of—

PORCELAIN for general insulation

REFRACTORIES for high-temperature insulation

FREQUELEX for high-frequency insulation

PERMALEX & TEMPLEX for capacitors

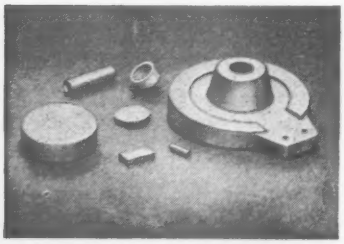

BULLERS LIMITED
MILTON · STOKE-ON-TRENT · STAFFS
Phone: Stoke-on-Trent 54321 (5 lines) · Telegrams & Cables: Bullers, Stoke-on-Trent
Ironworks: TIPTON, STAFFS Phone: Tipton 1691
London Office: 6 LAURENCE POUNTNEY HILL, E.C.4 Phone: MANsion House 9971

NEW! A 300-Mc/s VOLTMETER for £47

IMMEDIATE DELIVERY

The TF 1300 is the newest product of the Marconi voltmeter design programme. It has five a.c. measurement ranges, five d.c. ranges, and two ohms ranges. It is accurate, reliable, good to look at; and its price is low.

The indicating meter is direct reading on all ranges, for all measurements; no correction factors are necessary. Zero stability is of a high order; and only one zero setting is required for all a.c. or all d.c. ranges. Both a.c. and d.c. inputs are isolated from chassis.

All-in-all, the TF 1300 is an outstanding achievement. A skilful combination of performance and economy, it offers the highest value of any voltmeter in its class today. For full details, write for Leaflet G134.

VACUUM-TUBE VOLTMETER TYPE TF 1300

MEASURES A.C. up to 100 V 20 c/s to 300 Mc/s

MEASURES D.C. up to 300 V

MEASURES OHMS up to 5MΩ

★ *Please note that our Northern Office has been transferred from Hull to Harrogate, where extensive new premises provide improved service and showroom facilities for all our products.*

MARCONI INSTRUMENTS

AM & FM SIGNAL GENERATORS · AUDIO & VIDEO OSCILLATORS
FREQUENCY METERS · VOLTMETERS · POWER METERS
DISTORTION METERS · FIELD STRENGTH METERS
TRANSMISSION MONITORS · DEVIATION METERS
OSCILLOSCOPES, SPECTRUM & RESPONSE ANALYSERS
Q METERS & BRIDGES

MARCONI INSTRUMENTS LTD · ST. ALBANS · HERTFORDSHIRE · TELEPHONE ST. ALBANS 56161

London and the South: Marconi House, Strand, London, W.C.2. Tel: COVent Garden 1234. *Midlands:* Marconi House, 24 The Parade, Leamington Spa. Tel: 1408. *North:* 23/25 Station Square, Harrogate. Tel: 67455.

TC134

A near approach to professional standards

THE BRENELL MARK 5 TAPE RECORDER

is designed for the Hi-Fi enthusiast and incorporates all the features usually associated with equipment costing twice as much. 3 motors. 4 speeds. Frequency correction switch. Pause key. Rev. counter. Hi-Fi amplifier (can be used independently) with 4 watts output from large internal speaker. Facilities for playing back from external sound equipment. A semi-professional recording outfit by one of Britain's pioneers in this field at the amazingly low price of **64 gns.** Deck only **28 gns.**

BRENELL MARK 5 TAPE RECORDER

BRENELL HIGH QUALITY TAPE PRE-AMP.

Specially designed to provide the highest quality recordings and initial playback with Brenell or other decks using high impedance heads. Fre. response 3¾ i.p.s. 60 c/s to 6 Kc/s: 7½ i.p.s. 60 c/s to 10 Kc/s. 15 i.p.s. 50 c/s to 14 Kc/s., all ± to 3 db. Including most worthwhile features for home recording. **17 gns.** Optional power unit **£4/18/-.**

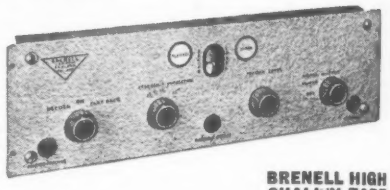

BRENELL HIGH QUALITY TAPE PRE. AMP.

Fully detailed leaflets of all Brenell tape recording equipment gladly sent on request.

Whatever your requirements we can usually supply all top quality Hi-Fi equipment from stock—CASH, EASY TERMS, PART EXCHANGE

CITY SALE & EXCHANGE LTD

The High Fidelity Specialists

93-94 FLEET STREET, LONDON, E.C.4 *Phone: FLEet Street 9391-2*

NEW CONDENSER FOR PRINTED CIRCUIT MOUNTING

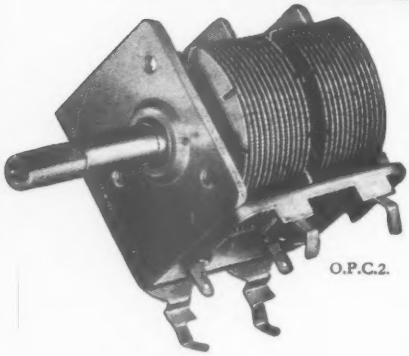

O.P.C.2.

Stator terminals and earthing tags for frame and rotor are formed to provide resilient plug-in mounting, for use in printed circuit technique. Provides instantaneous and accurate location which retains the component firmly until soldering is completed, no tags or wires to bend or clench.

Resilient stator tags make it possible to unsolder and remove if necessary. Trimmers are provided as standard (2-25pf). Specification otherwise same as for "O" gang.

It's Reliable if it's made by Jacksons.

REGISTERED TRADE MARK

JACKSON BROS. (LONDON) LTD KINGSWAY · WADDON · SURREY

Telephone Croydon 2754/5

GOODMANS

for High Fidelity

The **NEW** **IB3**

3-Way High Fidelity Loudspeaker System

Small Size BIG performance

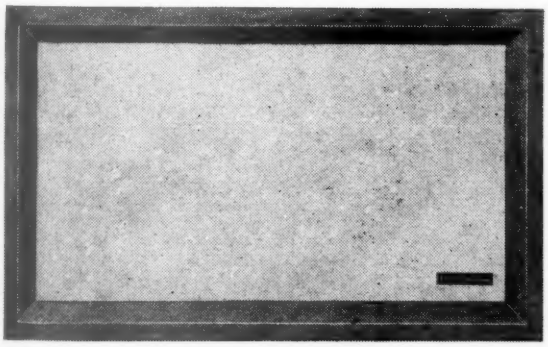

Q. What is the IB3?

A. *It is a complete FULL FREQUENCY RANGE* (35 c/s.-16,000 c/s.) *3-way High Fidelity Loudspeaker System, whose Enclosure measures only 24" x 12¼" x 14½".*

Q. How is it better than any other small system?

A. *There is no compromise on bass performance because of small enclosure size. The 12" bass unit is designed and built solely for a rigid enclosure of this size. The mid-range and high frequency units (both pressure driven and horn loaded) are the finest of their type.*

Q. How has this been achieved?

A. *This bass unit has a unique newly developed triple suspension system operating in conjunction with pneumatic air control. Perfect control is maintained by a very efficient* 22 lb. magnet system.

Q. What about power handling capacity?

A. *The IB3 will handle a maximum input of* 25 watts, *speech or music, without distress or distortion.*

Q. Where can it be placed?

A. *On a bookcase, in a room divider, on a table, window ledge, on the floor, in fact, in any convenient position.*

Q. Briefly then—?

A. *Briefly, this is a quart in a pint pot.*

Free on request: 1958 High Fidelity Loudspeaker Manual. Fully describes all Goodman's High Fidelity Products.

GOODMANS

...Europe's largest Manufacturers and the World's largest Exporters of High Fidelity Loudspeakers

GOODMANS INDUSTRIES, LIMITED,
AXIOM WORKS, WEMBLEY, MIDDLESEX.

WEMbley 1200 (8 lines) Grams: Goodaxiom, Wembley, England.

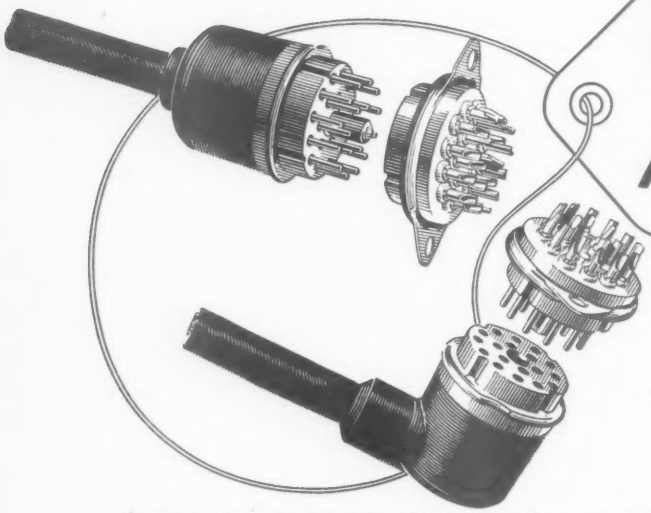

McMURDO Potted Pakonectors

18 WAY

★ No cover and cable clamp worries. We connect your cable to plug or socket and pot the assembly in polythene. ★ 18 connections in less than 1 inch diameter. ★ Standard B9A valveholder mounting. ★ Nylon loaded P.F. mouldings. ★ Cadmium plated or gold plated pins and contacts.

Send for full details to:—

THE McMURDO INSTRUMENT CO. LTD., ASHTEAD, SURREY. Tel: ASHTEAD 3401

MPC19

ABIX STEEL PARTITIONING *for* OFFICE or FACTORY

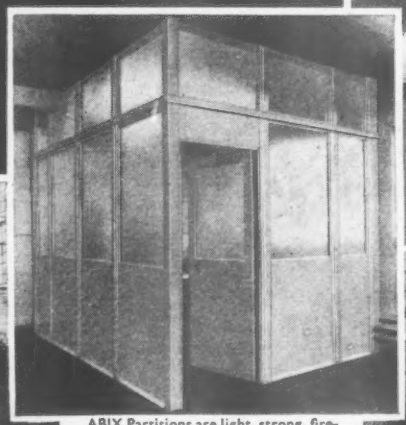

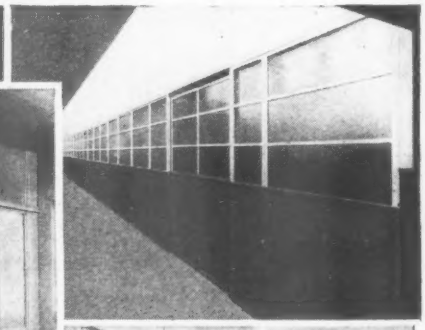

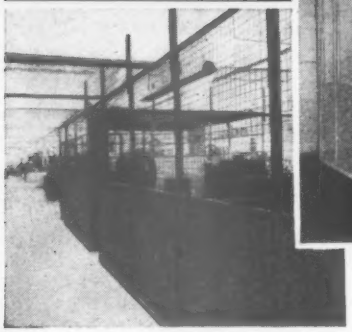

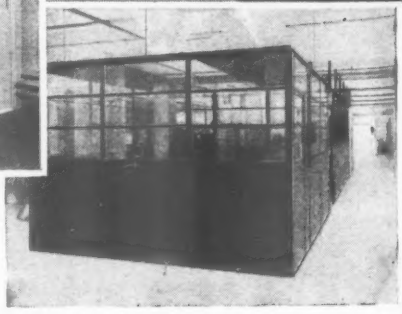

ABIX Partitions are light, strong, fire-resisting and easy to erect. Manufactured in standard units for quick installation, easy removal or extension to existing screens. We will be pleased to help and advise you on any partitioning problem.

OTHER ABIX PRODUCTS: Steel Cycle Stands, Clothes Lockers, Material Racks, Slotted Angles (Junior, Universal, Senior), Car and Cycle Shelters, Tool Lockers, Adjustable Steel Shelving.

please write for fully illustrated Catalogues to:

ABIX (METAL INDUSTRIES) LTD.

STEEL EQUIPMENT FOR OFFICE AND FACTORY

Phone: Molesey 4361/3 **POOL ROAD, EAST MOLESEY, SURREY** *Grams: Abix, East Molesey*

what's so **Special** about

VITAVOX?

There are many makes of direct radiator loudspeakers. The design principles may be considered stabilised and the published specifications frequently give little assistance in distinguishing between the ordinary and the first-rate. The features which place the Vitavox AK120 Series Loudspeakers in an exclusive category are the result of twenty-five years of continuous and conscientious development of the highest grade of precision audio components which has made Vitavox the choice wherever quality of performance, adherence to specification and utmost reliability are considered factors of more importance than low initial cost.

The range is comprehensive and includes models especially designed for horn loading. As a single unit reproducer, as part of a multi-channel system or as the foundation of such a system to which other components can be added at a later date, there is no more prudent choice than a Vitavox AK120 Series Loudspeaker.

Full details on request from:

VITAVOX LIMITED

Westmoreland Road, London, N.W.9

Telephone: COLindale 8671

—for Industrial Research

A simultaneous dual-channel Tape Recorder

Series 3C/FN

THE Ferrograph Series 3C/FN, illustrated here, is a simultaneous dual-channel instrument, using staggered heads, which offers special facilities to those engaged in medical, aeronautical and other scientific research. Besides the normal ability to record simultaneously time pulses on one track and intelligence on the other, it becomes immediately obvious that many forms of comparative measurement, stereophonic sound, or indeed, any two activities capable of being translated into electrical phenomena (within its frequency and phase shift limitations) can be recorded simultaneously and replayed when required. Thus, the scope of such an instrument, when used for Research purposes, is almost unlimited.

Full details and specification of this and other Ferrograph Tape Recorders will be sent on request.

The Incomparable

Ferrograph

BRITISH FERROGRAPH RECORDER CO. LTD., 131 Sloane Street, London, SW1. Tel: SLOane 2214/5 & 1510

A Subsidiary of Wright & Weaire Limited

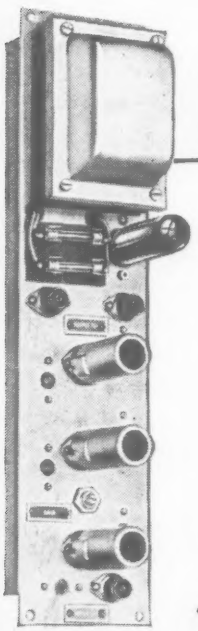

TELENG *Experience proudly presents*

DOUBLE CHANNEL AMPLIFIER TYPE U30 D

A Television Boost Amplifier for

SHOWROOMS REPAIR SHOPS or COMMUNAL AERIAL SYSTEMS

Gain 30 db on each of any two channels to your choice in Bands 1 and 3.

Internally combined output up to 150 m/V each channel for up to 40 outlets.

Net Trade Price £15

For V.H.F.—the U30 FM at £14 net trade, matches and couples to the U30 D without external combining units and losses.

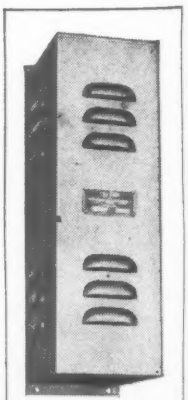

HOUSED IN STRONG METAL CASE

TELEFUSION ENGINEERING LTD.

ONE OF THE TELEFUSION GROUP OF COMPANIES

TELENG WORKS, CHURCH ROAD, HAROLD WOOD, ROMFORD, ESSEX

Tel.: Ingrebourne 2901

A.T.E + MARCONI

Combined Operations

The complexity of modern radio-multichannel systems involving hundreds of telephone channels has brought about a collaboration between the two leading specialist organizations in the field—Marconi's in radio, and A.T.E. in carrier transmission.

This completely unified approach to development, systems planning, supply, installation, maintenance of equipment and training of personnel covers radio-multichannel systems in the V.H.F., U.H.F. and S.H.F. frequency bands all over the world.

Full information may be obtained from either:
MARCONI'S WIRELESS TELEGRAPH COMPANY LIMITED, CHELMSFORD, ESSEX, ENGLAND.

or AUTOMATIC TELEPHONE & ELECTRIC CO. LTD., STROWGER HOUSE, ARUNDEL STREET, LONDON, W.C.2

S.C.R. 399 WHOLE INSTALLATION

INCLUDING SHELTER H.D. 17A & 10 KW. PETROL GENERATOR P.E. 95G AVAILABLE

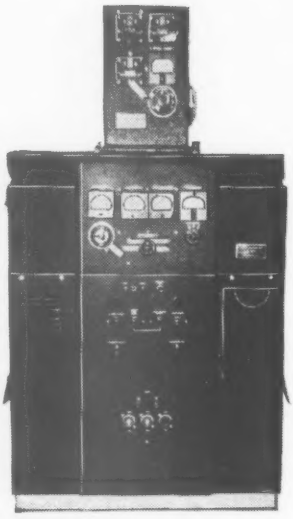

Also available separately

TRANSMITTER B610E

Frequency range 2 Mc.-18 Mc. Three pretuned channels selected by switch. Frequency control regulated either by manually tuned MASTER OSCILLATOR or crystal controlled oscillator.

Power output 450 w. telegraph, 350 w. telephone.

Power supply 120 v. A.C. 50/60 cycles special auto-transformer 120/220 v' made by Hallicrafters can be supplied additionally.

Tube complement oscillator 6V6, doubler or buffer 6L6, intermediate amplifier 807 (2). Power amplifier 250 TH. HV Rectifier 866A (2). Voltage regulator VT139(3). Audio drive 2A3(2). Modulator 100TH(2). Rectifier 5Z3(2).

Complete with Speech amplifier, aerial tuning unit, tank coils, tuning units microphone, key, connecting cables.

We guarantee full supply of all replacement parts for a minimum of 5 years after purchase.

P.C.A. RADIO

Offices and Works

BEAVOR LANE, HAMMERSMITH, LONDON, W.6

Telephone: RIV 8006/7

AVOMINORS in leather case, with leads, fully tested. **£5/10/-**. Packing and Carriage 2/6.

BRAND NEW ORIGINAL SPARE PARTS FOR ARS8 RECEIVERS.

I.F. TRANSFORMERS 1st, 2nd, 3rd, 4th (for type D) **12/6** each or complete set of 6, **60/-**.
I.F. Transformers. Crystal Load, **12/6** each.
Plates escutcheons (for D and LF), **15/-** each.
Dials (for type D), **10/-** each.
Logging dial (for D and LF), **10/-** each.
Filter Chokes (for D and LF), **22/6** each.
Output Transformers (for LF), **30/-** each.
Crystal phasing (D), **2/6** each.
Antenna trimmers (LF and D) **2/6** each.
Filter Condenser 3×4μF, **£2/10/-**.
Condensers 3×.25μF (D and LF), **2/6** each.
3×.01μF (D and LF), **2/6** each.
RF Antenna inductors (D and LF), **7/6** each.
Mains transformers (LF), **£3** each.
Medium knobs (for LF and D), **2/6** each.
Small knobs (for LF and D), **2/-** each.

INTERMEDIATE FREQUENCY TRANSMITTER TMJ (cw and phone) 200/400 kc/s, 150 w. output, built-in P.S.U. Manufactured by Bendix Radio Corp. Meas. 6ft. 4in. × 2ft. 6in. × 2ft. 2in. Bargain price without valves **£45.** Transport in U.K. £7/10/-.

ROTARY CONVERTOR UNIT. Input 11.5-12.5 v. D.C. Output 300 v. 200 mA. D.C. **30/-**, postage and packing 15/-.

R.109A RECEIVERS. Covering 2-12 Mc/s. 6 v. D.C. New and tested, **£4/5/-**. Carriage paid.

SLIDING RESISTANCE. 2 barrels, rotary action, 0.26 ohms, 20 amp. **12/-**, post and packing 3/6.

HIGH RESISTANCE HEADPHONES. 4,000 ohms. Brand new, ex-W.D., boxed, Type C.H.R., **8/6**, D.H.R., **12/-** per pair.

LOW RESISTANCE HEADPHONES. Brand new, Type C.L.R., **5/-**. D.L.R., **6/6** per pair.

VALVES

1D8, **4/-**, 3B24 **3/-**, 5U4G **6/6**, 6AG7 **8/-**, 6AK5 **4/6**, 6B4G, **4/6**, 6J6 **3/6**, 6K7GT **6/-**, 6K8GT **8/-**, 6SJ7 **7/6**, 6SL7GT **5/-**, 6SN7GT **5/6**, 6SQ7 **7/-**, 53A **3/-**, 446A **15/-**, 813 (RCA) **80/-**, 955 **1/6**, VR105-30 **5/-**.

AMPERITE RELAY VALVE 5 No. 4 G **7/6.**

C.R. TUBE 5CP1 **42/6.**

CRYSTALS 1N21 **2/-**, 1N21B **5/-**, 1N22 **7/6.**

All valves tested and guaranteed. Postage and packing 6d. per valve.

MODULATION TRANSFORMERS (U.S.A., Collins), primary imp. 6,000 ohms. C.T., secondary 6,000 ohms, 20 W., **9/6** each.

MICROPHONE TRANSFORMERS. Balanced input 30 or 250 ohms, U.S.A. manufacture, **7/6.** Post and packing 1/6.

813 CERAMIC VALVEHOLDERS 3/- each. P. & P. 1/6.

COMPLETE V.F.O. UNIT from TX53. Freq. range in 4 switched bands from 1.2-17.5 mc/s. Two V.T 501s as oscillator and buffer, 807 as driver, two S130s as voltage stabilizers. Output sufficient to drive two 813s in parallel. Slow motion drive directly calibrated in mc/s. Provision for crystal control, metering of buffer and driver stage. Power requirements 400 v. and 6.3 v. D.C. Can also be used as low power transmitter. In excellent condition with valves and circuit diagram. **£5.** P. & P. 15/-.

AMERICAN HANDY TALKIE. Type B.C. 611, including two operating crystals (5-6 Mc/s. band), **£19/19/-**. Postage and packing 10/-.

UNIVERSAL CALL 10 LINE TELEPHONE SWITCHBOARD. as new, fully tested with all accessories.
BC375, complete with T/U, PE73, etc.
BC221, Frequency meters.
Prices on application.

CONDENSERS, RESISTORS, COILS, TRANSFORMERS, etc. Very large selection in stock. BUZZERS SIGNALLING TRAINING. Bakelite or wooden base, adjustable buzzer key. New **7/6.** P. & P. 2/-.

MORSE KEYS, 8 amp. New **2/6.** P. & P. 1/-.

TANNOY LOUDSPEAKERS. New, **£1.** P. & P. 3/-.

P. C. RADIO LTD.
170, GOLDHAWK RD., W.12 SHEpherds Bush 4946

PERSONAL CALLERS WELCOME

"... a new approach to better listening..."

to satisfy the most discriminating...

NATIONAL RADIO SHOW

SEE it on STAND No. 30

HEAR it in DEM. ROOM 410

The Celestion "Colaudio" Loudspeaker with a substantially level response from 30-15,000 c.p.s., embodies two distinct techniques in order to provide a satisfactory answer to the ever widening demand for truer reproduction.

Utilising a 15in. direct radiator loudspeaker specially designed to produce the lower frequencies, particular features of this bass unit are the 3-inch Voice Coil and dustproof suspension of the anular type, permitting free cone excursion whilst reducing lateral movement to a minimum.

The high frequency reproducer incorporates two direct radiator pressure type units, mounted in column form within the cone of the bass radiator. This arrangement enables the higher frequencies to be dispersed over a wide area in the horizontal plane with a narrow vertical lobe, minimising unwanted reflections and improving efficiency.

The vertical position of this column can be adjusted to suit the position in which the loudspeaker is mounted in the cabinet.

The main housing is cast, finished in black crackle with silver trim.

CELESTION Colaudio

Full technical details available direct from:

Rola Celestion Ltd. THAMES DITTON, SURREY, ENGLAND. *Emberbrook 3402/6.*

MAXI-Q REGD.

TRANSISTOR COMPONENTS

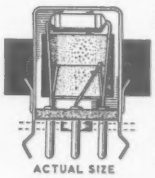
ACTUAL SIZE

IFT.13, MINIATURE 1st and 2nd I.F. TRANSFORMER, 7/6 each.
These transformers are wound in ferrite pot cores with an adjustable core for tuning. The aluminium screening can measures 17/32in. × 11/16in. high and is provided with two fixing clips. Nominal frequency: 470 kc/s. Q=110.

IFT.14, MINIATURE 3rd I.F. TRANSFORMER, 7/6 each.
Construction and dimensions as IFT.13. Nominal frequency: 470 kc/s. Q=130.

TOC.1, MINIATURE TRANSISTOR MEDIUM WAVE OSCILLATOR COIL, 7/6 each.
Construction and dimensions as IFT.13. For use with FSA.1.

FSA.1, MEDIUM WAVE FERRITE SLAB AERIAL, 7/6 each.
Wound on a ferrite slab with easily adjusted inductance for ease of alignment. Nominal coverage: 540-1550 kc/s. Overall dimensions: 4in. × 7/8in. × 3/16in. Tuning condenser; Jackson "00" gang with internal screen. Aerial section: 208 pF. Oscillator section: 176 pF. Padder: 200 pF.

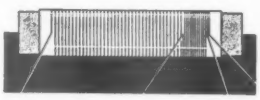

A suggested circuit diagram is supplied with each component or may be obtained separately at 3d. per copy.
A printed circuit board is in course of preparation and all components will be available in 10 weeks.
GENERAL CATALOGUE covering technical information on full range of components, 1/- in stamps.
TRADING TERMS for direct postal orders, C.W.O. plus appropriate postal charge. Please send S.A.E. with all enquiries.

DENCO (CLACTON) LTD. (Dept. W.W.), 357/9 Old Road, Clacton-on-Sea, Essex

STOP PRESS: TREBLE LIFT INDUCTOR FOR THE MULLARD TYPE "C" TAPE AMPLIFIER. Wound in ferroxcube pot core assembly. Price 22/6.

M. R. SUPPLIES, Ltd.

Well known for the past twenty-three years as suppliers of first-class material at attractive prices. Prompt delivery—careful packing. Satisfaction assured. Prices nett.
MEASURING INSTRUMENTS—some special offers—early application essential.
MAINS VOLTMETERS, best type, rectifier m/coil, even scale, dead-beat, 3½in. round flush panel mount, 0/250 v. A.C., 35/- (despatch 1/6). **D.C. AMMETERS**, 0/1.5 Ampere, 3½in. f.p.m. round, first-grade m/coil by E.T. Co., 35/- (des. 1/6). Small latest model E.T. Co., Microammeters, 2in. f.p.m. round, F.G. m/coil, 0/500 Microamps D.C., 22/6 (des. 1/-). **B.P.L. INSTRUMENTS**—will our regular customers please note that at the moment we have a good selection of sensitive meters, side and centre zero, available from stock—please enquire.
HIGH DUTY AIR BLOWERS, 220/240v. 50c 1 ph. Powered with BTH. (or Bull) induction motor, 0.4 H.P. Delivery 1,000 c.ft/min. Overall length 19in., width 16in., height 16in. Inlet 6½in. dia., outlet 5 x 4in. Weight approx. 56 lb. Very limited supply at £12/17/6 each (des. U.K. 15/-).
SPACE HEATERS—safe black heat. G.E.C. units for use on 220/240v. consuming 300-watts. Heavy spiral element fully enclosed in high-thermal efficiency box container, 12in. high by 7in. by 7in., suitable for greenhouses, garages and industrial uses, 35/- (des. 5/-).
SHADED POLE MOTORS (for very silent running) 200/250v. AC.-Delco super model, fan cooled, body 4½ by 3½in. shaft proj. 1½in., 1425 r.p.m., torque 600 grm/cms., perfect for tape recorders, stirrers, cooling fans, etc., 42/6 (des. 2/6). Also Met-Vick, 1200 r.p.m. with mounting flange, 27/6 (des. 2/-).
INDUSTRIAL EXTRACTOR FANS, powered with totally enclosed E.E. Co. 1/10th H.P. Motor, 220/250 v. 50 c. 1 ph (induction), in circular mounting frame 22in. dia. with 15in. 6-bladed impeller, ball-bearing, silent running, brand new first-class units, £11/17/6 (des. U.K. 7/6).
SYNCHRONOUS TIMER MOTORS, 200/250 v. 50 c. Compact units 2½ x 1½ x 1¾in. with 1in. shaft proj. Self-starting, high torque, 6 r.p.m. Suitable also for display turntables, 57/6 (des. 1/6). Also Sangamo 8.7 units, 200/250 v. 50 c. (synch.) self-starting. Final speeds available from stock: 1 r.p.m., 1 r.p.h. and 12 r.p.h., any one 37/6 (des. 1/6).
SYNCHRONOUS TIME SWITCHES (Sangamo) 200/250 v. 50 c. In compact black plastic housing 4in. dia. by 3½in. deep, providing up to 3 on-off operations per 24 hours, with day-omitting device (use optional). Capacity 20a mps., therefore suitable for tape recorders, radio, immersion heaters, electric fires etc. One of our most popular offers at £5/8/6 (des. 2/-).
EXTRACTOR FANS. Our huge sales of these confirm that this is the best offer being made of such units. Same high quality, same low price which has been maintained for the past ten years. 200/250 v. A.C., Induction motor, silent running, no interference. With mounting frame and back grille, ready for easy installation, with 8in. impeller, 12,000 c.ft./hr. £5/5/-, with 10in. impeller, 15,000 c.ft./hr. £5/12/6 (des. either 2/6).
NEON INDICATORS (Philips) 230/240 v. A.C., with B.C., 2/6 each or 24/- doz.
DELAY RELAYS (Western Elec.) 24 volt, 250 ohms coil, 2-pole, with precision adjustable delay action (max. 3 secs.). On base 4½ x 2½in. Brand new, boxed, 12/6 (des. 1/-). Also Londex ML/AC RELAYS, 200 volts A.C. coil, 2-pole C.O., 6 amps., 29/6 (des. 1/-).
SEWING MACHINE MOTOR OUTFITS complete. We are still selling these at only 26/15/- (des. 2/9). Details on request.
F.H.P. GEARED MOTORS—our great speciality. IMMEDIATE DELIVERY of many models and ratings. Series wound variable speed and capacitor/induction constant speed models, all reversible. Final speeds 1 r.p.m. to 840 r.p.m. and final torque up to 75 lb./in. Within those limits we offer you the best service in the country. Please send for our list GM.357, giving full details.
We are stockists of Stuart Pumps, BPL Measuring Instruments, Philips Variable Transformers—Immediate deliveries.

M. R. SUPPLIES, Ltd., 68, New Oxford Street, London, W.C.1
Telephone: MUSeum 2958

EDDYSTONE COMMUNICATION RECEIVERS

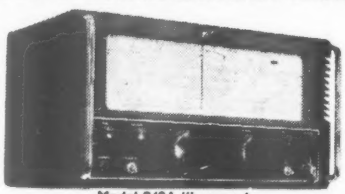

Model 840A illustrated
Cash Prices and Statutory Terms

Model	Cash Price	Deposit	8 Monthly Payments of
820	£31 18 0	£3 14 6	£3 14 6
870	£34 16 0	£4 1 6	£4 1 6
840A	£55 0 0	£6 8 4	£6 8 4
750	£78 0 0	£9 2 0	£9 2 0
888A	£110 0 0	£12 16 8	£12 16 8
680X	£120 0 0	£14 0 0	£14 0 0

Cash price if paid in 6 months by Bankers' order.
Carriage paid per passenger train.

Model 840A is for A.C. or D.C. 110/250 v.; 750 and 680X 110/240 v. A.C. These sets are the choice of the discerning professional and amateur users. Descriptive literature gladly forwarded.
Latest EDDYSTONE Component Catalogue 1/-.

HP RADIO SERVICES LTD.
The Eddystone Specialist

55 COUNTY ROAD, LIVERPOOL, 4
Telephone: AINTREE 1445 ESTAB. 1935
CALL US ON TELEX. 62-244

THE WAYNE KERR COMPONENT BRIDGE B.521

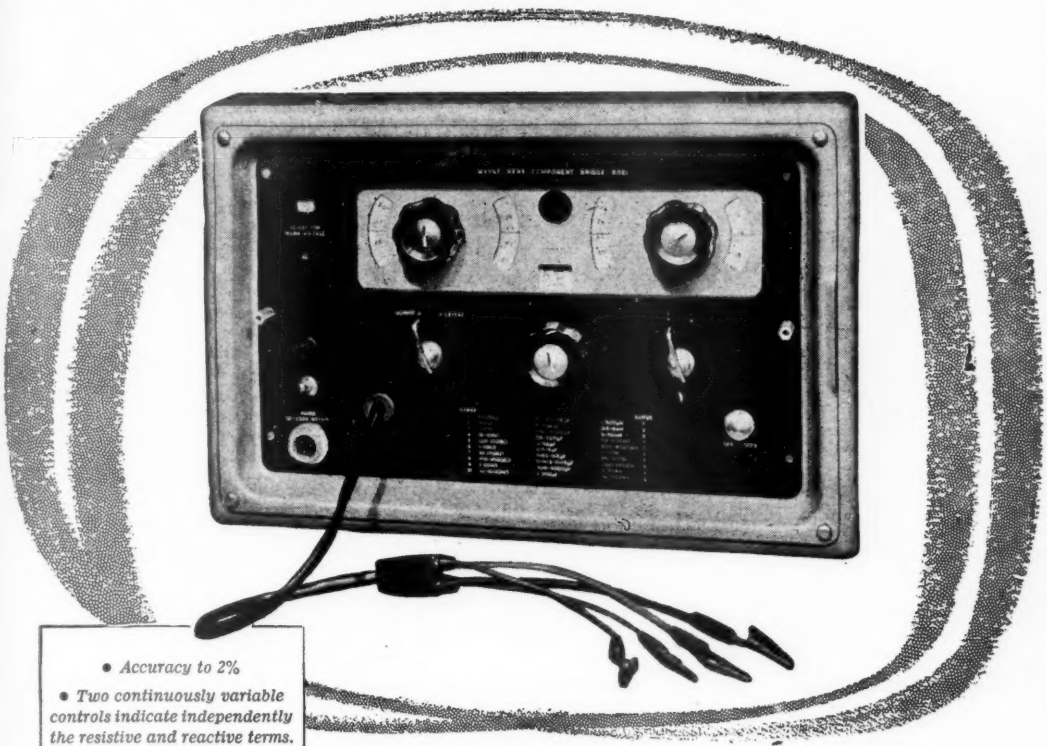

- *Accuracy to 2%*
- *Two continuously variable controls indicate independently the resistive and reactive terms.*
- *Two, three or four-terminal measurements over an extremely wide range.*

Specification

Capacitance: 1 pF to 5F.
Inductance: 1 μH to 0.5 MH.
Resistance: 1 m Ω to 1000 M Ω.
Accuracy 2%
Power Supply: 110/125 and 200/250v.
Dimensions: 17" x 7" x 11½" high.
Weight: 25 lbs. approx.
Price: £100.

Exceptional Range covers 1 picofarad to 5 farads
1 microhenry to infinity 1 milliohm to 1000 megohms

Operating at mains frequency, the B.521 has an effective ratio of 10^{13}: 1 and is intended for the rapid and direct measurement of virtually all components and networks likely to be encountered in electronic apparatus, whether in the laboratory or the service workshop.

The usual three-terminal facility associated with bridges of this design permits the measurement of complex impedances in situ, that is to say, an impedance between two terminals can be determined regardless of the presence of other impedances between either or both terminals and a third point. A simple rearrangement of the test leads covers four-terminal measurements when required.

The low impedance ranges together with the in situ facility make it possible to measure switch contact resistance, dry joints, earth bonding efficiency, high value electrolytics, etc.

WAYNE KERR

Radio Frequency Bridge
Type B601

A wide range transformer ratio-arm bridge for the measurement of resistance, capacitance, inductance and complex impedance between 15 kc/s and 5 Mc/s. Impedances between any two terminals of a three terminal network can be measured. Price £140.

Video Oscillator
Type O.22B

A portable instrument covering the range 10 kc/s to 10 Mc/s with an output of +10 dbs to —50 dbs on 1 volt p. to p. amplitude stabilised to 0.5 db over its full frequency range. Price £175.

THE WAYNE KERR LABORATORIES LIMITED, ROEBUCK ROAD, CHESSINGTON, SURREY. TELEPHONE: LOWER HOOK 1131

"YOU CAN RELY ON US"

Stockists of all Radio and Electronic components for manufacturers, laboratories, Educational authorities and the amateur

THE NEW AVO MULTIMINOR
Price £9.10.0 Leather Case 32/6
or 9 payments of 23/3
or Deposit 63/4 and 6 payments of 22/2

COSSOR 3v 3W Hi-Fi Amplifier Kit
Complete with twin speakers
Beautifully kitted and printed circuit.
£9.15.0 or Deposit 65/- and 6 months at 23/4
or Deposit 23/10 and 8 months at 23/10

ALL OTHER AVO INSTRUMENTS IN STOCK

RADIO SERVICING COMPANY

82, SOUTH EALING ROAD, LONDON, W.5 *Telephone : EAL. 5737*

Next to South Ealing Tube (TURN LEFT) 9 to 6 p.m., Wednesday 1 o'clock.

BROOKES *Crystals*

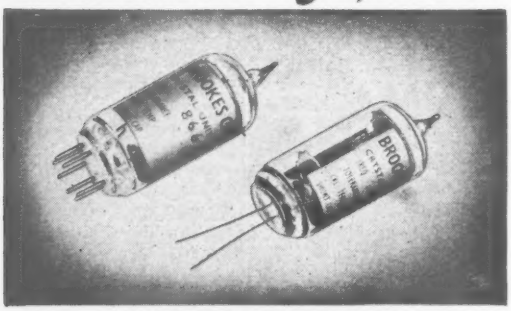

mean DEPENDABLE frequency control

● *Illustrated above are two Type G Crystal units from a range covering 111 kc/s to 500 kc/s, and 3 Mc/s to 20 Mc/s.*

ALL Brookes Crystals are made to exacting standards and close tolerances. They are available with a variety of bases and in a wide range of frequencies. There is a Brookes Crystal to suit your purpose—let us have your enquiry now.

BROOKES

Brookes Crystals Ltd.
Suppliers to Ministry of Supply, Home Office, B.B.C., etc.
LASSELL STREET, GREENWICH, S.E.10.
Phone: GREenwich 1828 *Grams:* Xtals, Green, London

Chapman

Elegance and simplicity of styling coupled with outstanding performance the keynotes of the 105 Tranquillo amplifier. The compact dimensions of 12in. by 4¼in. by 8¼in. have been achieved without sacrifice to quality, and the high-grade components operate with a wide margin of safety, most conducive to long life and long-term stability. In fact, the 10 watt push-pull output stage, feeding a grain-orientated Partridge transformer, reduces harmonic and intermodulation distortion to a very low level indeed, and the 105 is particularly suitable for use with all electrostatic loudspeakers. The Tranquillo amplifier is £29 18s 0d complete.

The FM 91 Tuner with a similar presentation is available at £23 10s 0d, and both units can be shelf mounted or cabinet mounted.

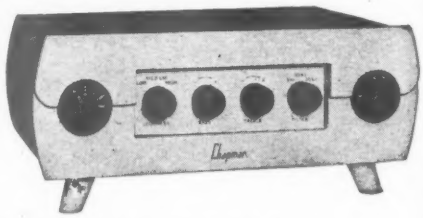

Full specification from your hi-fi dealer or:

C. T. Chapman (Reproducers) Ltd.
Chapel Lane, High Wycombe, Bucks.
Telephone: High Wycombe 2474

Accurate tuning at a glance

This monitor unit has been designed to facilitate accurate and speedy receiver tuning. The unique "V" presentation on the cathode ray tube provides a continuous, and instantaneous, presentation of any tendency towards frequency drift. The receiver can be retuned without interruption of the circuit.

A.T.E. Cathode Ray Monitor type 1 (C.R.M.1) for Frequency Shift Terminals

The A.T.E. C.R.M.1 can be used:—

- For tuning and monitoring of receivers with normal traffic in progress.
- For instantaneous presentation of frequency drift.
- To assess conditions on radio circuits by examination of the audio output of receivers.
- As an orthodox oscilloscope.

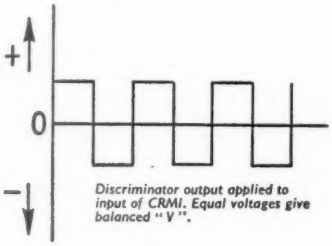

Discriminator output applied to input of CRM1. Equal voltages give balanced "V".

For full details write to:—

AUTOMATIC TELEPHONE & ELECTRIC CO. LTD.

STROWGER HOUSE, ARUNDEL STREET, LONDON, W.C.2. Telephone: TEMple Bar 9262. Cablegrams: Strowgerex London. Strowger Works, Liverpool, England.

AT14831

WEYRAD P.50 TRANSISTOR COILS AND I.F. TRANSFORMERS

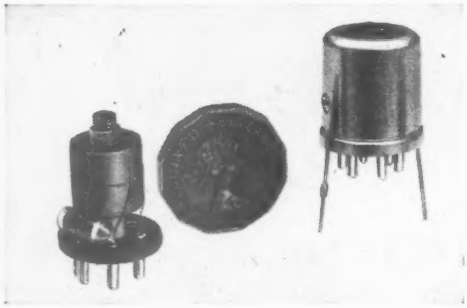

P50/1AC M.W. OSCILLATOR COILS.
TUNING RANGE (115pF SWING) ..... 545—1550 Kc/s
NOMINAL " Q " (IN CAN) 120
PRICE ..... 5/4 EA.

P.50/2CC 1st and 2nd I.F. TRANSFORMER
OPERATING FREQUENCY ..... 470 Kc/s
FIXED TUNING CAPACITY ..... 250 pF.
NOMINAL " Q " (IN CAN) 150
PRICE ..... 5/7 EA.

P.50/3CC 3rd I.F. TRANSFORMER
OPERATING FREQUENCY ..... 470 Kc/s
FIXED TUNING CAPACITY ..... 250 pF
NOMINAL " Q " (IN CAN) 170
PRICE ..... 6/- EA.

GIANT PERFORMANCE IN MIDGET CANS—ONLY 11/16" DIAMETER BY 3/4" HIGH

SPECIALLY DESIGNED FOR USE WITH THE LATEST TYPES OF TRANSISTORS. CAN BE USED WITH PRINTED CIRCUITS OR CONVENTIONAL CHASSIS. SUPPLIED COMPLETE WITH CONNECTION AND CIRCUIT DETAILS FOR A 6-TRANSISTOR LONG AND MEDIUM WAVE RECEIVER WITH PUSH-PULL OUTPUT.

SUITABLE FERRITE ROD AERIALS AND DRIVER TRANSFORMERS WILL BE AVAILABLE SHORTLY.

WEYMOUTH RADIO MFG. CO. LTD., CRESCENT STREET, WEYMOUTH, DORSET

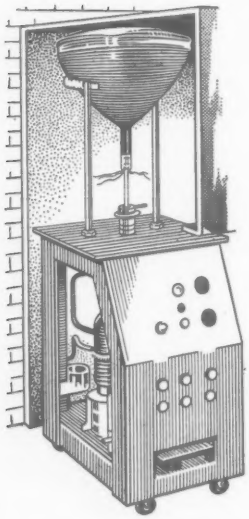

Cathode Ray Tube PUMPING UNIT

Complete with Baking Oven and Vacuum Reading before Seal Off.

VACWELL ENG., CO., LTD.

VACWELL ENGINEERING CO. LTD.

WILLOW LANE, MITCHAM, SURREY.

Telephone: MITcham 1177

Specialists in the design and manufacture of VACUUM EQUIPMENT

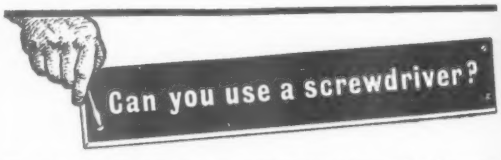

Then save 37% of standard manufacturing costs with this superb new range of ready-to-assemble Hi-Fi Cabinets. No gluing, no drilling, no polishing—no *mess*. Each cabinet comes to you factory-fresh in its own carton, complete with screwdriver, screws, and instructions for simple ten-minute assembly.

The RONDO range

Record Cabinet, Capacity 200 Records, Price £7.19.6.

Hi-Fi Equipment Cabinet (*illustrated*), Price £8.19.6.

Speaker Cabinet, Price £8.19.6.

See them at the RADIO SHOW STAND 104.

Write for full details and nearest stockist to:

RECORD HOUSING (Dept. W.W.88)

BROOK ROAD · LONDON, N.22 · BOWes PARK 1478/8

Build your own HI-FI

–with an entirely *NEW* range of Hi-Fi units and cabinets!

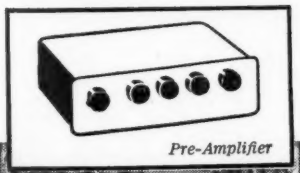

Pre-Amplifier

Amplifier

AM/FM Tuner

Tape Recorder

Record Player

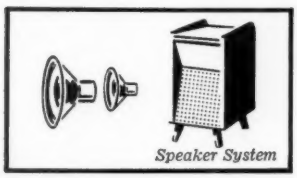

Speaker System

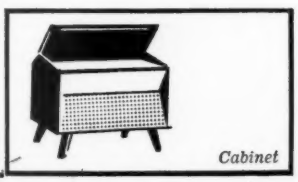

Cabinet

Imagine the pleasure of having this magnificent Hi-Fi equipment in its beautiful contemporary style furniture for your home . . . and experiencing an entirely new realism in sound reproduction. Yet the Emistructor Hi-Fi will save you money and give you all the *extra* fun and satisfaction of building it yourself—and being able to service and maintain it afterwards. Special instruction manuals guide you at each stage and teach you all about the equipment in simple terms as you build. No skill or experience is needed—only a few simple tools.

Emistructor equipment is made to the highest quality standards and is a product of E.M.I.—world famous for sound recording and reproducing equipment.

There is a wide variety of equipment and cabinets at different price levels to suit individual tastes and requirements. The range varies from a complete HI-FI installation with separate speaker enclosures to a simple all-in-one compact system for those with more modest requirements. All equipment is suitable for stereo or non-stereo reproduction of records. Full details and complete specifications will be sent with our free Brochure.

FREE BROCHURE–POST TODAY

To: "Emistructor," (Dept. H.F. 127),
43, Grove Park Road, London, W.4.
Please send, without obligation, details of your Hi-Fi equipment.

NAME _____

ADDRESS _____

_____

1C126 Aug., 1958

EMISTRUCTOR

Associated with one of the World's largest recording organisations comprising—

"HIS MASTER'S VOICE"

CAPITOL · COLUMBIA

PARLOPHONE · MGM · etc.

C

DEPENDABLE RELAY CO. LTD.

8A AINGER RD., CAMDEN TOWN, LONDON, N.W.3. PRImrose 8161
Head office, 12a Tottenham Street, W.1

P. O. TYPE 3,000 & 600 RELAYS

Typical 3,000 TYPE RELAY

—when only the best will do

Have you a Relay Problem?

The answer is at your elbow!

Just pick up your telephone and our long experience is at your service. —delivery—applications etc., etc. —we can help you in all of these

Service is our byword

Relays manufactured to your specification to A.I.D. & I.E.M.E. Standards

★ **COILS up to 80,000Ω**
★ **CONTACTS up to 8 amp.**
★ **INSULATION up to 5kv.**
★ **PROTOTYPES 7 DAYS.**
★ **SPECIALISTS in TROPICALISATION**
★ **TRANSISTORISED RELAYS**

Technical data leaflet on request.

YOUR TAPE RECORDER CENTRE

We specialise in Tape Recording and Hi-Fi Equipment

Illustrated is the

SOUND 777

TAPE RECORDER

Cash Price **44 GNS**
Microphone 55/- extra

An extremely low-priced, 3-speed, automatic tape recorder representing the best value in general purpose tape recorders. Delivery from stock.

Come to the Radio Centre for the most varied and exciting display of equipment anywhere.

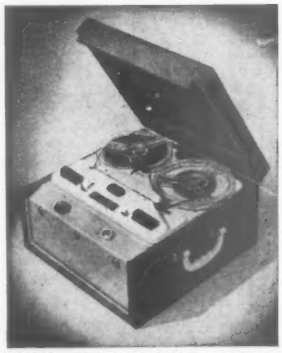

EASY REPAYMENT TERMS AVAILABLE

M·O·S **The E & G Radio Centre Ltd.**

33 Tottenham Court Road, London, W.1.
Telephone: MUSeum 6667.

Manufacturers are invited to write for details of

BELCLERE HIGH QUALITY TRANSFORMERS CHOKES & COILS

of every description

THE BELCLERE COMPANY

171, COWLEY ROAD, OXFORD

A.I.D. Approved **Oxford 3430 & 3432**

STEREOSOUND

the NEW name in SOUND REPRODUCTION

PRESENTS

The FINEST—INEXPENSIVE—HIGH QUALITY Sound Equipment obtainable. Designed and built by specialists, the PRICE/PERFORMANCE value is unbeatable. This is made possible because we not only manufacture the Amplifying Equipment, but also the Cabinets—ALL IN OUR OWN FACTORY.

STEREOPHONIC SOUND. "STEREOSOUND" offers you two different presentations of twin channel sound. Ready now for immediate delivery. A specially designed DOUBLE PUSH-PULL Amplifier with a pair of "Lancaster" Twin Loudspeaker systems. PRICE **43 gns.** OR a Pair of "Lincoln" Twin Speaker PUSH-PULL Amplifier units. PRICE **42 gns.**

MONAURAL SOUND. There is no better value for money for the sound enthusiast than a single "Lincoln" Baffle—and it can be paired with a similar matching unit later for Stereo Sound. The "Lincoln" has provision for the fitting of a "Stereosound" FM Tuner. The tuner, of the 3-station pre-tuned type with A.F.C. and Foster-Seeley discriminator, fits inside the "Lincoln" and ASSURES you of the best in both RECORD and RADIO reproduction. The TUNER can be bought immediately or later—and the price is only **15 gns.** The "Lancaster" Loudspeaker system used with your own amplifier or radiogram will give you results only obtained at double the cost with any other system. The "Lancaster" is the ideal loudspeaker system for School or Club use.

★ *Special Cabinet finishes available at a nominal extra charge.*

★ *Export Enquiries Invited.*

The *NEW*
"Stereosound"
"LINCOLN"
21 gns.
Tax Free
FM TUNER UNIT
15 gns. EXTRA

Push-Pull 6 Watts amplifier and Twin L.S. system mounted on a RESONANCE FREE Baffle, finished in beautifully veneered medium walnut. Negative Feed-back. Bass control gives variation of 15 dbs. Treble control gives variation of 6 dbs.

10,000 Line 12in. circular Speaker
10,000 Line 4in. circular Tweeter

Size: 20in. wide. 31in. high. 8in. deep.
For A.C. Mains only 200-250v.

FOR THE NAME OF YOUR NEAREST STOCKIST, OR FOR FURTHER DETAILS WRITE TO US DIRECT.

19 gns. Tax Free
The *NEW*
"Stereosound" PP5
Dual Channel Double Push-Pull Amplifier

6 watt Push-Pull output on each channel. Negative feedback. BASS AND TREBLE tone controls operate on both channels. Volume level is via separate controls to provide the necessary matched output to each speaker. The inputs are paralleled for Monaural recordings.
Size: 13½in. wide, 5½in. high, 7¼in. deep. For A.C. Mains only 200-250v.

The *NEW* **"Stereosound"**
"LANCASTER"
Loudspeaker System
12 gns. Tax Free

Twin Speaker Baffle. 2-3 ohm input. Dimensions and L.S. Specification identical with "Lincoln."

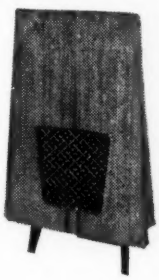

"Stereosound" is a trade mark of

CAPITAL RADIO

Capital Works, 12/14 Wakefield Road, Brighouse, Yorks. *'Phone Brighouse 2084.*

Proprietors Brighouse Television Finance Ltd.

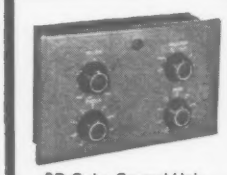
RD Cadet Control Unit

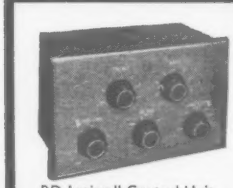
RD Junior II Control Unit

RD Junior Stereo Control Unit

The basic requirements of a Home High Fidelity System, operating from records, radio and tape, are provided at minimum cost by the ***RD CADET AMPLIFIER*** *used in conjunction with the* ***RD CADET CONTROL UNIT,*** *the inclusive price being only £17/10/-. By using the* ***RD JUNIOR Mk. II CONTROL UNIT*** *with the* ***RD CADET AMPLIFIER*** *the advantages of high sensitivity, sufficient to operate from any pick-up, and greater flexibility, including a Low Pass Filter, are gained and the price is still kept at the very modest figure of £21/10/-. For Stereo, two* ***RD CADET AMPLIFIERS*** *may be used with a* ***RD JUNIOR STEREO CONTROL UNIT*** *to provide 10 watts on either Stereo or Monaural operation for a total outlay of £38/10/-, related to performance probably the most inexpensive Stereo equipment at present available.*

Fully illustrated Literature may be had free and post free on request

Trade and Export enquiries invited

ROGERS DEVELOPMENTS (ELECTRONICS) **LTD**

DEPT. W/8 · 'RODEVCO WORKS' · 4-14 BARMESTON ROAD · CATFORD · LONDON S.E.6

Telephone: HITher Green 7424/4340 *Telegrams: RODEVCO LONDON S.E.6*

* M O T E K K9

This handsome all British Tape Deck with three speed Control Knob incorporates the very latest in design and construction

Details on request. Patents pending.

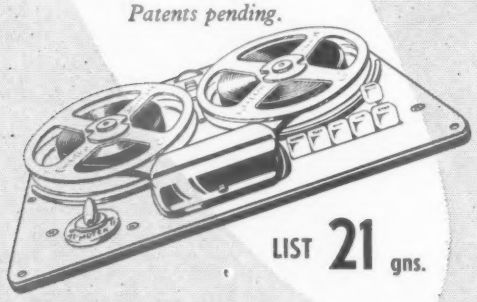

LIST 21 gns.

MODERN TECHNIQUES

Wedmore Street, London, N.19. Tel: ARChway 3114

BERRY'S

ANNUAL

STOCK-TAKING

SALE

COMMENCES

TUESDAY 5th AUGUST 1958

SLASHING REDUCTIONS!

BERRY'S RADIO

25 HIGH HOLBORN, LONDON, W.C.1. Tel. Holborn 6231-2

(OPPOSITE CHANCERY LANE)

For 40 years

the World's Widest Range of Gramophone Equipment

The arms of models having the plug-in head feature are wired and technically approved for stereophonic reproduction when used with the correct Pickup Cartridge, as specified by the Amplifier Manufacturer.

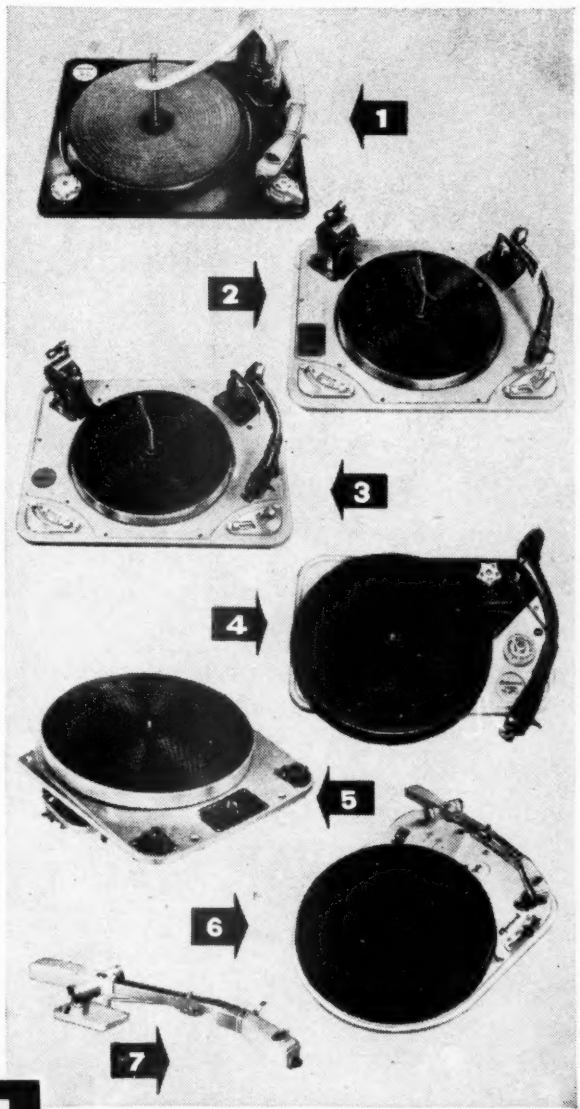

1 MODEL RC 121/4D MARK II

Will play automatically any number of records up to 10, either 7", 8", 9", 10" and 12" diameter, at 16-2/3, 33-1/3, 45 or 78 r.p.m. 10" and 12" records of the same speed can be mixed in any order. No setting for any record size required, the selection being completely automatic.

2 MODEL RC 98/4

This unit can be used as either a manually operated truly High Fidelity record player or a fully automatic record changer which will play any number of records up to eight. With 4 speeds, an electrical speed control and a switch click suppressor; it is indeed the record player for the connoisseur.

3 MODEL RC 88/4

This four speed automatic record changer will play automatically any number of records up to eight. It is superbly finished in cream and brown enamel.

4 MODEL TA/MARK II

This single record player has been produced to meet the demand for high quality units of minimum size at low cost. It is mounted on a rectangular unit plate and is considered the most suitable model for the home constructor.

5 MODEL 301

This motor has a 6 lb. accurately balanced die cast aluminium turntable. It is of the shaded pole induction type, is in heavy cast casing and is magnetically screened. The precise speed can be obtained by means of the eddy current brake. It is used by the B.B.C. and many broadcasting stations throughout the world.

6 4 HF

A high quality record player with 12" turntable complete with tone arm mounted on unit plate.

7 TPA 12

This precision chrome and white tone arm has been designed for the finest high fidelity system. Its length reduces track error to a minimum and permits the playing of 16" records if so desired. The universal plug-in head moulding will take any cartridge. All the best features of static balance, spring loading and viscous damping have been designed into the TPA 12 to provide maximum vertical freedom. The smallest possible number of pivots reduce traversing friction to absolute minimum.

RADIO SHOW · STAND No. 51
AUDIO HALL No. 438 · EARLS COURT

Garrard

THE GARRARD ENGINEERING AND MANUFACTURING CO. LTD.
SWINDON, WILTSHIRE, ENGLAND

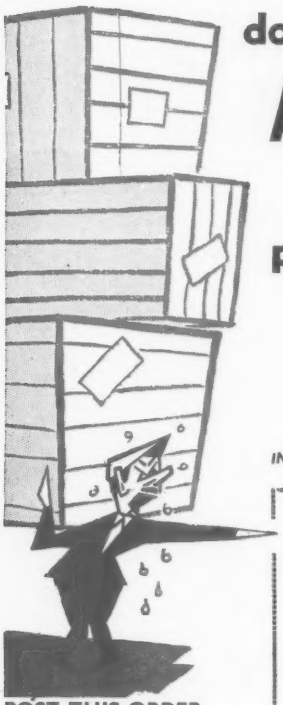

don't let your despatch problems pile up!

ABC GOODS TRANSPORT GUIDE

JULY : DECEMBER ISSUE NOW AVAILABLE

puts all the answers at your fingertips!

At a glance, the ABC GOODS GUIDE tells you the nearest, quickest means of despatching *any* kind of goods. Listed in town alphabetical order you'll find long-distance road haulage operators, parcels and local carriers, clearing houses, etc., as well as railway, air, coastal and other specialized services. ALL the transport information you require—for only 10s. a year. Order *your* copies of this vitally important reference NOW!

INVALUABLE TO TRANSPORT MANAGERS, DESPATCH MANAGERS AND ALL CONSIGNORS

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

Please enter my order for ..... copies of the JULY-DECEMBER 1958 and the JANUARY-JUNE 1959 issues of the ABC GOODS TRANSPORT GUIDE (at 10s per set) for which I enclose remittance of.....

NAME .....

ADDRESS .....

.....W.W.1.

POST THIS ORDER TODAY!

WALMORE ELECTRONICS LIMITED

PHOENIX HOUSE, 19/23 OXFORD STREET
LONDON, W.1

Telephone : GERrard 0522 *Cables : Valvexpor*
For immediate response Telex London 8752

EXPORTERS OF **RADIO, TELEVISION** AND **INDUSTRIAL TUBES,** HAVE PLEASURE IN INTRODUCING THEIR BRAND

RADIO **WALRAD** TUBE

AND INVITE ENQUIRIES FROM BUYING AND CONFIRMING HOUSES **EXCLUSIVELY FOR EXPORT**

SUPPLIERS OF RADIO COMPONENTS ELECTROLYTICS, AND CATHODE RAY TUBES

EXECUTIVES REQUIRE CRISP, CONCISE REPORTS—DICTATE THOSE DETAILS IN YOUR CAR! VALRADIO DC/AC CONVERTERS MAKE DICTATING MACHINES AND TAPE RECORDERS MOBILE

For use too with Record Changers, Radiograms, Electric Gramophones, Television Receivers, and T.V. from country house lighting plants. (Prices according to instrument.)
INPUTS . ENTREES . ENTRADAS
6, 12, 24, 32, 50, 110 or 200/250 v.
OUTPUTS . SORTIES . SALIDAS
110 v. or 230 v. AC, 50 or 60 c/s, 30 to 300 w.
Prices DC/AC Converters:
From **£3/18/**—for Small Motors.
From **£12/15/**—for Radiograms (including 3-speed Types).
Units complete and ready for use. **VALRADIO.** ***Write for descriptive folder, WW/C. ACCEPTED AS THE STANDARD by RADIO MANUFACTURERS, the Trade and the Aircraft industry.***

Les rapports destinés aux chefs de service doivent être rédigés d'une façon bien concise—dictez-les donc dans votre voiture!
Les convertisseurs C.C./C.A. " VALRADIO " consentent la mobilité aux machines à dicter et aux enregistreurs sur bandes.
Ils peuvent également être utilisés pour changeurs de disques, appareils combinés, électrophones, téléviseurs, etc., partant d'installations d'électricité, particulières.

Las relaciones destinadas a los jefes tienen que redactarse de modo muy conciso—dictenlas en el coche!
Los inversores C.C./C.A. " VALRADIO " les prestan movilidad a las máquinas de dictar y a los grabadores de cinta.
También pueden utilizarse para cambiadores de discos radio-combinados, gramófonos eléctricos aparatos de televisión, etc., aprovechando las instalaciones eléctricas privadas.

Specialists in converters since 1937. **VALRADIO LIMITED, BROWELLS LANE . FELTHAM . MIDDX. Phone: Feltham 4242/4837**
OVERSEAS ENQUIRIES TO:—DEMANDES D'OUTRE-MER A:—TODA INFORMACION DE EXPORTACION HA DE PELIRSE A:—E.M.I. SUPPLIES LTD. . HAYES . MIDDLESEX . ENGLAND

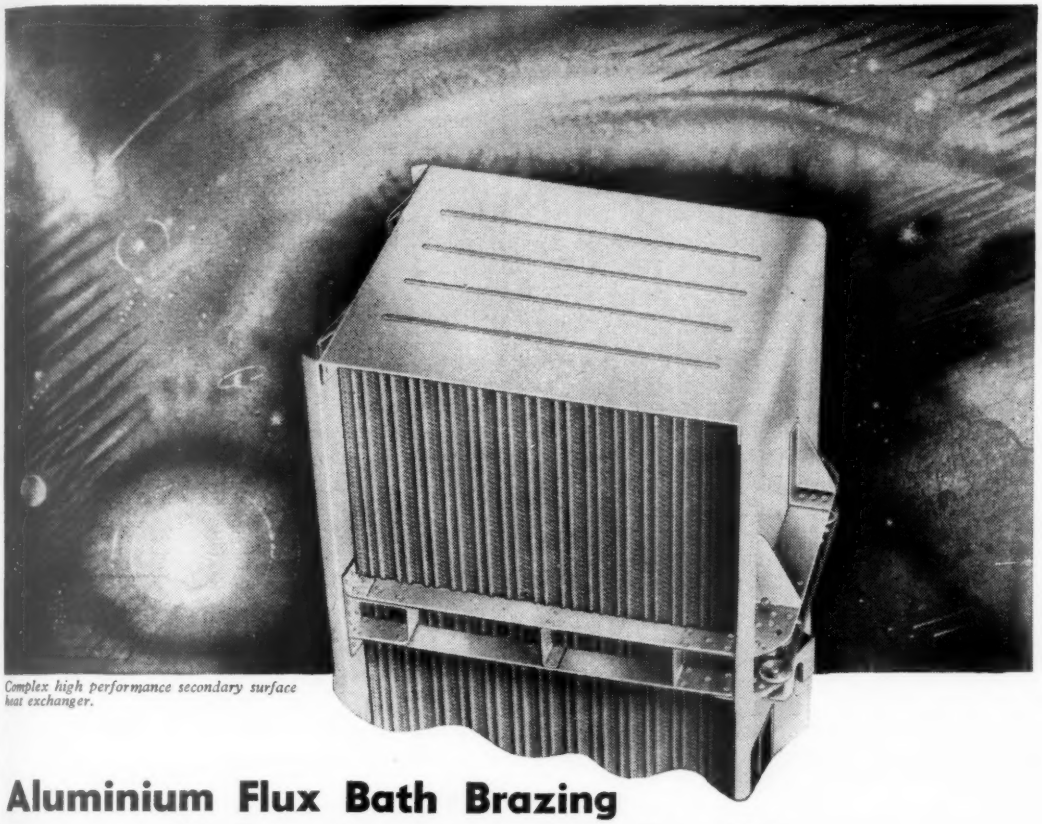

Complex high performance secondary surface heat exchanger.

Aluminium Flux Bath Brazing Makes the Impossible Possible

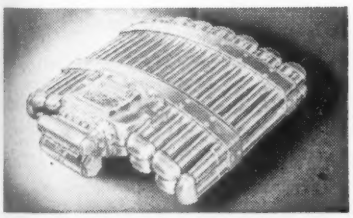

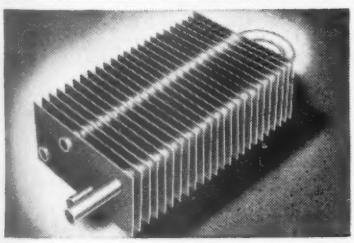

The tremendous advantages of aluminium dip brazing are at last readily available. The finest plant in the country is at your service.

Dip brazing makes the impossible possible. Design inaccessible joints—as many as you wish. Use aluminium as thin as foil. Think in terms of very close tolerances. All these things you can do. And you can combine them in units so small, so light and so efficient that it would be *impossible* to make them by any other method.

Designing for dip brazing need present no problems. We shall be happy to design for you, or if you prefer it, to discuss possibilities with you and then work to your design.

If you would like to know more about what can be done by this process please contact us. We are specialists in all types of brazing and welding.

Above: Fuel cooled oil cooler for high performanc gas turbine engines.

Below: Typical example of industrial heat exchanger.

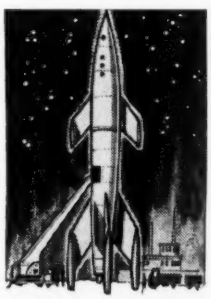

Delaney Gallay LTD

Specialists in heat exchange and heat insulation for the aircraft, automobile and marine industries.

Vulcan Works, Edgware Road, London, N.W.2. Telephone: GLAdstone 2201

For faultless service

operators everywhere are using *

S. G. BROWN Headphones

Are you? Even under the most adverse conditions, the weakest signal can be clearly heard with BROWN headphones. Reliable and highly sensitive, yet able to stand the rigours of everyday use, they can be worn for long periods without any discomfiture.

For full details of BROWN Headphones and other equipment write to Telephone Dept.

***Type A**

Embodying the adjustable reed principle, these instruments are capable of the utmost sensitivity.
The ideal choice when purity of tone and clear reception of weak signals is essential.

Brown

Headphones & Handphones
'Automatic Helmsman'
Marine Compasses
Echo Sounders
Navigational Equipment

S. G. BROWN LTD.
SHAKESPEARE STREET · WATFORD · HERTS
Telephone Watford 7241

HI-FI EQUIPMENT

(CABINETS See page 155)

RADIO CHASSIS

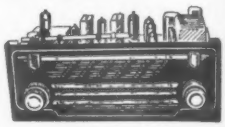

Empress 9-valve de luxe AM/FM with two speakers 26 gns.
Empress 6-valve AM/FM with 10in. speaker ..... 22 gns.
Empress 6-valve de luxe AM/FM self-powered tuner 22 gns.
Empress FM Tuner £13/15/-
Empress 5-valve AM £14/5/-
Armstrong PB 409 9-valve AM/FM 6-watt push-pull..... 28 gns.
AF 105 10-valve AM/FM 10-watt push-pull £37 0 0
DULCI
H.3 AM/FM 3 wavebands £20 17 0
H.4 AM/FM 4 wavebands £24 6 6
H.4.PP AM/FM push-pull 4 waveband £29 3 10
H.4.T2 AM/FM self-powered tuner £24 19 0
H.11 AM/FM tuner with pre-amplifier £29 3 10
FM self-powered tuner £17 10 3

AUTOCHANGERS
Garrard RC 98/4... £19 17 7
" RC 88/4.. £17 18 8
" RC 120/4 £12 17 2
" RC 121/4. £13 13 10
Collaro latest £9 19 6
B.S.R. Monarch ... £8 15 0

TRANSCRIPTORS
Garrard 301 ..... £26 8 3
Connoisseur £28 11 0
Goldring-Lenco 56 £23 7 0
Collaro 4T200 ..... £19 10 0
Garrard T.A. Mk. II £9 15 8

FERROGRAPH TAPE RECORDER 3 A.N. ..... 79 gns.

Tape Decks with Pre-Amplifier, absolutely complete ready to connect to radio or amplifier:
Collaro/Magnafon Mk. IV ..... 40 gns.
Telefunken..... £47 5 0
Brenell Mk. 5 Tape Deck..... 28 gns.
Truvox Tape Deck 29 gns. ..... with type 'K' amplifier £50 8 0
Motek Tape Deck K.9 ..... 21 gns.
Wearite Tape Deck 3C £45 0 0

Send for NEW 32 Page illusrtated catalogue on our range of Hi-Fi equipment. AU available on easy terms.

LEWIS RADIO

120 (Dept. W78), Green Lanes Palmers Green, N.13
(Nr. The Cock Tavern) Tel.: Bowes Park 1155/6

POTentiometer LOCKS

KNOB LOCK

The ideal method of locking panel mounted controls. Positive guard against vibration, etc.

This development of our popular p.e-set control lock is finished in black plastic and embodies control knob and instantaneous finger-tip locking knob. Send for List No. A.6.

Prices reduced!

Have you had a copy of our revised Knob Lock price list?

PRE-SET CONTROL LOCK

TYPE P.K.2

Very attractive appearance for panel mounting.

TYPE C.H.2

These units are designed to lock the spindles of pre-set potentiometers or trimmers without rotational or lateral displacement of shaft. Will accept wide range of panel thicknesses. Send for leaflet A.I.

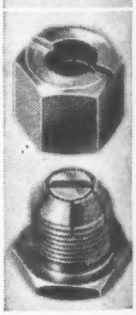

ARDEN Engineering Co.

REDDICAP TRADING ESTATE, SUTTON COLDFIELD
Phone: SUT 3088 & 5666

Variable Transistorised Regulated Power Supply TSV.12

with Current and Voltage Metering

- ***Fully Transistorised***
- ***Double Zener reference Diodes***
- ***Output can be Positive or Negative to Chassis***
- ***No warm-up period—instantaneous output***

PRICE £39/12/6

SPECIFICATION :—

Input Voltage:	200–260 Volts, 40–60 C.P.S.
Output Voltage:	0.5–12 Volts continuously variable
Maximum Current:	1.5 amp. at 12 Volts
Output Impedance:	<0.06 OHM up to 1 KC/s
Output Variation for ±10% mains change:	1 part in 1000
Output Variation with Load Current:	50mV no Load to full Load
Ripple:	Less than 1mV
Transient Recovery Time:	50 microseconds
Size:	13½in. length × 6½in. height × 8in. depth
Weight:	12 lbs.

RANSISTORISED POWER UNITS FOR OTHER APPLICATIONS

available on request, including :

- Transistorised constant current Power Units
- Open Chassis Units for plug-in applications with interchangeable voltage reference

Manufactured by

FARNELL *Instruments* LTD.

WETHERBY INDUSTRIAL ESTATE, YORK ROAD, WETHERBY, YORKSHIRE

Telephone: Wetherby 2544

Our comprehensive range of models include

Vortexion W.V.A.	£93. 13. 0
Vortexion W.V.B.	£110. 3. 0
Brenell Mk. 4	53 gns.
Elon	62 gns.
Ferrograph 3 A/N	79 gns.
Grundig TK5	53 gns. inc. mic.
Grundig TK8	72 gns. ex. mic.
Grundig TK830/3D	100 gns. ex. mic.
Elizabethan Essex	65 gns.
Magnafon FRS	55 gns.
Magnafon 58	62 gns.
Philips AG 8109	39 gns.
Philips AG 8108	62 gns.

★ ★ ★

Tapes

LP and Standard

E.M.I.
Scotch Boy
Ferrograph
Mastertape
Philips
B.A.S.F.

E.M.I. and BIB splicers

Jointing fluid and leader tape for editing in all colours

Wearite Defluxers

Modern Electrics Ltd

164 CHARING CROSS ROAD, W.C.2

Telephones : TEMPLE BAR 7587. COVENT GARDEN 1703
Cables : MODCHAREX, LONDON

HI-FI EQUIPMENT

We stock all the leading makes of amplifiers, control units, transcription units, pickups, loudspeakers and FM Tuner units.

We are approved Grundig distributors and service agents.

CONTINUOUS DEMONSTRATIONS

We offer a complete Tape Recorder Service

Send stamped, addressed envelope for our complete list of Tapes, Accessories and prices.

PROMPT ATTENTION GIVEN TO POST ORDERS · EXPORT ENQUIRIES INVITED AND WELCOMED

TRANSFORMERS

for every requirement

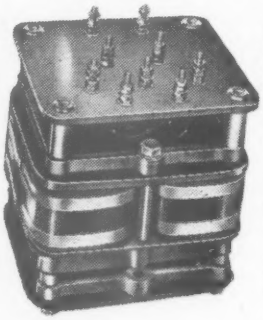

Electronics
Transmitters
Radar
Test equipment
M.V. discharge tubes
R.F. heating
L.V. heating

Range 1 volt—35 K.V. 1 M/A.—1,000 amps

STANDARD OR TROPICAL FINISH

We are on Admiralty and Ministry of Supply lists and A.I.D approved

Enquiries to:

STEWART TRANSFORMERS Ltd.
75 KILBURN LANE, LONDON, W.10 · LADbroke 2296/7

WAFER SWITCHES TO SPECIFICATION

As we specialise *only* in the manufacture of small quantities of wafer switches (to individual specification) we guarantee competitive prices and fast delivery.

SWITCHES TO PUBLISHED DESIGNS (FROM STOCK)

G.E.C. 912-PLUS

S1 (14061/B1) } 14/6 pair
S2 (14062/B1) }

S4 (SS/556/1) ... 11/6

S5 (SS/556/2) ... 10/6

Mullard Tape Amplifiers

Amplifier "A"

SS/567/A
SS/567/B } 32/6 the set
SS/567/C }

Amplifier "B"

SS/567/A ... 16/6

G.E.C. 88-50 Pre-Amplifier

Input Selector (state number of positions) ... 12/-
Treble Selector ... 7/9

Write for Price List and Design Chart.

SPECIALIST SWITCHES

23 Radnor Mews - Sussex Place
London W2 - AMBassador 2308

Suppliers to the leading electronics, aeronautical and automobile companies and to research institutions, the G.P.O. and Universities.

foremost for Quality, Performance and Reliability—

RELIANCE

POTENTIOMETERS

The name "Reliance," aptly chosen more than thirty years ago, is recognised for potentiometers of consistent accuracy, with a record of long-life reliability. The standard range—the most comprehensive available—covers from 1 to 500,000 ohms and includes linear, log, semi-log and non-inductive types, and, depending on characteristics, ratings up to 20 watts.
GANGED MODELS available of TT, TW, PIW and TS on common spindle. Fully tropical and concentric spindles type TW only. .

RELIANCE MANUFACTURING Co. (SOUTHWARK) Ltd., SUTHERLAND Rd. HIGHAM HILL, WALTHAMSTOW, LONDON, E.17
GD 10
Telephone No. (and Cables) LARkswood 3245

E·T·S Specialists in the preparation of TECHNICAL HANDBOOKS

ELECTRONIC TECHNICAL SERVICES

TELEPHONE – RAVENSBOURNE 8951-2

Contractors to

Ministry of Supply

Admiralty

Atomic Energy Authority

ETS DATA SHEETS for Joint Service Approved Electronic Components

EMERGENCY Drawing Office Services

1 NEWMAN ROAD BROMLEY KENT

Model 94A

T.V. WAVEFORM AND ALIGNMENT GENERATOR

Taylor

Model 32A

PORTABLE OSCILLOSCOPE

For Radio, T.V. and general laboratory use

4 JOBS—1 INSTRUMENT

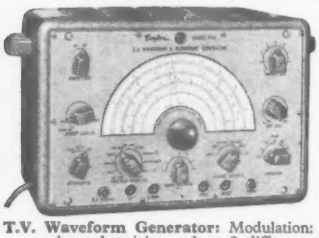

This is a combined signal source primarily for use in T.V. alignment setting up and fault finding in all kinds of T.V. receivers (405, 525 or 625 line systems). Four basic instruments are incorporated: (1) T.V. Waveform Generator; (2) A.M. Signal Generator; (3) F.M. Signal Generator; (4) T.V. Sweep Oscillator. All instruments cover frequencies from 4 to 220 m/cs.

T.V. Waveform Generator: Modulation: All with fully interlacing and synchronizing pulses, 8 different patterns and sound 1.5 to 4.5 Mc/s definition bars. Accuracy ±1 per cent.

A.M. Signal Generator: Accuracy ±1 per cent. Output 30 m.V.

F.M. Signal Generator: Accuracy ±3 per cent. Deviation continuously variable to 200 Kc/s.

T.V. Sweep Oscillator: Frequency deviation 7 Mc/s.

Sweep Frequency: 50/60 c/s. Sweep length controllable

PRICE **£75.0.0**

PROMPT DELIVERY

Carriage and packing paid in U.K.

Tube: 4in. electrostatic deflection. EHT 1,200 V. High brilliance trace.

"Y" Amplifier: Sensitivity 12.5 V. R.M.S. per inch. Input resistance 5 megohms (approx). Push-pull output, sensitivity 80 mV. per inch, frequency response 10 c/s to over 6 Mc/s. Input impedance 1 megohm. Maximum input 25 V. peak.

"X" Amplifier: Push-pull output sensitivity 0.45 V. R.M.S. per inch maximum. Frequency range 5 c/s to 500 Kc/s.

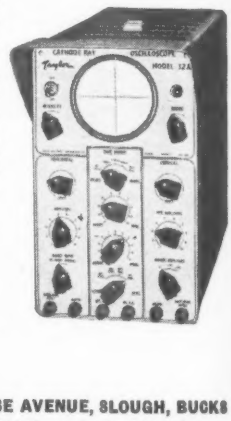

Time Base: 2 c/s to 100 Kc/s in 5 ranges free running or recurrent trigger. Exceptional *synchronization* characteristics, switchable internal/external. External synchronization impedance 1 megohm 20 p.f. Flyback suppression.

PRICE **£70.0.0**

PROMPT DELIVERY

Carriage and packing paid in U.K.

ALL TAYLOR INSTRUMENTS are available on 7 days FREE TRIAL

Credit Sale Terms available

WRITE NOW FOR FULL INFORMATION

TAYLOR ELECTRICAL INSTRUMENTS LTD

MONTROSE AVENUE, SLOUGH, BUCKS

Telephone: SLOUGH 21381

BRADMATIC

LIMITED

STEREOPHONIC HEADS

We have pleasure in announcing another BRADMATIC high class product–the type ST-RP Stereophonic Magnetic Head for Recording or Reproducing stereophonic magnetic tapes.

This unit is complete in its own screen can and is available with or without a fixing stem.

RETAIL PRICE: £6.0.0

(Without fixing stem)

ENQUIRIES INVITED — TRADE OR PRIVATE

from

BRADMATIC LIMITED

Station Rd., Witton Lane, Aston, Birmingham, 6

Telephone: East 2881-2. *Telegrams: Bradmatic Birmingham.*

Is this the answer?

P.O. Type 3000

The most versatile relay available today.

Coils up to 120,000Ω

Spring Set Insulation up to 5KV

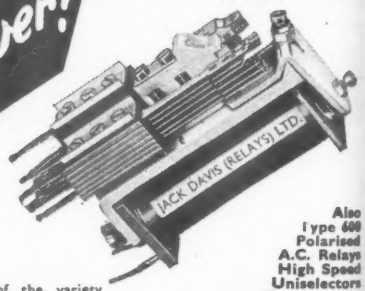

Are you aware of the variety of contact build-ups we can assemble? Your problem may not be as bad as it seems if you take advantage of our wide experience in the unlimited uses of this adaptable product.

- Quotation by return
- Prototypes within 48 hours
- Good delivery guaranteed

Also
Type 600
Polarised
A.C. Relays
High Speed
Uniselectors
Key Switches
Latching Relays
Magnetic Counters
to RCS and RCL specification if required

Consult the Specialists!

Jack Davis (Relays) Ltd.

(DEPT. W.) TUDOR PLACE, LONDON, W.1

TELEPHONES: MUSEUM 7960 LANGHAM 4821

cabinet racks & instrument cases

EARLY DELIVERY — HIGHEST QUALITY MATERIALS
ANY SPECIFIED COLOUR — COMPETITIVE PRICES

CABINET RACKS

Dynatron standard range Cabinet Racks are used extensively on Government contracts and comply to Post Office specifications for 19in. panels. They are robustly constructed of the best quality bonderised steel and outstanding features include ample ventilation, runner shelf brackets, cable entry facilities, bonded posts and mains input junction box together with earthing bus bar and cable clamps. Two versions are available, the 'A' type as illustrated and the highly flexible 'B' type racks, which can be supplied with or without doors, as single units or joined together to make bays of two, three or more units.

INSTRUMENT CASES

Dynatron Instrument Cases are available in two sizes, for 8¾in. and 10½in. × 19in. standard G.P.O. panels. Robustly constructed of the finest quality steel, they are designed for long life.

Write or 'phone for full details:

DYNATRON

NUCLEONIC & ELECTRONIC DEPARTMENT

DYNATRON RADIO LIMITED, *Maidenhead, Berks.* *Telephone: Maidenhead 2161*

AEL *for* **MEASURING INSTRUMENTS**

MOVING COIL • MOVING IRON • THERMO COUPLE • ELECTROSTATIC

IMMEDIATE DELIVERY

Most Basic Ranges available **ex-stock** for immediate despatch. Special ranges—delivery 7/14 days.

Round, Square or Rectangular patterns available, also full range of Industrial Switchboard Instruments. Portable and Laboratory Instruments.

We can supply Meters with Non-Standard Ranges in Current, Volts or Ohms. To B.S. 89. Industrial or Precision Grade accuracy.

We are the largest stockists of Electrical Measuring Instruments in the Country.

Clients are invited to inspect the display of instruments at our New Offices and Showrooms.

May we quote for your requirements?

Weston Model S157
Rectangular Flush 5" × 4" approx.

Stockists of Meters by Weston, Turner, Baldwin, E.A.C., Weir and other leading manufacturers.

Electronic Equipment and Test Apparatus manufactured to customer's design or specification

Contractors to G.P.O. and other Govt. Depts.

Anders Electronics LTD.

103, HAMPSTEAD RD., EUSTON, N.W.1. Tel. EUSton 1639

Arcolectric Signal Lamps

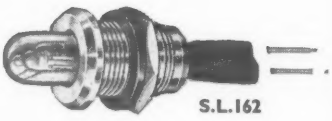

S.L.162

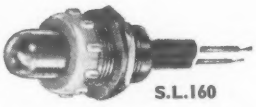

S.L.160

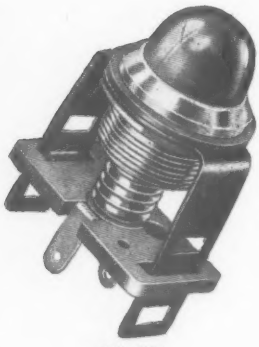

S.L.135
For M.E.S. bulbs

S.L.130
For M.B.C. (M.C.C.) bulbs

S.L.130 A high quality fitting for M.B.C. bulbs.
S.L.135 A new adjustable M.E.S. signal lamp.
S.L.160 } New miniature neon signal lamps
S.L.162 } for 80-600 volts. Fixing ½" hole.

Samples of above to manufacturers for design purposes AT ONCE—WITHOUT CHARGE—on request.

Many other signal fittings—M.E.S., B.C., S.B.C., etc.

Write for Catalogue No. 131

ARCOLECTRIC SWITCHES · LTD

CENTRAL AVENUE, WEST MOLESEY, SURREY. Tel.: MOLESEY 4336

ASK ARTHURS FIRST

LARGE STOCKS OF VALVES and C.R.T.s. METERS, Avo, Advance, Taylor and Cossor Oscilloscopes in stock. AMPLIFIERS, Leak, Trix and Quad. GRAM UNITS, Garrard and Collaro. Collaro TRANSCRIPTION UNIT 2010PX.

LOUDSPEAKERS, Goodmans, Wharfedale, WB Tannoy and leading makes. PICK-UPS and STYLI of most makes. TAPE RECORDERS, Grundig, Philips, Truvox, Playtime and Ferrograph.

LATEST VALVE MANUALS

Mullard, **10/6**; Osram and Brimar No. 6, **5/-** each; Osram Part 2, **10/-**.

Postage 9d. each extra.

PARTICULARS ON REQUEST

Terms C.O.D. OR CASH with order.

Arthurs EST. 1919

PROPS: ARTHUR GRAY, LTD.

GRAY HOUSE, 125 TOTTENHAM COURT ROAD, LONDON, W.1
EUSton 5802/3 *Cables: TELEGRAY, LONDON*

The Manning-Carr P.53C MINIATURE POLARISED RELAY

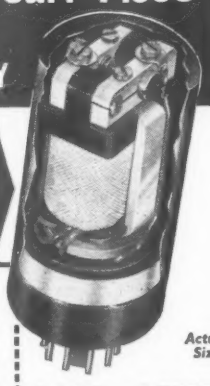

In dust-proof heavy gauge anodised aluminium can mounted on B9A base for plugging in.
(P53 original open non-plugging version still available.)
P53C BIASSED TO EITHER SIDE
P57 C/CS CENTRE STABLE
ALL TYPES FITTED WITH PLATINUM CONTACTS WHERE SPECIFIED

Data—A Sensitivity of 25 milli-watts and capable of handling mains voltage on the contacts with alternating currents up to 0.25 amps. Being polarised they have the advantage that the armature contact on P53 and P53C models can be biassed to lock in either direction by suitable adjustment of the contact screws which provides a useful facility where pulse operation is required. Speed of operation is high and the Relay will follow frequencies appreciably higher than 50 c.p.s. Resistance up to 7,000 ohms which is acceptable for Anode circuits. Alternatives to specification if required. **Sole Concessionnaires.**

Actual Size

POST OFFICE TYPES
3,000 & 600 RELAYS TO SPECIFICATION
Tropicalising, Impregnating and Services jungle finish if required. Delivery 3-4 weeks.

Manufacturers to H.M. Govt. Depts. and leading Contractors

L. E. SIMMONDS LTD.

5 BYRON ROAD, HARROW, MIDDX.
Tel.: Harrow 7797/9 Grams: SIMRELAY HARROW

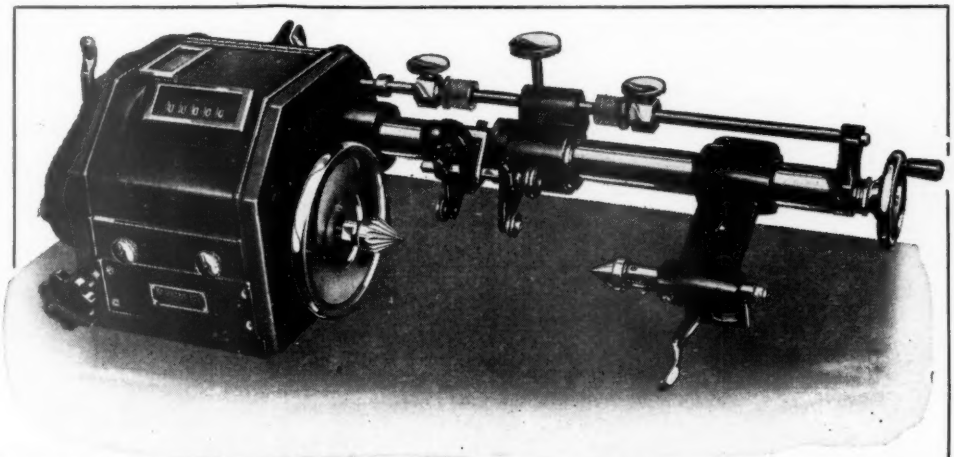

AUTOMATIC COIL WINDING MACHINE

TYPE A1/1 (25/50 S.W.G.). TYPE A1/X (19/46 S.W.G.)

THE MOST OUTSTANDING MACHINE ON THE MARKET!

Dustproof construction—up to four coils can be wound simultaneously—micrometer traverse setting—easily adjusted wire gauge setting—cadmium and chromium plated steel parts—Wire Tensioning Stand of novel design holds two reels. Machines to stop automatically at a required number of turns, can now be supplied to order.

We will be pleased to send you an illustrated leaflet giving a full technical specification on request.

KOLECTRIC LTD 73 UXBRIDGE ROAD, EALING, LONDON, W.5 *EALing 8322*

FLEXIBLE REMOTE CONTROL OUTFITS

offering facilities for making prototype flexible remote controls as required, without flexible casing.

The Remote Control Flexible Shafts in these Outfits cover the range of torque loadings required for volume controls, wave change switches and condensers used in electronic, radio and television equipment.

No. 130 (.130 in. dia.) for controls up to 4 inches long
No. 150 (.150 in. dia.) for controls up to 6 inches long

Longer controls with flexible casing made to order.
Detailed Parts and Price List available upon request to Dept. W.

THE S·S·White CO. OF GREAT BRITAIN LTD.
INDUSTRIAL DIVISION

BRITANNIA WORKS, 25-31, ST. PANCRAS WAY, N.W.1.
Telephone: EUSton 5393

R.C.4.

ARDENTE

make a wide range of

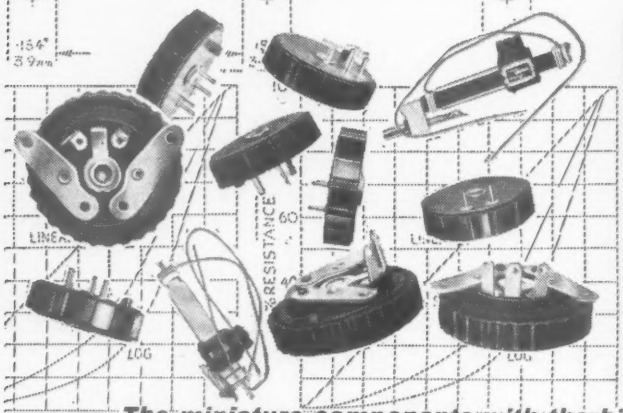

MINIATURE POTENTIOMETERS AND ELECTRONIC COMPONENTS

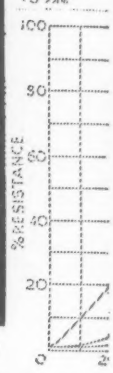

The miniature components with the big technical background

Sole Manufacturers and Exporters:

ARDENTE ACOUSTIC LABORATORIES LTD.

8-12 MINERVA ROAD, NORTH ACTON, LONDON, NW10 *Telephone: ELGar 3923*

Suppliers of components and hearing aids to the Government and manufacturers all over the world.

SONOMAG

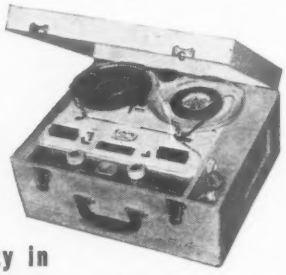

The sign of quality in

TAPE RECORDERS

Prices start at 46 gns. and, feature for feature, all are of the finest value attainable.

The Gaiety	**46 gns.**
The Classic	**54 gns.**
The Continental	**56 gns.**
Elon De Luxe	**65 gns.**
Porchester Console	**70 gns.**
... also The Adaptatape	**40 gns.**

High Fidelity at low cost awaits you at

THE HOUSE OF **SONOMAG**

2, St. Michael's Road, Stockwell, London, S.W.9. BRI. 5441/3

Sole wholesale distributors

J. E. DALLAS & SONS LTD.,

Dallas Building, Clifton Street, E.C.2. BIShopsgate 9981

RELAYS

NOW! A BRAND NEW 12 Change-over Magnetic RELAY

Enormous range of P.O. 3,000 Type Relays.
CONTACTS: 300 m/A to 8 amp.
COILS: Up to 100,000Ω.

P.O. 600 and High-Speed Type Relays. Built to Specification.

LARGE STOCKS OF KEYSWITCHES

PROMPT DELIVERY

THE KEYSWITCH CO.

2 Irongate Wharf Rd., Praed St., London, W.2 PAD 2231/2/3

Contractors to Home and Overseas Governments and H.M. Crown Agents

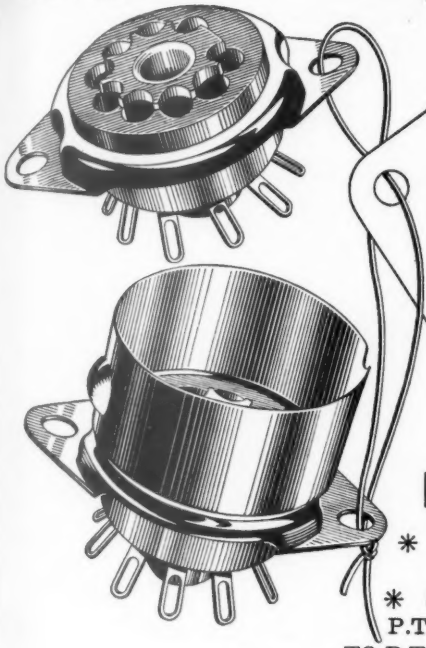

McMURDO

P.T.F.C.E. VALVE HOLDERS

B7G AND B9A

* LOW LOSS—**GRADE 1.**
* FULLY TROPICALISED—**CLASS H 1.**
* SILVER PLATED PHOSPHOR-BRONZE CONTACTS.

P.T.F.C.E. MOULDINGS HAVE SIMILAR PROPERTIES TO P.T.F.E. BUT THEY ARE LESS COSTLY TO PRODUCE.

FULL INTER-SERVICE TYPE APPROVAL TO Z.560092-Z.560094-Z.560095-Z.560134

Send for full technical details to:—

McMURDO INSTRUMENT CO. LTD., VICTORIA WORKS, ASHTEAD, SURREY. **Telephone: ASHTEAD 3401**

MVH. 14.

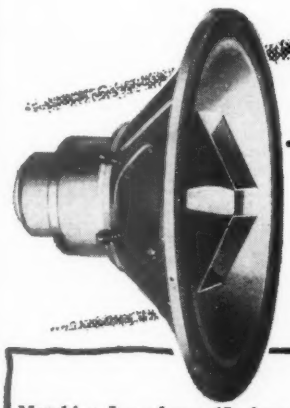

...fiddle, 'cello, big bass drum bassoon, flute and euphonium...

. . . each is reproduced perfectly in its own distinctive timbre by the BTH K10A Speaker. This is a unit designed to exploit to the full the capabilities of a modern 'Hi-fi' equipment.

Built to an exacting specification, the equipment comprises an 18-inch cone for low frequencies, with a co-axial pressure-type unit and horn for high frequencies, and is complete with cross-over network.

Matching Impedance 15 ohms
Cross-over Frequency 1700 c.p.s.
Total Weight (including filter) 38 lb.
List price £45.

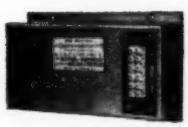

DESIGNS OF TWO SUITABLE CABINETS ARE SUPPLIED FREE WITH THE SPEAKER

Write for leaflet G12094 for full technical information

B T-H

A5208

BTH SOUND EQUIPMENT LTD.

REYNOLDS HOUSE, 5, GT. NEWPORT STREET, LONDON, W.C.2

an A.E.I. Company

D.C.R. 15 D

One of the earliest of the D.C.R. range, this cabinet, designed originally for the Tannoy 15in. dual speaker, was the first to bring fame to the corner reflector method. Known then as the D.C.R. 60 its impact on the listening world was considerable. For the first time listeners were able to hear a tweeter responding almost up to the top of human hearing, sounding perfectly natural, without "sting" and without "pin-pointing," indeed *without localisation at all.*

In these days, when large claims are made for effects obtainable from twin-channel ("stereo") tapes and discs, it is interesting to look back and see just what a big step that was, and what a happy one as well.

We may note that the D.C.R. speakers have a special suitability for twin-channel work, especially if mounted on castors. Corner or wall reflection meets the need for dispersal of the high-note beam; but more important is the flexibility and adaptability which they offer. The speakers can be oriented as well as moved from point to point, thus giving the widest choice in width of separation of the two apparent sound sources, and also control of the definition or diffusion of these sources. Experience is beginning to show that such adjustments are necessary not merely to meet the acoustic requirements of any particular room but the acoustics of any individual twin-channel record.

The most remarkable thing to be observed is the extent to which a single D.C.R. speaker anticipates the benefits conferred by twin-channel listening without getting involved in its attendant difficulties and false effects. All the "airiness" of the music is there, that ability to "come unstuck" from the speaker. Apparent width is there too, about as much as is got from two twin-channel speakers "playing safe" by keeping fairly close together, but there is no trouble with the common fault of splitting or spreading a solo instrument.

The illusion of depth or perspective is often better done on the single D.C.R. speaker, partly because one can buy one very good speaker for the price of two indifferent ones.

The step which six years ago brought listeners more than half the possible benefits of twin-channel listening without any of its snags must indeed be called a happy one.

1. D.C.R. 15.8.T
2. D.C.R. 15.P.M.T.
3. D.C.R. 15.D.
4. D.C.R. 12.8.
5. D.C.R. 12.T.
6. D.C.R. 12.D.
7. D.C.R. 12 Minor.

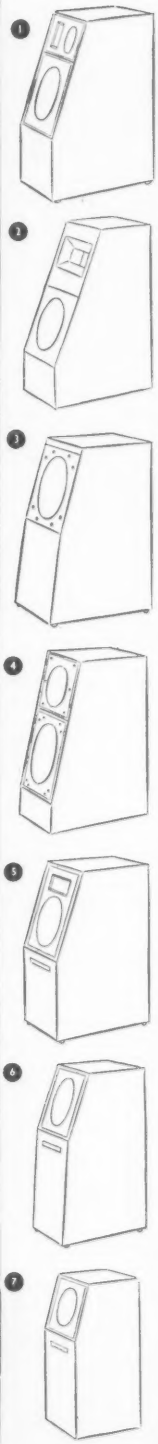

E · M · G

HANDMADE GRAMOPHONES LTD.
6 Newman Street, W.1.
MUSeum 9971

FREQUENCY METERS

SIZES: 2½" to 8"
UP TO 5000 CYCLES
PROMPT DELIVERY

also the new SYNCHROSCOPE and Phase SEQUENCE METER both up to 5Kc.
and full range of Switchboard instruments
Ask for illustrated Catalogue

THE ELECTRICAL INSTRUMENT CO. (Hillington) LTD.
HILLINGTON GLASGOW
London stockists, H. A. Patterson & Ptnrs., Ltd.,
Oxford House, 23 West Wycombe Rd., High Wycombe.
Telephone: High Wycombe 2769

MINIATURE COILS

FOR TRANSISTOR RADIO CIRCUITS

These are the smallest screened coils available on the British market or the Continent.

DIMENSIONS:—

Height (Excluding Lugs) ..	5/8in.
Diameter (Top)	9/16in.
Diameter (Base)	5/8in.

★Latest high-efficiency ferrite pot cores and litz windings.

★High Q for maximum gain and selectivity.

★Coupling ratios carefully designed to match latest R.F. transistors. I.F.—460/470 Kc/s.

★Low-loss moulded nylon formers.

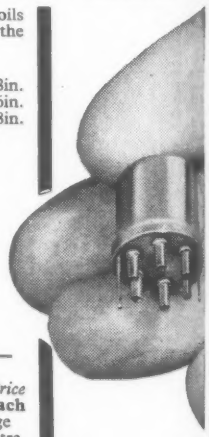

THREE TYPES AVAILABLE:—

List		*List Price*
735	Oscillator Coil	11/3 **each**
736	1st or 2nd I.F. transformer.	postage
737	3rd I.F. transformer	6d. extra.

Connection diagram supplied.
DELIVERY: Ex Stock.
C.W.O., or C.O.D. (1/6d. extra).

Trade, Manufacturers, and Export enquiries invited.

Orders and enquiries direct to the manufacturers :—
CHANNEL ELECTRONIC INDUSTRIES LTD.
COMPONENTS DIVISION
DUNSTAN ROAD BURNHAM-ON-SEA SOMERSET. Phone 316

Train for a Wonderful future in RADIO & TELEVISION...

Radio and Television techniques are continually advancing and their applications ever increasing. These fields offer to the trained technician a career with an assured and remunerative future.
Here is your opportunity to enter for:—

1 YEAR COURSE Full-time day course in the Principles and Practice of Radio and Television. Designed for the training of Radio and Television Servicing Engineers and others similarly engaged in the Electronics Industry. Next course commences September 9th 1958; others in January and May 1959.

The E.M.I. College of Electronics. Dept. 127,
10, Pembridge Square, London, W.2.
Telephone: Bayswater 5131/2.

*The College is part of the **E.M.I.** Group . . . Britain's foremost electronic engineers . . . Pioneers of the world's first public television service.*

THE E.M.I. COLLEGE OF ELECTRONICS

1A62

All good 'labs' use Radiospares

quality components for design development and prototype work

Service Engineers!

Remember- Radiospares components are delivered absolutely "by return"

You're coming close to perfection...

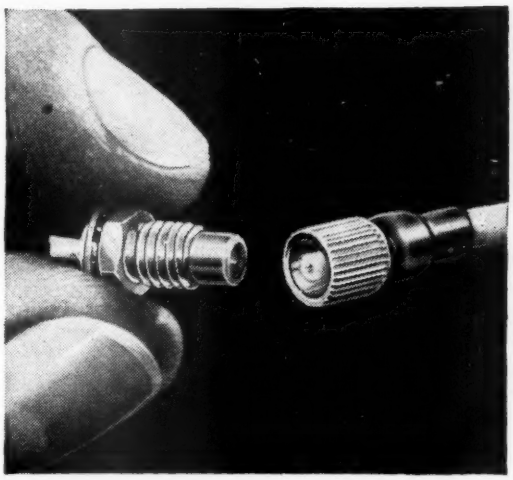

A close view of an Amphenol SUBminax Connector reveals only superficially the perfection of design and engineering that follows naturally from more than 25 years' experience. A deep store of understanding of the problems and needs of this field is behind the brilliant techniques now producing the thirty different types of SUBminax R.F. Connectors currently available, in both 50-ohm and 75-ohm impedances, with "push-on" or "screw-on" mating.

Designed for use with subminiature cables such as RG196/V, RG174/V or RG188/V, these miracles of compact engineering feature full-size electrical characteristics compressed into space-saving, weight-saving form.

Amphenol "AN," "Miniature AN," "Blue Ribbon" and "Micro-Ribbon" Connectors in a wide range of types and sizes are also available from stock.

AMPHENOL

Write now for details of these and other Connectors from the vast Amphenol range, covering literally thousands of applications.

SUB*Minax* miniaturised R.F. CONNECTORS

AMPHENOL (Great Britain) LTD.,
Victoria Road, Burgess Hill, Sussex
Burgess Hill 85616

AMPHENOL ELECTRONICS CORPORATION, CHICAGO, U.S.A.
AMPHENOL CANADA LIMITED, TORONTO 9, ONTARIO.

Make the most of your slower speeds with

THE HIGH TOP RESPONSE OF *-Mastertape*

The superb quality of Mastertape ensures a high and extended 'top response'. High top response means that Mastertape can record at *lower speeds* with maximum possible brilliance—in fact *more for your money* with Mastertape, for both quality and *longer playing time.*
Praised by experts and connoisseurs of good recording.

Attractive, ideal tape storage. Stoutly bound book containers in red-black and gold, with transfer numerals holdings 2 7½" reels of tape. Price 7/6d. Book rack to hold six books—17/6. Set six books and rack 62/6d.

Mastertape

MAGNETIC RECORDING TAPE BY
M.S.S. RECORDING CO. LTD., COLNBROOK, BUCKS, ENGLAND.
Telephone: COLNBROOK 2431 (8 lines)
SHOWROOM & STUDIO 21, BLOOMSBURY STREET, LONDON, W.C.1. *Telephone: MUSEUM 1600*

TRANSFORMERS
COILS *LARGE OR SMALL QUANTITIES*
CHOKES *TRADE ENQUIRIES WELCOMED*

SPECIALISTS IN
FINE WIRE WINDINGS
MINIATURE TRANSFORMERS, PICK-UP,
CLOCK AND INSTRUMENT COILS, ETC.
VACUUM IMPREGNATION TO APPROVED STANDARDS

ELECTRO-WINDS LTD.

CONTRACTORS TO G.P.O., M.O.S., L.E.B., ETC.
123-5-7 PARCHMORE ROAD, THORNTON HEATH, SURREY
LIVINGSTONE 2261 EST. 1933

EVERYTHING FOR THE AMATEUR

RADIO HAM SHACK LIMITED

Convert to a modern radiogram and save money

● **COLLARO "CONQUEST"**
Latest 4-speed Autochanger with "Studio" P.U. In maker's sealed carton.
£9.0.0 (*plus 3/6 postage*)

● **B.S.R. "MONARCH"**
Latest 4-speed Autochanger in sealed carton, as advertised.
£9.0.0 (*plus 3/6 postage*)

● **FTAAR GALAXY**
4-speed Autochanger in sealed carton but without guarantee.
£4.0.0 (*plus 3/6 postage*)

1/- BRINGS THE MOST COMPREHENSIVE LIST yet compiled of equipment—components, materials, accessories, valves, books, etc., etc.—it will save you pounds.

RADIO HAM SHACK LTD., 155, SWAN ARCADE, BRADFORD 1, YORKS
THE W. RIDING MAIL ORDER SPECIALISTS

TELEVISION AERIAL COMPONENTS
DESIGNED FOR CONSTRUCTING BAND I & BAND III T.V. AERIALS
ELEMENT DIMENSIONS SUPPLIED FOR ALL CHANNELS

Selecting at random from our new multi-page catalogue :

★ Band III Folded Dipoles *(As illustrated)*
★ Reflector and director rod holders
★ Masthead Fittings for ¾", 1", 1½" and 2" Masts
★ Mast Coupling units for 2" Masts
★ Insulators, both Rubber and Plastic *(As illustrated)*
★ Alloy Tubing for Elements, Cross boom and masting

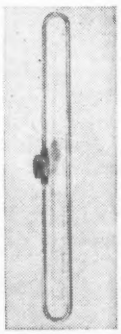

Send 1/- P.O. for the revised, fully illustrated catalogue to :

FRINGEVISION LTD., Marlborough, Wilts. ***Phone 657/8***

SYMBOLS OF SOME IMPORTANCE .... TO ENGINEERS ENGAGED IN ELECTRONICS, RADIO & AUTOMATION

MODEL 351

★ STOCK DELIVERY

NEW PORTABLE

TRANSISTOR TESTERS

POWER TYPE. Simple controls provide speedy testing of Power Transistors with a Collector dissipation of 1W-15W.

- Measurement at grounded Emitter configuration, of Collector leakage current and current gain at two pre-set Base currents.
- Current gain 0-100 and 0-200. Leakage current 0-20 mA.
- Provision is made for testing of all types of Power Transistors, Germanium or Silicon, P.N.P. or N.P.N.
- Built-in A.C. operated Power Supply. MODEL 352 **£48**

STANDARD TYPE. For junction transistors up to 100mW dissipation. Similar in appearance and controls to Power Type, with built-in 4.5V battery and provision for additional external Collector voltage when required.

19GNS.

★ FULLY GUARANTEED

Leaflets on request from sole concessionaires for the United Kingdom :—

AVELEY ELECTRIC LTD.

AYRON ROAD, AVELEY INDUSTRIAL ESTATE,

SOUTH OCKENDON, ESSEX *Telephone: SOUTH OCKENDON 2021/3*

AVELEY ESSEX

doing sums?

HIVAC wire-ended subminiature cold cathode tubes (including these three triodes) are ideal for calculating, switching and controlling circuits where reliability, stability and low cost are essential. These tubes will provide the answer to your problems because

you can count on Hivac cold cathode tubes

Our Technical Service Department will be pleased to supply further information and assist in any problems arising from the use of Hivac tubes.

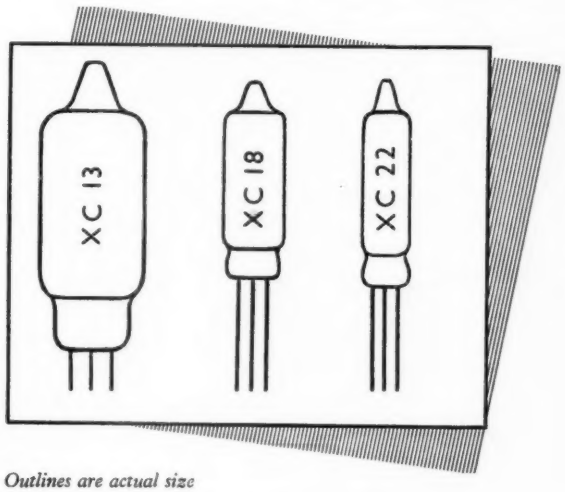

Outlines are actual size

RATINGS (nominal)	XC13	XC18	XC22
Anode strike volts (min)	200	210	210
Anode maintain volts	70	73	70
Trigger strike volts	75	68	69
Trigger maintain volts	55	55	55
Continuous cathode mA	7.5	1.0	0.25

C12.

Hivac Limited *A member of the Automatic Telephone & Electric Group.*

STONEFIELD WAY · SOUTH RUISLIP · MIDDX.

Telephone: Ruislip 3366 *Cables: Hivac, Ruislip*

A FLIGHT SPECIAL

Outstanding annual survey of the world's commercial aircraft

Out 25 July, this magnificent FLIGHT special issue is brimful of up-to-date information on all significant commercial aircraft—from every nation, including Russia. Profusely illustrated with photographs and cutaway drawings—many published for the first time. Don't miss *your* copy—order from your newsagent today!

FLIGHT

OUT 25 JULY · FROM ALL NEWSAGENTS · 1s.6d.

commercial aircraft of the world

Precision
WAVEMETER
CAVITY TUNED

110-230 v. A.C. Complete with mains power lead, aerial assembly. New in transit case. Size: D. 9in., W. 7½in., L. 8½in. 440 Mc/s—466 Mc/s.

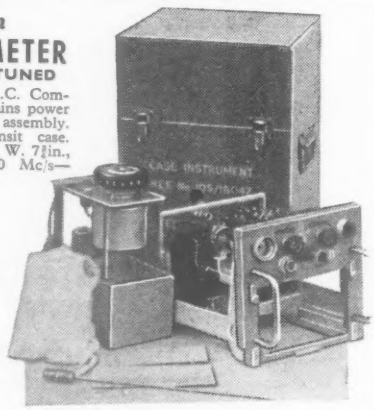

£2.15.0
P. & P. 5/-

LOUDSPEAKERS

18in. L. × 18in. W. × 8in. deep cabinet. 8in. Speaker with Transformer in good condition. **£1.0.0** P. & P. 5/-

17in. L. × 17in. W. × 8in. deep cabinet. 10in. loudspeaker. **£1.5.0** P. & P. 5/-

A Strobe Unit complete with 8 valves and 2 relays. **£1.10.0** P. & P. 5/-

A. PRESTON & SONS
186 Sussex Way, London, N.19 Phone: ARChway 5951

The 'VESCO'
THREE HI-FI CABINETS

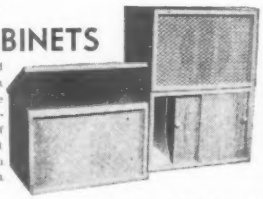

These cabinets are in highly polished light oak, and have been designed as a unit of three, consisting of one storage cabinet with two sliding doors (as illustrated) giving ample room for storage of records and tape spools, a speaker cabinet with a very pleasing gold silk fret, and an amplifier and tape deck cabinet with a lift-up lid.

The dimensions of each cabinet are 1ft. 8in. long × 1ft. 3in. deep × 1ft 2in. high. Nett Trade Price for the complete unit of three £8, plus 20/- carriage and packing.

SEND FOR OUR CABINET LIST FOR DETAILS OF THESE AND MANY OTHER TYPES

Send also for our detailed Wholesale list for Cabinets, Wired Chassis FM/AM. Complete TVs, Radio Aerials, Converters and Sundry Electrical components, e.g., Electrical Shavers, etc.

VES
V.E.S. WHOLESALE SERVICES LTD.
Dept. (W.W.) 11, Gunnersbury Lane, Acton, London, W.3. Acorn 5027

TESTOSCOPE MAINS TESTER

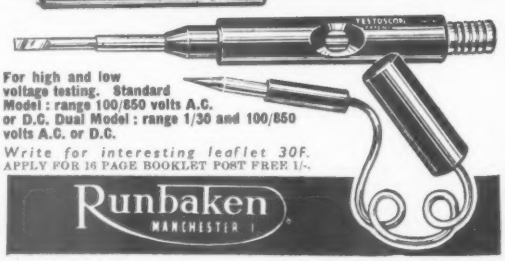

For high and low voltage testing. Standard Model: range 100/850 volts A.C. or D.C. Dual Model: range 1/30 and 100/850 volts A.C. or D.C.

Write for interesting leaflet 30F.
APPLY FOR 16 PAGE BOOKLET POST FREE 1/-.

Runbaken MANCHESTER 1

HI FIDELITY FM RECEPTION..

FM/4U
Head only - **£3.7.6d.**

FM/4L
4′ 6″ mast & lashings - **£4.17.6d.**

FM/4M
9′ mast & lashings - **£7.2.6d.**

FM/Y4 LOFT
£2.17.6d.

demands a fine aerial

Audio engineers and other critical users will find their best answer is a Wolsey FM 4 Element Yagi. These are available in two types and have been carefully engineered to provide optimum signal/noise ratio, whilst maintaining the necessary bandwidth. The folded dipole and reflectors offer a unidirectional directivity pattern, providing high gain combined with mechanical rigidity that have made Wolsey Aerials famous.

PERFORMANCE FIGURES

Forward Gain 8 dBs - - - - Impedance 70 ohms
Bandwidth - - - - - - 10 mc/s at 3 dB points
Front to Back Ratio - - - - - - - - - 25 dBs
Acceptance Angle - - - - - - 90° at 3 dB points

WOLSEY ELECTRONICS LIMITED

CRAY AVENUE · ST. MARY CRAY
ORPINGTON · KENT
TELEPHONE: ORPINGTON 26661-6

(Electronics Division, Gas Purification & Chemical Co. Ltd.)

So easy!

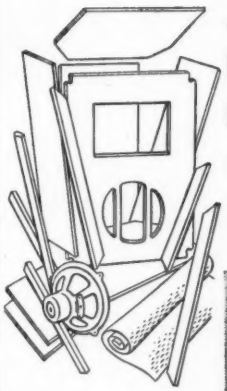

A simple kit brings true high-fidelity within your means

NO HEADACHES with this kit of parts. Everything you need to build an acoustically perfect loudspeaker is here; including the famous Grampian 1255/15 speaker unit, grille material and working diagrams. All parts are accurately finished, machined and drilled, only assembly and polishing to suit your taste remains to be done. Ingeniously designed for either a corner or flat against the wall, the cabinet will enhance your room — to say nothing of your listening!

PRICE of complete kit including 1255/15 Grampian high-fidelity speaker £20

Deferred terms available if desired on complete kit or speaker and cabinet purchased separately.

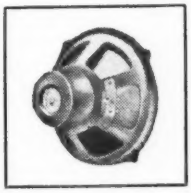

The well-known Grampian 1255/15 high-fidelity speaker unit may be purchased separately if required. It is a 12in unit especially designed for use with high quality amplifiers. It has an extended frequency coverage of from 20 to 15,000 c/s with exceptional performance over the useful audio range. Price of 1255/15 unit only £9.

Write for full details of complete cabinet, copy of the response curve and information about suitable amplifiers today—

GRAMPIAN
REPRODUCERS LIMITED
Makers of High-Quality Sound Equipment
17 HANWORTH TRADING ESTATE, FELTHAM, Middx
Telephone Feltham 2657/8. Telegrams: Reamp Feltham

Andec LIMITED

ELECTRONIC ENGINEERS
& TRANSFORMER SPECIALISTS

TRANSFORMERS
Up to 50 K.V.A.

F.H.P. MOTORS

ELECTRONICS

Your enquiries are invited and we shall be pleased to supply you with a complete catalogue.

ANDEC LIMITED
A.I.D., A.R.B. approved
BENNET ROAD · READING · ENGLAND
Tel. 82401/2

359pp. Illustrated
17s.6d. net; by post 18s.6d

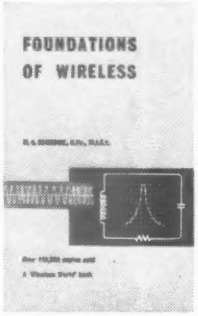

388pp. Illustrated
15s. net; by post 16s.4d.

Ideal books for students

BASIC MATHEMATICS FOR RADIO AND ELECTRONICS 3rd. Ed.

by F. M. Colebrook, B.Sc., D.I.C., A.C.G.I. Revised and enlarged by J. W. Head, M.A.(Cantab.). A complete course in fundamental mathematics including the application of mathematics to radio.

FOUNDATIONS OF WIRELESS 7th. Ed.

by M. G. Scroggie, B.Sc., M.I.E.E. Covers the whole basic theory of radio starting from the most elementary principles and assuming no previous knowledge on the reader's part. This new edition has been almost entirely rewritten and a great deal of new material added.

from leading booksellers
Published for "Wireless World" by Iliffe & Sons Ltd.
Dorset House, Stamford St., London

THE WORLD'S GREATEST BOOKSHOP
FOYLES
FOR BOOKS
FOR ALL YOUR
Technical Books

'That's what I call quick service—I telephoned Foyles at 10 a.m. and the book (although it was out-of-print) reached me by the next morning's post.'
—A Customer's Letter

119-125 CHARING CROSS ROAD, LONDON, W.C.2.
Gerrard 5660 (20 lines) ★ *Open 9-6 (Thurs. 9-7)*
Nearest Station : Tottenham Court Road

Insulating Sleevings

P.V.C.
SLEEVINGS
INSULATED WIRES
and FLEXIBLES
A.I.D. and A.R.B. Approved

PLASTICABLE LIMITED
HAWLEY LANE
FARNBOROUGH, HANTS
Phone: FARNBOROUGH, HANTS 85

The Osmor "SATELLITE"
F.M. RECEIVER
a Sensitive Unit of Quality

A completely stable and drift-free tuner for adding to an existing radio or radiogram, or hi-fidelity amplifier. Installation is simple and convenient because of the small size of the unit and the fact that a tuning scale is not required. The special frequency control circuit ensures that the switch-tuned stations are held precisely.
Complete Kit £7/5/- (less valves).

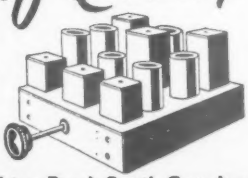

Get these
FREE
CIRCUITS & WIRING DIAGRAMS

T.R.F. Circuits
Battery Circuits
Portable Circuits
S'het Circuits
Mains Circuits
Filter Circuits
T.V. Converter Circuits, etc., etc.

Send 1/- in stamps for the lot!

OSMOR
Dept. (WW25) 418 Brighton Road, South Croydon, Surrey
Telephone: Croydon 5148/9
OSMOR

TRANSFORMERS

All for 220/250V Input, Other Supply Voltages as Required
CONTINUOUS RATING. Short Rating Transformers also available

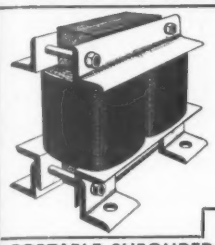

£5/12/- each.
OUTPUTS:
3-6-9-12 V. at 40 amps.
6-12-18-24-30 V. at 12 amps.
5 V. at 125 amps.
12 V. at 50 amps.
110-120 V. at 4 amps.
55 V. at 12 amps.
3.5-8-14-15-16 V. at 20 amps.
6.3 V. at 18 amps or 12.6 V. at 9 amps.

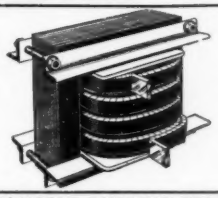

10 V. at 1,000 amps £38.
10 V. at 500 amps £28.
3-5-8-10-15-17-21-25 V. at 100 amps £20.
60 V. at 100 amps £23
110/120 V. at 25 amps £19.
5 V. at 300 amps £12/10/-.
13-13.5-14-15 V. at 60 amps £9/12/-.

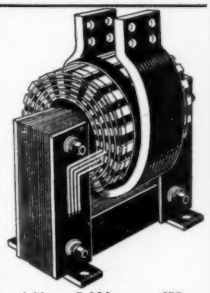

4 V. at 5,000 amps £55.
2 V. at 10,000 amps £52.
3.5 V. at 20,000 amps £110.
2 V. at 30,000 amps £115.
10 V. at 2,000 amps £58.

PORTABLE SHROUDED TRANSFORMERS £8/5/- ea.
6-8-12-18-24-30 V. at 12 amps.
24 V. at 30 amps.
110-120 V. at 4 amps.
12 v. at 50 amps.

MANY OTHER STOCK TRANSFORMERS.

VARIABLE CURRENT TRANSFORMERS. Infinite Variation of Output Current. Amps values apply to short-circuit or near short-circuit loads. Designed for Technical Colleges to demonstrate Electric Arc Welding, Stray Flux, Series-Parallel and High Reactance Phenomena. 70 Volts Open Circuit. 25 Volts on load. Intermittent Rating. 10-100 amps £20. 25-60 amps £17. 35-200 amps £36.

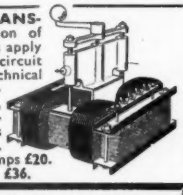

RECTIFIER SETS

All for 200/250 AC (Other supply voltages available)

Rectifier Sets with DC Output Control by internal taps and external Rheostats. DC Volts ON LOAD are stated.
110/120 V. DC at 8 amps £20 0 0
200/250 V. DC at 6 amps £27 0 0
200/250 V. DC at 18 amps £34 0 0
35/38 V. DC at 50 amps £28 0 0
Fitted Ammeters and Voltmeters £2/10/- per Meter.

Rectifier Sets with DC Output Control by Tap Switches and Rheostat. Fitted with Fuses and Ammeter. DC Voltages ON LOAD are stated:
12/25 V. DC at 12 amps £15 10 0
12/25 V. DC at 20 amps £19 0 0
12/15 V. DC at 15 amps £13 10 0
90/115 V. DC at 25 amps £40 0 0
6/12 V. DC at 5 amps £6 0 0

TRANSFORMERS WITH SWITCHED TAP CONTROL
Available with one or more Switches, Ammeters, Fuses etc.

Many other STOCK RECTIFIERS

Enquiries are invited for Transformers and Rectifiers. We specialise in HEAVY CURRENT Equipment.

HARMSWORTH, TOWNLEY & CO.
2 JORDAN STREET, MANCHESTER 15 Central 4281

The BARGAIN of a LIFETIME

5,000 v. INSULATION TESTERS

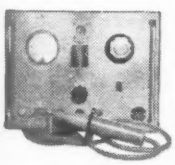

5,000 Insulation Testers

Output voltage 0-5,000v. A.C. or D.C. continuously variable from zero.
Output current 5 milliamp max. for D.C. 10 milliamp max. for A.C.
Voltage indicator meter for both A.C. and D.C.
Voltage reading drops to zero and Magic Eye closes.
Voltage indication by Magic Eye.
Power supply 200-250 A.C.
Dimensions 18 x 18 x 13in.
Weight 30lb.

Made for flash testing and for the measurement of the breakdown voltage of electrical components and insulation. A spring-loaded switch is fitted in the test prod which keeps the 200/250v. supply switched off.

Original cost £75 . 0 . 0.
Our price Brand new
£17 . 10 . 0
LIMITED QUANTITY ONLY.

UHF. MARCONI WAVEMETERS TF643B
NEW IN FITTED CASE £10 EACH
Much Below Maker's Price

HARRINGAY SUPPLIES LTD.
423 Green Lanes, Harringay
London, N.4.
Telephone : MOUntview 5241/2.

HOME RADIO OF MITCHAM

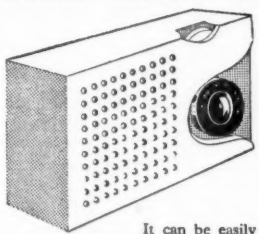

invites you to build
the amazing new

MINI-7

This 7-transistor superhet pocket portable, with 2½in. speaker, gives guaranteed results on its internal ferrite rod aerial.

It can be easily assembled in four stages, and all parts are available from our stock. Make one of these amazing little sets for your holidays.

Full constructional details, including wiring diagrams and price list, sent on request. Write for your copy today—price 1/9 post paid.

London and Home Counties Distributors for
PANDA TRANSMITTERS
The 'Explorer' and 'Cub' available for immediate Delivery

EDDYSTONE
RECEIVERS—
prices from £34 . 16 . 0

Immediate delivery (as we go to press) of 820, 870, 840A, 750 and and 888A. Send 3d. stamp for full details and specification.

THE EDDYSTONE '870'

HOME RADIO (MITCHAM) LTD
Dept. W.
187 LONDON ROAD, MITCHAM, SURREY. *Tel: MITcham 3282*

TRANSISTORWISE

"RECO" ONE TRANSISTOR POCKET RADIO

Complete kit with ferrite rod vari Q aerial. 3 position on/off and wave band switch. Personal phone etc. Case size 1½in. x 4½in. x 4½in. Yours for **30/-** and 2/- p.p.

"RECO" MIDDY TWO-TRANSISTOR POCKET RADIO

This fine receiver is similar to the Middy-3, but is less sensitivity control. Amazing performance. Covers medium and short wave band or medium and long waves **3/6** extra. Nothing else to buy. Complete kit with balanced armature output unit **49/6** or with "Sonotone" miniature dynamic earpiece **55/-**, p.p. 2/3.

"RECO" SPECIAL TRANSISTOR THREE

This fine receiver has now been greatly improved with the addition of a handsome looking chromium plated telescopic aerial 11½in. closed, 48in. extended. Has sensitivity control and High "Q" Frame aerial. Complete kit with choice of "Sonotone" miniature earphone or balanced armature output unit which, in areas of reasonable signal reception, can be mounted inside case. Case size 6¼in. x 4¾in. x 1¼in. with red plastic ornamental unit cover, **77/6.** Less telescopic aerial and with balanced armature output unit **65/-**. p.p. 2/6.

"RECO" MIDDY THREE TRANSISTOR POCKET RADIO

Small in size, big in performance. Ideal for invalids. Take it on holiday. Vest pocket size 4¼in. x 3½in. x ⅞in. In areas of reasonable signal reception receives local stations on built-in ferrite rod Vari "Q" aerial. Covers 180 to 500 metres. Complete with three transistors and pencell. Price including "Sonotone" miniature earphone with moulded ear insert and lead **65/-**. P.P. 2/3. Overseas orders. Carr. 10/- extra. All "Reco" kits with ferrite rod aerials can now be supplied either for medium and long waves **(3/6** extra) or medium and short wave band. Case finish for Middy 3, Red/Black or Red/Coral Pink. Please state preference. Circuits, Pictorial wiring diagrams, parts price list for all the above, **2/6.**

RADIO EXCHANGE CO., DEPT. W.W.
27A. Harpur Street, BEDFORD. Phone : Bedford 2367

Essential to all in the electrical industry

This valuable reference book, compiled by ELECTRICAL REVIEW, meets a real need in the electrical profession and industry. Containing about 8,000 entries, it gives particulars of the education, careers and general activities of leading men and women in the consulting, manufacturing, contracting, trading and other branches of the electrical industry, Government departments, etc.

27s 6d net by post 29s 3d

ELECTRICAL
WHO'S WHO, 1958-59

from leading booksellers

Electrical Review Publications Ltd.
Dorset House, Stamford Street, London, S.E.1

Send us your enquiries for all types of

QUARTZ CRYSTALS

for:

RADIO FREQUENCY CONTROL
FILTER PURPOSES
ULTRASONIC PURPOSES

METALLIZED TO SUIT REQUIREMENTS.
ANY SHAPE AND SIZE CUT TO SPECIFICATION.

PIEZO LIMITED

26 St. Albans Rd., Watford, Herts. Tel: Watford 7808

A. C. SOLENOID type SAM

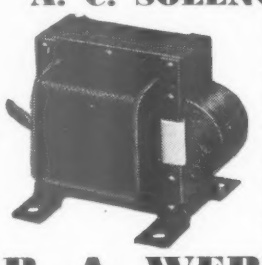

Increased Performance
Continuous 14 ozs. at ¾"
Instantaneous to 5½ lbs.
Same dimensions as Type SA.

Larger and smaller sizes available. Greatly increased discounts for quantities. Also Transformers to 7kVA 3 Phase.

R. A. WEBBER LTD.
18, FOREST ROAD, KINGSWOOD, BRISTOL. Phone: 67-4065

Hi - Fi

Obtainable from

L. WESTWOOD 46 GEORGE ST. PHONE OXFORD 47783

AMPLIFIERS

Quad. Mk. II and Control Unit	£42 0 0
Leak T.L.12	£18 18 0
Leak Varislope III	£15 15 0
R.D. Amplifiers. Complete from	£17 10 0
T.S.L. (with cabinet)	£13 13 0
Tripletone 12 w. Hi-Fi Major	£15 18 9
Tripletone De Luxe	£9 7 6
Tripletone Junior	£6 19 6
Armstrong A10	£32 0 0

TUNERS VHF/FM
Quad - Eddystone - Rogers - Jason - T.S.L. - Armstrong

TRANSCRIPTION MOTORS

Garrard 301	£26 8 0
Connoisseur	£28 11 0

Lenco and Collaro Transcription Units.

TAPE DECKS. Tandberg Stereo, Truvox, etc.

MICROPHONES. Moving Coil and Crystal.

SPEAKERS

Tannoy Dual Concentric 15in. with X-over	£35 12 0
Tannoy Dual Concentric 12in. with X-over	£29 5 0
Tannoy Direct Radiator 12in.	£14 0 0
Goodmans Axiom 300	£11 5 9
WB.HF.10/12	£4 19 9

Tweeters and a range of Wharfedale Units stocked.

CABINETS. Goodmans and W.B., etc.

PICK-UPS AND STEREO CARTRIDGES

Garrard TPA10 T/O Head Diamond L.P. £15 9 4
Connoisseur, Leak, Acos, B.J.
Tannoy and Goldring Cartridges.

EDDYSTONE Communications Receivers

Model 680.X	£120 0 0
Model 750	£78 0 0
Model 840A	£55 0 0
Model 870	£34 16 0

EXCELLENT STOCKS OF VALVES AND COMPONENTS ALWAYS AVAILABLE

SAMSON'S SURPLUS STORES LTD.

HEAVY DUTY L.T. TRANSFORMERS. No. 1. Pri. 230 v. Sec. 50 v. 50 amps., adjustable by voltage regulator stud switch on primary. Built in steel case with meter reading 0-100 v. Mains switch and O.P. sockets, will stand 100% overload. Supplied brand new **£15.** Carr. according to distance.
No. 2 Pri. 230 v. Sec. tapped 4 v., 6 v., 10 v., 200 amps. **£8/10/-.** Carr. 7/6.
No. 3. Pri. 200-250 v. Sec 50 v. 30 amps. **£6/10/-.** Carr. 7/6.
No. 4. Pri. 200-250 v. Sec. tapped 28, 29, 30, 31 volts, 21 amps. **£4/10/-.** Carr. 7/6.

ADMIRALTY HEAVY DUTY DPCO. 15 amp. knife switches, metal shrouded, 7/6. P.P. 2/6.

ADMIRALTY VOLTAGE REGULATORS. 1,000 ohms. 0.59-0.16 amps. rotary stud switch type. 32 contacts, completely enclosed, with brass control handle. Supplied brand new in maker's cartons, 10/6. P.P. 3/6.

EVERSHED AND VIGNOLES BRIDGE MEGGER TEST SET. 100 volt, complete with resistance box and instructions. An ideal instrument for technical schools and laboratories, **£10/10/-.** Carr. 5/-. Brand new.

SPECIAL OFFER OF EQUIPMENT WIRE. 100-yard drums. Rubber 40/0076 stranded copper by famous manufacturers. Brand new, 8/6 per drum. P.P. 2/6.

TELEPHONE CABLE. Single D3, 1/3rd-mile drums, 19/6. Carr. 4/6. Commando Telephone Cable, P.V.C., 1,000-yard drums. Very useful in the home and garden, **8/11.** P.P. 3/6. Five drums in maker's carton, 42/6. Carr. 7/6.

WILLARD 24-VOLT 11 A.H. AIRCRAFT BATTERIES. Completely enclosed in metal containers. Size 8 × 7½ × 7½in. Supplied new in maker's cartons with charging instructions, 62/6. Carr. 5/-.

ADMIRALTY 24-VOLT 3 A.H. BATTERIES. Wood cases. Size 12 × 7 × 4½in., 29/6. Carr. 5/-.

ADMIRALTY 4-VOLT ACCUMULATORS. Cap. at 12-hour rate, 18.5 A.H. Size 7 × 4¼ × 3¾in., 10/6. P.P. 3/6.

169-171 EDGWARE ROAD, LONDON, W.2

Tele. PAD. 7851 and AMB. 5125

CONDENSERS

AR88 FILTER PACK. 3×4 mfd., 500 v. (new). 25/- each. P.P. 2/6.

BLOCK PAPER CONDENSERS
0.25 mfd., 2 kv. wkg., 2/6 each. 1 mfd., 400 v wkg., 2/6 each. 1 mfd., 2 kv wkg., 3/6 each. 2 mfd., 600 v. wkg., 4/- each. 3 mfd., 400 v. wkg., 4/- each. 4 mfd., 400 v. wkg., 4/6 each. 4 mfd., 1 kv. wkg., 5/6 each. 6 mfd., 400 v. wkg., 5/6 each. 8 mfd., 1,200 v. wkg., 11/6 each. 0.1 mfd., 4 kv. wkg., 4/6 each. 0.5 mfd., 5 kv. wkg., 7/6 each. 0.5 mfd., 2 kv. wkg., 2/6 each. 1 mfd., 750 v. wkg. 3/- each. 2 mfd., 400 v. wkg., 3/6 each. 2 mfd., 1.5 kv. wkg., 4/6 each. 3 mfd., 400 v. A.C. wkg., 5/- each. 4 mfd., 600 v. wkg., 5/- each. 4 mfd., 2 kv. wkg., 6/6 each. 8 mfd., 500 v. wkg., 4/9 each. 10 mfd., 440 v. A.C. wkg., 12/6 each. 80 mfd., 300 v. wkg., 27/6 each. 50+50 mfd., 300 v. A.C. wkg., 30/- each.

VARIABLE CONDENSERS, air spaced, 5 pf., 15 pf., 25 pf., and 50 pf., with 1in. spindle, 2/- each. Pre-set types, 1/6 each. Double spaced, 25 pf., 3/6 each., 100 pf., 4/- each.

19 SET AERIAL VARIOMETER MK. II. As new, 25/- each. P.P. 2/-.

INSULATORS (Pyrex feed through), new, 7/6 each.

RHEOSTATS (by OHMITE). 25 ohms, 2 amps., 17/6 each (new). W/W pots, 6 ohms, 5 watts, 1¼in., spindle, 2/6 each.

R.F. UNITS, type 26B. Brand new in cartons, 18/6 each. P.P. 2/6.

RECEIVER BC 624C (part of SCR 522) This well-known receiver covers 100 to 156 M/c., the "C" is the latest type which incorporates several mods. over the earlier models, noise limiter. AVC, squelch circuit and extra audio stage. The power requirements are 300 volts 70 m/a. H.T. 12 volts 3 amp. L.T. New and complete with 11 valves, £2/2/6 each with circuit. P.P. 3/6.

SLIDING RESISTORS, 26 ohms 6.5 amps. Brand new, 30/- each. P.P. 2/6.

ROTARY CONVERTERS, 24 volt D.C. output, 50 volts A.C., at 200 watts, £3/10/0 each. P.P. 7/6.

TRANSMITTERS BC 640B, 100-156 mc/s. Complete unit, £30/0/0.

AMPLIFIER for BC 640. Complete with valves, £3/10/0. P.P. 10/-.

DRIVER UNIT for BC 640. Complete with valves, £3/10/0. P.P. 10/-.

MODULATOR UNIT for BC 640. Complete with valves, £4/0/0. P.P. 10/-.

POWER UNITS for BC 640. £6/10/0. P.P. 15/-

CONTROL UNIT, £1/10/0. P.P. 5/-.

VARIAC PANEL. 0-230 volts at 9 amps, £11/10/0. P.P. 15/-.

VALVE HOLDERS I.O., UX., B7G, Ceramic etc., quantities available.

MASTER OSCILLATOR RCA MI-19427-B. This is a highly stable source of radio-frequency power which may be used between the limits of 2-20 mc/s to a radio transmitter. As new, less valves, £12/10/0.

SLYDLOK FUSE HOLDERS, 100 amp 25/- each. P.P. 2/-. 5 and 15 amp 2/- each. P.P. 1/-.

TERMS C.W.O. All goods offered are ex-WD. S.A.E. for Enquiries.

W. MILLS
3-B TRULOCK ROAD, TOTTENHAM, N.17
Phone: Tottenham 9213 & 9330

120 INCHES OF SCALE

The CR50 Bridge covering 10pFd to 100mFd and 1 ohm to 10 Megohms in fourteen ranges has a total length of scale of over 120 inches thereby ensuring easy and accurate readings. A leakage test is incorporated for condensers. Complete with valves, instructions and ready for operation from 200/250 volt A.C. mains. **£8/2/6** plus 4/6 carr./packing.

SG50 SIGNAL GENERATOR covers 100kc/s to 80Mc/s in six ranges on fundamentals. A de luxe instrument in heavy gauge metal case with engraved perspex scale. Ready for operation from 200/250 volt mains. **£9** plus 6/- carr./packing.

VV60 AUDIO VOLTMETER measures 1 milli-volt to 100 volts in five ranges. **£14** plus 4/6 carr./packing.

Further details sent by return of post on receipt of stamped addressed envelope.

TRADE supplied direct. CREDIT TERMS available.

GRAYSHAW INSTRUMENTS
126 Sandgate High Street, Folkestone, Kent
Phone: Folkestone 78618

▶ **RADIO and TV ENGINEERING**
▶ **RADIO and TV SERVICING**
▶ **ENGINEERING MATHEMATICS**
▶ **PRODUCTION ENGINEERING**
▶ **ELECTRONICS · MANAGEMENT**

▶ **Examination Courses for:** Brit. I.R.E., C. & G. Telecommunications, R.T.E.B. Certificate Society of Engineers, Brit. Inst. of Management.

▶ **PRACTICAL RADIO COURSE.**
A course in radio, electronic and electrical theory. You build a T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.
You learn at home in your own time, under expert tuition. Moderate fees include all books.

POST THIS COUPON TODAY for FREE book on careers in Radio, etc. and full details of I.C.S Courses.

Start today the **I.C.S. way!**

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 223L, International Buildings, Kingsway, London, W.C.2.

Name.....Age.....
(Block letters, please)
Address.....
.....
Occupation.....8.58

INTERNATIONAL CORRESPONDENCE SCHOOLS

CHAS. H. YOUNG, LTD

Dept. "W," 110 Dale End, Birmingham, 4. *CENtral* 1635

Headphones. High resistance (4,000 ohms). Very sensitive, **12/6.** Low resistance. C.L.R. **8/6**; p. and p. on either, 1/6.

Heavy-duty adjustable rheostats. 0.4 ohm, 25 amp. Beautifully made, **5/-** each. P. & P. 2/-.

Multi-Way Cable ¼in. diameter. 7 colour coded wires, any length cut. **1/3** per yard. P. & P. min. 1/6. **10-Way cable** (5 pairs). Screened and plastic covered, **2/-** per yard. P. & P. min. 1/6.

Don't miss this special offer:

CRYSTAL CALIBRATORS

1,000 kc/s crystal controlled, with switched 100 kc/s and 10 kc/s locked multi-vibrators.

This excellent unit is as new, and is contained in polished Bakelite case with carrying handle. The circuit uses 6 valves and operates from 2 v. l.t. and 120 v. h.t.

PRICE—only **£3.10.** complete with crystal and valves; or with A.C. power unit, **£6.10.**

3in. Aerial Insulators. Ribbed glass, **1/6** each or 6 for **7/6.** P. & P. 1/6.

Condensers. 8 mfd. 750 v., **5/6** each. Post 1/6. Type III, 8 mfd. 1,000 v. 10/6. P. & P. 1/9.

Copper Aerial Wire. 14 g. H/D 140ft., **17/-**; 70ft. **8/6.** P. & P. 2/-. Stranded 7/25, 140ft. **10/-**; 70ft. **5/-**; P. & P. 2/-.

Dual Range Voltmeters. 0-5 and 0-100 v. m.c., 1,000 Ω/v. Ranges easily extended. Complete with leads and prods. Solid leather carrying case, 6¼ × 5 × 2¼in. Only **25/-**, post free.

Rack Mounting Panels, all 19in. long by 5¼in., 7in., 8¼in., or 10¼in., **5/9, 6/6, 7/6, 9/-** respectively. Post 2/-.

Absorption Wavemeters. 3 to 35 mc/s. in 3 switched bands complete with indicator bulb, **17/6.** Post free.

Parmeko Made H.D. Transformers. 30 v. primary, secondary 620/350/375/0/375/350/620, 275 v.A. Gives 620 v. at 200 mA. simultaneously with 375 v. at 250 mA. Also 2-5 V, 3 A. for 5R4GYs, etc. Worth at least £7. Our price **£3,** carr. paid. Inland only, not Eire or overseas.

We have the most comprehensive stock of Hi-Fi equipment in the Midlands, including QUAD, LEAK, W.B., RCA, ROGERS, WHARFEDALE and GOODMANS. Send for details, or call for a demonstration today.

No C.O.D. under £1. *Please print your name and address.*

MIDLAND INSTRUMENT CO.

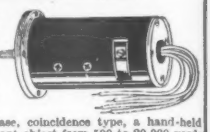

HUGHES MOTOR, shunt wound, 12-v. 1½-amp., speed 5,000 r.p.m., reversing, size 3¼in. long, 1¼in. dia., ¼in. shaft, weight 20 oz., a very superior motor designed for anti-radar equipment, new, unused, **10/-**, post 1/6. Ditto fitted reduction gear, giving a final drive (¼in shaft) of either 320 or 160 r.p.m., state which required. **12/6,** post 1/9.

BARR & STROUD RANGEFINDERS, 1-metre base, coincidence type, a hand-held instrument that gives a range in yards of any distant object from 500 to 20,000 yards (13 miles). The variable focus 14× right eyepiece provides two images of the object viewed; one from the right objective the other from the left. When these two images are brought into coincidence the range in yards can immediately be read in the left eyepiece. Fitted two filters and other refinements. A very high-quality instrument, original cost £180, our price new or near new condition, supplied in stout fibre containers, **£5,** carriage 100-m. **7/6,** 200-m. **10/-,** 300-m. **12/6.** N.I. **20/-.**

CHASSIS. U.S. manufacture all aluminium, 12½ × 8 × 5¼in. complete with top cover, some items have been removed, remaining are:—25 Amphenol midget ceramic B7G type v/holders, complete with cans, over 70 colour coded 5% resistors, also many ceramicons and other conds., trimmers, padders, fixed and variable inductances, transformer, v/control, etc., new, unused, bargain, **10/-,** post 3/6.

ZAMBONI PILES, dry voltaic type, consists of 3 piles, each 6in. long by 1in. dia. in high insulation mount to give 1500-v., taken from new unused infra-red receivers, **5/-,** post 1/6, also variable focus eyepieces and Wratten filter backed objectives taken from same instrument, **5/-** set, post 1/6.

RELAYS, all new unused, U.S. type, 7600-ohms, single pole make, size 2½ × 2 × 1¼in., **3/6,** post 9d., ditto, 60-ohms, 3-pole 3-make, size 1½ × 1½ × 1in., **2/6,** post 9d., Siemens H.S. relays, 145-ohms, single-pole changeover platinum contacts, in metal cases with terminal block, **5/-,** post 1/6, 5C/649 relays, 26-ohms, 9-14 v., single make 40-amp. D.C. contacts, in Bakelite cases, 2½ × 2½ × 1¾in., **2/6,** post 1/-.

SIGHTING TELESCOPES by Ross, Taylor, Hobson, etc., these high quality instruments contain four 40 mm. dia. achromats, 2 of 3in. focal length, 2 of 3¼in. focal length, also an 18 mm. dia. image erector achromat, 4 screw fine adjustment cross graticule, length 16in., weight 7 lbs., new and boxed, **35/-,** post 3/3.

TELEPHONE SETS, consists of two combined microphones and receivers, which when wired up by ordinary twin flex, provides perfect 2-way communication, excellent results at 1 mile range have been reported, self-energised, no battery required, set complete, new unused, **7/6,** post 1/3; suitable twin 14/36 p.v.c. up to 300ft. lengths at 1d. per ft. supplied, postage each 20ft. flex 3d. extra.

TIME DELAY SWITCHES, 24 v. clockwork type by "Venner," in smart metal cases with external press wind, in addition to clockwork mechanism contains two electromagnets, 5-pole cam-operated contacts, etc., new and boxed, **5/-,** post 1/6.

ELECTRIC PUMPS suitable for most liquids, the popular cylindric immersible type, 24-v., at which they deliver 10-g.p.m. at 20ft. head, also give excellent performance at 12 v., new in sealed cartons, 4ft. long, **35/-,** carriage 5/-.

MOTOR GENERATORS, 4½in. long, 2¼in. dia., weight 3-lb., totally enclosed, black crackle finish, input 27-v., 1.5-amps., output 285-v., 60-m/A., from 12-v. output is approx. 130-v. at 40-m/A., ideal for operating electric razors from 12-v. car battery, new, unused, **12/6,** post 2/-.

GRAMOPHONE MOTORS, dual voltage 100/130-v., 200/250-v. A.C. mains, size 2½ × 2 × 1¾in., weight 18-oz., ¼in. long, ⅛in. dia. shaft, speed 1350 r.p.m., rubber bushed mounting bracket, a superior motor of recent manufacture, brand new, boxed, **15/-,** post 1/6.

Many other Bargains; send stamped addressed envelope for lists.

MIDLAND INSTRUMENT CO., MOORPOOL CIRCLE, BIRMINGHAM, 17

Tel.: HAR 1308

MIDDLESEX COUNTY COUNCIL
Education Committee

WILLESDEN TECHNICAL COLLEGE,
Denzil Road, Willesden, N.W.10.

Part-time Day and Evening Courses—Session 1958-59.

Higher National Certificate Radio Course leading to Graduate Membership of the British Institution of Radio Engineers; Higher National Certificate Power Course.

City and Guilds of London Institute Telecommunications Courses for the preparation of students to Full Technological Certificate level.

Advanced courses in Electronic Measurements, Computers and Industrial Electronics.

PROSPECTUS FREE on application to the College.

C. E. GURR, M.Sc., Ph.D.,
Secretary to the Education Committee.

NORTHERN POLYTECHNIC

SESSION 1958/59

ADVANCED PART-TIME COURSES IN:—
ELECTRONICS AND MICROWAVE PHYSICS
ELECTRICAL DISCHARGES IN GASES
SOLID STATE PHYSICS

Students with a suitable degree in Physics, following one of these courses, accompanied by practical work, can proceed to the M.Sc. degree of the University of London.

The lectures are not confined to such students, but are open to any student working in appropriate fields.

Enquiries should be addressed to the

Head of the Department of Physics,

Northern Polytechnic, Holloway, London, N.7.

JASON TAPE UNIT *jsm/1*

An exclusive Somerset Murray design

- Instantaneous monitoring, adjustable record replay characteristics, and bias control.
- Distortionless square-wave, reproduction between 40 and 18,000 c/s at 15 i.p.s.
- For decks with, or capable of being fitted with 3 heads.
- Controls can be set to C.C.I.R. and N.A.R.T.B. recommendations.
- Self-powered and styled for shelf mounting in conformity with Jason Matching Equipment.
- AN ORIGINAL SOMERSET MURRAY DESIGN EXCLUSIVE TO JASON
- *Advance information sheet on request.*

£37 . 0 . 0

THE JASON MOTOR & ELECTRONIC CO. 3-4 (E) GT. CHAPEL ST., OXFORD ST., LONDON W.1. *(Between Oxford Circus & Tottenham Ct. Rd. Stns. Und.)* GER 0273/4

THE LONG PLAYING RECORD LIBRARY (Selective) CLASSICAL CATALOGUE AND HANDBOOK FOR 1958

INCLUDING POSTAGE & PACKING **3/6** INCLUDING POSTAGE & PACKING

EASILY THE BEST VALUE IN THE GRAMOPHONE WORLD TODAY AND AN ESSENTIAL PURCHASE FOR THE RECORD COLLECTOR AND AUDIO ENTHUSIAST

CONTENTS

- A selective list of *all* L/Ps of good music well reviewed by the critics—over 4,000 recordings listed.
- A basis for a 1958 record collection—100 recommended L/Ps.
- 50 L/Ps specially suitable for demonstrating high fidelity equipment.
- The care and reproduction of L/Ps.
- Groove jumping and groove repeating.
- The use of amplifier controls.
- Full details of Library membership (at approx. 1/- per week each L/P borrowed).

SEND 3/6 FOR YOUR COPY NOW

ANNOUNCING

THE PERFECT STYLUS CLEANER

- Its use is essential for High Fidelity disc reproduction.
- Increases stylus life. Reduces record wear!

STYLCLEAN

Research has shown that if foreign matter is left adhering to the stylus, increased record and stylus wear results. Furthermore, so high are the temperatures generated at the stylus tip by the stresses of modern recording that dust can be literally welded into the L/P surface as it is played.

- STYLCLEAN REMOVES ALL DUST AND FOREIGN MATTER.
- A SINGLE SUPPLY OF STYLCLEAN WILL LAST INDEFINITELY.

ONLY **1/9** PLUS 3d POSTAGE & PACKING

THE L/P RECORD LIBRARY
SQUIRES GATE, STATION APPROACH
BLACKPOOL, LANCS.

FACTORY FRESH SALES SERVICE

FACTORY FRESH — THE LONG PLAYING RECORD LIBRARY — FFSS — SALES SERVICE

ALL NEW L/Ps SUPPLIED TO ORDER BY THE LONG PLAYING RECORD LIBRARY ARE NOW TREATED BY THE "PARASTAT" PROCESS AND THUS BECOME PERMANENTLY ANTI-STATIC AND RESISTANT TO DUST.

OTHER FEATURES OF THIS UNIQUE SERVICE ARE:

Any record purchased is not only a band new, guaranteed unplayed factory copy but it has been obtained from the manufacturers by special order for the purchaser. Besides being unblemished the disc is also *as up-to-date a pressing as currently available in this country.* This is tremendously important when it is realised that many of the older L/Ps (especially Decca) are currently being recut from the master tapes by the manufacturers *with marked improvement in reproduction.*

ANNOUNCING

THE MACKIE PARALLEL TRACKING ARM

Offering at last to the audio-connoisseur, perfect radial and tangential tracking.

- The arm is carried on two steel balls only, thus reducing bearing friction to an absolute minimum.
- Side pressure on stylus—virtually nil.
- Stylus and record wear reduced almost to a point of non-existence.
- Arm length of 2in. eliminates inertia.
- Usable with any cartridge.

(Send s.a.e. 2½d for introductory leaflet)

★ **Completely up-to-date, revised impressions**

TELEVISION RECEIVER SERVICING

Volumes I and II *by E. A. W. Spreadbury, M.BRIT.I.R.E.*

This work, comprising two volumes, has been specially written for radio and service engineers who wish to acquire a thorough knowledge of television servicing. Both of those volumes have been thoroughly revised and enlarged. In volume 1 there are new sections on S/C Linearity Coils, Complete C.R.T. Renovation; and Wide-Angle Tubes. The section on Flywheel Sync has also been expanded. In addition the section on Instruments has been brought up to date and re-illustrated. The whole of volume 2 has been revised to bring it up to date, and 46 pages have been added to deal with the new techniques and circuits necessitated by the introduction of alternative programmes. Most of the new material has been added to the chapter on Aerials, which has been enlarged to include Band III aerials and dual band aerials that receive both sets of programme. Most of the many unconventional and complicated types of aerials, and the manner in which they operate are described. There is also a new section on Communal Aerial Systems.

from leading booksellers

Vol. I: Time base circuits . Vol. II: Receiver and power supply circuits

21s. net by post 22s. 3d. each volume profusely illustrated

Published for "Wireless & Electrical Trader" by
ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

PREMIER

207, EDGWARE ROAD, LONDON, W.2. Tel: AMB 4033 & PAD 3271

YOUR LEADING DO-IT-YOURSELF

THE "Petite" PORTABLE

MAY BE BUILT FOR **£7-7-0** plus 3/- post & packing.

Batteries extra.
HT 10/- (Type B126) or equivalent.
LT 1/6 (Type AD 35) or equivalent.

- ★ Size only 8in. x 8in. x 4½in.
- ★ Weight including batteries 5½lb.
- ★ 4 valves of the economy type.
- ★ Medium and long wave superhet circuit.
- ★ High Q frame aerials.
- ★ High sensitivity on both wavebands.
- ★ Prealigned IF transformers.
- ★ 5in. speaker of the latest type.
- ★ Automatic on/off switch operated by lid.
- ★ Designed in our own laboratory.
- ★ Backed by an up-to-date Technical Information Dept.
- ★ Components available separately if desired.
- ★ Simple to construct, using normal soldering methods.
- ★ Instruction book 1/6.

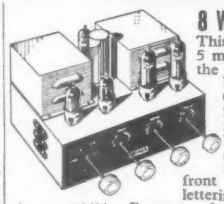

8 WATT AMPLIFIER

This design includes 5 miniature valves of the latest types, an Ultralinear Output Transformer suitable for Speakers of 3 and 15 ohms, and a very attractive Perspex front panel with gold lettering, complete set of parts £8/8/-. Postage and packing 5/- extra. Or £10/19/6 built and tested.

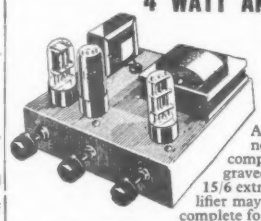

4 WATT AMPLIFIER

MAY BE BUILT FOR **£4.10.0** plus 2/6 P.P. Instruction Book 1/- post free.

A steel case is now available, complete with engraved panel, for 15/6 extra. The amplifier may be supplied complete for £5/5/- plus pkg. and post 3/6, or fitted in case at £6 plus pkg. and post 3/6. Engraved panel 3/6. Post free.

DRAMATIC PRICE REDUCTIONS

SUPERHET may be built for £7.7.0 plus 3/- p.p.

T.R.F. may be built for £5.10.0 plus 3/- p.p.

These two receivers use the latest type circuitry and are fitted into attractive cabinets 12in. × 6½in. × 5½in. in either walnut or ivory bakelite or wood (1/- extra). Individual instruction books 1/- each, post free.

PREMIER BATTERY ELIMINATOR

Housed in two containers which are to replace AD 35 and B126 Batteries.

KIT **37/6**

Plus 2/- post and packing.

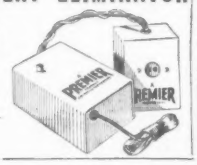

WHY BUY SURPLUS OR RECONDITIONED TUBES WHEN THESE FULLY GUARANTEED WICE ANGLE TUBES ARE AVAILABLE? THE LATEST TYPE 17in. RECTANGULAR TUBE AT £17 (INCL. TAX), POST AND PACKING 21/- EXTRA.

The Latest COLLARO 4-speed single player £4/12/6
Plus 2/6 packing and carriage.

Build the
ONE VALVE BATTERY RECEIVER
AS SHOWN ON B.B.C. T.V.

This Receiver contains a DAF96 valve and a pair of 4,000 ohm headphones and is powered by a combined 67½ and 1½ volt battery.
Price complete with headphones and including battery **45/-**
Send for free diagram.

★SEND 3d. STAMP FOR OUR LATEST CATALOGUE.

Read what a customer says about the "MAYFAIR" Televisor :—

"I am writing to tell you hat this set is a complete success, it is all you claim for it—Plus.

Some 40 miles from the station a picture was obtained with a short length of flex, while a somewhat crude loft aerial produces results which astound my neighbours with their expensive factory-made sets.

Construction was begun in some trepidation, the groaners implying that this was a somewhat risky operation to undertake, that the picture received wou'd be an inch wide stripe on the screen, that the coils would be out of line, etc. You can imagine my delight when I switched on for the first time to find that all the controls performed their various functions exactly—on sound and vision. This achievement on your part and mine gives added pleasure to viewing. Congratulations on an excellent circuit and kit."

★ B.B.C. & I.T.A. DESIGN
MAY BE BUILT FOR PLUS COST OF C.R.T. **£33-7-11**

Build in 5 Easy Stages. Full Construction details available. Instruction Book 3/6 Post Free.

PLEASE ADDRESS ALL MAIL ORDER ENQUIRIES TO

RADIO CO

SELF SPECIALISTS 23 TOTTENHAM COURT RD., LONDON, W.1. Tel: MUSeum 3451

Build this New

TAPE RECORDER KIT

for only

£38.15.0

This Kit comprises:

2-speed Lane Mk. VI Deck	£18/10/-
Premier Tape Amplifier complete with separate plug-in type power pack	£14/-/-
7x4 Elliptical Speaker	£1/1/6
De Luxe Cabinet with gilt fittings and detachable lid	£4/19/6
Reel of Scotch Boy 1,200ft. Tape and empty Spool	£1/11/6
Latest Type ACOS microphone	£2/15/-

All the above sections can be purchased separately.

The New De-Luxe

TAPE RECORDER TR3

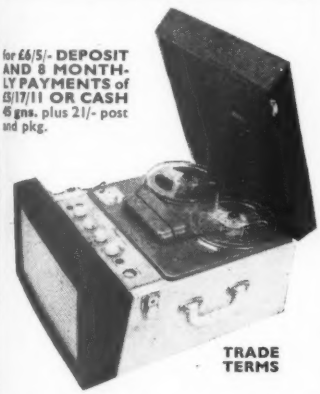

for £6/5/- DEPOSIT AND 8 MONTHLY PAYMENTS of £3/17/11 OR CASH 6gns. plus 21/- post and pkg.

TRADE TERMS

Case finished in Red and Cream with Gilt styling and fittings. Size 18½ × 15 × 9in. For A.C. mains 200/250 v. 50 cycles. Complete with tape and latest Acos microphone. 2-speed twin track giving 1 or 2 hours' recording respectively, incorporating a 10 × 6in. high flux loudspeaker.

SPECIAL ANNOUNCEMENT

WEARITE 3A Decks	£35/0/0
or 3B Decks	£40/0/0
COLLARO Decks Mk. IV	£25/0/0

Packing and Carr. 10/- extra on all three items.

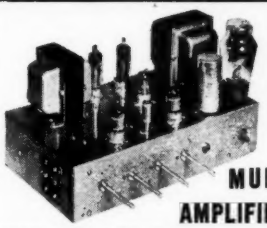

Why not make the best!

MULLARD AMPLIFIER KIT

NOW SUPPLIED WITH ULTRALINEAR OUTPUT TRANSFORMER.

All the components for model 510, PLUS pre-amplifier on one chassis (total six valves), chassis gold hammer finished. May be purchased for £12/12/- plus pkg. and post 7/6. This version complete and tested £15/15/-. Or pre-amplifier and tone control in a separate unit £14/14/- plus pkg. and post 7/6.

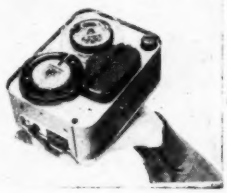

Introducing the

PHONOTRIX

BATTERY TRANSISTOR MINIATURE

TAPE RECORDER

Supplied complete with Microphone and small Loudspeaker, operates on 4 U2 Torch batteries, weighs only 4 lb. and plays for 30 minutes. Size 6½ × 4¾ × 3¾in. complete plus 5/- Retail Price **26gns.** pkg. and post. OR on Credit Terms: Deposit £3/8/- and 8 monthly payments of £3/8/9

THE JASON "ARGONAUT"

MW/FM DESIGN

★ **All Premier components are designer approved ALL components to build the complete Receiver, including output stage, may be purchased for £15/5/-, or all components less output stage but including Power Supply, for £13/19/6, plus packing and postage 3/6 on each.**

COMPACT GRAM AMPLIFIER

Complete ready to connect to any type of Pick-up and Speaker (3 ohms) A.C. Mains 200/250 v. Volume and tone control on 9in. extended leads. 1 valve. Overall size 5in. long × 2½in. wide × 3½in. high. Suitable speaker for above 7in. × 4in. elliptical 21/10.

Price £2.19.6

Plus pkg. & post 2/6.

CABINETS—PORTABLE

MODEL PC/S

Grey Lizard Rexine covered 45/-
Overall dimensions 15in. × 13½in. × 6½in.
Clearance under lid when closed 3in.

MODEL PC/2 DE LUXE

Two colours, wine and grey, with cut-out for speaker and amplifier 55/6
Dimensions 15in. × 14in. × 7½in.

MODEL PC/3

Grey Lizard Rexine covered 69/6
Overall dimensions 16½in. × 14½in. × 11in.
Clearance under lid when closed 3½in.

MODEL PC/3 DE LUXE

As above but with cutouts for Speaker and Amplifier 79/6
Dimensions as above.

THE ABOVE CABINETS ARE COMPLETE WITH CARRYING HANDLE, FASTENERS AND PANEL.

Packing and Postage 3/- each

Junction Transistors 10/- each

LORENZ MODEL PL 562 4-speed gram. motor. Price **£3/13/6.**

MERCURY SWITCHED FM TUNER *by* JASON

5 valves Foster-Seeley Discr minator

Complete set of parts can be purchased for £9.19.6 plus 2/6 p.p.

All the components can be purchased separately. The main components are as follows:—

Chassis	6/6
2 side panels, pair	3/-
Prefabricated front-end completely wired and tested with IEF80 and IECF80 (incl. P.T.)	£6/5/-
Discriminator	11/6
2 I.F. Transformers at 5/9 each	11/6
Complete instruction book	2/-

JASON FM TUNER

Jason dial, chassis and Tuning condenser completely assembled £2/6/3. Set of coils, complete with cans and silver mica condensers £1/6/-. Complete tuner can be built for £6/15/-, plus 3/6 post and packing. Write for Instruction book 2/-.

PUT IT TOGETHER YOURSELF

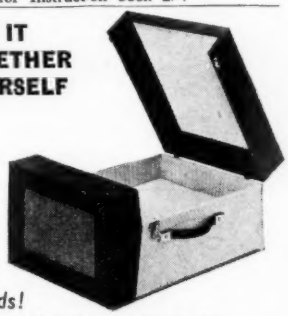

and save pounds!

Cabinet £2/19/6, *plus* 5/- *pkg. and post.*
Premier 1 valve Gram. Amplifier £2/19/6, plus 2/6 *pkg. and post.*
Premier 2-valve Printed Circuit Amplifier £3/5/6, *plus* 2/6 *pkg. and post.*
8in. × 5in. Speaker 27/6, *plus* 1/6 *pkg. and post.*
Collaro 4-Speed Changer £8/19/6, *plus* 5/- *pkg. and post.*
BSR 4-Speed Changer £8/15/-, *plus* 5/- *pkg. and post.*
If a set of parts is purchased together pkg. and post will be 10/-.

We carry a comprehensive stock of components by all leading manufacturers.

(Dept. WW) 207 EDGWARE ROAD · LONDON W.2.

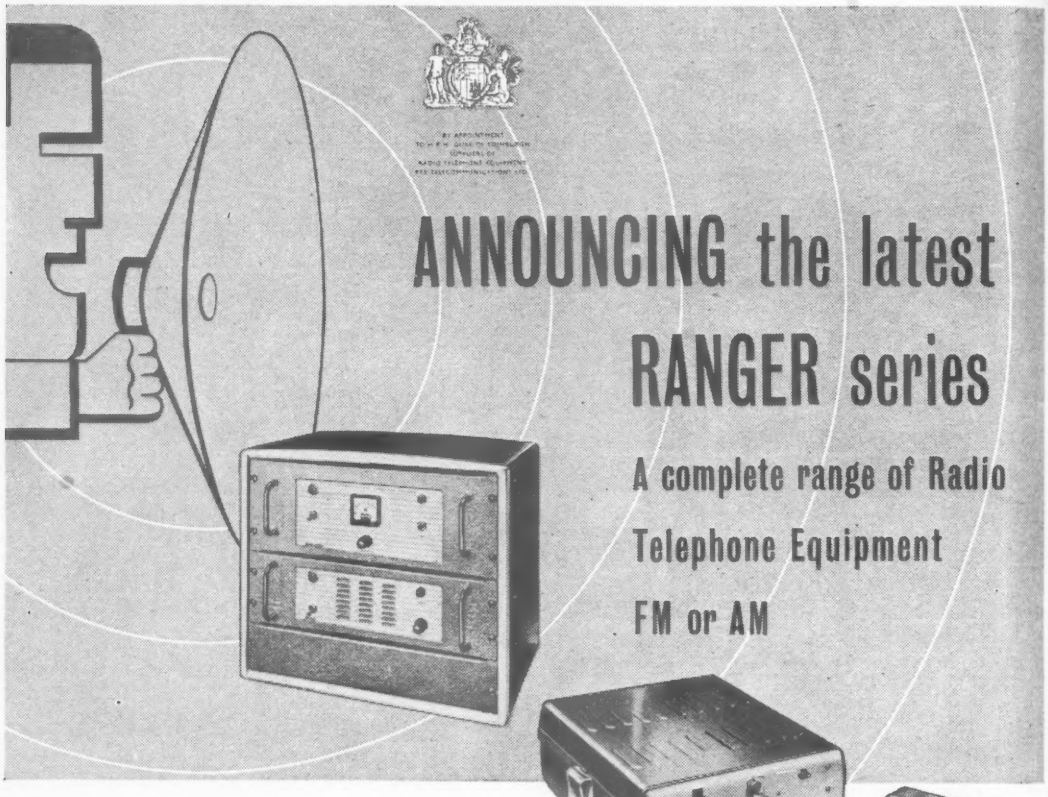

ANNOUNCING the latest RANGER series

A complete range of Radio Telephone Equipment FM or AM

All Ranger Mobile Models are available for 6, 12 or 24 volts power supplies.

Please write for further details.

MAIN FEATURES:

- Available from 25 Mc/s to 174 Mc/s.
- F.M. or A.M. simplex or duplex.
- Low battery drain.
- Split-channel selectivity.
- Unit chassis construction.
- Up to 6 switch-selected channels.
- Light weight.
- Low cost installation and maintenance.

The following features are optional:
Channel spacing:—A.M. Type V: 20, 25, 30 kc/s. Type N: 40, 50, 60 kc/s. Type W: 100 kc/s or greater. F.M. Types: 40, 50 or 60 kc/s.
Public Address and Re-broadcast facility on A.M. Types.
Fist microphone or telephone handset.

Mobile Ranger Equipment.

A. 20 watt F.M. Boot-Mounted Unit PTC 8201/2.
B. 15 watt A.M. Boot-Mounted Unit PTC 2201/2.
C. 10 watt F.M. Boot-Mounted Unit PTC 8101/2.
D. 5 watt A.M. Boot-Mounted Unit PTC 2101/2.
E. 10 watt F.M. Dash Mounted Unit PTC 8001/2.
F. 5 watt A.M. Dash Mounted Unit PTC 2001/2.

Fixed Stations.

G. 20 watt F.M. Fixed Station PTC 8701/2.
H. 15 watt A.M. Fixed Station PTC 723/4.
I. 50 watt A.M. Fixed Station PTC 753/4.

PYE Telecommunications

THE SHORTEST DISTANCE BETWEEN TWO POINTS

PYE TELECOMMUNICATIONS LTD., NEWMARKET RD., CAMBRIDGE. Phone: TEVERSHAM 3131. Cables: PYETELECOM CAMBRIDGE TA1

Wireless World

ELECTRONICS, RADIO, TELEVISION

Managing Editor: HUGH S. POCOCK, M.I.E.E.
Editor: F. L. DEVEREUX, B.Sc.

AUGUST 1958

In This Issue

353	Editorial Comment	
354	Guided Weapon Techniques	*By Lieut. P. Cave*
360	French Components Show	
361	Electro-Medical Congress	
362	Video Tape Recording	
364	World of Wireless	
367	Personalities	
368	News from the Industry	
369	Transistor Test Set	*By J. N. Prewett*
372	Short-wave Conditions	
373	Doppler Effect in Radio and Radar—2	*By N. M. Rust*
378	Servicing American Car Radios	*By Jack Darr*
381	Zener Diode Voltage Stabilizer	*By S. Welldon*
384	Divided Output Transformers	*By R. Guelke*
385	Inexpensive Photographic Timer	*By J. H. Jowett*
388	Letters to the Editor	
390	Technical Notebook	
391	Photocells	*By "Cathode Ray"*
395	Wide-band Oscilloscope	*By G. H. Leonard*
398	Colour Receiver Development	
399	Exhibitions and Conferences	
400	Random Radiations	*By "Diallist"*
402	Unbiased	*By "Free Grid"*

VOLUME 64 No. 8

PRICE: TWO SHILLINGS

FORTY-EIGHTH YEAR OF PUBLICATION

Offices: Dorset House, Stamford Street, London, S.E.1

Please address to Editor, Advertisement Manager or Publisher, as appropriate.

Telephone: WATerloo 3333 (60 lines)

Telegraphic Address: "Ethaworld, Sedist, London."

PUBLISHED MONTHLY (4th Tuesday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. *Telephone:* Waterloo 3333 (60 lines). *Telegrams:* "Iliffepres, Sedist, London." *Annual Subscriptions: Home and Overseas*, £1 13s. 0d. *Canada and U.S.A.*, $5.00. Second-class mail privileges authorised at New York, N.Y. BRANCH OFFICES: *BIRMINGHAM:* King Edward House, New Street, 2. *Telephone:* Midland 7191. *COVENTRY:* 8-10, Corporation Street. *Telephone:* Coventry 25210. *GLASGOW:* 26B, Renfield Street, C.2. *Telephone:* Central 1265. *MANCHESTER:* 260, Deansgate, 3. *Telephone:* Blackfriars 4412. NEW YORK OFFICE: *U.S.A.:* 111, Broadway, 6. *Telephone:* Digby 9-1197.

Transistor 200mW Amplifier for 6V Supplies

The circuit below shows an amplifier, suitable for use with high-output crystal pick-ups, capable of giving 200mW output. It consists of three Mullard OC72 transistors, the stages being transformer-coupled. Negative feedback is applied to the driver stage, reducing the transistor input and output impedances, improving the base response of the driver and input transformers, reducing transistor spread effects, and reducing harmonic distortion.

The input is coupled to the OC72 driver stage by a 30 : 1 input transformer, which provides sufficient sensitivity for use with high-output crystal pick-ups. If the primary inductance of the input transformer is 500H the frequency response will be good down to 100c/s.

The output stage is transformer-coupled to the driver stage. It uses a matched pair of Mullard 2-OC72 transistors in common-collector Class B push-pull. The main advantages are reduced cross-over distortion, and the ability to use the resistance of the primary of the output transformer to obtain the required thermal stability.

For 250mW into the output transformer primary, an output of 200mW into a 3Ω load is obtained. The average sensitivity for this output is 1·7Vr.m.s. (minimum is 2·0Vr.m.s.). The frequency response is good from 160c/s to 6kc/s. This is obtained by placing a capacitor across the feedback resistor, to limit the high-frequency gain and partly compensate for the loss in low-frequency gain, arising from the transformers.

The quiescent currents of the driver and output resistors are, respectively, 6·5mA and 1·0mA. The maximum collector current of the transistors is 83mA.

Total amplifier current consumption is:

Zero drive	10mA
Average speech and music	32mA
Sinewave full drive	83mA

Transformer Details

Input Transformer	
Turns ratio	30 : 1
Primary inductance	>500H
Primary resistance	<10kΩ
Secondary resistance	<100Ω
Driver Transformer	
Turns ratio	1 : 1·6+1·6
Primary inductance	>4·5H at 6·5mA
Primary resistance	<70Ω
Secondary resistance	<200Ω per half winding
Output Transformer	
Turns ratio	4·5+4·5 : 1
Primary inductance	>0·5H total
Primary resistance	=6Ω±1Ω per half winding
Secondary resistance	<0·3Ω

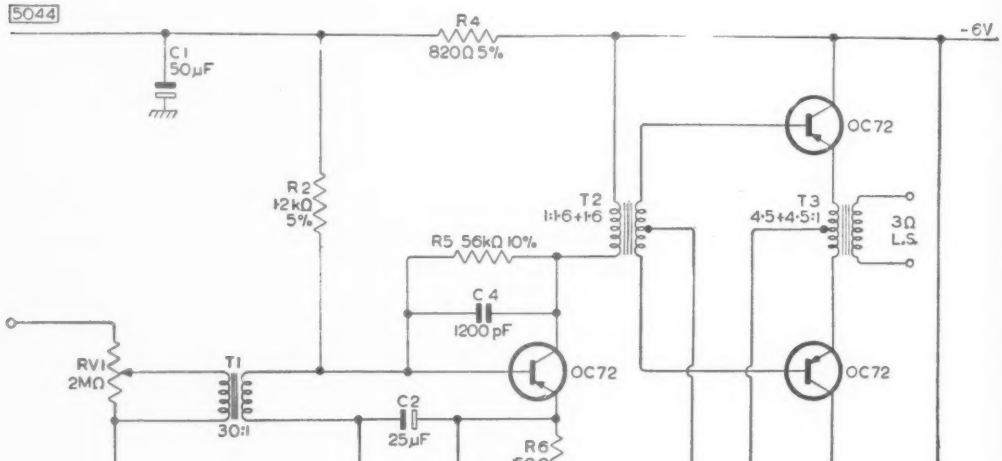

Mullard TSD DATA and PUBLICATIONS SECTION. MULLARD LTD. MULLARD HOUSE, TORRINGTON PLACE, LONDON, W.C.1

MVM 394

AUGUST 1958

Vol. 64 No. 8

Wireless World

A Tax on Thrift

THE ruling by H.M. Customs and Excise that reconditioned television tubes may in certain circumstances incur liability to Purchase Tax has touched off a wave of indignation and much heated argument.

The official statement "clarifying" the position, was given in last month's issue of this journal (page 314). In essence it says (1) that reconditioned tubes may be sold as such without further payment of purchase tax if the treatment is external and has not involved the opening of the tube, and provided that secondhand tubes are segregated physically and in the trader's accounts from new tubes; (2) that extensive repairs involving the opening of the tube will not incur tax provided that the customer's own tube including all its principal component parts is returned to him; but (3) that if a fresh, not necessarily new gun is fitted or the work is such as to amount to the manufacture of a virtually fresh tube, the transaction is a sale and is liable to a tax at the same rate (60%) as on a new tube.

The general indignation which was first aroused by this pronouncement seems subsequently to have channelled itself into two main criticisms: first, that there is no precedent for demanding Purchase Tax twice on the same goods and, second, that the cost of a new gun is such a small part of the total cost of a tube that its introduction cannot by any stretch of the imagination amount to the manufacture of a new tube.

The resolution of this paradox is simple. In fact there is literally nothing in it, for the main item, and the most expensive, in a cathode-ray tube is the vacuum. This is the "commodity" on which most of the tax is levied, and it is difficult to avoid the conclusion that when air is let into a tube it is destroyed, and that when it is pumped out again a virtually new tube is created. To those who retort that it is the same vacuum which has been restored, the answer would be that a new cost has been incurred and that it is mainly on this new value that tax is to be levied.

While we are sorry to have to disappoint those who may look to us for support in fighting this latest detail ruling, we are glad of the opportunity it gives us of returning to the question of Purchase Tax in general and the anomaly of its incidence on radio valves and cathode-ray tubes in particular.

No one likes to pay taxes, least of all Purchase Tax which has borne heavily and unpredictably on the radio industry and its customers in the home market. No two people will agree on what is a fair and equitable distribution of the burden of taxation, but we say that it is a gross injustice that a television viewer should have to pay tax on valves and cathode-ray tubes to keep his receiver in commission while a motorist gets an exchange replacement of his car engine tax free.

For the time being the radio industry, having failed to get the tax abolished by representations through all available channels, is compelled to accept this anomaly. That being so we cannot complain if those charged with the duty of administering the law take steps to anticipate the many possible means of evasion which ingenious and unscrupulous people will always find. The higher the rate of taxation the more intensive will be the search for loopholes, and the higher the dissipation of tax receipts in salaries and expenses of the customs officers detailed to the task of enforcement. (H.M. Customs and Excise will need no reminder of the work involved by the phenomenal increase in the stocks of repaired and secondhand jewellery which appeared in the shops during the period when P.T. was standing at 100%.)

As many man-hours and as large a proportion of the tax receipts could well be expended on establishing the borderline between "minor" and "extensive" repairs to cathode-ray tubes on the basis of case-law built slowly by a succession of arbitrary rulings by authority. Since arguments founded on justice and equity seem to have fallen on stony ground it is to be hoped that this tax may be abandoned on grounds of expediency, as no doubt it was decided to give up the idea of taxing the potentially more lucrative trade in motor car spares.

Guided Weapon Techniques

A Review of Possible Systems of Guidance

By LIEUT. P. CAVE, Grad.I.E.E., R.N.

IT is not generally realized that there is a wide variety of established guidance techniques, each one with its own application in the guided weapon field. This review will compare the different systems that are available and establish the limitations in each case.

If guided weapons are to be classified by the guidance system that is used, then they fall readily into two main groups. In one group are those systems where the target position data is continuously available and hence moving targets may be dealt with, whilst the other group contains systems which use pre-determined target data. The range of the target will determine which system is to be used, and as the first group is to be preferred from the point of view of accuracy, it would be quite possible for a long-range missile to be launched on pre-determined information, but to have a terminal guidance system using instantaneous target data.

Reference to the "family tree" of guidance systems in Fig. 1 shows that these two main groups may each be sub-divided into two groups, the first into homing and command systems and the second into ballistic and "flat top" or constant-altitude systems. The difference between homing and command guidance may be summarized by defining a homing missile as one where the flight path required to effect an interception is determined within the missile itself, whilst in a command system the flight path is computed at a point external to the missile and steering orders are then transmitted to the missile by radio or other means. A ballistic trajectory system is one where the missile is uncontrolled for a large percentage of its journey and the shape of the trajectory is parabolic or elliptical,

Fig. 2. "Curve of pursuit" trajectory. The dotted lines indicate the line of sight of each successive position of missile and target.

whilst a "flat top" system is similar to a fast, high flying, pilotless aircraft which is continuously controlled. It is interesting to note that the first guided weapon brought to the public notice in this country, i.e., the German V1, was of this latter group, whilst the V2 was a ballistic missile.

Homing Missiles.—One method of producing a homing missile would be to arrange that the missile points continuously at the target, i.e., that the missile heading changes at the same rate as the line of sight from missile to target. This trajectory may be expressed mathematically by the equation

$$\dot{F}=\dot{\theta} \quad .. \quad .. \quad .. \quad .. \quad .. \quad .. \quad (1)$$

where F is the missile heading and θ is the line of sight, both with respect to the same reference in space, and $\dot{F}$ and $\dot{\theta}$ are the first time derivatives $\frac{dF}{dt}$ and $\frac{d\theta}{dt}$.

This system will produce a "curve of pursuit" trajectory as shown in Fig. 2 and a consideration of this trajectory will show that it is uneconomical and that it will always result in a stern chase. Furthermore it can be shown that an infinite lateral acceleration is required at the end of the course. As this is impossible to produce in practice, a definite miss distance is inherent in this system.

The homing trajectory may be improved by making the missile head for a calculated interception point and this method reaches its ideal when the missile flies in a straight line between the launcher and the interception point. The method most commonly used in G.W. is called proportional navigation where equation (1) is extended to a general case of $\dot{F}=K\dot{\theta}$ .. .. (2)

Fig. 1. Family tree of guidance systems.

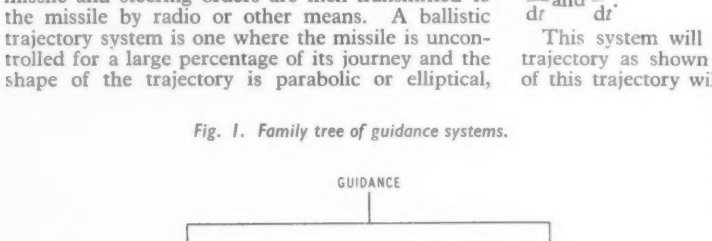

where K is the "navigation constant." The advantage of this system is that no knowledge of range is required, other than that the target must be within the range capabilities of the missile.

If the missile is to fly in a straight line from launcher to target then $\dot{F}=0$ and to satisfy equation (2) either $\dot{\theta}=0$ or $K=\infty$. The former case will involve aiming the missile at the interception point before launching, as in the case of normal predicted gunfire, while the second case will require an infinite rate of turn and hence an infinite lateral acceleration as soon as the missile is launched. A very reasonable compromise may be obtained by giving K a value between 3 and 10 and allowing the missile to turn through the initial error in aim in a finite time. When this has been achieved the missile will fly along an interception course and K must be chosen as a compromise between the acceleration that may be applied to the missile and the time available for the turn. Fig. 3 illustrates the change of trajectory with different values of K.

The functions of the instrumentation of this system may be summarized in the following stages:—

(1) Establish the sight line in space (θ).

(2) Measure the sight-line rate ($\dot{\theta}$).

(3) Make missile heading change by $K\dot{\theta}$.

With small variations in technique the major differences between homing weapons lie in the methods used to establish the sight line.

Active Homing.—In this class of missile the sight line is established by a lock-follow radar set mounted in the missile. This systems leads to some enginering difficulties but the maximum range of such a set is severely limited by the size of aerial reflector that may be used, as this must be smaller than the diameter of the missile.

Semi-active Homing.—Here the sight line is still established by radar but an improvement in range capabilities and a reduction in weight of electronic equipment in the missile is effected by installing the transmitter of the radar set on the ground and arranging for it to illuminate the target continuously. Reflected energy is then used by the receiver in the missile to auto-follow the target. The improvement in range over active systems may be as much as five times, since the power transmitted and the size of the transmitter aerial dish may both be greatly increased when the equipment is mounted on the ground. This makes the missile suitable for the surface-to-air role and a salvo of missiles may be fired without mutual interference taking place.

Passive Homing.—No transmitter is used in this system and the missile uses energy radiated by the target to establish the sight line. For missiles which use infra-red radiation there is a limit to the range at which targets can be detected.

A special feature of the lock-follow systems in use in homing missiles is that they must establish the sight line with respect to a space reference and not with reference to any missile axis. This calls for gyro stabilization of the reflector and hence the misalignment signals from the radar or infra-red receiver must be arranged to precess this gyro.

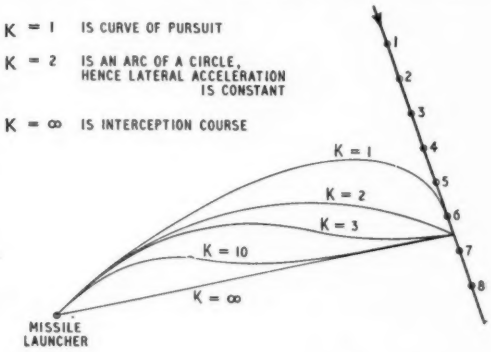

Fig. 3. Homing trajectories for different values of K.

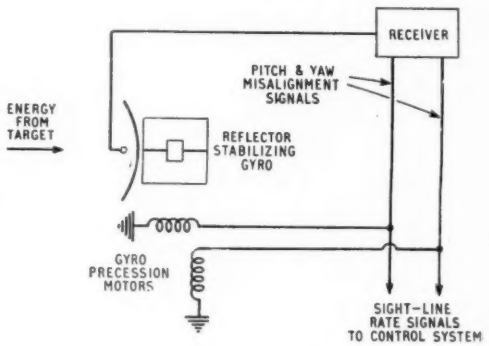

Fig. 4. Basic arrangement in a homing missile to measure sight-line rate.

Below : Fig. 5. Elements of a command link system.

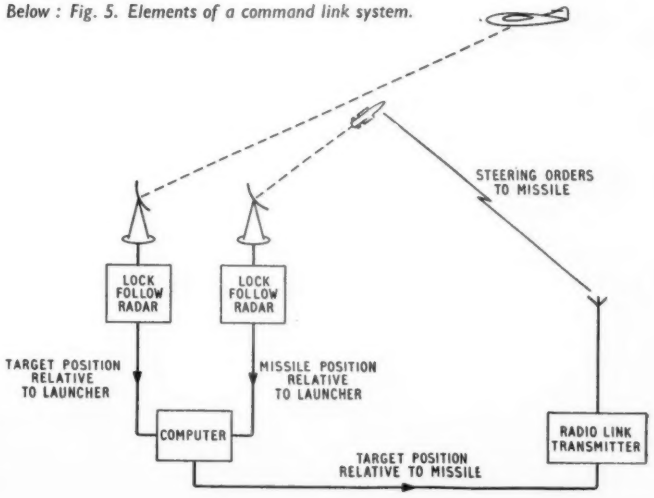

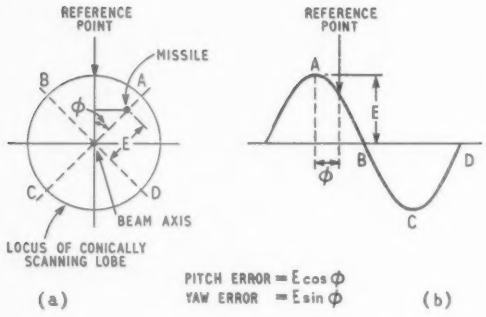

Fig. 6. Beam-riding system. (a) Cross-section of beam and (b) resultant error measuring signal.

Since the gyro precession rate, i.e., the sight-line rate, is proportional to the applied signal, this signal may be used as a measure of sight-line rate. This is shown diagramatically in Fig. 4.

Command Systems.—The basic command link system is shown in Fig. 5 and from this it will be seen that the required missile course is computed continuously from two lock-follow radars, measuring missile and target positions with respect to the launcher. From this a computer gives target position relative to the missile and the required course is converted to steering orders which are transmitted to the missile by a radio link.

This system is capable of many variations ranging from the system as shown to the manually guided missile where the radars are replaced by optical sights and the computer by a human operator. Only the radio link remains and even this may be replaced by a wire trailed from the missile! The main disadvantage of this system is that only one missile can be fired at a time and if a salvo of two is required then all the ground equipment except the target following radar must be duplicated. Among the advantages are those of a very simple missile equipment and a longer range compared with some of the present homing systems. However, the guidance accuracy decreases as the missile approaches the target as against a homing system where the reverse is true. A method which can be adopted in medium range missiles where the miss distance required is beyond the computation capabilities of the system, is to fit the missile with a short range homing system to control the missile in its terminal phase.

Fig. 7. Typical ballistic trajectory.

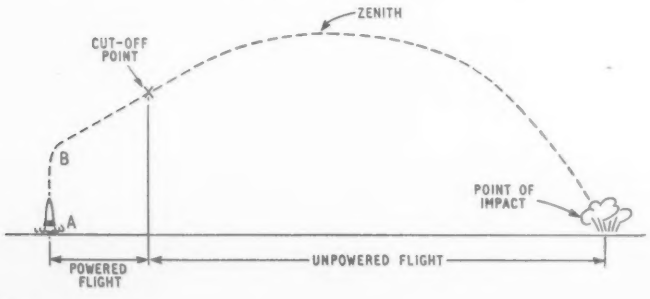

Beam-Riding Systems.—In a beam-riding or line-of-sight guidance system, the missile is made to fly in the centre of a conically scanning radar beam similar to that used by a lock-follow radar set, and this beam is made to point at the target. If the missile is within the cone but not in the centre, then the signals received by the missile from the radar will be amplitude-modulated at the conical scan rate. This modulation signal is indicative of the error in position of the missile from the centre of the beam, the amplitude being proportional to the distance, and the phase having a direct relationship to the direction of the error with reference to a fixed point in the conical scan. This reference point (generally the pitch or yaw axis) may be transmitted independently from the ground to the missile by pulse position modulation of the guidance radar transmission. The error modulation may then be resolved along the pitch and yaw axes and used as steering orders to the missile's control system. This is shown diagramatically in Fig. 6. It will be noted that a salvo of missiles may be fired without any increase of ground equipment since, whilst this is still a command system, it is the flight path which is transmitted to the missile, rather than the actual steering orders required. The disadvantages of this system are that its accuracy decreases with range and its trajectory is not very economical, as too much time is spent at low altitudes where aerodynamic drag is large.

Ballistic Missiles.—The trajectory followed by a ballistic missile is similar to that of a long range shell and the same factors control the range in both cases, i.e. the angle of elevation and the velocity at the end of powered flight. In the case of the shell the powered flight is short—from the breech to the muzzle of the gun—and range is controlled by the angle of elevation. The ballistic missile may be powered for 60 seconds or more before it reaches the required velocity; this velocity is controllable in order to vary range, whilst the elevation angle is held constant. As will be seen in Fig. 7 the ballistic trajectory may be divided into three parts. In the first, AB, the missile is launched vertically. This is done to allow the missile to accelerate slowly and thereby economize on the strength and weight of the missile airframe. This is highly desirable since the maximum velocity that the missile can attain is governed by the "mass ratio," i.e.

$$\frac{\text{Mass of missile when launched}}{\text{Mass of missile when fuel all burnt}}$$

Due to the low velocities attained during the first few seconds of flight, the missile cannot be stabilized by control surfaces and is maintained in a vertical position by such a method as moving the direction of the jet stream from the motors. This may be accomplished by gyro-controlled swivelling rocket motors or by the use of deflecting plates in the jet stream. When the missile has attained sufficient velocity, the vertical control gyro is precessed by about 45° and the missile continues to accelerate at 45° elevation until the required "cut off" velocity

has been reached. This will depend on the required range and for a missile at 45° launching elevation,

Range $= u^2/g$ for the unpowered section of the flight where u is the cut-off velocity if air resistance is neglected and g is acceleration due to gravity. From this it will be seen that the velocity must be determined accurately if large errors in range are to be avoided. Measurement of velocity may be made (1) inside the missile by integrating the output of an accelerometer, or (2) outside the missile by measuring the Doppler frequency shift of the signal from a transponder unit.

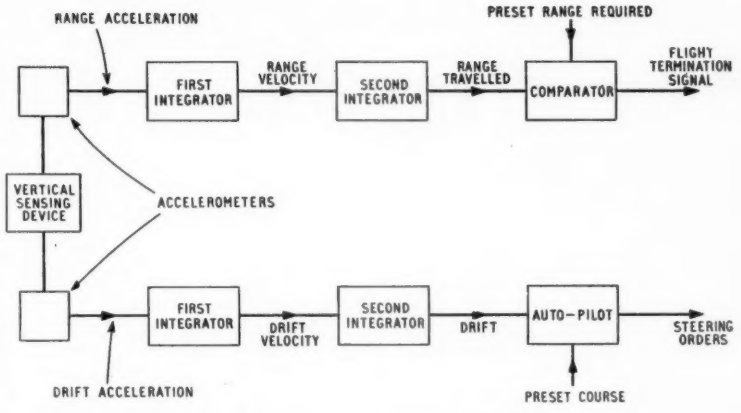

Fig. 8. Elements of an inertial guidance system.

When the correct cut-off velocity has been reached, the fuel supply is cut off and the missile follows a ballistic trajectory. The other main problem in launching a ballistic missile is to ensure that it is launched on the correct bearing to the target. The missile will be maintained on course by a gyro-controlled auto-pilot and in the V2 missile the correct bearing was ensured by lining up the axis of this gyro before launching. This method did not permit any adjustment after launch but later methods, such as automatic alignment with a radar beam or one of the methods used to steer "flat top" trajectory missiles, permit corrections to be made after launch.

"Flat Top" Trajectory Missiles.—In contrast to the ballistic missile which is powered for a short time only and attains a high velocity, the "flat top" missile is powered throughout the flight and travels at a relatively slow speed. As its trajectory is all within the earth's atmosphere an air breathing motor can be used, e.g. turbo-jet, ram-jet or pulse-jet engine, but this advantage in the amount of fuel to be carried is offset by the fact that continuous guidance is required to control the missile's behaviour in the earth's atmosphere.

Terrestrial Guidance.—The simplest form of direction indicator that will function satisfactorily in a fast-moving missile is a magnetic compass, and indeed this forms the basis of navigation in most aircraft. Thus a missile could have a pre-set magnetic course set before take off and deviations from this course used as steering orders. A refinement in this system would be to use a gyro magnetic compass and this was the system used in the V1, range being determined on a dead reckoning basis by counting the revolutions of a small propellor. The best accuracy obtainable is of the order of 1° to 2° and this only if the magnetic deviations along the route are known and compensated in the missile. A further refinement might be to correlate the variations in the vertical component of the earth's field, but again an accurate magnetic survey would be needed.

Inertial Guidance.—The range through which a missile has travelled from the launching point may be measured by double integration of the acceleration of the missile along the line of flight and normal to the local vertical, the first integration converting acceleration to velocity and the second converting velocity to distance. The accelerations may be measured quite accurately with an accelerometer, but accurate integration over long periods of several hours' duration is difficult, due to drift. A more difficult problem still is the determination of the local vertical. This may be measured by a pendulum in the case of a body that is not accelerating, but accelerations will render a pendulum system useless. A suitable pendulum can, however, be simulated by a specially controlled gyroscope. Such a missile must be launched on the correct course, but once this is done it may be kept on course by a similar measurement of the distance travelled *across* the line of flight, i.e., drift, and arranging for this to be brought to zero by appropriate steering of the missile. A block diagram of this arrangement is shown in Fig. 8.

Celestial Guidance.—The techniques of celestial navigation are well established in the marine and aeronautical fields, but the application to missile guidance is a complicated matter. A "fix" may

Fig. 9. Method of obtaining a position fix from the observation of the altitude of two stars.

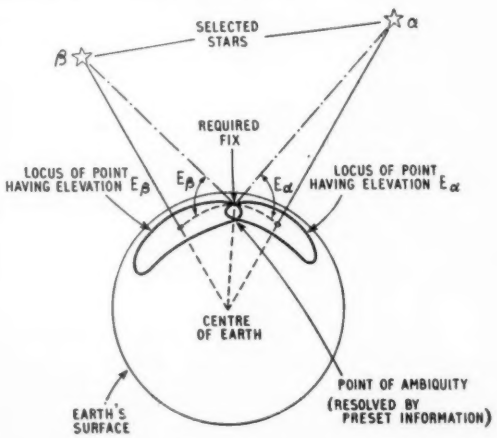

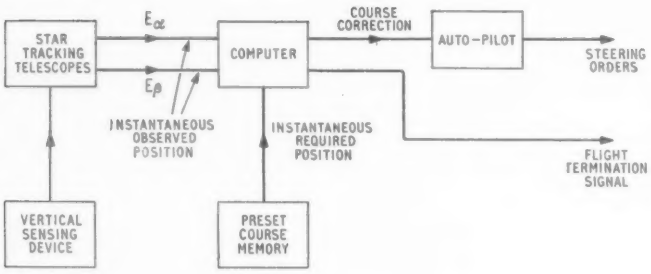

Fig. 10. Celestial guidance system.

be obtained by observing the altitude of two stars, as shown in Fig. 9, and hence for continuous guidance, constant observation of two selected stars is necessary. To measure the altitude, an artificial horizon must be provided and since this must be independent of missile accelerations, a device similar to that mentioned in the preceding paragraph would be suitable. Arrangements must now be made for two automatic star-tracking telescopes to be mounted on this platform. These will measure the altitude of the selected stars continuously and their auto-following action is accomplished by a similar system to that used in passive homing missiles to establish the sight line to an infra-red source of energy. Hence a continuous position fix of the missile may be calculated and compared with an instantaneous, pre-determined position which may be stored in the missile on tape or in a magnetic store. Errors between "observed" and "required" position are then used as corrections to the setting of the missile auto-pilot.

The system is shown in block form in Fig. 10, from which it will be seen that the computer, having "observed" and "required" star altitudes as its input, will produce the course corrections for the auto-pilot and also the flight termination signal when the observed position coincides with the target position. In a missile using celestial guidance it will be most important to correct for time and the system must either be continuously corrected or launched at the precise instant for which the system is pre-set.

Radio Guidance Systems.—Systems employing radio guidance may be divided into two main categories, those deriving range along and drift across a pre-determined course and those relying on a radio field derived from static transmitters. All radio systems are liable to jamming, a disadvantage when compared with inertial and celestial guidance systems, but this need not be as serious as it might be thought, especially in the first type of system mentioned. This system relies on the measurement of the ground speed of the missile by a radio Doppler system. Speeds are measured along and across the missile heading and integration of these speeds will give range from launcher and drift. A comparison of the block diagram in Fig. 11 with the inertial system as shown in Fig. 8 will illustrate the parallels between the two systems.

The radio field systems work on similar principles to the "Gee" and "Oboe" blind bombing systems employed in World War II. Radio position lines are established from fixed transmitters. The co-ordinates of the target are established with reference to these position lines and the missile's position is measured continuously with respect to the same reference. The missile course in terms of the radio position lines is pre-set and stored in the missile. Hence continuous comparison of the desired and observed positions may be made and differences used as correction signals to the auto-pilot. Radio position lines are of three types:—

(a) Orbital lines at a constant range from the launcher generally determined by a transponder system between the missile and a fixed station near the launcher.

(b) Radial lines on constant bearings from a fixed point determined by a directional aerial system. It is interesting to note that a beam-riding missile might be considered to come under this heading.

(c) Hyperbolic position lines determined by a comparison of the arrival at the missile of two signals known to have been radiated at the same instant from two fixed stations. This is the basis of the Decca and Loran navigation systems.

To obtain a fix, two position lines will be necessary and whether they are both of the same type or not will depend on the ease of getting a good intersection. The greatest accuracy will be obtained by the hyperbolic lines since these do not depend on the transmission speed, but it must be also noted that orbital and radial position lines from the same reference will always give an intersection at right

Fig. 11. Radio guidance system using the integrated velocities measured by Doppler radio.

 

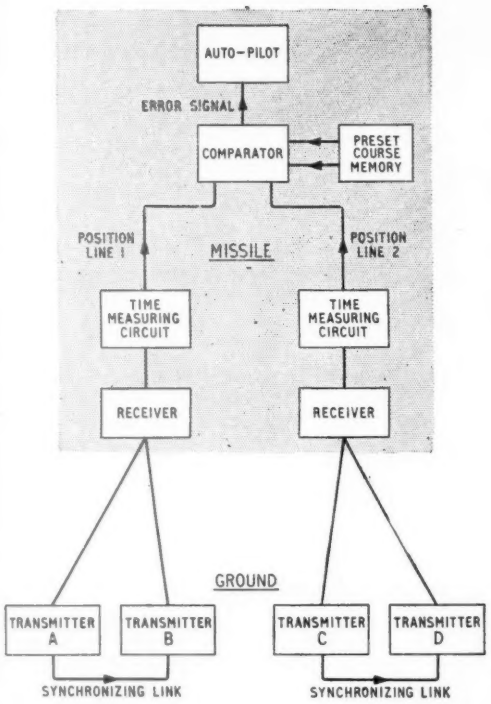

Fig. 12. Radio field system using two hyperbolic position lines.

angles and hence a choice must be made to suit each case.

Another advantage of this radio system is that there need not be a close liaison betwen the stations launching the missiles and those providing the guidance field. Once the field is set up missiles may be launched into it from a number of points. In general, a parallel between radio field guidance and celestial guidance may be observed and this will be shown by a comparison betwen Figs. 10 and 12.

Security regulations will not permit description of the missiles that are in current production or under development. Such information that has been released, however, shows that this country has concentrated its first efforts on defence weapons against aircraft attacks, as this is the main threat against our islands, and that the majority of attack weapons have been developed in the U.S.A. or in Russia, though we may be quite sure that defence weapons have not been neglected in these countries. The author's view is that future developments in guidance systems should be directed towards the extension of detection ranges of radar and infra-red systems, together with the development of increasing accuracy in manufacturing techniques for such pieces of equipment as gyros, accelerometers and actuating systems. Moreover, the ability of manufacturing processes to "produce the answer" in smaller and smaller packages is of prime importance. These are essentially engineering problems and as such present a vital challenge to the engineers of to-day.

Transistorized V.H.F. Airborne Equipment

A NEW range of airborne v.h.f. equipment for use in modern civilian aircraft and embodying the latest design techniques with printed circuits, transistors and sub-miniature valves where applicable, was shown at the 75th Anniversary Exhibition held by Standard Telephones and Cables at the Waldorf Hotel during the first week of July.

Known as the STR23/34/35/36 it is a complementary and comprehensive VHF/ILS/VOR airborne communications and navigational equipment approximately half the weight, half the size and consuming half the power of the earliest sets it replaces. It will be fitted in the B.E.A. Vanguard and Comet fleets of aircraft.

The STR23 provides two-way v.h.f. communication in the band 118 to 135.95Mc/s, with remote selection of 360 channels of 50-kc/s spacing and with a transmitter power output of 20 watts. The modulator is fully transistorized and embodies speech clipping. The companion receiver is a 560-channel, 50-kc/s spacing, double-frequency changing superhet with transistors and crystal diodes in all stages from the second i.f. amplifier to the output stage inclusive. It covers the band 108 to 135.95Mc/s and is remotely controlled. Transmitter and receiver each weigh 16lb.

This equipment can be used either as a separate self-contained v.h.f. airborne radio telephone or in conjunction with the complementary VOR/ILS localizer receiver, SR34, and glide path receiver, SR35. The former is a combined 100-channel, 100-kc/s spacing receiver and instrument drive unit and is interchangeable with the receiver part of STR23. It provides navigational and glide path approach information with instrument presentation and covers the band 108 to 117.9Mc/s. Three valves only are used in this set, the remaining stages being transistorized. It weighs 30lb.

The complementary glide-path receiver, SR35, provides 20 channels spaced 300kc/s apart in the band 329.3 to 335Mc/s. It is a double superhet and all stages from the second mixer to the output use transistors and the set weighs 8lb.

Each of these units has a built-in power pack for operation from the 115-V, 400-c/s a.c. supply found in the most up-to-date civil aircraft, but 28-V transistorized power packs are under development for each of these sets.

The final unit, the SR36, is a 75-Mc/s marker beacon receiver and uses one valve only the remaining stages being either transistors or crystal diodes. This receives the vertically radiated signals which fix pre-determined spot distances from the end of the landing runway. The unit weighs 6lb only, has a built-in power pack and the information is given by three lamps included in the display unit.

NATIONAL RADIO EXHIBITION

(Earls Court, Aug. 27th—Sept. 6th, 11 a.m.—10 p.m.)

***WIRELESS WORLD* SHOW NUMBERS**

September: **Show Guide** (publication date August 26th). Plan of the stands with stand-to-stand guide to the exhibits.

October: **Show Review** (publication date September 23rd). An assessment of trends in the design of television and sound receivers.

French Components Show

THIS year the 21st Exhibition of the French components industry, held at the Parc des Expositions, Porte de Versailles, Paris, was distinguished by its title of 1st International Components Exhibition—which it justified by the presence of 37 foreign firms amongst the 314 exhibitors. Apart from this the Salon is different in a general way from our own components show in that it places much more emphasis on electro-acoustic equipment and test and measuring instruments—hence the greater number of stands.

Many other differences were, of course, observed in the detailed things—for example, the large number of a.c. voltage regulators for television sets on display (evidence of the fact that the mains supply voltage in France can vary as much as $\pm 30\%$). And in the electro-acoustics section one became accustomed to seeing amplifiers and tuners with variable response curve indicators on their front panels. A horizontal wire representing the curve behind a transparent graticule is automatically moved up or down at either end when the bass or treble controls are operated.

The electro-acoustics section was actually dominated by large numbers of portable record players in mock leather attaché cases, most of which had the loudspeakers in the detachable lids. One model, the Teppaz 336, had two $7\frac{1}{2}$-inch speakers and a piezo-electric "tweeter" in its lid. Another multiple loudspeaker system, intended for "hi-fi" and called the Armad "acoustic screen," had two loudspeakers mounted back-to-back in a cube of expanded polystyrene. One side of the cube is open to the listener while the opposite side is closed by a large sheet of the same material (see photo.). The two speakers work in phase, so that the cones compress the air in the cube during their backward movement and the air outside during their forward movement. This arrangement is said to improve the acoustic loading and response curve of the speakers, to propagate the sound laterally over an angle of 180 degrees, to attentuate standing waves on the cones and to avoid spurious cabinet vibrations.

Also in the "hi-fi" category was an unusual pickup for long-playing records, shown by Avialex, which combined a piezo-electric element with an electromagnetic element. The first, giving a voltage proportional to the amplitude of the stylus movement, covers reproduction of low frequencies, while the second, responding to the velocity of movement, deals with the high frequencies.

Tuning-coil packs with push-button or piano-key station selection seem to be very popular in France (see photo.), and many of the examples on show were designed for portable transistor sets. Many transistor receivers are intended for use inside motor cars, and to cater for this several detachable car aerials were on display. One type clips on the top edge of a lowered window glass while another is a rod fixed horizontally on the inside of the windscreen by suckers. Aerials in general were fairly conventional, except perhaps for one "skeleton slot" v.h.f. type with its feeder branches in the

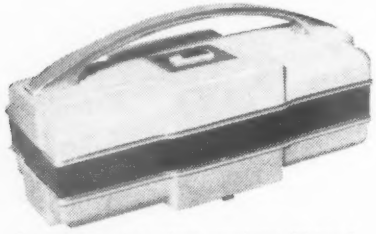

Automatic mains voltage regulator (Voltam)

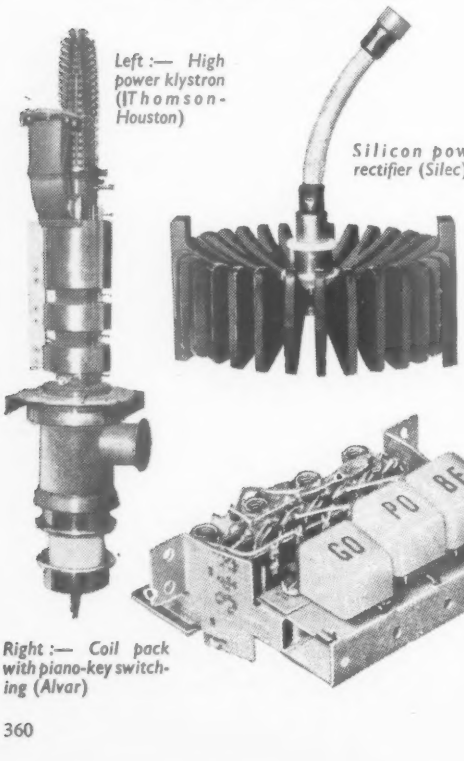

Left :— High power klystron (Thomson-Houston)

Silicon power rectifier (Silec)

Right :— Coil pack with piano-key switching (Alvar)

Two versions of the Armad "acoustic screen" (S.A.T.I.)

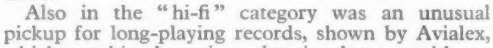

same plane as the "slot" structure and two reflectors fixed behind on the mounting bracket.

Semiconductor devices—germanium, silicon and selenium—appeared to be in much the same state of development as in Britain. Some of the more advanced devices noted were n-p-n high-speed switching transistors (La Radiotechnique), sensitive Hall-effect elements (Siemens & Halske) and a selenium "solar battery" of 20 cells working a transistor receiver (Westinghouse).

An interesting item in the test gear section was a portable transistorized capacitance meter, shown by Chauvin Arnoux, capable of measuring capacitances from 2pF to 0.1μF directly on a pointer indicator. The capacitor under test is charged repetitively by a transistor square-wave generator and the resultant discharge waveform is rectified to give the mean discharge current, which is indicated on the meter in terms of capacitance.

Amongst the oscilloscopes, one unusual model had its c.r.t. external to the main cabinet in a horn-shaped enclosure which was mounted on a ball joint so that the tube could be swung to any viewing angle. Another c.r.o. was capable of superimposing four waveforms from different sources on the screen for comparison purposes. This was done by an electronic commutator sampling each waveform 10^4 times per second. Yet another instrument had electronic commutation (for two channels) in a detachable Y amplifier which could be interchanged with a standard (single channel) Y amplifier.

The new 110-degrees scanning angle for television c.r. tubes was represented by new deflector-coil assemblies, and a complete receiver chassis with a 110-degrees tube and appropriate e.h.t. and deflection components was demonstrated by Cicor. For small television camera tubes of the photo-conductive type, Telco were showing a compact coil assembly called the "Vidibloc" which contained three separate elements—one coil for focusing, another for deflection and a third for aligning the electron beam on the tube axis. Matched groups of three "Vidiblocs" are available for colour television.

In the realm of high power operation, two exhibits of particular interest were an S-band amplifying klystron capable of giving 30 megawatts peak output (Thomson-Houston), and a silicon junction rectifier which would deliver 150 amps mean current with 200 volts peak inverse (Silec).

Among new connecting devices a notable exhibit from America was the "Interlock" system, in which the plug has a hook on its end and is locked firmly into the socket cylinder by pressure from a spring-loaded ferrule. The two parts are separated by pulling on the ferrule.

Medical Electronics Conference

AN experimental ultrasonic "telescope" for producing "radiographic" type pictures of internal biological structures was perhaps the most technically advanced device described at the recent Paris conference on medical electronics (see page 364). Constructed by Dr. C. N. Smyth, of University College Hospital, London, it depends on the varying opaqueness of different body tissues to ultrasonic waves and displays the pictures by a television type of scanning system.

In the present early state of the work the biological subject is represented by a test object immersed in a tank of water. Low power ultrasonic waves of 12Mc/s frequency are directed from a transducer at one end of the tank on to the test object. The pattern of energy transmitted through the object is then focused by a plastic lens on to a 0.5mm thick quartz plate at the other end of the tank. This plate also forms the target of a television pick-up tube outside the tank. Because the plate is mechanically damped by the water the ultrasonic waves do not spread over its surface and vibration is confined effectively to the points of impact of the beam. Consequently the voltage pattern set up in the plate by the piezo-electric effect corresponds to the ultrasonic energy distribution. This charge pattern is scanned by the electron beam of the pick-up tube and the resultant signal is displayed as a television picture. To allow more than one image to be displayed the charge pattern on the plate is removed by ion bombardment.

The definition is limited by the thickness of the quartz crystal plate, but this thickness cannot be reduced too far because of the atmospheric pressure resulting from the vacuum in the pick-up tube.

Direct stimulation of the auditory nerves of deaf people by pick-up coils enclosed in the skull has already been mentioned in *Wireless World* (Sept. and Dec. 1957 issues, p. 457 and p. 613). Details of these experiments were given by Dr. A. Djourno at the conference and X-ray pictures were shown of the embedded coils. When signals were induced in the coils by magnetic induction the patients could discriminate between low frequencies below about 100c/s. At 15c/s they reported "noises" like motor-cycles, and anything above this gave the effect of sheets being torn up. Words were generally unintelligible, but "Papa" could be distinguished from "Mama" and rhythms and code patterns could be recognized. It was suggested that voice frequencies might be heterodyned down to the low frequencies which could be perceived, or possibly converted into pulse codes.

A topographical method of displaying the distribution of e.e.g. potentials on the scalp, described by Dr. A. Rémond, involved scanning a line of pick-up electrodes in turn and integrating the voltages obtained from each. The resulting "contour" of voltage against position was displayed on a c.r.t. repetitively at 7-ms intervals and recorded photographically to show the changes taking place with time. Dr. Rémond was also working on a two-dimensional system of plotting potentials with interpolation between scanning points. This gave a record on a diagram of the scalp rather like height contours on a map.

The presence of lung cancer cannot always be detected by ordinary X-ray examination, but Dr. M. Marchal described an auxiliary radiographic technique based on the fact that a cancer inhibits the normal blood pulsation in the lung it infects. Photocells are placed on the patient's chest during fluoroscopic examination in such positions that the blood pulsations appearing in the image are detected and converted into electrical signals. According to the shape of the recorded signal waveforms, it is possible to see whether the blood pulsations are normal or not.

Other communications dealt with low-noise transistor amplifiers, integration methods on biological traces to overcome noise, X-ray image intensifiers with television display, intracardiac pressure measurements and statistical diagnosis using electronic computers.

Video Tape Recording

DEMONSTRATION OF THE AMPEX VR1000 EQUIPMENT

RECENTLY Associated-Rediffusion took delivery of a modified Ampex video tape recorder and *Wireless World* was given the opportunity of seeing it put through its paces.

The principle used in the Ampex machines*, which are modified to British 405 line standards by Rank-Cintel Limited, is to provide the equivalent of a very high tape speed by recording across a 2in-wide tape with a set of rotating heads whilst it is moving past the head assembly at 15in/sec. Four video heads are used, spaced at 90° intervals round a drum rotating at 1500 r.p.m. and the effective tape speed is about 1550in/sec past the head. The heads "overlap" so that no signal is lost during the changeover from one head to the next: this is arranged to fall during a line blanking period so that any disturbance is not seen on the picture. A servo-control system is used to maintain tape and head speed at the correct values and the block diagram shows the main features of this. The theoretical horizontal resolution on a 405 line standard is about 380 picture elements per line, ten lines being recorded as one transverse "stripe" by each head in turn. Signal-to-noise ratio (picture) is better than 30dB and some machines have provided a ratio as high as 50dB. (26dB is accepted as being the minimum desirable figure for a television picture.)

Joins in the tape could lead to instability of frame synchronization if the splice comes in such a place that one field is shortened or lengthened.†

Editing facilities are provided by recording longitudinally, on one edge of the tape, a control track (this is similar to the sprocket holes in a cine

* Technical Notebook, Sept. 1957.

† Technical Notebook, April 1958.

Block diagram of the Ampex recorder video system. The processing amplifier (bottom right) removes the "syncs" from the playback and substitutes "clean" ones.

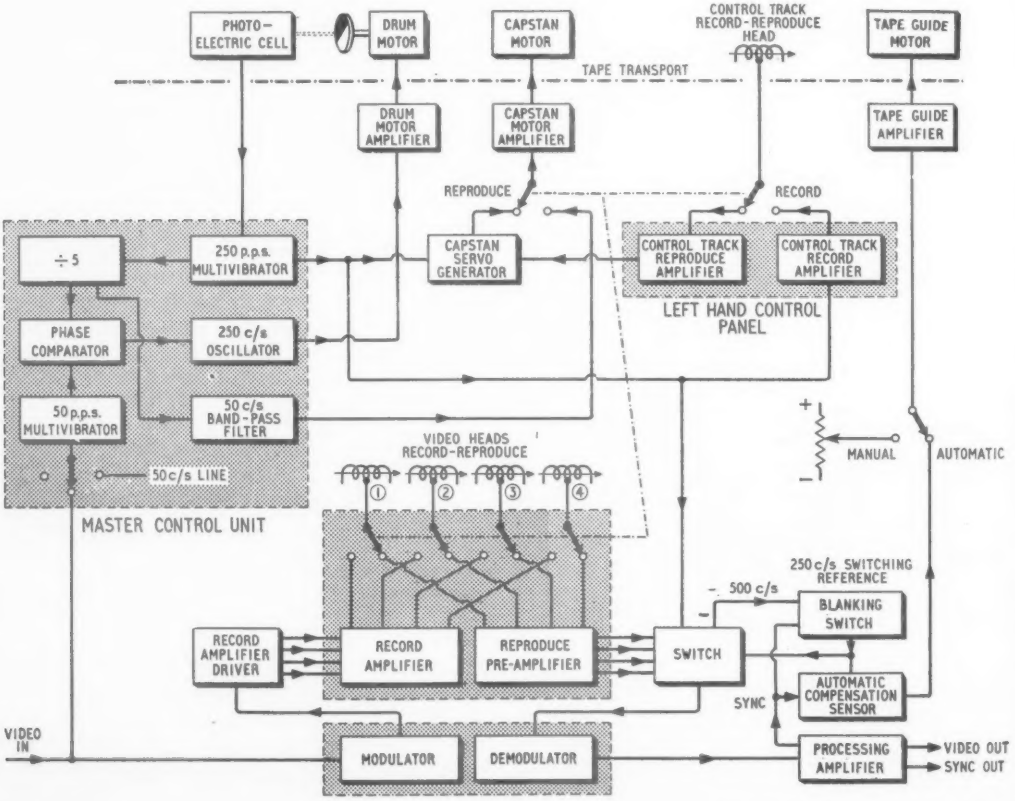

film) which includes pulses marking the frame blanking periods and 250 p.p.s. sync. These are rendered visible by applying a finely divided magnetic powder to the tape: this sticks to the magnetized parts and thus enables the modulation to be seen so that a cut can be made during the frame blanking period. Once the splice has been made the particles are wiped away. The sound track is also longitudinally recorded; but on the opposite edge of the tape to the control track pulses.

Associated-Rediffusion provided for the demonstration a studio performance which was first seen "live" on monitors placed about the studio and then as a replay from the Ampex machine. It would, of course, be an exaggeration to say that the magnetically-recorded picture is indistinguishable at close quarters from the original. It is, however, quite hard to say whether the picture is a playback or not when looking at a monitor from such a distance that the line structure disappears. Watching a 21in monitor about four or five feet away it was obvious that the signal-to-noise ratio was worse and the definition was not quite so good as on the "live" transmission. Synchronization of the line time base was fairly good; some slight "wander"—about one tenth of an inch in amplitude—was visible. This, on a 21in tube, represents a timing error of about half a microsecond, which is a quite good performance. Unfortunately it is not possible to comment on frame synchronization and black level retention because the monitors provided showed either an inability to interlace correctly, or a loss of d.c. component, on the "live" programme. One rather disconcerting feature was that one head seemed to have rather better performance than the other three, so that thirty lines of picture exhibited a lower signal-to-noise ratio than the next ten. When questioned, one of the technicians in charge said that this could have been caused by dirty or worn heads and, in fact, the recorder demonstrated had been in use for many hours for the training of operational staff.

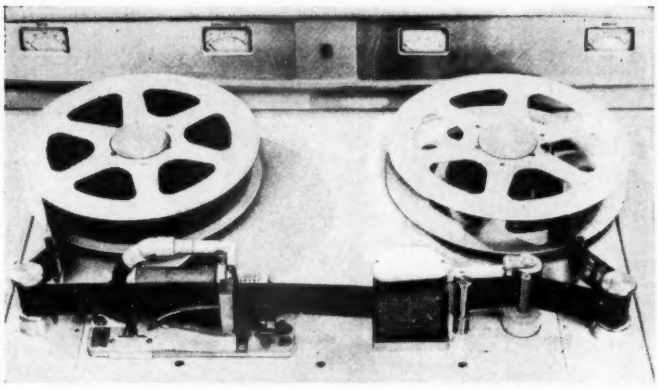

Tape transport mechanism of the Ampex recorder. The pipe on the back of the video head (left) evacuates the space between the tape and the rotating head so that air pressure maintains an intimate tape-to-head contact. The large right-hand assembly contains the control track and sound record and erase heads.

A few "drop-outs" appeared on a second run-through of the tape; these take the form of white dots rather like extremely well-limited ignition interference. On a third run-through of part of the tape drop-outs were even more evident, but again these were blamed on dirt on the head assembly. Overall, the performance of the machine can be considered very satisfactory and the slight defects noted above under critical comparative examination probably would not be noticeable under domestic conditions.

The recording system consists of three main units—the recorder itself and two racks containing the power supplies and control equipment. The recorder weighs 1,350 pounds, costs £20,000 and plays for 65 minutes from a 12½ inch reel of tape, which costs about £100 and can be used at least 100 times. This tape is imported from the U.S.A. and it is coated with a special fine-grain oxide mix. One head assembly will normally last for at least 100 hours running time (three "spares" are provided with the machine) and there is a "trade-in scheme (operated by Rank-Cintel, Limited) for servicing worn heads.

TV Aids TV Advertising

A LARGE closed-circuit television system is to be installed by Marconi's Wireless Telegraph Co., Ltd. for L.P.E. Television, Ltd., the advertising agents, to enable executives in 43 offices and 3 conference rooms to judge the merits of films and to see the performances of artistes as they would appear to television viewers.

Marconi's have developed new cameras (BD871) with pedestal mounting so that they can be swivelled to pick up the output from either of three projectors (two 35mm and one 16mm) or stills from a slide projector.

Distribution is by modulated crystal-controlled r.f. in a cable system supplied by Belling & Lee, Ltd., and the film projectors and associated sound systems are by R.C.A. (Gt. Britain), Ltd.

A four-position switch at each viewing point gives the choice of two internal circuits as well as the B.B.C. and I.T.A. broadcast programmes.

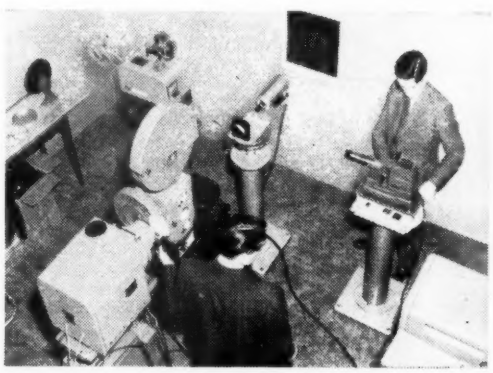

WORLD OF WIRELESS

N.T.S.C. Colour in Europe

DEMONSTRATIONS of N.T.S.C. colour television working on 625-line standards were witnessed by *Wireless World* recently at the laboratories of Hazeltine-Aga in Paris. This organization is a fairly new one, formed by Hazeltine, of America, and Aga, of Sweden, with the intention of making available American technical experience and patents to Continental radio manufacturers if the N.T.S.C. colour system is established in Europe.

The demonstrations were conducted on a closed circuit, using N.T.S.C. coding equipment built by Aga, with an RCA 21-inch colour receiver adapted to work on 625-line standards. A flying-spot scanner provided the picture source and was used on both still colour transparencies and "live" material in a small studio. The displayed pictures were of excellent quality but were not superior to the 405-line colour demonstrations we have seen recently in Britain, except perhaps in lack of "lininess".

Colour Television Training

TECHNICAL education almost invariably tends to lag behind the work being undertaken in industrial research and development laboratories. This, however, will hardly be true of those studying colour television at the Northern Polytechnic (London, N.7) during the coming session. John Gilbert, head of the Polytechnic's Department of Telecommunications, with the co-operation of V. J. Cooper, Marconi's Chief Television Engineer, has set up colour demonstration apparatus and test gear for an evening course of lectures covering the fundamentals of colour transmission and reception.

Entry qualifications for the course, which presupposes some knowledge of monochrome principles, are at least the C. & G. Radio III level, or the R.T.E.B. Television Servicing Certificate.

The syllabus covers the perception of colour, colour synthesis, photometry, and a résumé of monochrome transmission techniques. Possible colour transmission systems are compared, the N.T.S.C. system being dealt with in detail, leading to considerations in receiver design.

Telecommunications Technicians

DESIGNED to meet the needs of employees of the Post Office Engineering Department and of organizations engaged in the manufacture of telecommunications equipment, the City and Guilds telecommunications engineering course is one of the most successful run by the Institute. Experience has shown, however, that the complete five-year course is beyond the capacity of the majority of students, many of whom fall out after the third year, while a number of the entrants in the fourth and fifth years are found to be graduates and those already possessing advanced qualifications of various kinds.

It has, therefore, been decided to introduce a four-year telecommunication technicians' course with supplementary studies covering, for instance, microwave techniques, sound and television broadcasting and radar and radio navigational aids. This new four-year course is roughly equivalent to the first three years of the existing five-year scheme which it will eventually replace.

The Full Technological Certificate, now awarded at the end of the fifth year, will, in the new scheme, be awarded to those holding a Telecommunication Technicians' Certificate who pass in two of the examinations in the group of supplementary studies.

Examinations covering the first two years of the telecommunications technicians' course will be introduced in 1959.

Medical Electronics Conference

TWO British representatives were elected to the executive committee of a new international organization on medical electronics formed recently at a planning conference in Paris. Dr. C. N. Smyth, of University College Hospital, becomes a vice-president, while B. Shackel, of the Psychological Research Laboratory of E.M.I. Electronics, becomes the treasurer. Dr. V. K. Zworykin, the well-known television pioneer, now at the Rockefeller Institute for Medical Research, New York, was elected president. The purpose of the organization is to promote international co-operation and co-ordination in medical electronics, through existing national organizations, with the immediate aim of arranging another conference, probably next year in Europe.

The planning sessions were followed by two days of technical sessions, consisting of 34 short and informal communications on work in progress. Some of the topics discussed are summarized on page 361.

Sandwich Courses

THE popularity of sandwich courses leading to higher qualifications in engineering and technology, consisting of alternate periods (usually about six months) of study in a technical college and experience in industry, has increased considerably over the past few years. This is borne out by the latest list of approved sandwich courses in technical colleges in the U.K.* which includes details of 263 courses—65 more than were approved in 1957/58.

The definitions "works based" and "college based" are used in the list; the first denoting a course for employees of a particular firm who gain their practical experience with that firm, and the second a course for which students enrol at a college and gain their works experience with a variety of firms under the guidance of the college.

The courses are listed both under subjects and colleges. Three electronics courses are quoted:—a four-year course at East Ham Technical College (leading to the H.N.C. and Grad. Brit. I.R.E.); a four-year physics and technology of electronics course at the Northern Polytechnic (Dip. Tech. and Grad. Inst.P.) and a four-year course in physics with electronics at Glamorgan College of Technology (College Diploma and Grad. Inst.P.). There is also a light-current electrical engineering course at Salford Royal Technical College and a number covering

* List 182 (1958) H.M.S.O. (1/6)

telecommunications and electrical engineering generally.

Whilst on the subject of sandwich courses mention should be made of the list of full-time and sandwich degree and diploma courses in London and the Home Counties issued by the Regional Advisory Council for Technolgical Education.

"Oboe" Awards.—For their war-time development of "Oboe"—the radar blind-bombing device—whilst at T.R.E., Alec H. Reeves and Dr. Frank E. Jones have been jointly awarded £3,000 on the recommendation of the Government Departmental Awards Committee. Mr. Reeves was with Standard Telephones and Cables before the war and in 1946 joined the Standard Telecommunications Laboratories where he is now head of a division. Dr. Jones, who was at T.R.E. from 1940 until 1952 when he went to the R.A.E. as deputy director of equipment, retired from Government service two years ago and is now a director of Mullard.

U.K. Radio Backbone.—Nearly three years ago it was announced by the Post Office that a chain of radio relay stations extending through the country from north to south was to be built to carry some thousands of telephone circuits and two television circuits. This was to be completed by 1960. It is now learned from the annual report of the Telecommunication Engineering and Manufacturing Association that this work has not yet been put in hand and, says the report, "it would appear to be one of the projects to have fallen under the axe of the Chancellor of the Exchequer."

Receiving Licences.—Combined television and sound licences in the U.K. increased by 53,765 during May, bringing the total to 8,201,098. Sound-only licences totalled 6,425,530, including 343,085 for car radio, bringing the overall total to 14,626,628.

TV in Australia.—Production of television receivers in Australia rose from 49,000 in 1956 to 208,000 last year. At March 31st there were just over 220,000 television licences in force in the country. They are concentrated in Victoria and New South Wales, the only states in which there are stations.

Receiver Manufacture.—Instead of the summary of estimated sales of domestic receiving equipment issued in the past by B.R.E.M.A., the Association is compiling a monthly survey of "estimated despatches to the home market by all manufacturers." The first figures to be issued (April) are: television receivers 73,000, sound (including car radio) 83,000 and radio-gramophones 12,000. Compared with the estimated average for April in the previous two years, the television figure is up by 3,000 but sound receivers are down by 6,000 and radio-gramophones by 4,000.

Information Processing.—An International Conference on Information Processing sponsored by U.N.E.S.C.O. will be held in Paris next June. Assistance will be given by a new organization, the Provisional International Computation Centre, established in Rome by agreement between U.N.E.S.C.O. and the Italian Institute of Higher Mathematics. The main function of this Centre is to ensure mutual assistance and international collaboration between existing computation and information processing bodies. Its Bulletin No. 1 was published in April, 1958, from the Secretariat, Palazzo degli Uffici, Zona dell'Eur, Rome.

Computer Conference.—The first conference of the British Computer Society will be held in Cambridge from 22nd to 25th June, 1959.

Air Traffic Control.—Plans are being made by the Guild of Air Traffic Control Officers to hold a convention on October 23rd and 24th at Southend-on-Sea. Information on the convention is obtainable from the Guild, 118, Mount Street, London, W.1.

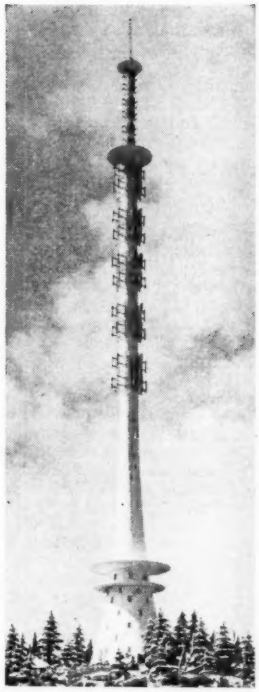

NOVEL TV TOWER.—This model shows the novel construction of the tower built by the Bayerische Rundfunk on the summit of the Ochsenkopf, north east of Bayreuth, to carry the aerials for a television and v.h.f./f.m. station. The transmitting equipment is housed in the eight stories in the lower part of the tower. The first of the four platforms carries the parabolic reflectors for the radio links and the second platform is provided to protect the reflectors from falling ice. The Band II aerials are mounted above the third platform below which are the Band I television aerials. Provision is made to extend the height of the tower from 166 m to 180 m to accommodate the arrays for a Band IV television transmitter. The base of the tower is 1,013 m above sea level.

Institute of Physics.—The Institute's report for 1957 shows that during the year the membership rose to close on 6,000. Of the 68 candidates who took the recently established graduateship examination only 21 passed.

S.I.M.A. Council.—New members elected to the council of the Scientific Instrument Manufacturers' Association for 1958/59 are G. C. Fairbanks, representing Elliott Brothers, H. R. A. de Jonge (Rank Precision Industries), E. R. Ponsford (Solartron), and J. Rock Cooper (Oertling).

Plastics Travel Scholarships.—Two £500 European travel scholarships have been given to the British Plastics Federation by the Iliffe Associated Press. Nominations for the scholarships, which are open to men and women in the plastics industry, should be submitted to the Federation, 47-48, Piccadilly, London, W.1, by August 31st.

Norwood Technical College.—The 1958/59 prospectus of the Norwood Technical College, London, S.E.27, includes details of full-time, part-time and evening courses in telecommunications engineering, v.h.f. techniques, electronic instrumentation, radar maintenance, radio and television servicing and advanced radio operating.

S.E. London Technical College, Lewisham Way, S.E.4, is running a six months' full-time course starting in October in preparation for Part III of the I.E.E. Examination. Provision is made for specializing in industrial electronics and radio communication.

Amateurs' Courses.—The East London Group of the R.S.G.B. is again organizing in conjunction with the Essex County Council a course in preparation for the radio amateurs' examination. The eight-month course will be held at the Ilford Literary Institute, High School for Girls, Cranbrook Road, Ilford, Essex, on Wednesday evenings commencing September 24th (fee 30s). A morse class (fee £1) will be held at the Institute on Monday evenings.

I.E.E. Radio Section.—The chairman of the Radio and Telecommunication Section of the I.E.E. for 1958/59 is G. Millington (see Personalities). Two new vice-chairmen have been elected; they are: R. J. Halsey, C.M.G., B.Sc. (G.P.O.); and T. B. D. Terroni, B.Sc. (A. T. & E.). The five new ordinary members of the committee are: D. A. Barron, M.Sc. (G.P.O.); G. G. Gouriet (B.B.C.); C. G. Mayer, O.B.E. (R.C.A.); J. Moir (B.T.H.); and A. J. Young (English Electric Valve).

Television Convention.—The British Amateur Television Club will be holding its fourth amateur television convention on September 6th from 10.0 to 7.0 in the Conway Hall, Red Lion Square, London, W.C.1. There will be displays of amateur-built television equipment in operation, including demonstrations of colour television. The charge for admission of non-members is 5s (2s 6d after 2.0 p.m.). Further particulars are obtainable from D. S. Reid, 27, Rose Valley, Brentwood, Essex.

Research Fellowship.—The Committee representing the Royal Society and the Armourers and Brasiers' Company has appointed Dr. T. E. Faber, of Corpus Christi College, Cambridge, as Armourers and Brasiers' Company Research Fellow from October 1st, to work at the Cavendish Laboratory, Cambridge, on the electronic properties of liquid metals.

American films previously distributed in this country through the U.S. Embassy are now available from the Film Library of the Central Office of Information. Among the 150 American films listed in a supplement to the Library's main catalogue are two 16-mm films on the diode and triode and another (running for 31 minutes) on the life of Edison.

E.F.F.I.—The first name in the list of organizations participating in the Electronic Forum for Industry given in our last issue should have been the British Electrical and Allied Manufacturers' Association, and not B.R.E.M.A., as inadvertently stated.

QSL cards have in the past been issued free to amateurs by Mullards, but owing to the increased cost of production it has been necessary to make a nominal charge for supplying and overprinting. The charges are:—250 cards, £1; 500 cards, £1 10s; and 1,000 cards, £2.

Evening Courses for the Radio Amateurs' Examination and in radio and television servicing will be conducted at the Brentford Evening Institute, Middlesex, commencing September 22nd. Particulars are obtainable from the Education Office, Town Hall, Chiswick, London, W.4. A radio and television maintenance course will be conducted at the Wesley Evening Institute, Stonebridge Road, London, N.W.10, commencing in September. At the Northwood Evening Institute, Potter Street, Northwood Hills, Middx., two radio courses will be held next session. One covers the Radio Amateurs' Examination syllabus the other being a more advanced course. Classes commence on September 23rd.

Courses for Overseas Trainees.—Home and overseas distributors of Pye equipment have for some time been able to send their technical staff for factory training at Cambridge, and for this purpose Pye have now set up a training school. Three training courses—elementary radio, advanced radio and television servicing—will be held each year for overseas trainee engineers. At present 30 students are attending these courses.

Capitol Radio Engineering Institute, which has been established for some years in Washington, D.C., where it provides both residential and postal courses in radio and electronic engineering, is establishing an overseas headquarters in London. Arthur F. R. Cotton, who went to the United States 11 years ago, has been appointed Director of European Operations for the Institute.

"Science Recorded" is the title of the tape recorded magazine issued monthly by Science for the Blind, a subsidiary of the Philadelphia Association for the Blind. According to a note in *General Radio Experimenter*, one source from which radio material is extracted, over 4,000 tapes were dispatched during the 12 months ended last October.

For the DXer.—"World Radio Handbook for Listeners," now in its 12th edition, includes not only frequencies of transmitters but also tuning signals, times of regular transmissions, names of broadcasting personalities and other useful information on the broadcasting organizations of the world. Although published in Denmark it is printed in English and is available in this country from Surridge, Dawson & Co., Ltd., 136, New Kent Road, London, S.E.1, price 13s 6d.

AIR TERMINAL TELEVISION.—Closed-circuit TV equipment has been installed at the West London Air Terminal as an aid to making announcements. The announcement is spoken once only, the announcer appearing on the screens of eight 21-in Pye receivers in various parts of the building, then a "caption" giving the details is screened. The equipment uses a standard Pye Staticon tube camera which covers both the announcer and the bilingual captions, which are inserted in a carrying cradle in the control panel (right). The total cost of the equipment, installed by Audio and Video Rentals, was in the region of £2,000.

Personalities

G. Millington, M.A. (Cantab.), B.Sc., the new chairman of the Radio and Telecommunication Section of the I.E.E., has been with Marconi's since 1931 specializing in theoretical and experimental studies relating to wave propagation. He has headed the company's propagation section since the retirement of T. L. Eckersley in 1946. A native of Southwark, London, he was a pupil of St. Olave's grammar school and later graduated at Clare College, Cambridge, For two years Mr. Millington was engaged in research work on beta-rays at the Cavendish Laboratory. In 1953 he was appointed international vice-chairman of the C.C.I.R. study group investigating the problems of ground-wave propagation.

G. MILLINGTON

D. H. Black, M.Sc., Ph.D., who for the past two or three years has been principal director of electronics research and development in the Ministry of Supply, has been appointed director of the Ministry's Armament Research and Development Establishment at Fort Halstead. Dr. Black has been in the Civil Service since 1939, before which he spent 14 years in industry, the last seven being with Standard Telephones & Cables. He was at R.R.D.E. (now R.R.E.), Malvern, for two years before being appointed in 1947 director of electronics research and development (defence) in the M.o.S. He held this post until 1953 when he went to Australia for two years as head of the United Kingdom Ministry of Supply staff in the Commonwealth.

C. H. Banthorpe recently became technical director of Central Equipment, Ltd., of which Derwent Television is a part. He joined the company in 1936 as a radio service engineer. Throughout the war he was at the Telecommunications Research Establishment, after which he returned to Central Equipment to take charge of radar production and test, transferring to television shortly before the B.B.C. transmissions recommenced. For several years he has been works manager of the Derwent factory at Perivale, Middlesex, and has been responsible for the designing of their television receivers since 1951.

W. E. C. Varley, Associate I.E.E., has been appointed by the B.B.C. assistant superintendent engineer (transmitters) on the retirement of **C. W. Skinner,** M.B.E., after more than 33 years' service. Mr. Varley joined the Corporation in 1933 as an assistant maintenance engineer at the Daventry transmitting station. In 1935 he was appointed assistant to the superintendent engineer (transmitters) in London. In this capacity he was responsible for the development and maintenance of precision equipment for the control of frequency of medium- and short-wave transmitters. He has carried out a number of broadcasting surveys in Africa and elsewhere on behalf of H.M. Government.

W. J. Phillips, for the past 18 years with Siemens Edison Swan in charge of their cathode-ray tube and valve life test department, has joined Perth Radios, Ltd., as works manager.

R. W. Addie, M.A., who joined E.M.I. Electronics six months ago as export manager, has been appointed to the board as marketing director.

P. G. A. H. Voigt, B.Sc., the well-known loudspeaker designer, who has lived in Canada since 1950, has been elected chairman of the Canadian Society of Music Enthusiasts, the aim of which is "to provide its members with a better understanding of both music and the technical means to attain its reproduction in high fidelity." Mr. Voigt's tape-recorded address given at the 21st anniversary celebration of the B.S.R.A. was repeated at a recent meeting of the Canadian S.M.E.

A. H. Dickinson, A.M.Brit.I.R.E., who was an assistant engineer in the B.B.C. research department during the war and since 1945 has been with Broadcast Relay Services as chief engineer in their overseas branches, has left the company to join the broadcasting section of the Colonial Office as chief engineer, Department of Information and Communications, British Honduras. He is well known for his work on the development of vertical incidence broadcasting.

D. L. Phillips, M.M., M.Inst.B.E., A.M.Brit.I.R.E., has resigned his appointment as works manager of Technograph Electronic Products, Ltd., the development and manufacturing company of Technograph Printed Circuits, Ltd. He will be undertaking consulting work and has been appointed consultant to Mills & Rockleys, Ltd., of Coventry. During the war he served as a technical signals officer in the R.A.F. Prior to joining Technograph he was in Plessey's components division at Swindon.

OUR AUTHORS

J. N. Prewett, M.A., Grad.I.E.E., author of the article describing a transistor test set, obtained his degree in natural sciences at Clare College, Cambridge, and after serving for two years in the Royal Signals joined the Central Electricity Research Laboratories in 1953. At the laboratories he has been mainly concerned with electronic circuit designing.

S. Welldon, who in this issue discusses the use of the Zener diode as a voltage stabilizer for small motors, joined the research laboratories of the G.E.C. in 1947 where he initially worked on the development of equipment for the London-Birmingham television link. He has more recently been working on semiconductor evaluation and applications.

J. H. Jowett, B.Sc.(Eng.), who describes a photographic timer on page 385, recently joined the J. Langham-Thompson organization at Bushey Heath, Middlesex, as a trials engineer. After graduation at Bradford Technical College in 1952 he took a two-year graduate apprenticeship course with the G.E.C. at Coventry, and from 1954 until March this year was on the staff of the G.E.C. applied electronics laboratories. His interest in photography is purely as a hobby.

OBITUARY

Reginald Charles Bulgin, a director of A. F. Bulgin & Co., died on June 6th at the age of 52. He had been with the company since its inception in 1923, and was in charge of the Purchasing Department.

EDITORIAL ASSISTANT WANTED

Our sister journal *Electronic & Radio Engineer* invites applications for a post as editorial assistant. The duties are of a varied nature and call for an ability to write clearly as well as a wide technical knowledge. A good background of general physics is desirable and experience in radio and electronics is essential.

Applications should be addressed to the Editor, *Electronic & Radio Engineer*, Dorset House, Stamford St., London, S.E.1.

News from the Industry

75th Anniversary.—An exhibition to mark the progress of design in telecommunications over the past 75 years was organized last month by Standard Telephones & Cables who started business with a staff of three in Moorgate, London, in 1883 as agents for telephone apparatus. They now employ 25,000 at eight major factories throughout the United Kingdom.

B.T.M.-Powers-Samas Merger.—The British Tabulating Machine Company and Powers-Samas Accounting Machines have reached agreement in principle for a merger of their businesses. A new operating company will be formed to take over the undertakings of both companies.

Mullard.—A new division to be known as the Government and Industrial Valve Division has been formed, which will mainly embrace the former Communications and Industrial Valve Department and the Government Radio Valve Department. Head of the new division is H. St. A. Malleson. Within the new division four product groups have been established with a commercial manager in charge of each: electron optical devices (J. V. S. Tyndall), receiving valves (D. R. Rolinson), special industrial valves (K. F. Gimson), and transmitting and microwave valves (P. S. Britton).

Heath Kits, which cover receivers, amplifiers, test equipment, etc., are to be marketed in this country. Daystrom, Ltd. has been set up over here by Daystrom Inc. (Murray Hill, N.J.), of which the Heath Company is a subsidiary. Temporary factory accommodation has been secured in Gloucester and production is planned to start before the end of this year. George Tillett, formerly chief engineer and a director of Armstrong Wireless and Television, has been appointed chief engineer.

Ultra's turnover for the year ended last March was a record for the company with a net profit of £114,191, nearly double that of the previous year. In his report the chairman, Edward Rosen, said that "the diversified activities of the special products division are now larger than that of the company's founder business, radio and television."

Ever Ready.—The annual report of the Ever Ready Company (Great Britain) records that the net profit before taxation for the year ended March 1st was £1,926,303 compared with £1 797 810 for the previous period. Taxation will absorb nearly £1M. The report also states that 355 members of the staff have received gold watches for twenty-five years' continuous service with the company.

Evershed & Vignoles, Ltd., have established a Scottish area office at 13, Rutland Street, Edinburgh, 1. (Tel.: Fountainbridge 3058.) R. M. Wardrop, who for some years prior to joining the company in 1955, was in the G.E.C. Research Laboratories, is in charge of the office.

Cosmocord, Ltd., have set up a stereophonic test laboratory at their works at Waltham Cross, Herts. The company is producing a stereo cartridge (Acostereo) and is developing a combined cartridge for stereo, L.P. and standard records.

Winston Electronics, Ltd., have been appointed U.K. distributors of the Beckman-Berkeley (Richmond, Cal., U.S.A.) range of electronic equipment for industry.

Air Surveillance Radar.—The new Decca long-range air surveillance radar announced last month, was inadvertently quoted as operating in the 3-cm band. The D.A.S.R.1 operates on a wavelength of 10 cm.

Electronic Rentals Association, Ltd., has been formed by a number of sound and television receiver rental concerns "to promote the consideration and discussion of all questions affecting rental services . . .". The registered office of the association is at 75, Cannon Street, London, E.C.4.

Jason (France) has been formed by the Jason Motor and Electronic Company to manufacture high-fidelity equipment in France. The offices are at 19 Boulevard des Capucines, Paris, 2e. The company's first products will be the Jason J10 amplifier and the CQ speaker, which is being made under licence from CQ Audio, Ltd.

Vibration and shock testing service for potential users of isolating mountings is one of the activities of the new engineering laboratory of Cementation (Muffelite), Ltd., Molesey Road, Hersham, Surrey, who manufacture anti-vibration mountings under licence from Barry Controls Inc. (U.S.A.).

Simon Equipment, Ltd., has supplied a multi-channel recording installation for the Central Electricity Generating Board in Manchester. It is capable of eighteen hours uninterrupted recording on four channels simultaneously and incorporates a time injection unit which superimposes time signals on all channels at one-minute intervals. The company also announces the appointment of J. A. Wright, previously with Ericsson Telephones and Siemens Edison Swan, as works manager.

Plessey's chemical and metallurgical division, at Towcester, Northants, has recently moved a section of its plant engaged in the production of ferromagnetic memory planes to a new factory at Water Lane, Towcester.

Philips' North-East Regional Headquarters are now at 72, Wellington Street, Leeds. The building includes a large lecture room, a showroom and a trade advice centre.

Murphy Radio v.h.f. mobile radio equipment was used by motor cycle travelling marshals during the Tourist Trophy races in the Isle of Man this year.

OVERSEAS TRADE

Britain in Europe Committee.—An organization under this title has been set up with offices at 61, Catherine Place, Palace Street, London, S.W.1 (Tel.: Victoria 4165) to promote interest in the proposed European Free Trade Area. Among the 50 or so members of the committee, of which Sir David Kelly is chairman, is C. O. Stanley, chairman of Pye, and D. Maxwell Buist, export director of B.E.A.M.A.

V.H.F. radio-telephone equipment has been supplied by Marconi's for the port of Karachi. Ten-watt f.m. transmitter-receivers have been installed in five harbour craft and there are three base stations.

Data control system suitable for use with large skin-milling machines of the type used for manufacturing large aircraft components has been developed by E.M.I. in collaboration with the Cincinnati Milling Machine Co., of Ohio. Equipment for the system is being manufactured at Hayes for the Air Materiel Command of the U.S. Air Force.

V.H.F. equipment valued at £15,000, including 15 f.m. radio links, is being manufactured by A.T.E. (Bridgnorth), Ltd., for connecting the administration headquarters of the Bahrein Petroleum Company at Awali, Bahrein Islands, with the refinery, wharf and other locations.

Manufactured exclusively in Great Britain by

BRIMAR

The BRIMAR 5965 is a Trustworthy miniature double triode designed for use in high-speed digital computers. Each triode section features a high zero-bias anode current, a sharp cut-off characteristic, and a separate cathode connection. In addition, the balance of the cut-off characteristic between the two sections is controlled. The heater-cathode construction is designed for dependable service under conditions of intermittent operation. When used in "on-off" control applications, the 5965 will maintain its emission capabilities after long periods of operation under cut-off conditions.

THE TRUSTWORTHY Type

5965

MINIATURE DOUBLE TRIODE

for use in

HIGH SPEED DIGITAL COMPUTERS

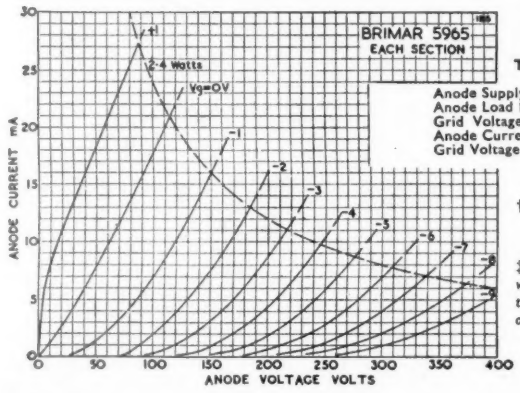

Heater Voltage (A.C. or D.C.) 6.3 } or { 12.6 volts
Heater Current ... ... 0.45 } or { 0.225 amp.

TYPICAL OPERATION (Computer Service, Each Section)

	On Condition	Off Condition
Anode Supply Voltage	150	150 volts
Anode Load Resistor	7,200	7,200 ohms
Grid Voltage	0†	— volts
Anode Current, approximate	10.5	— mA
Grid Voltage for I_a = 150μA approx.‡ ...	—	—5.5 volts

† *Approximate value of grid voltage with grid current adjusted for approximately 140μA.*

‡ *The grid voltage required to produce 150μA in one section normally will not differ by more than 1.5 volts from the grid voltage required to produce 150μA in the other section with an anode supply voltage of 150 volts and an anode load resistor of 7,200 ohms.*

Standard Telephones and Cables Limited

(Regd. Office: Connaught House, 63 Aldwych, London, W.C.2.)

FOOTSCRAY, KENT. Footscray 3333

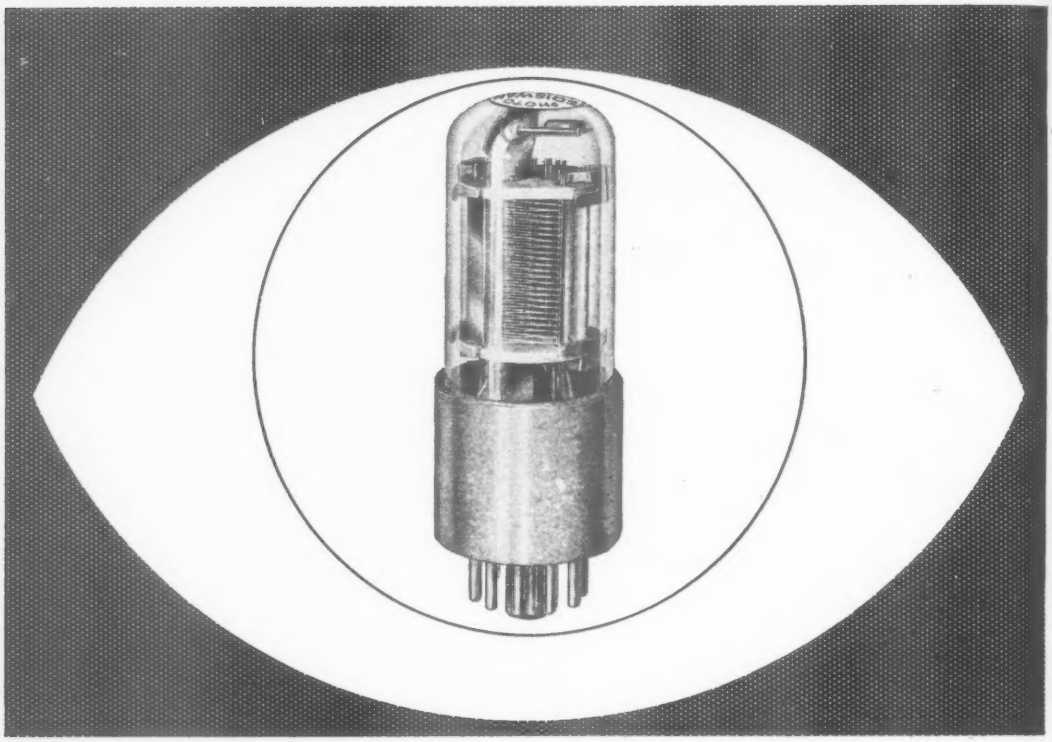

Announcing
two new EDISWAN Photomultipliers

We are pleased to announce two new Ediswan Photomultipliers : Type 27 M12 and Type 27 M13.
Both are based on the well-known Ediswan Photomultiplier Type 27 M1.
Here are brief details of the new types (further particulars will be gladly given on request) :

27 M12

Nine-stage Photomultiplier specially designed for use in aircraft and other locations where strong vibration is experienced.

Base:	Flying Lead
Cathode:	Blue Sensitive
Av. Cathode Sensitivity:	20 μA/lumen
Max. Anode Current:	1 mA
Typical Operation:	
Volts per stage	65V
Volts anode to secondary cathode	65V
Sensitivity (white light)	1.0 A/lumen
Average Current Amplification	60,000
List Price: £18.0.0	

27 M13

Seven-stage Photomultiplier with twin anodes. These provide a double output, which remains well matched under all conditions.

Base:	11 pin sub-magnal
Cathode:	Blue sensitive
Av. Cathode Sensitivity:	15 μA/lumen
Max. Anode Current:	1 mA
Typical Operation:	
Volts per stage	125V
Volts anode to secondary cathode	50V
Sensitivity (white light)	2·0 A/lumen
Average Current Amplification	13,000
List Price: £16.0.0	

Other Photomultipliers in the Ediswan range.

27 M1 Standard high sensitivity type (9 stage)	List price £15.0.0.
27 M2 Lower sensitivity (9 stage) type	List price £ 8.0.0.
27 M3 Sensitive to near ultra violet (9 stage)	List price £16.0.0.

SIEMENS EDISON SWAN LIMITED
AN A.E.I. COMPANY
155 CHARING CROSS ROAD, LONDON, W.C.2 AND BRANCHES
Phone: GERrard 8660. Grams: Sieswan, Westcent, London
CRC 16/5

Transistor Test Set

Measurement of Collector Leakage and Current Gain

By J. N. PREWETT*, M.A., Grad. I.E.E.

WHEN designing or maintaining transistor equipment, some means of measuring the "goodness" of a transistor is required. Ideally, six or more characteristic curves should be plotted and compared with the manufacturer's data. Since this operation is lengthy and involves the use of a lot of expensive equipment, a simpler means of testing transistors was devised.

The parameters measured are I_{cbo}, the collector leakage current with the base open circuit (also called I'_{co}), and β, the common emitter current gain with short-circuited collector (also called α'). The majority of transistor faults will show up on these two measurements. To avoid accidental damage to transistors under test, the measurements are made at fixed low values of current and voltage.

The following measurements may be made:

(a) I_{cbo} from 0 to 1 mA (V_{cb}=2·5 to 1 V depending on leakage current)

(b) β from 5 to 100 (V_{ce}=2·5V, I_c=1.3 to 2·3mA).

The equipment is suitable for testing p-n-p or n-p-n germanium junction transistors with up to about 200 mW dissipation. Silicon units may also be tested, but the measured value of β will be rather lower than the true value.

Measurement of I_{cbo}—The collector leakage current is not very dependent on voltage until the collector breakdown voltage is approached. For convenience, the measurement is made at a supply voltage of between 1 and 2·5 V, depending on the value of the leakage current. The basic measuring circuit is shown in Fig. 1. Should the transistor have a short circuit fault, R_5 will limit the meter current to 1·65mA.

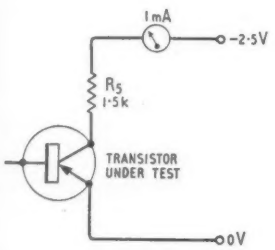

Fig. 1. Measurement of I_{cbo}.

Measurement of β—The method employed is to set up the transistor in a common emitter circuit, so as to pass 1·3 mA collector current. If the base current is now increased by i, the collector current will increase by βi, assuming that the value of β does not change when the collector current is increased.

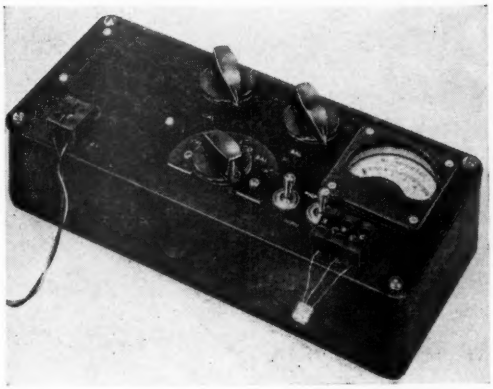

External view of test set.

In practice there is a small variation of β, but this does not greatly affect the measurement. If we make i=10 μA, and allow for a maximum value of β of 100, then βi = 1 mA when β = 100. Provided the initial 1·3 mA collector current can be backed off, the increase in collector current may be displayed on a 0 to 1 milliammeter calibrated 0 to 100, so that β may be read directly.

Fig. 2 shows the circuit used to measure β. With S1 open, the collector current is controlled by RV_1 which adjusts the base current. When I_c = 1·3 mA, the voltage drop across the collector load R_3 is such that V_c = 2·5 V. Since both sides of the milliammeter are now at the same potential, no current can flow through it, and it will read zero.

When S1 is closed, an additional 10μA (2·5V/R_1 approximately) will flow into the base, increasing the collector current by 10β μA. If the meter resistance is very much less than the collector load resistance, all the additional collector current will flow through the meter. Since the meter has a 1-mA movement, and is calibrated 0 to 100, the meter reading now gives the value of β.

When using this method of measurement, there are a number of small errors, most of which can be eliminated or reduced. The sources of these errors are: (a) the meter, (b) the current i through R_1, (c) the fraction of i injected into the base of the transistor due to finite base resistance, (d) the fraction of the increase in the collector current which passes through the meter, determined by the meter resistance and internal resistance of the 2.5 V source and (e) the variation of β with collector current.

If a small ex-Government meter is used, there may be up to 10% error on the full scale reading of the meter. This error may be eliminated as follows. The meter, in series with a 2·5-kΩ, 1% tolerance, high-stability resistor is placed across the 2·5-V and 0-V points, and the voltage of the 2·5-V source adjusted for full scale deflection. If the meter reads 10% high, say, the 2·5-V source will be 10% below its nominal value (neglecting the meter resistance compared with 2·5 kΩ). Reverting now

* Central Electricity Research Laboratories.

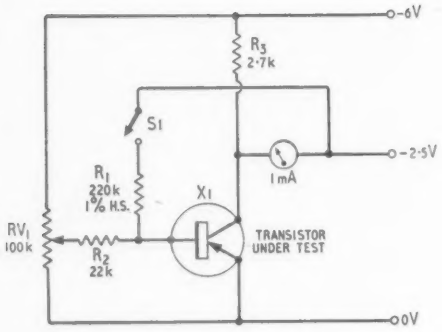

Fig. 2. Measurement of β.

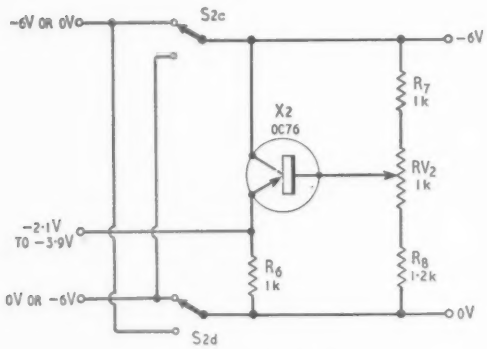

Fig. 3. Voltage supplies.

to Fig. 2, the current flowing through R_1 will be 10% low, and the additional collector current will be 10% low. But as the meter reads high by the same amount, the error will be corrected.

For the majority of transistors under test, the base-emitter voltage will be approximately 0·15 V, and the input slope resistance of the order of 1,000 Ω. Thus the current flowing through R_1 is only $(2{\cdot}50-0{\cdot}15)/R_1$ instead of $2{\cdot}5/R_1$. Also a small percentage of this current flows up R_2 instead of into the transistor base, the amount depending on the position of RV_1. Furthermore, at the collector, the meter plus source internal resistance will be about 100 Ω (meter resistance about 80 Ω), so that a small percentage of the additional collector current flows up the load resistor R_3 instead of through the meter. The error due to these three causes gives a meter reading which lies between 10 and 14% low for most transistors. Therefore, the value of R_1 should be reduced by, say, 12% of its value calculated from the simple theory. The simple theory requires 10μA to flow with 2·5 V across R_1.

i.e. $R_1 = 2{\cdot}5/10 = 0{\cdot}25\text{M}\Omega$

The corrected value is therefore given by $88/100 \times 0{\cdot}25\ \text{M}\Omega = 220\ \text{k}\Omega$. This is a preferred value and a 1% tolerance, high-stability type should be used.

The error due to variation of β with collector current can only be estimated from published data on the transistor type under test. The error should be negligible for small amplifying types having a maximum collector current of 10 mA. In the case of transistors designed for class-B audio output stages or for switching, such as the OC72 and OC76, the maximum value of β occurs at about 4 mA collector current, and the value of β measured on this test set may be 10 or 20% below the maximum.

Supplies.—The supply voltages required for testing a p-n-p transistor are:

Collector load supply	$= -6$ V
Meter supply	$= -2.5$ V
Emitter supply	$= 0$V

The corresponding voltages for an n-p-n transistor are:—

$$\left.\begin{matrix} +6\text{ V} \\ +2{\cdot}5\text{ V} \\ 0\text{ V} \end{matrix}\right\} \text{which may be expressed as} \left\{\begin{matrix} -\ 0\text{ V} \\ -\ 3{\cdot}5\text{ V} \\ -\ 6\text{ V} \end{matrix}\right.$$

Therefore, to be able to test both p-n-p and n-p-n transistors, it is necessary to be able to change over the polarity of the supply to the collector load and the emitter, and to adjust the meter supply between, say, −2.1 and −3.9 V. The extra range of adjustment allows for battery voltage deterioration and the setting up procedure for eliminating meter errors described above. The meter supply may be obtained from a low-resistance (100 Ω) potentiometer passing 60 mA, or from an emitter follower having a total circuit drain of about 5 mA. For the same low output impedance of about 25 Ω, the latter system has the obvious advantage of very much lower current drain.

The basic circuit is given in Fig. 3. The base potential of transistor X2 is controlled by the CALIBRATE potentiometer RV_2. The emitter potential of X2 remains a small fraction of a volt more positive than the base for tens of milliamperes change in emitter current. The emitter of X2 is therefore a low impedance source, and is ideal for supplying the meter. With the circuit values shown, the emitter output impedance is about 25 Ω.

S2 is a reversing switch. Since the meter supply current flows in opposite directions for p-n-p and n-p-n transistors, a reversing switch must also be provided for the meter.

Complete Test Set.—Fig. 4 shows the circuit diagram of the test set, which incorporates the circuits of Figs. 1, 2 and 3, with additional switching.

S2 is a 4-pole change-over switch whose position is selected for p-n-p or n-p-n transistors. S1 is a combined on/off and function selector switch. It was considered that the set would be less likely to be left on after use if the on/off switch was combined in this way. The functions of the switch positions are as follows:—

Position 1: Battery off.
Position 2: Meter supply voltage can be set up by RV_2 (marked CAL. or CALIBRATE).
Position 3: Circuit of Fig. 1 is set up, and I_{cbo} can be read from the meter.
Position 4: Circuit of Fig. 2 (with S1 open) is set up, and RV_1 (marked BAL. or BALANCE) is adjusted for zero meter reading.
Position 5: An additional 10 μA is injected into the base of the transistor being tested and the value of β can be read directly from the meter.

Where it is intended to operate the test set from a $4\frac{1}{2}$-V battery, the value of R_3 should be reduced to 2.2 kΩ. β will now be measured in the collector

current range 0.9 to 1·9mA if the meter supply voltage is still fixed at 2.5 (i.e. 2V across R_3).

Materials and Construction.— The test set was built on the underside of the lid of a box 9in × 4in × 2in as shown in the photographs. The layout may be varied to suit the size and shape of box used. If the set is likely to be standing idle for long periods it is best to use an external battery, since a burst cell in the same compartment as electronic equipment may cause considerable damage.

The function selector switch S1 is a 4-pole 5-way Yaxley switch. The wiper of S1a must be double width, so that when it is in position 5, number 4 contact is still made. The wiper of S1c should preferably be non-shorting when changing switch positions. The p-n-p/n-p-n selector switch S2 may either be two adjacent double-pole change-over toggle switches, or a Yaxley switch. If the latter, the wipers must be non-shorting, to avoid damaging the battery when changing from p-n-p to n-p-n. Alternatively, a three-position Yaxley switch may be used with a dummy middle position (in which the battery will still be on).

The meter may be a small robust ex-Government meter calibrated 0 to 1 mA. It is so easy mentally to sub-divide the scale into 100 parts, that it is barely worth marking it specially to read β.

An OC76 has been chosen for X2 because at the time of writing it is one of the most suitable transistors on the market, and is also reasonably priced. An OC72 is equally suitable if one is available, but any small transistor (other than a sub-miniature type) whose β is greater than 30 will be satisfactory.

R_1 and R_4 should be 1% tolerance high-stability carbon resistors. Selected 5% or 10% tolerance resistors may be used instead, but the accuracy of the set may be affected as the resistors age. All the remaining resistors are ¼-watt, 10% tolerance.

5-amp terminal blocks are used to bring in the battery supply and for connecting the transistor under test. The physical connections to emitter, base and collector are the same, whether a p-n-p or n-p-n transistor is being tested. The battery used is type

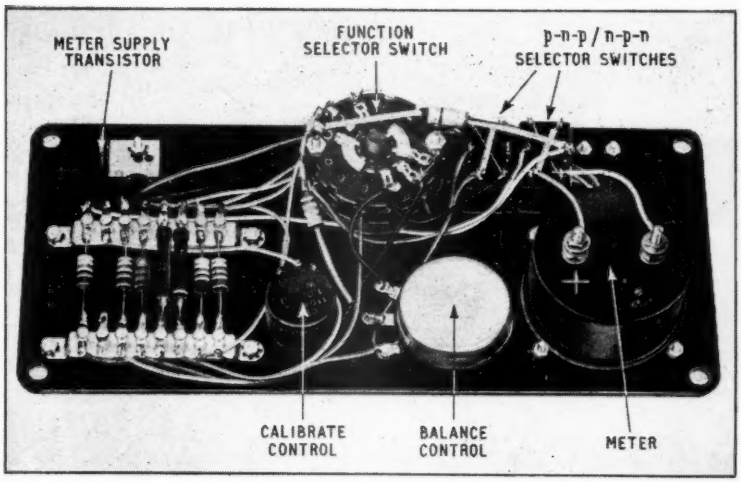

Layout of components on underside of panel.

Fig. 4. Circuit diagram of test set. All resistors ¼ watt, 10% unless otherwise marked.

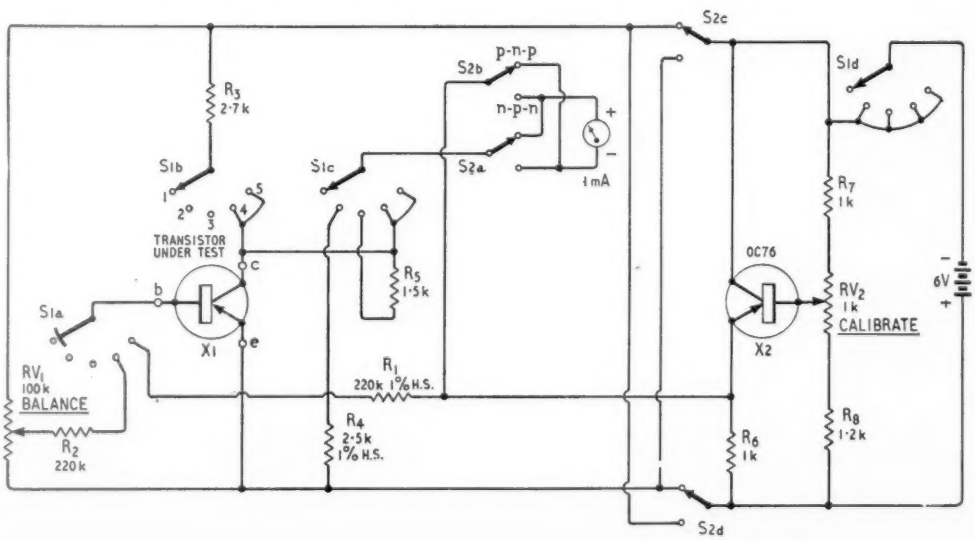

L15 Drydex hand-lamp battery or equivalent.

Operation of Test Set.—Connect the battery with the correct polarity to the test set. Incorrect connection will not damage the test set, but will be made obvious by the negative reading on the meter when the function selector switch is turned to CALIBRATE.

Set the polarity switches to p-n-p or n-p-n as required. Incorrect setting will not damage the transistor under test, but the current measured will be the emitter leakage current I_{ebo}, which is usually very much less than I_{cbo}. In addition, it is unlikely that the meter will be able to be set to zero when the function selector switch is turned to BALANCE.

Insert the transistor to be tested into its socket. Changing over emitter and collector connections will not damage the transistor, but due to the very low value of β when the transistor is operated in this connection, it is unlikely that the meter will be able to be brought to zero.

Turn the function selector switch to CALIBRATE, and adjust the CALIBRATE potentiometer RV_2 for full scale deflection on the meter.

Turn the function selector switch to I_{cbo}, and read off the value. For most transistors at room temperature it will lie between 10 and 400 μA. If the meter goes off scale, short together the emitter and base leads. If the meter reading falls to a very low value, the transistor is a satisfactory amplifying device, but care should be taken only to use it in circuits incorporating a high degree of d.c. stabilization of the transistor working point. If the meter remains off scale, the collector-base junction has been damaged and the transistor is useless.

Turn the BALANCE control fully anti-clockwise to avoid damaging the meter and the transistor at the next stage of testing. Turn the function selector switch to BALANCE, and adjust the meter to zero with the BALANCE control RV_1.

Turn the function selector switch to β, and read off the value of β on the meter (f.s.d. corresponds to $\beta = 100$).

Turn the function selector switch back to OFF, and remove the transistor under test.

Results.—A V10/30 and an OC72 had their β values measured both on this test set, and on an a.c. test rig. In the latter case, a 1-μA, 1,000-c/s current was injected into the base of the transistor under test, and the voltage across a 330-Ω resistor in the collector circuit was measured to obtain the a.c. collector current. The measurement was made with the d.c. conditions as close as possible to those in the test set, i.e. $V_{ce} = -2.5$ V, $I_c = -1.5$ mA. The estimated maximum error of the value of β measured by the a.c. method is 4%.

TABLE I

Transistor	Measured value of β	
	D.C. Test Set	A.C. Test Set
V10/30 ...	45	43
OC72 ...	72	70

The values of β obtained by the two methods are given in Table 1.

The agreement between the two methods is considered to be quite satisfactory, especially as the primary purpose of the d.c. test set is to check transistors rather than to make accurate measurements of their characteristics.

To test the sensitivity of the test set to battery voltage changes, several transistors were tested using a $4\frac{1}{2}$-V battery, and the values of β compared with those obtained with a 6-V battery. It was found that the former values were less than 5% low for small transistors, and less than 10% low for low-power transistors. This lowering of the measured value of β is caused by the lowering of the actual value of β due to the fall of the initial value of collector current from 1.3 mA to 0.75 mA.

Conclusions.—The test set described in this report will measure the collector leakage current and current amplification factor of transistors with up to 200 mW collector dissipation with sufficient accuracy to determine their suitability for a particular circuit. It can be constructed quite cheaply, is simple and virtually foolproof in use, and has proved its worth over the last eighteen months.

SHORT-WAVE CONDITIONS

Prediction for August

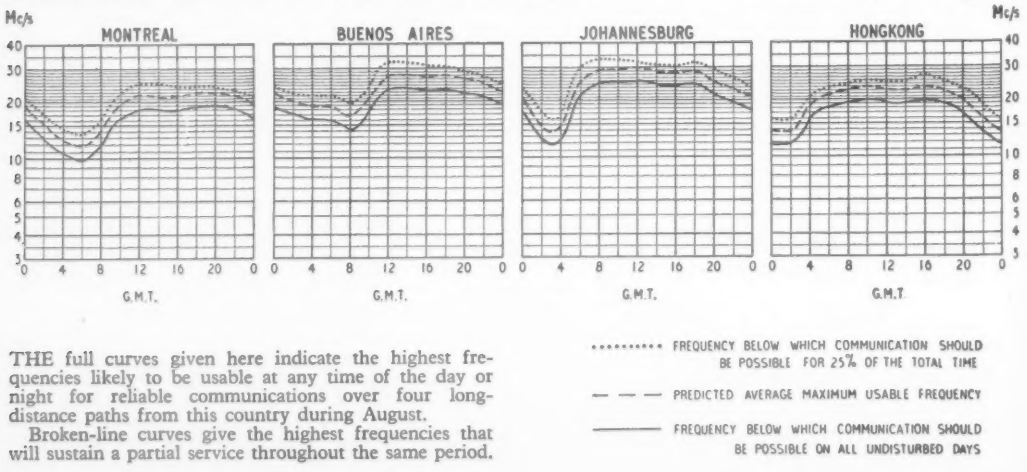

THE full curves given here indicate the highest frequencies likely to be usable at any time of the day or night for reliable communications over four long-distance paths from this country during August.

Broken-line curves give the highest frequencies that will sustain a partial service throughout the same period.

..... FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE FOR 25% OF THE TOTAL TIME

— — — PREDICTED AVERAGE MAXIMUM USABLE FREQUENCY

——— FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS

Doppler Effect in Radio and Radar

2.—Practical Applications

By N. M. RUST

THE determination of velocity by Doppler effect has been in the news recently as a result of its use by the traffic police in Britain, America and on the Continent for detecting violations of the speed limits. In this application the direction of motion is self-evident, so no special means of directional discrimination, as discussed last month, is required.

Another topical application in which the direction of motion is self-evident is the measurement of the velocities of artificial satellites of the earth. The author is not aware of any published information on this, but it is presumed that coherent pulse methods would be used. This means that the radar pulses, instead of being "self-oscillating," are derived from, or locked to, a drive of very stable frequency. The oscillations in each transmitted pulse are thus coherent with this drive, and the received pulses form a group of oscillations that can be made to beat with the drive oscillations, forming a Doppler note when the target is moving. If the Doppler and pulse repetition frequencies are integrally related, interference effects take place that result in "blind spots" at the corresponding radial velocities.

Range information can be obtained with c.w. Doppler radar by several different methods. The most obvious way would seem to be to combine Doppler indication with f.m. radar. D. C. G. Luck describes a use of this in "Frequency Modulated Radar" (McGraw-Hill, 1949). A triangular frequency sweep cycle is employed, and use is made of the fact that the Doppler shift raises the f.m. beat frequency on one stroke of the triangular frequency sweep, say the upward, and lowers it on the other, say the downward, or vice-versa according to the direction of motion. The principle is illustrated in Fig. 1. This method was actually used in apparatus developed for the American air force in the war as a bomb-release device. It was set up in accordance with the speed and height of the aircraft, and was claimed to be effective in securing a high percentage of hits.

Another method* is applied with a sawtooth frequency modulation sweep. In principle this is very similar to a coherent pulse system. A small section of the beat note is examined with a short gating pulse recurring at the sawtooth repetition frequency. Stationary targets produce steady signals, whilst moving targets give an output that is amplitude modulated at the Doppler note frequency.

Fig. 2 illustrates this method: (a) shows successive sawtooth frequency sweeps, and the position of a short gating pulse which occurs at exactly the same part of the sawtooth sweep on every stroke; (b), (c) and (d) show what happens stroke by stroke, to a very much larger scale. At (b), for fixed targets, exactly the same part of the beat note cycle is intercepted each time, and there is no output component within the range of the Doppler frequency filters used. At (c), owing to approach motion there is a progressive advance in phase of the beat note part intercepted by the gating pulse and there is consequently an a.c. output acceptable to the Doppler filter. The filtered output is shown at (e) by the full line. At (d) is shown a similar stroke-by-stroke phase shift for a receding target: the gating pulse sees a progressively retarded beat note phase. The filtered Doppler output is now of opposite phase, as shown by the dotted line in (e).

The range is defined by the beat note frequency. As the beat note will in practice be much higher in frequency than the Doppler note, the Doppler

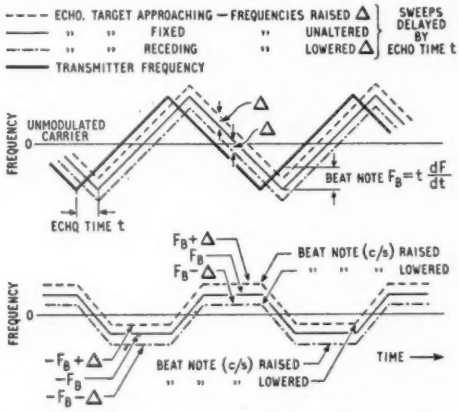

Fig. 1. Principles of a system combining Doppler indication with f.m. radar for range measurement. Above is the triangular frequency sweep and below is the variation of beat note on the same time scale.

shift of beat note is not sufficient to affect the accuracy of the range display. Range can therefore be displayed in the manner normal for frequency modulated radar. Analysis of the Doppler note defines the target velocity. This method produces "blind spots" when the Doppler note is a multiple of the frequency modulation repetition frequency, in the same way as a coherent pulse system does in relation to the pulse repetition frequency.

Amongst other methods which might be mentioned, two are of special interest as illustrating general principles that may find useful application. The first may be described as the two-frequency method. Going back to the illustration used in last month's article on general principles, the phase indicator can record radial distance in half wavelengths. If it is impracticable or inconvenient to count the number of turns representing half wavelengths, there is no means of determining the radial motion if it is over one half wavelength. Furthermore, even if the distance moved radially could be recorded in this way, in most cases the initial conditions would remain unknown, and hence the absolute range cannot be defined.

* British Patent 660,631.

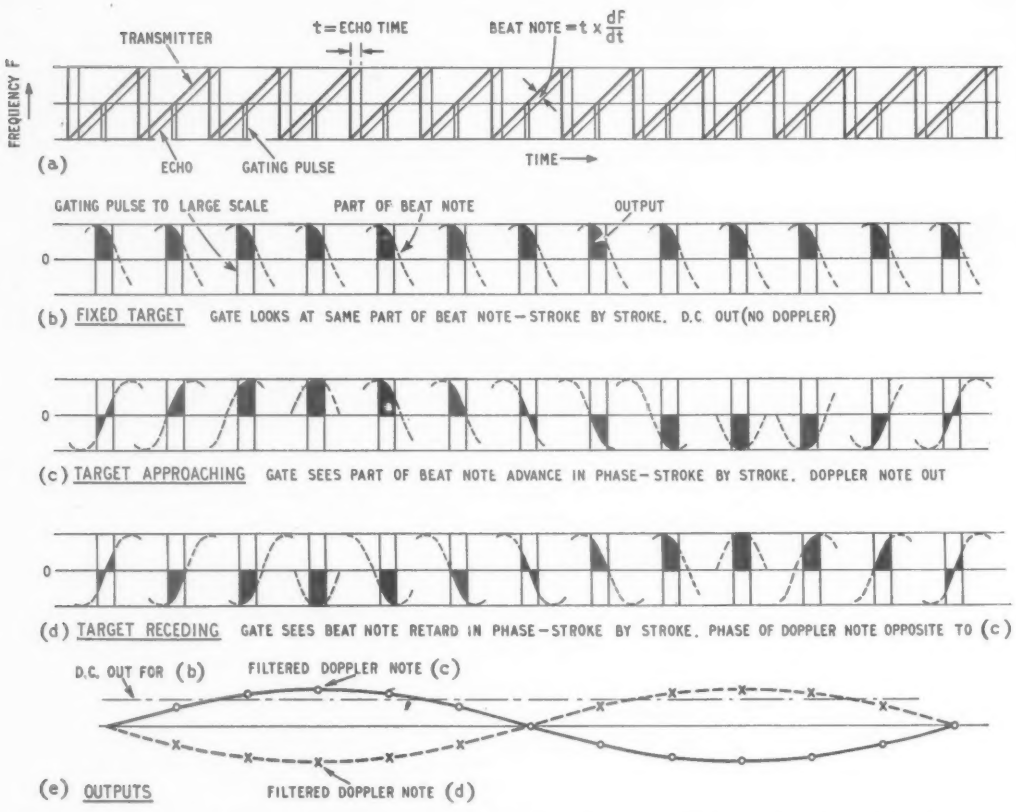
TRANSMITTER
t = ECHO TIME
BEAT NOTE = t x dF/dt
FREQUENCY F
(a)
ECHO
GATING PULSE
TIME
GATING PULSE TO LARGE SCALE
PART OF BEAT NOTE
OUTPUT
0
(b) FIXED TARGET GATE LOOKS AT SAME PART OF BEAT NOTE—STROKE BY STROKE. D.C. OUT (NO DOPPLER)
(c) TARGET APPROACHING GATE SEES PART OF BEAT NOTE ADVANCE IN PHASE—STROKE BY STROKE. DOPPLER NOTE OUT
(d) TARGET RECEDING GATE SEES BEAT NOTE RETARD IN PHASE—STROKE BY STROKE. PHASE OF DOPPLER NOTE OPPOSITE TO (c)
D.C. OUT FOR (b)
FILTERED DOPPLER NOTE (c)
(e) OUTPUTS
FILTERED DOPPLER NOTE (d)

Fig. 2. Another system for range measurement combining Doppler with frequency modulation. Diagrams (a), (b), (c), (d) and (e) are explained in the text.

Both these objections can be overcome by radiating a second, slightly different frequency. As the relationship betwen Doppler phase and range is linear for all transmitted frequencies, it is apparent that the differences of phase between the Doppler notes from a double frequency source must also be linear with respect to range. Fig. 3 illustrates this. Now if frequencies are chosen so that this difference of phase just reaches one complete phase cycle at a given radial distance of the target, we can make radial measurements within this range by extracting the Doppler note for each frequency separately and then measuring the phase difference between these Doppler notes. The range is then proportional to the phase difference.

There is a very simple numerical relation which gives the correct range scale factor. The fraction of a cycle difference in phase between the Doppler notes directly represents the fraction of one half-wave radial distance moved, for the wavelength corresponding to the frequency difference between the transmitted frequencies. Thus if we wish to measure ranges up to 15km without ambiguity, we must make the frequency differences correspond to a wavelength of 30km. The frequency difference must then be 10kc/s, and the phase meter will read to a scale of one turn equals 15km radial distance.

The other method was originally proposed by the late E. H. Armstrong, and was tried experimentally for long-range radar. He adapted his f.m. radar station at Alpine, New Jersey, for the purpose. It has subsequently been developed in this country by Marconi's*. This method of range determination goes back to Newton, but was used by him in the opposite sense to determine the velocity of sound. It is related that in a college quadrangle at Cambridge he clapped his hands at a steady rate which he adjusted until he could not hear the return echo from the quadrangle wall, as it synchronized with the direct clap sound. The time interval between the hand claps was thus made equal to the time taken for the clap to reach the wall and return. As the distance from the wall was known, the speed of sound was directly calculated. If he had known the speed of sound he could equally well have calculated his distance from the wall.

Armstrong's experiment was carried out by frequency modulating his transmitter, sinusoidally, with an oscillation whose frequency he could control. Moving targets then gave a clear, uninterrupted Doppler note (corresponding to the radial target velocity and the wavelength radiated) when the modulation frequency was adjusted so that the radar return arrived exactly one modulation period later than the transmitted cycle. The range was then equal to half of the wavelength corresponding to the modu-

* British Patent 620,568.

Right:—Fig. 3. Doppler range measurement using two frequencies, f_1 and f_2. This graph shows that the phase difference between the Doppler notes ($T_2 - T_1$) is also linear with respect to range.

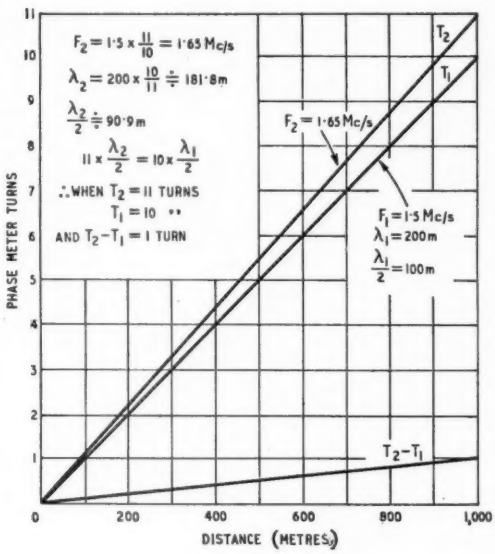

lation frequency. The Doppler note determined the target radial velocity in the normal manner.

Fig. 4 shows, in principle, how Armstrong carried out his experiment. To avoid difficulties due to the transmitter blotting out the echo signal, only alternate frequency-modulated cycles were transmitted, although the drive circuit carried on without interruption. Adjustments of modulation frequency were made until the echo signal from a transmitted cycle just fell on top of the next non-radiated drive cycle. When correctly synchronized, as the diagram shows, the Doppler note is steady. When not correctly synchronized the beat note is wobbled, and the response from the Doppler analyser is therefore greatly reduced.

An interesting point about this method is that, so long as each frequency modulation cycle is made the same as the preceding one (whatever modulation waveform is used), the Doppler note is exactly the

Below:—Fig. 4. E. H. Armstrong's radar system involving Doppler indication. A block schematic of the transmitting and receiving equipment is shown above, with the frequency modulation sweep and change of Doppler notes below.

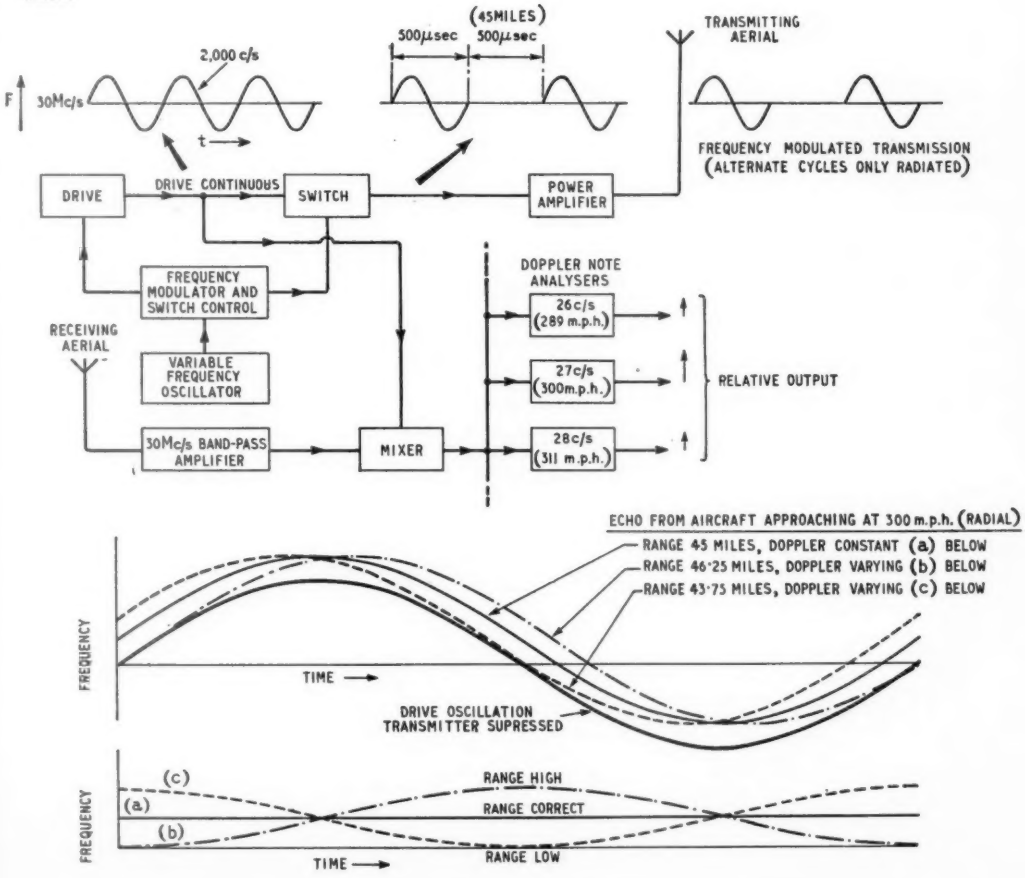

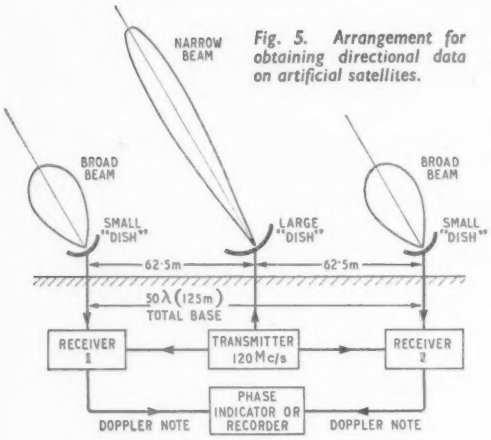

Fig. 5. Arrangement for obtaining directional data on artificial satellites.

same as if the carrier had not been frequency modulated, if the repetition frequency is correctly synchronized. Any alteration from synchrony tends to break up the Doppler note. The sensitivity to the break-up effect is dependent principally upon the frequency deviation of the modulation. As a result of this the range selectivity can be controlled by varying the deviation.

A very simple, single-target radar system can be devised, in which, when a Doppler response is heard, the frequency is modulated with a small deviation cycle (at first). After the approximate range has been found (by increasing the modulation frequency from the value representing the maximum range until the Doppler note is uninterrupted), the deviation is increased to measure the range more precisely. Finally, with the full deviation available, a setting will be obtained in which a very slight alteration of frequency to one side or the other will obliterate the Doppler note. The main practical difficulty in the use of this principle is to adapt it to multi-target use. Velocity and range resolution have to be performed simultaneously, and the design of a practical method of displaying the information clearly becomes difficult.

A principle that can be employed for the very precise discrimination of direction is that the instant-by-instant phase of the Doppler beat note is determined by the instant-by-instant relative phase of the transmitted and received oscillations. This enables the phase comparison of two Doppler notes, originating from the same transmitter and received at points separated in space, to be used as a very convenient means of determining the corresponding high frequency phases. This provides very precise directional information when the receiving points are many wavelengths apart.

By the use of u.h.f. or microwaves very high discrimination can be obtained with quite short bases, and when necessary ambiguities can be resolved by the use of auxiliary shorter bases. Moreover, the results obtained have an advantage over the ordinary multi-lobe interferometry technique as applied, for example, with the Cambridge interferometric aerial for tracking the "sputniks." This advantage lies in that not only does the phase comparison define the position of the lobe maxima and nulls (by noting the in-phase and anti-phase positions), but also the exact position in any part of a lobe may be determined by the measurement of relative phase at intermediate points.

The possible application of this principle to provide accurate data for the determination of satellite orbits is interesting enough to warrant an illustration. Fig. 5 shows an arrangement that could be used, and in Fig. 6 the track of a satellite is plotted in relation to the lines that indicate the relationship of phase of the Doppler notes. Fig. 5 shows a big "dish" for the transmitter (radiating 120 Mc/s c.w.). Smaller "dishes," giving relatively broad beams in order to facilitate tracking, are used at the spaced receivers. The transmitter oscillation is fed to the receiving points, and the Doppler note obtained by beating it with the signals is fed back from both receivers to

(*Continued on page 377*)

Fig. 6. Track of a satellite plotted in relation to lines indicating phase relationship of Doppler notes.

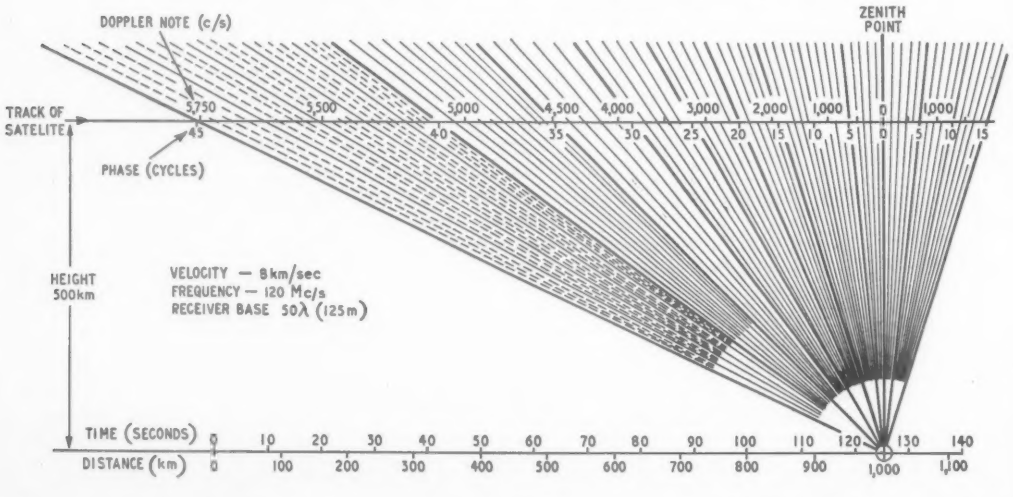

"BELLING-LEE" MINIATURE UNITORS

WITH 8 OR 12 CONTACTS

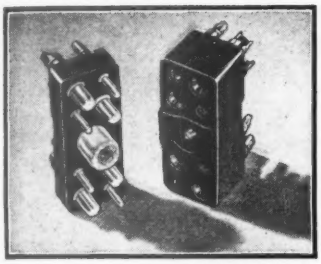

L.1387/P L.1387/S

Moisture — and tracking - resistant nylon-filled phenolic material is used for body mouldings. Pins are of gold-plated* or silver-plated brass. Sockets of high grade beryllium copper, slotted to ensure good contact with pin.

Each assembly has a shaped centre pin which polarizes the plug on engagement, and the back of this pin carries an 8BA stud for mounting the Unitor on chassis or panel.

Various pin combinations and arrangements are possible within the same chassis cut-out, to give a highly flexible method of obtaining an individual connection for each group of interconnections.

** As distinct from gold flash*

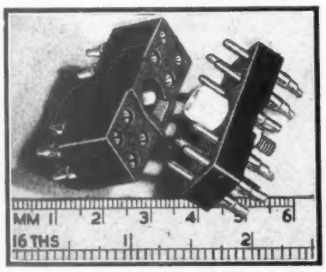

L.1388/P L.1388/S

L.1387/P. PLUG, with four small and four large pins.

L.1387/S. SOCKET FOR L.1387/P.

L.1388/P. PLUG, 8-pole (8 small pins)

L.1388/S. SOCKET FOR L.1388/P.

L.1389/P. PLUG, 12-pole (12 small pins)

L.1389/S. SOCKET FOR L.1389/P.

These miniature Unitors and other new developments are fully described in the Supplement (No. P490/H) to our General Catalogue: copies are available on request.

BELLING & LEE LTD
GREAT CAMBRIDGE ROAD, ENFIELD, MIDDX. ENGLAND
Telephone: Enfield 3322 Telegrams: Radiobel, Enfield

"BELLING-LEE" NOTES

Recently our research unit was called in to improve reception at a site famed for a poor picture, but where cost was not a limiting factor. The best picture was being received from a transmitter 84 miles away, but it was too noisy to be of entertainment value. The site was slightly lower than the average altitude for the district, but the nearest higher ground was at least two miles away, and should not have been unduly troublesome. The house or mansion was a large one and it was possible to get an aerial at least 65ft. above ground level, in fact an aerial was in position.

We started by measuring the field strength of the signal on the higher ground in front of and behind the site and felt that these should be enough to work with. The aerial already in position was not a " Belling-Lee " one but was a broadside six erected in such a manner as to bring discredit to the riggers employers, and to the manufacturers of the aerial. Granted, it was a temporary installation but it was badly executed. Being a very large house, it necessitated a long cable run, but ordinary feeder had been used, whereas low-loss air-spaced was the only feeder to use in the circumstances. The aerial was so fixed that it swayed considerably in very little breeze, and only for fractions of a second could it have been pointing in the direction of the transmitter. By far the worst feature of the installation was the choice of exact site, which was over a part of the roof covered with lead sheeting. At long ranges the dipole likes to " see " mother earth below it, and certainly loaths to see earthy material like lead roofs. Other suitable chimneys were available without lead below and one was used.

A " Belling-Lee " double nine was erected to the satisfaction of the customer. Incidentally, the new aerial was supplied through the dealer who originally did the job. " Belling-Lee " do not supply goods direct to the public, but are always very glad to hear from them. The " Belling-Lee " double nine is the most sensitive and efficient band III aerial on the market at the time of going to press with these notes.

We would like to emphasise that careless installation does, in the long run, a tremendous amount of harm to television. There is no excuse for shoddy workmanship. Enough has been written to enable aerials to be correctly installed. In the case described here, granted, it was a " no mans land," neither B.B.C. nor I.T.A. claimed to get a picture into the area, but a good picture was there as a reward for a little trouble. There are many cases where the customer could not afford the kind of aerial that was necessary, and certainly not the cost of specialist services from London, but there are still people who are prepared to pay for service of this kind. The programmes may not be required for the entertainment of the owner, but could be the means of bringing him the staff he needs to run his home situated as it may be, off the beaten track.

BURNHOPE AERIAL for Tyne Tees Television

This illustration is to remind readers that work really is proceeding in connection with TV for the North East. This is the aerial that will be used at Burnhope with the pilot transmitter now at Chillerton Down. The main I. of W. transmitter is expected to be on the air about August 1st when the pilot transmitter will be released. It will have to be taken to the new site adjusted to channel 8, and a certain amount of maintenance carried out before the transmitter will be ready for service towards the middle of September.

It is no secret to say that the erection of the main Burnhope mast is progressing so well, that the pilot aerial will be secured to the side of the main mast at about 400ft. level. High power tests are expected to commence mid-December and programmes early in the New Year.

Advertisement of
BELLING & LEE LTD.
Great Cambridge Rd., Enfield, Middx.
Written 17th June, 1958

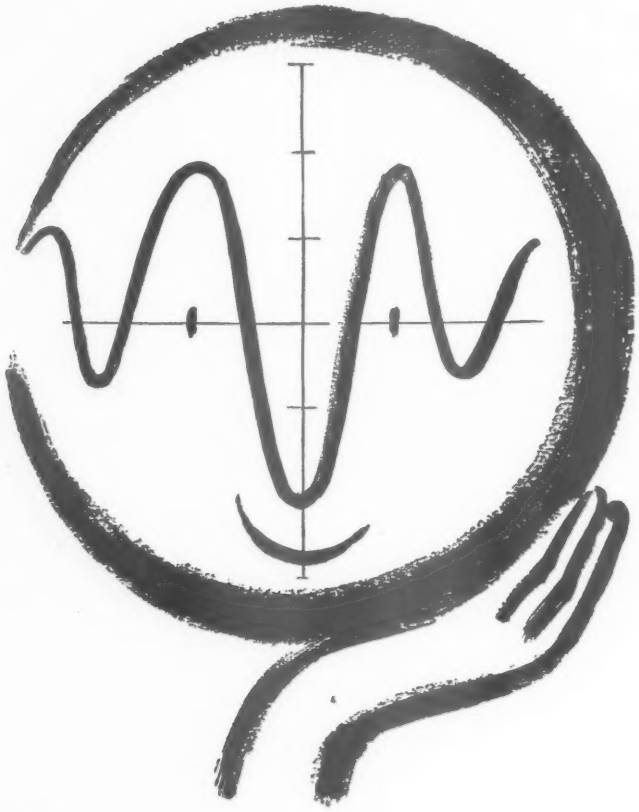

Thinking about an oscillograph?

If you are experienced in the design of high quality instruments, our Technical Director would be glad to hear from you.

The choice of the *correct* instrument can be a difficult one. Before selecting, we invite you to apply for technical details of our range of oscillographs which include low-frequency types for Industrial, Medical and Research purposes; wide-band instruments for high-frequency and pulse work; kit-type oscillographs and a range of special single-purpose instruments.
Published specifications are free of ambiguities and equivocation and are *rigidly* maintained: this is your safeguard against disappointment in the behaviour of your chosen instrument.
The Technical Advisory Service will be glad to help you with your selection.

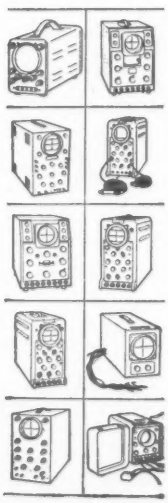

Write for information to:—

COSSOR INSTRUMENTS LIMITED

The Instrument Company of the Cossor Group

COSSOR HOUSE, P.O. BOX 64. HIGHBURY GROVE, N.5. ENGLAND
Phone: CANonbury 1234 (33 lines). Grams: COSSOR NORPHONE, LONDON. Codes: BENTLEY'S SECOND. Cables: COSSOR, LONDON
TAS/CL.2

the centre of the base. The notes are then compared in phase, either by a Lissajous figure method using a c.r.t. display, or preferably by a Decometer* type of phasemeter. With the arrangement shown, and a satellite flying at 8km/sec at a height of 500km, one complete cycle of phase change between the Doppler notes takes just over a second when the phase is changing at the fastest rate, so that such an arrangement should be practicable. It would be of advantage to record and count the beats of the interacting Doppler notes on a tape recorder, with auxiliary time markings.

The grid lines of Fig. 6 are really hyperbolæ of similar nature to those used for hyperbolic navigation systems. As the distance of the track from the base is very big compared with the base, the hyperbolæ have, for all practical purposes, merged into straight joining at the centre of the base. This is illustrated in Fig. 7, which shows the slope of the grid lines near the base to a very big scale compared with Fig. 6. In Fig. 6 the Doppler notes for a straight line track of constant height are shown above the track. The phase difference between the two notes is marked cycle by cycle under the track line, starting from the zenith point as a reference. It will be seen that in moving from a distance of 1,000km to the zenith point 45 beat cycles are swept through. It would be quite practicable to record or note the quadrature points in these cycles up to about 500km from the zenith.

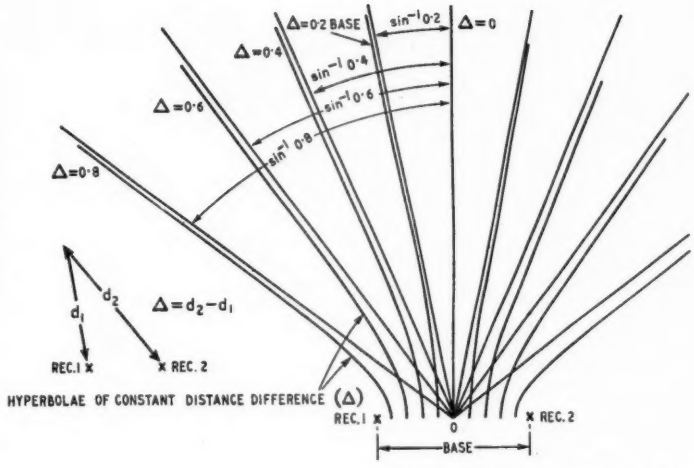

Fig. 7. The hyperbolæ of Fig. 6 shown in more detail at the base between the two receivers (Fig. 5).

Velocities can be determined by analysis of the beat notes before mixing. A complete set of data could thus be obtained for orbit calculation. This could easily be supplemented by very precise range data, obtained at definite intervals (using the Armstrong method) by frequency modulating the transmitter with a very accurately known frequency, using a relatively big frequency deviation, and noting the very sharply defined instants at which the Doppler note was pure. It should be added that, for the purposes of the illustration, the curvature of the earth was not taken into account although it would affect matters considerably in practice.

The *Wireless World* article by G. E. Beck referred to last month ably deals with an aeronautical application in which Doppler effect is used to determine the true ground speed and drift angle of an aircraft in flight. An interesting application of the method described might prove possible for marine navigation in coastal waters, by using underwater echo-sounding technique. Barium titanate transducers make it possible to produce the requisite sharp beams, but as relatively high frequencies for echo-sounding purposes would have to be used, the depth of range would be restricted. Certain extreme conditions which induce the production of layers of warm or cold water might cause errors at times due to ray bending effects.

Such a system would provide a ship's log that gave valuable data for coastal navigation. Besides true distance run, "ground" speed, drift velocity, true course, and drift angle could be indicated.

Towards the end of the last war the Germans used a secondary radar application of Doppler for the control of V2 missiles. A continuous wave signal was radiated from the ground control station. This was received by the missile in flight, doubled in frequency and re-radiated. These signals were then picked up by the ground station and mixed with a signal derived from the signal transmitted from the ground by frequency doubling. The Doppler note thus obtained, as a little consideration will show, was exactly the same as if the doubled frequency signal had been radiated and returned as an echo. The signal-to-noise ratio was very much better than for primary radar because of the detection and re-radiation at the missile, and allowed the Doppler beats to be counted without errors. As has been pointed out above, the "integrated Doppler" obtained in this way gives a direct method of measuring the radial distance traversed by the missile—this being directly proportional to the number of beats counted. Controls were set so that when the missile reached the required height in its take-off track, as defined by the number of beats counted, the missile was set off on its target course.

A German concern has exploited the same principle for harbour and river echo depth sounding surveys. In this case the transmitter and beat recorder are placed on the vessel carrying out the survey. The repeating station, which can be portable, is set up at a convenient place ashore. The distance-moved data is supplemented by d.f. bearing information obtained from the repeater signal. An accurate position fix of the vessel is thus obtained at each sounding position.

It seems obvious that this secondary radar method could be adopted for air navigation purposes. It has the advantage over most other navigational methods of giving a direct indication of velocity.

The writer gratefully appreciates permission given by the Marconi Company to refer to work carried out whilst in their employment.

* As used in the Decca Navigator system.

Servicing American Car Radios

By JACK DARR*

NATIONAL characteristics seem to differ widely in the way in which each ethnic group meets adversity: the British confront their daily difficulties with the impassive countenance and the world-renowned "stiff upper lip"; the French shrug them off with an insouciant "C'est la vie". The Yank, on the other hand, loves to "maximize" his troubles. "So you think *you* got troubles? Boy, lemme tell you what happened to *me* the other day. Why, I . . .", etc., etc. The following is a typical example of this national characteristic. In defence of countrymen and self, I must contend that one segment of the American radio maintenance industry really seems to have an undue amount of troubles. I refer, of course, to those inverted brethren who make what they laughingly refer to as a living servicing, or attempting to service, the modern automobile radios. A situation which was fairly bad in the beginning has rapidly grown worse: from the merely difficult, we have gotten to the improbable stage, and in some cases, to the entirely impossible! We are apparently faced with an organized conspiracy to render it as difficult as possible for us to do a service job! (The reference above is to an old saw of these parts, which reads, "only acrobats and auto-radio mechanics have to stand on their heads to make a living!")

A DIFFICULT JOB MADE IMPOSSIBLE!

As concisely as possible, the subject of this diatribe will be the difficulty we find in removing the radios from modern U.S. automobiles. Although the writer is comparatively inexperienced with respect to English cars, having encountered only the ubiquitous M.G., Triumph, Morris Minor, and a few others, mostly in the sports-car class, he is quite certain, in the good old American tradition, that no vehicle, British or any other, could possibly offer as much trouble as any American product, selected purely at random!

Auto-radios have been quite troublesome for years past. In the beginning, about 1928, they consisted of a large box (the radio) on the firewall, or, as you would say, the bulkhead, another large box (the speaker), a control head on the dash, connected with a variation of the Bowden shaft and, finally, another larger box, usually beneath the chassis or seat, which held the h.t. batteries! Later models developed into one box, including speaker, on the firewall, with the control head on the dash. After this came the single-unit models mounted in the instrument panel, containing all the parts. It was at this point in history that the devil reared his ugly head!

Cleverly designed to fit into the restricted space available, they were marvels of performance, sensitivity etc. (if you could just get the ignition noise out of the little beasts!), but they were becoming just a touch hard to get in and out. Now, the fiendish intent of the designers began to dawn upon an unsuspecting group of technicians: with forebodings, they glumly studied the future, appalled by what they could foresee! If they had been blessed with *accurate* foresight, only 10 short years ago, there would be *no* old-timers in the auto-radio business today! They would have resigned *en masse* and gone back to raising rhubarb! Not being endowed with the giftie, however, they remain, hopelessly striving to wrest a pittance from one of the most cantankerous and infuriating mechanical devices ever invented!

Allow me to state, at this point, that the target of my slings and arrows is absolutely *not* the gentry who design the sets themselves: the quarry I am baying is that group of unco-operative idiot-savants, in Detroit and elsewhere, who "design" the instrument panels and dashboards of the vehicles! Let us, as briefly as possible, set forth a few indisputable facts in the case: even the most ardent partisan of said fiends in human form cannot disput their veracity!

Question: Of the many gadgets festooning the instrument panel of the modern car, which one requires the most frequent service attention, many times more than all other parts together, during the life of the car?

Answer: The radio, of course.

Question: Of the above-mentioned units, which is the most difficult and inaccessible for servicing?

Answer: The radio, of course!

(Proof: the radio is installed firmly in the centre of the dash, as near the top as possible. Below it are the glove pocket, heater controls, ashtray and as many pieces of ductwork, levers, Bowden shafts, dash-braces (of heavy metal), brake levers, etc., as can be crammed into this restricted space. In a normal car, about 75% of these must be either removed completely or loosened and swung aside in order to allow very limited access to the radio.

Question: But surely these chaps have allowed enough room for the radio to be removed easily, after these impedimenta have been loosened up?

Answer (by many thousands of disgruntled U.S. servicemen): HAH!

Question: But isn't it possible to change tubes, vibrators, and so forth, by taking a lid off the case, without havin' to pull the whole bloomin' set?

Answer (by same group): You're joking of course.

(Author's note: Once upon a time, it was. This seems like the Golden Age of auto-radio, to those few survivors who still remain limber enough to participate in this contortionistic sport. We can still dimly remember those halcyon days when one could take the bottom lid off the radio and see inside the thing! Alas, those days are gone for ever.)

In addition to the facts outlined above, the design

* Ouachita Radio-TV Service, Mena, Arkansas.

of the vehicles themselves has contributed greatly to our difficulties. In common with other of Dame Fashion's caprices (The Sack!), car-styling has introduced new hazards, such as the "wrap around" windscreen, to complicate matters further. There not being sufficient room for this mobile picture-window on the front of the car, the designers have bent it around until the lower corners of it come out as a large triangular protrusion in the opening previously used for the front door! This is extremely convenient for the radio technician. As he arises from the prone position necessary to work with the radio, it is in exactly the right place to catch him a stunning crack on the forehead, resulting in a still further addling of what few brains he has left after struggling with the radio for an hour!

Instrument panels also partake of this trend; instead of being straight up and down, they now slant steeply back and inward toward the firewall: this was the only way they could find to reduce the limited space behind it!

In The Beginning.—We survivors of that bruised and battered group of old-timers have some remarkable memories. Of one 1937 model which had a factory-installed radio: we firmly believed that the set was installed and the car built around it, because we couldn't get it out! Of the 1938 model which required draining of the radiator and removal of the heater. Of another which had the radio and all instruments mounted on a panel, open on the front side, so that they were actually in the engine compartment! By the expedient of leaving off the splash-pans on the bottom of the engine, this resulted in the radio and other gear acquiring a thick coating of mud, oil, grease, and anything else thrown up by the front wheels. This was the first completely encapsulated radio; after a few months, it resembled a large cocoon. To service, the mud was chipped off with screwdrivers, wire-brushes, etc.; one irate technician is reported to have turned a high-pressure hose on it! Another car required removal of not only the hand-brake but the steering column, in order to install the radio. This one was also equipped with a mounting bolt fixed to the very top of the tuner chassis, easily accessible, if one happened to be an octopus; for those still using the standard human arms, with only one elbow, it was rather difficult. We remember the maker who mounted the set with the speaker plug on the back of the set, exactly 1⅛in from the firewall, 2in up from the bottom. The year after, this was further complicated by the addition of another speaker: a dual socket was used, with both plugs alike: it was simple to insert the plug into the wrong one. A two-piece set in which the units were connected with a very small, completely "ambiguous" plug, which could be inserted into the socket easily in any position. The socket in question was, of course, located on top of the radio chassis, entirely invisible from the serviceman's viewpoint. Incorrect insertion of this plug resulted not only in the radio refusing to work, but in blowing the fuse and burning up a small resistor, necessitating the removal of the radio once again!

It has long been a cherished belief of American servicemen that the car manufacturers maintained special, underground groups of designers, whose only function was the designing of dashboards. These groups are rated on an Inaccessibility Quotient: the more difficult the radio to remove, the higher the I.Q. for that year. They are paid on a bonus system, we believe. The higher I.Q. they can achieve, the more they make. Each year, they receive from the builders of the "custom-built" radios the dimensions of the sets for that year's cars. Their job is to work out a set of specifications which will enable the body department to accommodate the radio within the dashboard. The set must go into this space during manufacture, but leave no room for getting it out! This is achieved by adding heater-ducts, etc., to block access paths. Catastrophe was narrowly averted during one year's production by a large heavy brace which was added at the last moment, under the dash, to block up an overlooked opening through which the radio could have been removed easily!

Heads fell in bunches some years ago in Detroit. Some novice designers so far forgot themselves as to design a radio for a 1951 model which was mounted in its entirety on a metal panel, speaker and all. This panel was fixed to the dash by four small metal screws: it could be removed in less than *one minute* with a pocket screwdriver, while sitting upright in the front seat! Needless to say, the luckless wights responsible for this tragic blunder were summarily executed, after a whole year's production had slipped through. Next year, things were well in hand again: the same radio was used, in the same place, but now the dash was the usual immovable mass, and the radio had to be taken down, back and out, over heater controls, ashtrays, etc., in the usual manner. Two completely inaccessible fixing-bolts were added, at the very top of the chassis, in an effort to get revenge for the previous model.

Some of the very late models have I.Q.s which are simply wonderful. Some have reached the ideal of 100%, by adding air conditioners. These consist in the main of a great hulking cabinet, squatting on the floorboards between driver and passenger, in such a position as to render the radio (incidentally, all the dashboard instruments, too) entirely, absolutely inaccessible! To remove this unit, it is necessary to call in an air-conditioning mechanic, who closes valves, etc., and pumps down the unit, so that the blower cabinet may be disconnected and removed. One historic job recently performed by one of my associates resulted in a total of 11 hours, to replace a defunct r.f. amplifier valve. Removal of air-conditioner, 6 hours; replacement of valve, 6 minutes: Replacement of air-conditioner, 4.8 hours. Total charge, $1.80 for tube, $37.50 labour!

Transistorized Radios.—With the advent of transistorized radios in the early 1957 and 1958 cars, servicemen felt a faint surge of hope. "Surely," they said, wistfully, "they'll make the sets smaller, and they'll be easy to get out!" Alas, their hopes were dashed. Instead of the tiny chassis they had hoped for, the sets were built into cases of the same dimensions, to allow for a large impressive dial scale and a multitude of ornate knobs. Inside, of course, was a plenitude of unoccupied space, but outside they were the same as ever. In addition, there was a great lump protruding from the back of the set with several aluminium cooling fins, making the newer sets even more troublesome to remove! To add insult to injury, these sets did not use vibrators: thus, they were deprived of even this slight clue to possible troubles by listening to the tone of the vibrator!

Mountings.—Most sets use at least three-point suspension, some four or even more. In front the control knobs protrude through threaded bushes, which are held to the dash by large, thin nuts. In the early sets, these were flush with the dash, and could be removed with ease by an adjustable wrench, of the type known as a "Crescent," "Mexican Speed-Wrench," or knuckle-buster. When this was discovered, the designers took immediate steps to correct it. Now, these nuts are found at the bottom of very deep, special fittings, making it utterly impossible to remove them without a very special socket wrench indeed.

The back end of the set is held in place by one or two bolts, fixed to braces, etc. These used to screw into threaded holes in the cases. Now they fit special brackets and other added attractions. Extreme ingenuity is displayed by some designers in the location of these brackets. In one recent model it is necessary to remove the heater vent-control arm, and a large chrome-plated cover, 8 by 16 inches, the ashtray, and part of the glove pocket. This is an exquisite example of Applied Technological Stupidity: if the bracket on the set had been moved back exactly 1 *inch*, it would have been possible to fix them to the exposed lower edge of the dash! However, by placing these pitfalls in our path, the designer made it possible for us to spend an added 15 minutes each in removing and replacing the radio. The additional charge necessitated by this is deeply appreciated by our customer of course; so much so that he seeks out our competitor the next time the radio goes out! (Of course, he finds that competitor charges the same price as we do; hence, after making the rounds, he generally returns to the fold in a few months!)

Constructive Criticism Department.—Never having been one to grouse merely for the sake of hearing one's own teeth rattle, the writer is hereby prepared to offer a set of suggestions for the boffins in Detroit, which should, but probably will not, carry a great deal of weight in the design of next year's cars! He feels, having been engaged in this contortionistic trade since its inception in 1928, more or less qualified.

General Design.—Why not affix the sets in the dash so that they would be removable from the front? The only disadvantage to this would be that there would be four small screwheads visible. For some reasons, designers seem to have an utter horror of leaving screwheads showing. Just why, I've never been able to discover. I have conducted a survey among my customers on this point over a period of at least five years, and I have yet to hear a negative answer! Not one of them would object to screwheads! Front-mounting, for one thing, would remove the major obstacle to the installation of the popular air-conditioners. To secure the back of the sets, a large metal pin, about ½ to ¾in in diameter could be fixed to the back of the cabinet; this would slide into a mating hole in the firewall, possibly cushioned with a heavy rubber bush. Alternatively, the sets could be held by special braces for the dash, no more complicated than the ones already in use today: by forming them so that they provided grooves, the sets could be slid into place like desk-drawers, held by a few very small screws on the front.

Plugs and Sockets.—These must be mounted on the backs of the sets, to allow clearance at the sides for the set to be slid in and out. Interconnecting plugs should be slightly larger, and very definitely polarized, so that there is no possibility of inserting them into the socket wrongly.

Fuses.—These should be mounted in accessible places. Present cars use very short leads on very obstreperous holders, requiring a minimum of two hands to open. In their present location, only one hand can reach them—stalemate. Only Pontiac has taken cognizance of this problem, Allah bless them: they include the radio fuse in a fuse-panel, in an easily accessible location on the firewall! May their tribe increase!

So, in summation, although we, with other Americans, take an insular pride in Detroit's accomplishments, both in quantity and quality, we feel that there is still much, much room for improvement in this one particular section. For some reason, though, they have failed to seek our expert advice on the subject, and are muddling along in their own profitable way! We would dearly love to see an automobile radio that we could remove without feeling as if we had removed the largest speaker from a folded corner horn the hard way, by crawling up the bell after it! The very latest development of the 12-volt valves, for automobile radios, led one serviceman at a recent meeting to a bitter comment. After hearing the lecturer advise against attempting to test the low anode voltage valves, he said, "Well, that makes it complete. Now, after making radios we can't get out of the cars, they've finally made valves we can't test!"

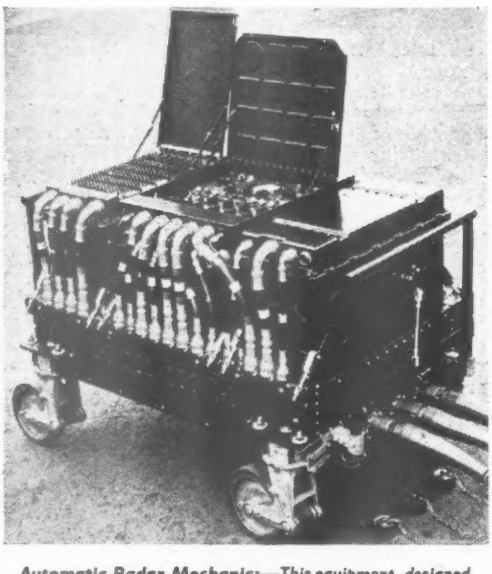

***Automatic Radar Mechanic:**—This equipment, designed and developed by the General Electric Co., tests automatically 300 inter-unit radar system voltages and waveforms at high speed. For instance, four d.c. measurements are made in one second, to an accuracy of ±0·2%, a "no go" signal appearing if the limits ±1% are exceeded. G.E.C. state that the machine is easily adapted to testing practically any equipment and it can be provided with recording facilities.*

EMI

"HIS MASTER'S VOICE"

MARCONIPHONE · COLUMBIA

Announce NEW PRACTICAL WAY OF LEARNING AT HOME

NEW — completely up-to-date methods of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teaching staff.

NEW — experimental outfits and lesson manuals are despatched on enrolment and remain the student's property. A tutor is allotted to each student for personal and individual tuition throughout the course.

Radio and television courses, with which specially prepared components are supplied, teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern Radio and T/V equipments.

If you are studying for an examination, wanting a new hobby or interest, commencing a career in industry or running your own full-time or part-time business, these practical courses are ideal and may be yours for moderate cost. Send off the coupon to-day for a free Brochure giving full details. There is no obligation whatsoever.

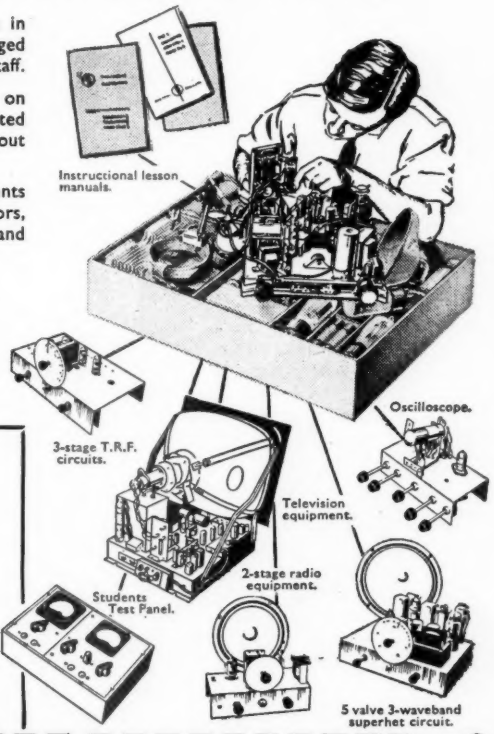

Courses with Equipment

RADIO • SHORT WAVE RADIO
TELEVISION • MECHANICS
CHEMISTRY • PHOTOGRAPHY
ELECTRICITY • CARPENTRY
ELECTRICAL WIRING
DRAUGHTSMANSHIP • ART etc.

E.M.I. Factories at Hayes, England

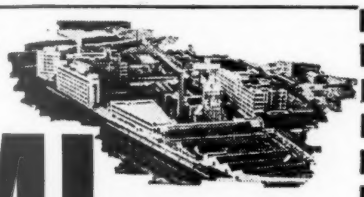

EMI INSTITUTES

Fill in for FREE BROCHURE
E.M.I. INSTITUTES, Dept. 127x, London, W.4.

FREE

Name .....
Address ..... Age ..... (If under 21)

BLOCK CAPS PLEASE

I am interested in the following subject(s) with/without equipment

AUG. '58 (We shall not worry you with personal visits) IC 107

The only Home Study College run by a World-wide industrial organisation

Marconi in Radar

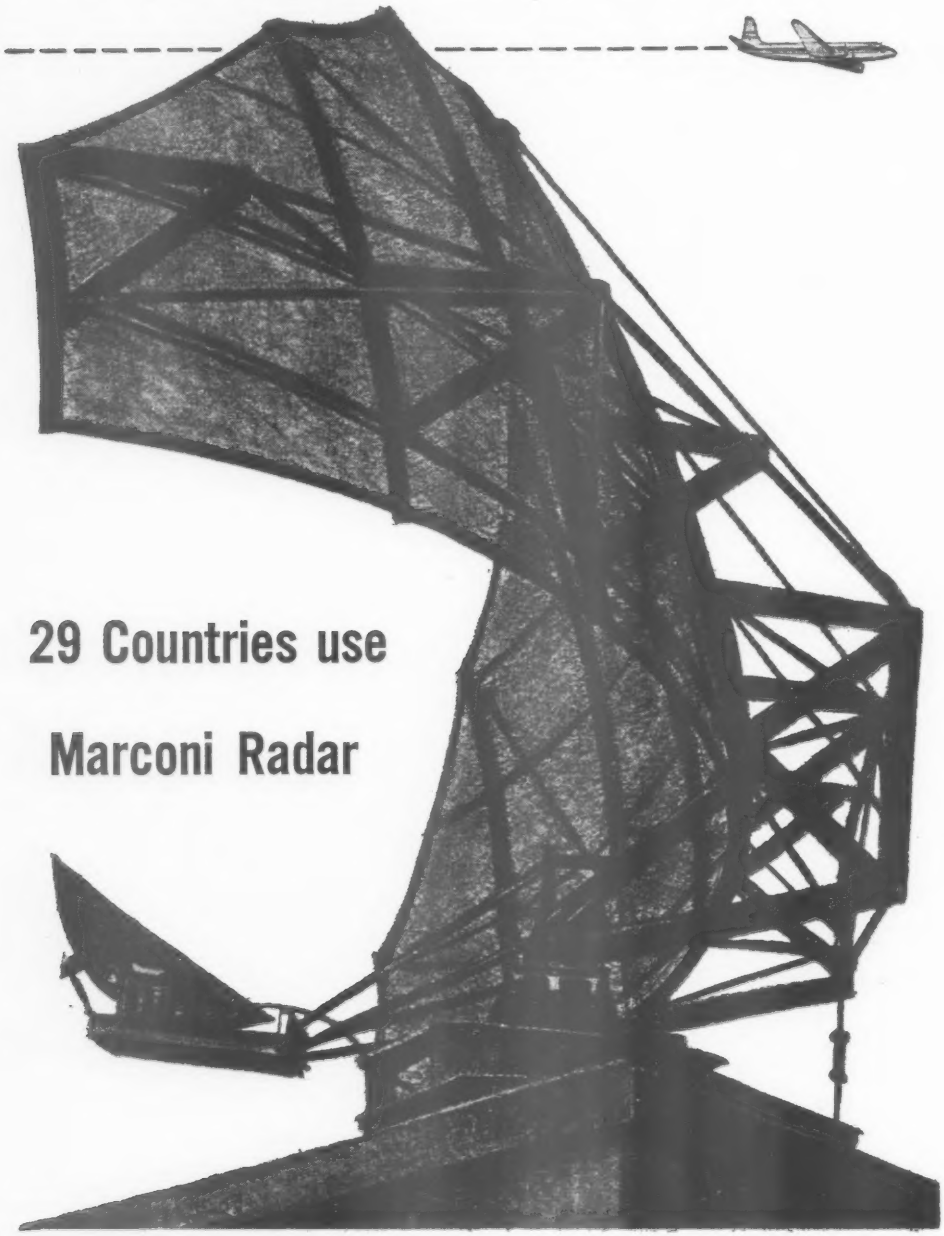

29 Countries use

Marconi Radar

MARCONI COMPLETE CIVIL AND MILITARY RADAR INSTALLATIONS

MARCONI'S WIRELESS TELEGRAPH COMPANY LIMITED, CHELMSFORD, ESSEX, ENGLAND

M.6.

Zener Diode Voltage Stabilizer

APPLICATION TO SMALL BATTERY MOTORS

By S. WELLDON*

THE advent of the transistor has stimulated interest in the use of miniature portable equipment for sound recording and reproduction. Incorporated in much of this equipment, for example in record-players and tape and wire recorders, are electric motors designed to be operated from small batteries. This type of motor is usually driven from a 4.5, 6, or 9V battery. The "dry" Leclanché cell, however, has neither a constant terminal voltage, nor a constant value of internal resistance, with life. A typical curve of the terminal p.d. of a 1.5-V cell is given in Fig. 1; this shows a sharp fall at the beginning of life, followed by a more gradual decline. In fact, it is often advisable to design apparatus on the assumption that the battery supplying the power will have a working voltage rather less than 1.5V per cell. A value of 1.35V per cell is often chosen, since the terminal p.d. of a cell having intermittent use tends to "level off" at this voltage.

*Research Laboratories of the General Electric Co. Ltd.

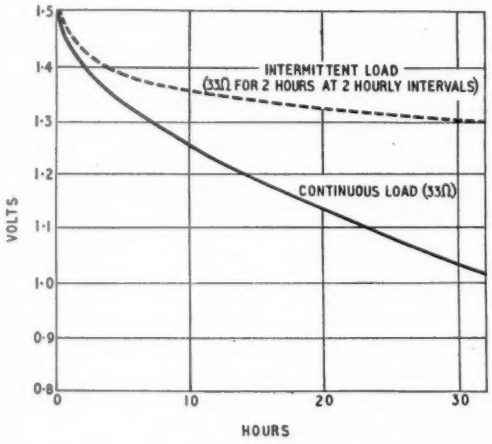

Fig. 1. Typical variation of terminal p.d. of a 1.5V dry Leclanché cell with life.

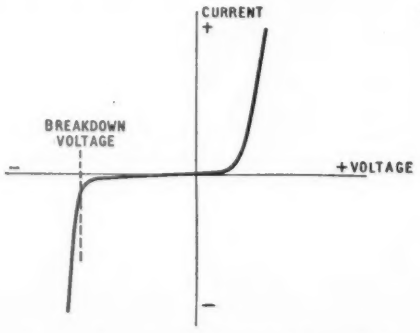

Fig. 2. Characteristic of a typical Zener diode.

The value of internal resistance is rather indeterminate. It increases with the age of the cell, and it also varies with the amount of current drawn. Also to be considered is the effect of polarization which will occur momentarily if the battery is required to deliver a relatively large current pulse.

Battery Motors.—The terminal voltage variations caused by the above effects may become embarrassing when a stable voltage is required to drive a recorder or record-player motor. Such a motor usually has a permanent-magnet field, and is provided with a centrifugal, friction-controlled governor. The regulating efficiency of the governor is generally made rather low to keep power losses low. In addition, the associated flywheel or capstan is often quite small, and may not have sufficient inertia to compensate adequately for short-term variations in battery voltage. The motor is similar to a shunt-wound motor in that a constant voltage rather than a constant current source is required, and a fairly large surge current is drawn when starting. If the motor *is* operated from a constant current source, it will take an appreciable time to reach its final speed and in some cases may not start at all.

If an attempt is made to run the motor in conjunction with a class-B audio amplifier, and a common battery of small capacity is used, the fluctuations in supply voltage caused by current changes in the output stage can be sufficient to vary the motor speed. Even where separate batteries are employed, the initial high voltage may overload the governor and raise the speed of the motor. The usual solution here is to place a variable resistor in series with the armature winding; but the disadvantage of this system is the need for fairly constant adjustment of the resistor during the life of the battery. There is also a tendency to over-run the motor, because the voltage applied to it is not known exactly.

Zener Diode Stabilizer.—A method of providing a stabilized voltage makes use of the breakdown characteristic of a Zener diode. This is a p-n junction diode, made from silicon and having a well-defined reverse breakdown voltage. By careful choice and control of the materials used in its manufacture, the voltage at which breakdown occurs can be decided within fairly close limits, and this voltage is stable with life. Currently available Zener diodes have breakdown potentials ranging from 3 to 15V. The shape of the characteristic is indicated in Fig. 2.

After the breakdown voltage has been exceeded, the characteristic has a very steep slope. The voltage/current gradient of this part of the characteristic is known as the Zener slope resistance R_z, and, for optimum regulation, should be as small as possible. It is not a constant, however, and there can be significant variations from one device to another. The slope resistance also depends to a great extent on the diode breakdown voltage and tends to a minimum value of 5Ω or less at breakdown voltages between 6 and 7V. At the present time there appears to be no generally accepted method of accurately defining breakdown voltage for a particular diode. For convenience here we will assume it to be the voltage across the diode when the reverse current is 5mA, since this usually ensures that the beginning of the linear portion of the voltage/current characteristic has been reached.

A suitable stabilizing circuit is given in Fig. 3.

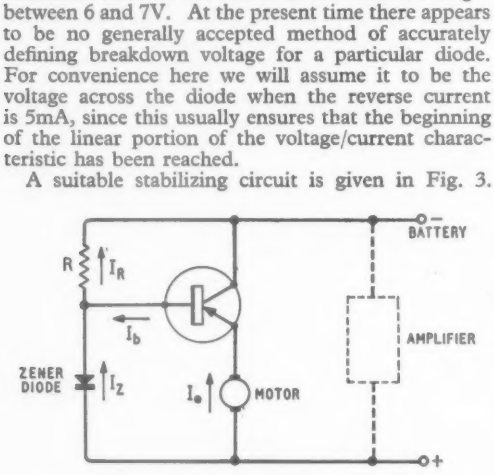

Fig. 3. Voltage stabilizing circuit using a Zener diode.

The load is placed in series with the emitter of a transistor in the common-collector arrangement; and the Zener diode is placed in the base circuit. A limiting resistor R in series with the diode across the supply is made greater than the Zener slope resistance. The diode should have a breakdown voltage slightly in excess of the voltage required for the load, to allow for the voltage drop across the base-emitter junction. The transistor serves to isolate the load from the diode, and must, of course, be capable of handling the required load current.

Numerical Example.—It is useful to examine the method of operation by considering a practical example. A miniature record-player and a transistor class-B push-pull audio-amplifier were to be operated from a small, common, battery. The record-player needs at least 4.5V at about 60mA, and the amplifier was intended to be operated from 6V. It was envisaged that four small unit cells could provide the power. An experimental EW77* diode having a breakdown voltage (as defined above) of 5V was selected.

It will be assumed that the Zener slope resistance is 20Ω, this being a typical value for a 5V diode. It will also be assumed that the slope resistance is linear beyond the breakdown voltage point indicated in Fig. 2.

Referring to Fig. 3, the minimum current through the diode should not be less than 5 mA, since the slope resistance increases appreciably at lower values of diode current. The maximum current in the diode is determined by the maximum dissipation allowed in the device. With an EW77 rating of 150mW for ambient temperatures of up to 40°C, the maximum current for a 5V diode will be 30mA. For reasons of power economy, however, it may be advisable to limit this current to a slightly lower value. If, for example, it is limited to 25mA, the diode current I_z can change by a maximum of 20mA, and with a (linear) slope resistance of 20Ω, this will cause the voltage across the diode to vary from 5 to 5.4V. The voltage drop across the base-emitter junction is about 300mV, so that the corresponding variation in motor voltage is from about 4.7 to 5.1V. This variation should be easily controllable by the motor governor.

The current I_b in the base of the transistor is equal to $I_e/\bar{\alpha}_{cb}$ where I_e is the emitter current and $\bar{\alpha}_{cb}$ the d.c. or large signal current gain of the transistor. Since the load is inductive and the current is commutated, the final value of I_e is not readily calculable. However, assuming it to be about 60mA, and using a transistor with a current gain of 30, I_b will be 2mA. The current I_R $(= I_b + I_z)$ in the limiting resistor R will therefore have a minimum value of 7mA, and a maximum value of 27mA.

The value of R required depends on both the Zener slope resistance and the supply voltage chosen. If the latter is 6V, the maximum p.d. across R will be $6 - 5.4 = 0.6$V, and therefore R will be $600/27 = 22\Omega$. The minimum voltage across R is equal to $22 \times 7\text{mA} \approx 150\text{mV}$, so that the minimum battery voltage required for the stabilizing action to occur is 5.15. In this case, operation from a 6-V supply would give a very short battery life, and it would be more economical to increase the supply to, say, 7.5V (e.g. five unit cells). The value of R should then be increased to 82Ω (to the nearest preferred value), and the minimum battery voltage becomes 5.57. If R is reduced to its limit to allow a maximum current of 30mA through the diode, the minimum battery voltage is lowered. However, since the initial current drain is higher, the life of the battery will tend to be reduced rather than extended.

If the 7.5-V supply is chosen and the same battery used for both stabilizer and amplifier, the latter must, of course, be capable of operating at the increased voltage. Such an arrangement, however, should present no difficulties.

The power dissipated in the transistor is $I_e \times (V_{battery} - V_{motor})$, so that its value will depend on the supply voltage and the load current. The former will vary during the life of the battery, and the latter will change with variations of torque. With a 7.5V supply, the power in the transistor with the motor running normally will be about 140mW, dropping to 50mW towards the end of the life of the battery. The transistor must have a higher dissipation rating than the former value, however, because of the high starting current, and it should be borne in mind that this would be a continuous rating if the motor were accidentally or deliberately prevented from rotating while switched on. For most of these surge conditions, the GET15 transistor is a suitable choice, since it has a dissipation rating of 250mW at ambient temperatures up to 40°C, increasing to 500mW if mounted on a 3in × 3in cooling fin. The peak emitter current for this transistor is 350mA. In practice it is unlikely that the motor will be left in a " seized up " condition for any length of time, and the starting pulse is not long enough to raise the junction temperature excessively.

Stabilizing Factor.—The amount of stabilization

*A more recent commercial near equivalent with a greater allowable dissipation is the 5.6V, 300mW SX56.

that can be achieved will depend mainly on the Zener slope resistance and the value of the limiting resistor. However, because of the many other variables involved, it is difficult to predict the degree of regulation exactly, though a simple description will give a useful indication.* Suppose in the above example, the battery and diode voltages stand at 7.5 and 5.4V respectively. The current through the limiting resistor ($R = 82\Omega$) is 25.6mA. Now if a reduction in supply voltage is sufficient to decrease the diode current by 1mA, the voltage across the diode will drop by 20mV, and this will in turn produce a drop of 20mV in the motor voltage. The current through R is then 24.6mA, and the p.d. across it is 2.02V. This gives a battery potential of 2.02 + 5.38 = 7.4V. There is, in fact, also a change in I_b, due to the change in I_e, but this is very small compared with the reduction in the current in the Zener diode. Thus a battery voltage variation of 100mV is required to produce a 20mV change in load voltage, giving a stabilizing factor of 0.2.

As mentioned earlier, the slope resistance increases at very low values of diode current. Thus, when the battery voltage falls below the minimum values given earlier, the stabilizing action becomes rapidly poorer, though it does not immediately cease.

Apart from the short-term voltage regulation afforded by the use of this circuit, there is also the advantage that no voltage adjustment whatever is required during the life of the battery. This is particularly useful where tape and wire recorders are concerned.

It is possible to obtain superior stabilization with more elaborate circuits, but the circuit given in Fig.3 is adequate for most small motors of the type described here. It is simple and compact, and reasonably economical in power consumption.

Thermal Stability.—The thermal stability of a Zener diode depends on several factors, including the value of the Zener voltage, and the operating current. The temperature coefficient tends to be negative at the lower ranges of breakdown voltage, and positive at the higher. With a typical 5V diode, the temperature coefficient is negative, and has a value between 0.01% and 0.02% per °C (i.e., between − 0.5mV and − 1mV per °C rise in ambient temperature). The transistor base-emitter voltage also varies with temperature, typically between − 2mV and − 2.5mV per °C. The variation in motor voltage with temperature is therefore typically equal to

− 0.5mV − (− 2mV) per °C = + 1.5mV per °C.

This is a small, and relatively long term, variation and as such is insignificant in this application.

*It can be shown that $\frac{\delta V_{in}}{\delta V_{out}} \approx 1 + \frac{R}{R_s} + \frac{(1-\alpha)R}{R_L}$ where R is the limiting resistor, R_s the Zener slope resistance, R_L the load resistance, and α the emitter-to-collector current gain of the transistor. The third term is very small compared with the first two, so that $\frac{\delta V_{in}}{\delta V_{out}} \approx 1 + \frac{R}{R_s}$ and the stabilising factor $\approx \frac{R_s}{R+R_s}$.

REFERENCES

Keller, J. W., "Regulated Transistor Power Supply Design," *Electronics*, Nov. 1956, p. 168.

Aspinall, D., "A Low-voltage Stabilizer," *Electronic Engineering*, Sept. 1957, p. 450.

Jones, D. D., and Hilbourne, R. A., "Transistor A.F. Amplifiers," p. 138 (Iliffe & Sons, Ltd.).

BOOKS RECEIVED

Design of a Linear Phase-shift Low-pass Filter by L. E. Weaver, B.Sc. B.B.C. Engineering Monograph No. 17 dealing with the choice of circuit and practical realization of a 3-Mc/s cut-off filter for removing noise from a television camera control unit. Supplementary note by R. D. A. Maurice, Ing Dr., A.M.I.E.E., on random fluctuation noise in image orthicon camera tubes. Pp. 23; Figs. 14. Price 5s. B.B.C. Publications, 35, Marylebone High Street, London, W.1.

The Use of Electronic Valves. British Standard Code of Practice CP 1005: Part 4: 1958. Section 9 gives additional recommendations on magnetrons relating to special characteristics, heater operation, h.t. supply, magnet design, stray field, cathode and output connections, installations, dangerous radiations, storage and transit. Section 10 deals with special quality valves, their ratings, choice of type and circuit, heater surges, effects of interface impedance growth, mounting and temperature considerations, handling and preventive maintenance. Pp. 20. Price 5s. British Standards Institution, 2, Park Street, London, W.1.

The Radio Amateur's Handbook, 1958 edition; by the headquarters staff of the American Radio Relay League. A recognized standard manual of amateur radio, it explains basic theory, design and construction of all types of amateur equipment and the latest developments in suppressed-carrier, single-sideband and teletype (teleprinter) techniques for amateur communications. Pp. 616 including 32 pp. of valve and semiconductor data with over 1,350 illustrations. Obtainable from the Modern Book Co., 19-23, Praed Street, London, W.C.2, or from the Radio Society of Great Britain, New Ruskin House, Little Russell Street, London, W.C.1; price 32s 6d (34s 3d by post).

Proceedings of the Third National Conference on Tube Techniques (New York, September, 1956). Selection of 29 papers on details of the design and manufacture of valves (principally receiving). Pp. 128; Figs. 149. Price $5.

Proceedings of the Transistor Reliability Symposium (New York, September, 1956). Selection of 19 papers dealing mainly with the performance of transistors in military applications. Pp. 128; Figs. 140. Price $5. Both the above are published by the New York University Press, Washington Square, New York, 3.

Practique Electronique by J. B. Oehmichen. Survey of transducers available for industrial measurement and control systems, basic circuit elements and their integration to form complete systems. Pp. 302; Figs. 162. Price 1,350 Fr. Editions Radio, 9, Rue Jacob, Paris, 6.

The Ionosphere by Karl Rawer. Survey of existing knowledge of the physics of the ionosphere, regular and irregular changes in its constitution and their influence on radio propagation. Translated from the German by Ludwig Katz. Pp. 202; Figs. 72. Price 42s. Crosby Lockwood & Son, Ltd., 26, Old Brompton Road, London, S.W.7.

Lauffeldröhren by Dr. Werner Kleen and Dr. Klaus Pöschl. Mathematical treatise (in German) on travelling wave tubes, with an extensive bibliography. Part II of "Einführung in die Mikrowellen-Elektronik." Pp. 192; Figs. 127. Price DM28. S. Hirzel Verlag, Birkenwaldstrasse 185, Stuttgart, N.

XUM

Divided Output Transformers

Use of Separate High- and Low-Frequency Units

By R. GUELKE*, Ph.D., M.I.E.E., F.Inst.P.

THE design of the output transformer for an audio-frequency amplifier of wide-frequency range presents a number of problems. The self-capacity of the primary winding can be high enough to interfere with the working of the transformer at high frequencies. Leakage inductance can also be troublesome at these frequencies, particularly if a considerable amount of negative feedback is to be applied.

It is therefore not surprising that suggestions have been made that the audio-frequency range should be divided into two regions and two transformers used, one for the high- and the other for the low-frequency region; similar to the well-known use of two loudspeakers. For example, P. W. Klipsch has described[1] a parallel dividing network for separating the two frequency ranges just prior to the output transformers, greater freedom from low-frequency distortion and its intermodulation products being claimed. A well-known manufacturer (Philips) has used two output stages driven by separate valves.

It is well known that thermionic valve amplifiers are capable of dealing with the entire audio-frequency range without difficulty. It would therefore appear to be unnecessary to divide the frequency range prior to the output valves.

In this paper a circuit is put forward in which the audio-frequency spectrum is divided into two sections prior to the output transformers, but subsequent to the output valves of the amplifier. The output from the secondaries of the transformers can be combined for purposes of overall feedback.

* Cape Town University.

Fig. 1. Theoretical frequency dividing circuit.

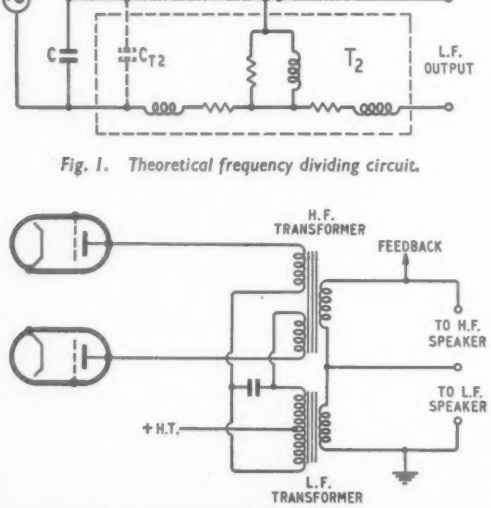

Fig. 2. Practical application of Fig. 1.

Circuit Details

Fig. 1 shows the principle of the circuit. A generator is followed by a simple dividing network consisting of an inductance L and a capacity C in series. This is followed by the equivalent circuits of the transformers, T_1 (high-frequency), and T_2 (low-frequency). The capacity C_{T2} represents the self-capacity of the winding of the low-frequency transformer. L and C can be calculated from the following formulæ:—

$$L = \frac{R}{2\pi f}, \quad C = \frac{1}{2\pi f R}$$

where R is the load resistance, and f the dividing frequency.

If it is possible to connect two transformers in series, the primary inductance of the high-frequency transformer could be used in place of the inductance L, and the self-capacity of the windings of the low-frequency transformer absorbed into the capacity C. Because the high-frequency transformer would have few turns and also be much smaller than the low-frequency transformer, the self-capacity of this transformer would not be important. The leakage inductance would also be comparatively small. For the low-frequency transformer leakage inductance and capacity would not be of any consequence, because at the higher frequencies where they become significant the high-frequency transformer would take over. This means that the low-frequency transformer need not be specially wound to reduce this self-capacity. Thus simpler (and cheaper) methods of winding can be used; and as these require less space, the size of the transformer is reduced.

In order to test the possibilities of this scheme an audio-frequency amplifier was constructed to the specification of D. T. N. Williamson[2] but with the output modified as shown in Fig. 2. It was found that this output stage gave the same frequency response and power output as a standard high-quality transformer if the following conditions were observed:—

1. Any transformer having a sufficiently high primary inductance could be used as the low-frequency transformer. Even standard mains transformers were found adequate using the h.t. windings as the primary and tappings on the mains or l.t. windings as the secondary.

2. The high-frequency transformer had to be

constructed of low-loss core material, and the primary inductance adjusted to a suitable value by means of an air gap.

For the high-frequency transformer Ferroxcube was found very suitable as a core material. A core having a cross-sectional area of about 1 sq cm and a "window" for the windings of about 2.5 sq cm was wound with a total of 2,400 turns on the primary (1,200 each side) to make a suitable transformer. This transformer was able to deliver 15 watts at frequencies above 2000 c/s. With a cross-over frequency of 1000 c/s and a suitable low-frequency transformer 15 watts could then be obtained over the full audio range.

The cost of the two transformers is considerably lower than that of a single high-quality transformer because the method of winding is not critical. Furthermore, the high-frequency transformer takes the place of an inductance in the dividing network. The frequency division is carried out at high impedance so that the condenser for the dividing network is smaller and less expensive than usual.

Care has to be taken to obtain the correct polarity for the addition of the two outputs in the feedback circuit. The two primary windings on the high-frequency transformer must also be well insulated because they are subjected to the full primary a.c. output voltage from the low-frequency transformer.

For an amplifier which is to be used with a frequency dividing network the use of two output transformers is both economical and satisfactory.

REFERENCES

[1] Klipsch, P. W. "Low-Distortion Crossover Network," *Electronics*, Vol. 21, No. 11, p. 98, Nov. 1948.

[2] Williamson, D. T. N. "Design for a High-Quality Amplifier," *Wireless World*, Vol. 53, Nos. 4 and 5, Pp. 118 and 161, April and May 1947.

Inexpensive Photographic Timer

Simple Compensation for Variations in Enlarger-Lamp Supply Voltage

By J. H. JOWETT, B.Sc. (Eng.)

AN excellent design for a precision photographic timer was given in *Wireless World* for February, 1956, by J. G. Thomason. Compensation was provided, through the use of Atmite discs, against the differing exposure periods required with variation of mains voltage, in this way improving the operational use of such a device for professional work.

In the circuit suggested below sufficient compensation is obtained for the average experimenter's purposes, and possibly also for some professional purposes. This is accomplished by the use of a single-valve assembly which may be quickly constructed within a very small space. Many readers will consider that the advantage of simplicity outweighs the more elaborate, if more accurate, arrangement of J. G. Thomason. No apologies are therefore offered for a further design.

The basic circuit used in the timer to be described is that of the "bootstrap" amplifier*, as shown in Fig. 1, a device which is commonly used for the generation of linear sawtooth waveforms. It consists of what is virtually a cathode follower, the anode being at h.t. potential and the cathode returned to earth through a resistor R_k. One end of a d.c. voltage source V is connected to the cathode, while the opposite pole is connected to the grid through a charging resistor R and charging capacitor C.

As this is a cathode follower, for valves of short grid base

$$V_k \simeq V_c$$

Then, the voltage across R is given by $(V+V_k-V_c)$, i.e., V approximately, independent of other potentials. Hence, as the voltage drop across R is V volts, the current through the resistor has a constant value of V/R amps.

This is the basis of the operation of the "bootstrap" circuit. The capacitor C is charged at a constant rate and the potential across it rises linearly with respect to time. As the output voltage and capacitor voltage are raised simultaneously, the two poles of the externally applied d.c. source, V, are both raised in potential together, as if by their own bootstraps. The time taken for C to charge to a given potential V_1 is given by the rate of charge multiplied by the value of final potential, or,

$$t = \frac{CR}{V}.V_1$$

If R were connected directly between grid and cathode, i.e., V made equal to zero in the above expression, from this theory C would only be charged within an infinite time. In practice, however, a small potential difference exists between grid and cathode, depending on the grid characteristic of the valve. Capacitor C would therefore be charged at a low rate from this voltage difference, and the cathode current would rise until limited by the valve.

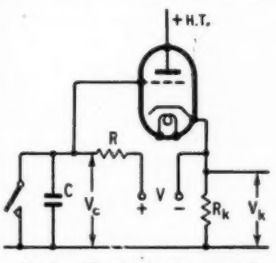

Fig. 1. The basic "bootstrap" circuit.

The full circuit of the practical design is shown in Fig. 2. It can be seen that this circuit differs from the standard bootstrap arrangement in that the anode supply is taken directly from the 240-V

* F. E. Terman, "Electronic & Radio Engineering", 4th edition p. 651

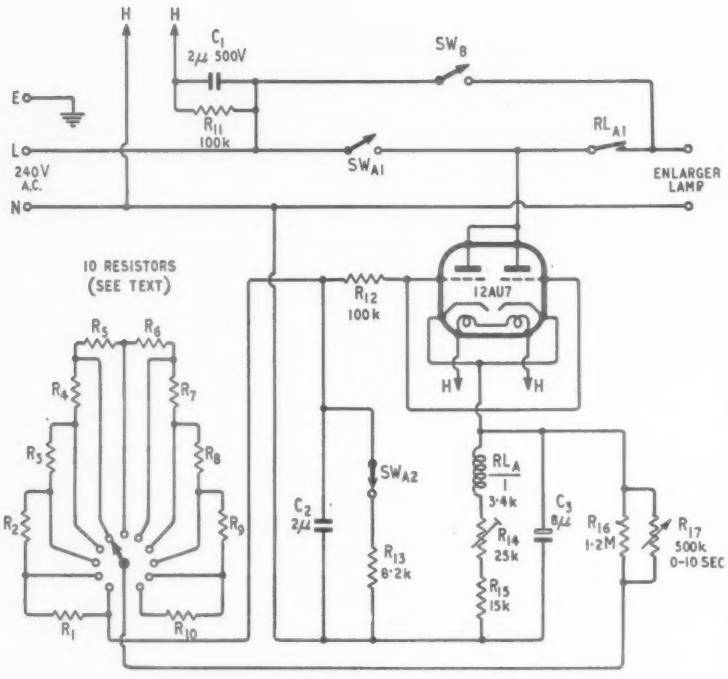

Fig. 2. Circuit of the complete timer.

a.c. mains. Not only does the valve operate as a bootstrap amplifier (with the charging resistor directly between grid and cathode), but it also acts as a rectifier with load $R_{14}+R_{15}$ and relay $\frac{RL_A}{1}$ and reservoir capacitance C_3. It will be appreciated that this dual function complicates considerably the previous arguments, and in fact makes a rigorous mathematical expression of the circuit conditions somewhat involved. The basic principles of operation will nevertheless be clear from the foregoing explanation.

In the initial condition, capacitor C_2 is short-circuited by one contact of SW_A, and the anode voltage is removed by means of the second contact. When this switch is operated, the cathode current rises quickly to a small value determined by the grid characteristic, in the region of 1mA for the valve used. It then begins to rise much more slowly, until, when a suitable value of cathode current is reached (in this case 3.5mA) the relay contacts open, concluding the timing period. Switch SW_A may be returned to its original position at any later time to reset the cycle of operations; thus a simple double-pole toggle switch is satisfactory for this application.

It was found that the circuit, as described above, was sensitive to mains voltage changes to an extent shown in the curve of Fig. 3. As the mains voltage rises or falls from the nominal, so the nominal timing period decreases or lengthens. On the same graph is plotted the theoretical curve showing the variation of timing period necessary to compensate for a fourth power law between enlarger lamp output and mains voltage, as suggested by J. G. Thomason.

These two curves show a fair measure of agreement over part of the range, indicating that a certain amount of mains voltage compensation would be obtained without further measures being necessary. As stated previously, a full mathematical analysis of this circuit is difficult and uncalled for in an article of this kind, so a simple qualitative test was carried out to verify the source of the variation of timing period.

The anode voltage was first held constant and the heater voltage varied; only small changes were noted. From 200 volts to 260 volts, the change in period due to heater variations was from 19 to 21 seconds, on the 20-second range. Thus the major variations occur, as was also verified, through the change in anode voltage. The effect of increased voltage at the anode is of course an increase in the rectified output at the cathode, and consequently greater voltages in general throughout the circuit. Capacitor C charges more rapidly and the point at which relay RL_A operates occurs in a shorter time interval. The law is not linear owing to the curvature of the valve characteristics, particularly at the lower voltages, and the variation of r_a with anode current.

To investigate the suitability of the time-voltage characteristics for photographic work, the following short experiment was carried out. First, a sheet of bromide paper was exposed to the enlarger for 10 seconds, timed by a stop-watch, with the values of mains voltage between 210V and 250V as marked in Fig. 4. The variation of density between successive strips of the paper is quite noticeable. In the second part of the experiment, the timer was set to the 10-second range and the strips were again

(Continued on page 387)

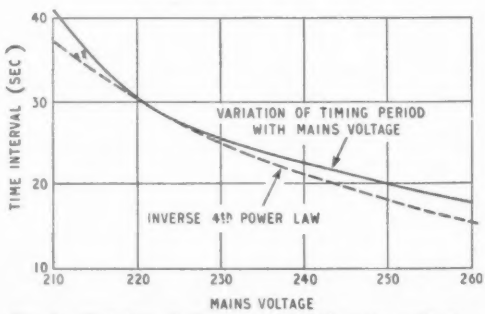

Fig. 3. Variation of timing period with mains voltage, compared with a theoretically desirable fourth power characteristic.

PRECISION OSCILLOSCOPES

from the E.M.I. range

✻ *with exclusive direct reading measurement system*

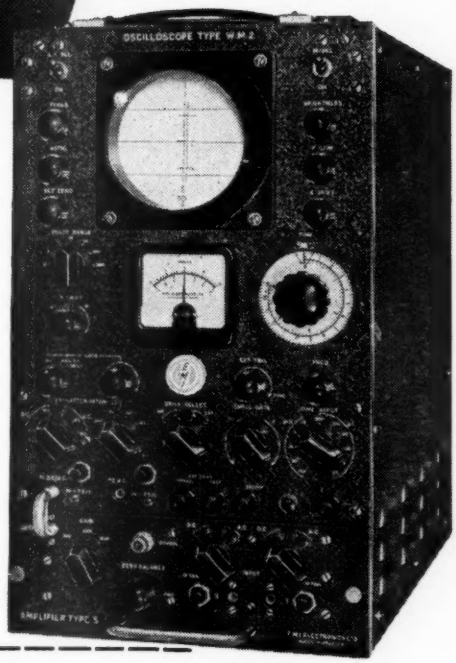

An outstanding and versatile wideband oscilloscope

Well suited to a variety of applications — such as production testing, single shot photography and design and maintenance work on radar, television and computers.

- ✻ Direct time and voltage measurement with 2% accuracy
- ✻ Differential inputs
- ✻ Built-in signal delay
- ✻ Bandwidth DC to 12 Mc/s
- ✻ Y sensitivity at full bandwidth 100 mV/cm
- ✻ Maximum Y sensitivity 3 mV/cm

TYPE WM2 Price £285

(Plug-in preamplifier £75)

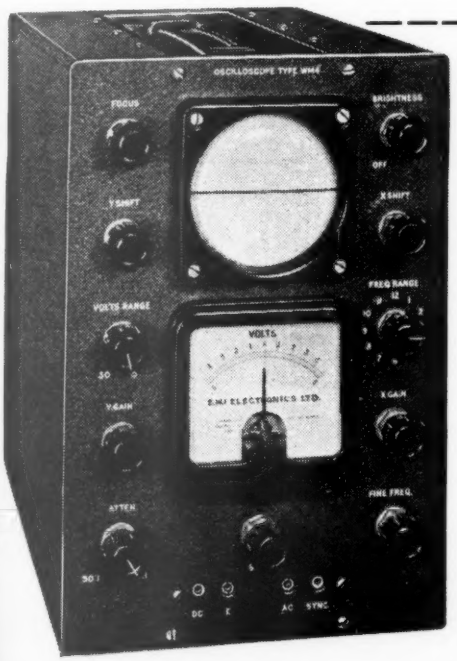

A remarkably compact oscilloscope

With direct reading measurement system. For testing and development work on radio, television and other electronic equipment. Dimensions 9½″ x 6½″ x 10½″. Weight 15½ lb.

- ✻ Accuracy : direct 2% via attenuator 5%
- ✻ Maximum frequency response DC — 10 Mc/s (—3 db): Sensitivity 4 V/cm
- ✻ Maximum Y Sensitivity 185 mV/cm at reduced bandwidth

TYPE WM4 Price £65

For further details of these instruments, telephone or write to:

E.M.I. ELECTRONICS LTD.

INSTRUMENT DIVISION · HAYES · MIDDLESEX

Tel : SOUthall 2468 Exts. 1071 and 655

EE 145

Triumph!

B.S.R. ARE THE FIRST WITH THE ONLY STEREO TURNOVER CRYSTAL CARTRIDGE IN THE WORLD

the revolutionary

Ful-Fi

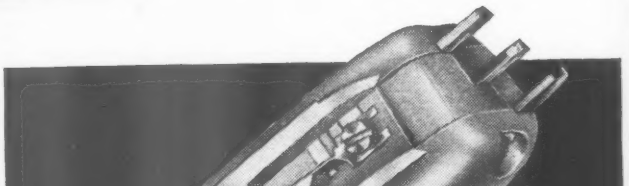

UNIVERSAL TURNOVER CRYSTAL CARTRIDGE

for stereophonic, microgroove and standard discs

This is the news everybody has been waiting for. Now—at last—a universal turnover crystal cartridge which plays stereo records with no more fuss or bother than for standard records.

No complicated plug-in heads which are so easily lost and damaged—just a simple turnover cartridge which plays stereophonics, all microgroove and 78 r.p.m. records. The sleek " Ful-Fi " lines and snap-fork housing facilitate easy servicing and cleaning.

The " Ful-Fi " universal turnover crystal cartridge is available *only* in the UA8 and UA12 ' Monarch ' record changers. Where stereophonic reproduction is contemplated, the only logical choice is a record player which has the ' Monarch ' UA8 or UA12 record changer incorporated with this revolutionary universal cartridge.

now, *more than ever,*

BSR

means business!

BIRMINGHAM SOUND REPRODUCERS LIMITED · OLD HILL · STAFFS.

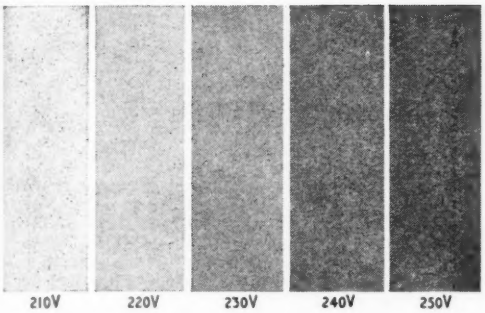

Fig. 4. Test exposures on normal paper at 10-volt increments of mains voltage. Constant exposure of 10 seconds on each voltage, timed by a stop-watch.

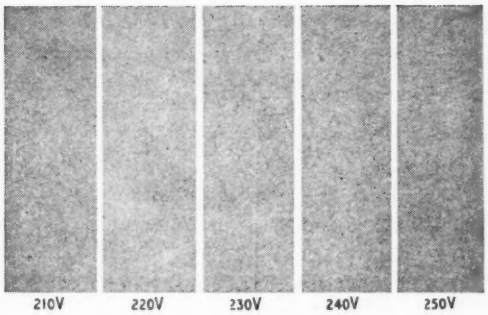

Fig. 5. Test exposures again at 10-volt mains voltage increments as in Fig. 4, but using the timer, on the 10-second range, throughout.

exposed at the 10-volt intervals, as in the first part, between 210 and 250 volts. The results of this second test are shown in Fig. 5, and it can now be seen that the difference in densities between the 210-V and 250-V strips is much reduced—only of approximately the same order as between 10-volt intervals without the use of the timer. This variation in exposure is negligible under mains voltage fluctuations likely to be encountered in practice.

The aim of the circuit design has been simplicity, and the only complication introduced is the necessity for a multiplicity of timing period ranges. These are selected by means of an 11-way Yaxley switch which introduces the correct values of charging resistors. In series with these resistors is a variable resistor, which is calibrated up to 10 seconds, allowing a wide variety of times to be selected up to a maximum of 200 seconds. The values of the range resistors are given in the accompanying table, but no tolerances are given as their accuracy will depend upon the requirements of the user and also upon the exact value of C_2. The last-mentioned should be a good quality paper capacitor of about 200 volts working, with high insulation resistance; if the insulation is poor, it will be found that operation of the circuit is affected on the higher ranges. The operating period of the timer with all controls at minimum is about 0.2 second.

TABLE OF RANGE RESISTORS

Resistor No.	R1	R2	R3	R4	R5	R6	R7	R8	R9	R10
Time Interval Seconds ...	10	20	30	40	50	60	80	100	150	200
Nearest Prefd. Resistor Value	330kΩ	330kΩ	330kΩ	330kΩ	330kΩ	330kΩ	560kΩ	750kΩ	1.5MΩ	1.0MΩ

The selection of valve type 12AU7 (CV491) was made first because the heater is suitable for operation from the mains supply through a 2-μF capacitor, allowing further simplification and space reduction. Secondly, the permissible heater-to-cathode potential is 200 volts, which gives an ample margin of protection. Resistor R_{11} in parallel with C_1 allows the last-mentioned to discharge on withdrawal of the mains plug, for safety reasons.

As previously mentioned, relay $\frac{RL_A}{1}$ operates with a current of 3.5 mA, and if any other relay is used it is recommended that a more sensitive type be selected and that it be shunted if necessary to operate at this current. If this cannot be arranged, the circuit values given will have to be altered to provide the correct ranges, and some experiment will undoubtedly be called for. The relay contacts should have voltage and current ratings adequate for the enlarger lamp; if not, a back-up relay must be used, possibly energized from the mains via a half-wave rectifier. The switch SW_B by-passes the unit when adjustments of the enlarger are desired for an indefinite time period. If a metal chassis or case is used it should be isolated from the rest of the circuit and preferably earthed.

The variable resistor R_{14} was provided to allow initial setting-up in spite of circuit component tolerances. The 20-second range is recommended as a suitable range for this purpose, as adequate accuracy is obtainable without the expenditure of too much time. When the adjustment has been made on this range the other ranges will be found to be in their correct proportions and no further adjustments should be necessary, except for the calibration of the variable resistor controlling the 0-10 second range.

Consistent and accurate results are obtainable through the use of this timer, even for exposure periods of 0.5 second. Such short exposures are, of course, impracticable by manual methods, and a consequent speeding up of operations is therefore possible when a number of prints are being made. Certainly the use of the timer transforms the most tedious part of an otherwise interesting hobby.

Thanks are due to M. A. Newman, B.Sc., for helpful suggestions in preparing this article.

"Electrical Who's Who."—The 1958-59 edition of this valuable directory of people in the electrical and radio industry, research organizations, the Services and Government Departments, includes about 8,000 brief biographies. These entries are supplemented by an index in which the names are classified under companies and organizations. Compiled by *Electrical Review* it is obtainable from Dorset House, Stamford Street, London, S.E.1, price 27s 6d (postage 1s 6d).

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents

Direct-coupled Transistor Amplifier

MR. OWENS is right in stressing the severe temperature dependence of the circuit shown in Fig. 2 of my article (May issue). It is unfortunate that this figure should have been labelled as a "practical amplifier" since it was mainly intended to show the conditions of measurement when plotting Figs. 3 and 4. For example, the 1 MΩ resistor in series with the first base was included solely to provide a constant-current drive to the amplifier and the 1 MΩ resistor in the feedback loop was selected to give the correct class-A operating condition, and only incidentally gives a small measure of d.c. stabilization.

The practical amplifier which was modified to yield Fig. 2 did in fact have a battery in the feedback loop, allowing the d.c. feedback resistor to be reduced to 100 kΩ, and thus giving a useful measure of a.c. and d.c. feedback whilst maintaining an absolutely flat low-frequency response. Unfortunately this arrangement did not allow the adjustments of feedback ratio necessary to yield the curves of Fig. 4.

Where a floating battery is an embarrassment, Mr. Owens' Fig. A provides a convenient alternative. His Figs. B and C are interesting in their own right, but depart somewhat from the principle of direct-coupling *without bias adjustment or loss of available current swing.*

Hounslow. D. A. G. TAIT.

[In Fig. B which accompanied Mr. Owens' letter in last month's issue the connection between the top of R_3 and the right-hand end of R_8 should be deleted.—ED.]

Variable Transformer Windings

MR. H. E. STYLES' transformer (p.262, June issue) requires considerable arithmetical effort on the part of the user. This could be greatly reduced if secondaries of 1, 2, 4, 7, 10, 20, 40, 70 and 100 volts were used, giving virtually the same maximum output (254V) and requiring the addition of only one switch.

Ewell, Surrey. J. S. SINGLETON.

The Author Replies

THE modified series of windings proposed by Mr. Singleton certainly offers the advantage of somewhat simplified addition although, in practice, my original series is not found to offer any particularly difficult arithmetic.

Apart from necessitating the use of an additional switch for voltages up to a maximum of 254, the modified series proposed by Mr. Singleton has other drawbacks which might militate against its use in some circumstances.

In the first place, with my own series any particular voltage can only be obtained by one particular combination of windings whereas the modified series permits alternative combinations of windings to be employed for quite a number of values of voltage. Thus, for example, a voltage of 14 can be achieved either by a combination of the 10 and 4 volt windings or by a combination of the 1, 2, 4, and 7 volt windings. The same voltage can only be attained in one way with the original series i.e. by a combination of the 2, 4, and 8 volt windings.

Bearing in mind the inevitable minor differences which must arise between differently disposed transformer windings, it is likely that two combinations giving the same nominal output voltages will in practice yield slightly different actual values. For many purposes this may not matter but in some circumstances such possibility of inconsistency might be undesirable.

A second minor objection arises from the same cause. Starting at the low-voltage end, the original series of windings provides a steady progression of voltages by working successive switches in a regular manner (left-hand columns below).

With the modified series, however, one is apt to run into repetition, as indicated in the right-hand columns.

Switch Combination	*Output Voltage*	*Switch Combination*	*Output Voltage*
1	1	1	1
2	2	2	2
1, 2	3	1, 2	3
4	4	4	4
1, 4	5	1, 4	5
2, 4	6	2, 4	6
1, 2, 4	7	1,2, 4	7
8	8	7	7
1, 8	9	1, 7	8
2, 8	10	2, 7	9
1, 2, 8	11	1, 2, 7	10
4, 8	12	4, 7	11
1, 4, 8	13	1, 4, 7	12
2, 4, 8	14	2, 4, 7	13
1, 4, 8	15	1, 2, 4, 7	14
16	16	10	10
		1, 10	11
and so on		2, 10	12
		1, 2, 10	13
		4, 10	14
		1, 4, 10	15
		2, 4, 10	16

Finally, if auto-connection is employed to achieve higher maximum voltage, the modified series necessitates a primary tapping at 200 volts and gives a maximum of 454 volts compared to the value of 511 volts obtainable with the original series.

It is thus evident that a choice between the two must largely depend upon the precise purposes for which it is desired to use the transformer and, in particular, the importance attached to the somewhat greater ease of adding together numbers from the second series.

Pinner, Middlesex. H. E. STYLES.

"TV DX"

SOME observations on the reception of Channel 2—ABN Sydney (64-70Mc/s) Australian television in Auckland, New Zealand, during the period 18th November, 1957 to 24th January, 1958, may be of interest. Distance approximately 1,250 miles.

Receiver, untouched, standard, domestic, 17in fringe model. Aerial 5-element Yagi, at a height of approximately 200 feet above sea level, but in a comparative dish compared with adjacent hills.

Reception has been accomplished some 17 times, the periods being a maximum of four hours and a minimum of just a few minutes. On at least three occasions the signal could hardly have been better, even close to the transmitter. Times of reception were completely unpredictable and varied from 3 p.m. to 12 p.m. This would of course coincide with transmission times (New Zealand 2 hours forward.) Vision without sound was quite common, but rarely the other way round. Fading and ghosting were sometimes severe, and at other times non-existent. The longest period without any fading of either vision or sound was of 45 minutes on the evening of 24th January, 1958—(6 p.m. to 6.45 p.m.) During one evening when an experimental local transmitter was testing, it was possible to make a direct comparison of the pictures (405 as opposed to 625) and there could be no doubt as to which was superior. Incidentally, it was also possible to appreciate f.m. sound even though it was

heard through a poor loudspeaker system. Once the receiver was adjusted no attempt was made to improve results as it was found that a minimum signal would "hold" if it was sufficient to modulate the tube to a grey level, fading then varied the contrast level.

Auckland, New Zealand. C. A. ROUSE.
Bell Radio Television Corporation.

Optical Illusion

READERS with access to a double beam oscilloscope may be interested to observe an unusual optical effect which I discovered by chance the other day.

Set a presentation on the tube face of any waveform to hand and lock it with about 4 complete waves showing. Now set another wave shape on the second beam at a few cycles short of the second harmonic of the former so that it is on a slow shift. If you now look at the tube face but endeavour to focus your eyes at a point some three feet past the screen then the four waves on beam one can be made to overlap and show as five waves. When this is achieved the two presentations will be floating on different planes some distance inside the tube.

Leeds. TERENCE JOHN HALL.

Swamp Interference Stopper

THIS is written for the benefit of all those who have built the "Unconventional (Pulse Counter) F.M. Receiver" described by M. G. Scroggie,* and enjoyed

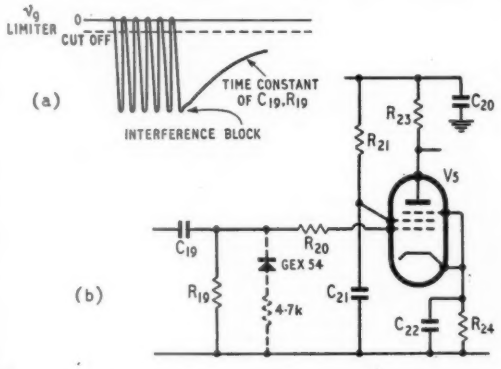

excellent results until they found themselves (as I did) receiving violent jamming. One hundred yards away from the receiver is the main local police transmitter which caused receiver paralysis. The likeliest place for this to occur is at the grid of the limiter, as indicated in diagram (a).

As can be seen, this is effectively negative d.c. restoration in which the positive excursion of the waveform is clamped to the cathode potential. At the end of the interference block the grid is left greatly negative and the valve cannot conduct for some time, i.e., it is paralysed. There are several ways of curing this:—

(a) By stopping the grid current which produces d.c. restoration.

(b) By using d.c. coupling.

(c) By counteracting the negative d.c.r.

Methods (a) and (b) aim at getting rid of any d.c.r. effect.

Method (a) could be practically achieved only with a cathode-coupled limiter (see for example, G. G. Johnstone, *W.W.*, August, 1957).

Method (b) is impracticable because of attenuation.

Method (c) entailed building-in positive d.c. restoration.

(c) was tried since only a diode and a resistor needed to be added to the existing circuit (see diagram (b)). Ideally the diode should have been returned to a potential corresponding to cut off for the limiter. However, the diode was taken to earth as a reasonable compromise and was left there after it was found that the clamping potential was not very critical. This modification should cure all except very bad cases: these could very well have the same trouble occurring on the grid of the last i.f. valve. If this is so, similar measures will prevent paralysis there also.

On a conventional receiver with a 10.7-Mc/s i.f. strip a diode would probably effect an improvement, although it would lower the Q of the last i.f. transformer for large inputs, due to the grid current of the limiter and the diode current. As a simple, inexpensive remedy, however, it would probably be worth a trial.

Bristol. G. J. ANDRIESSEN.

* *Wireless World*, April and June, 1956, April 1958

Tape Spools

I HAVE read with interest the letter from D. J. Kidd in the May issue. There can be no doubt that with the type of reels available at the moment much undesirable fiddling is necessary in order to thread them up.

To my knowledge, only one manufacturer has made any effort to improve matters by providing a reel with a novel form of spring clip which nips the end of the leader. Apart from this, most of the others seem content to plod along, marketing the same old reels which appear to be designed to waste the maximum time when one is frantically endeavouring to thread up for a recording.

In contrast, the many ingenious reels available to the cine film enthusiast make me green with envy. I realise that improvements cost money, but feel sure that most tape recordists would gladly pay a little extra in order to obtain easy-to-handle reels.

London Tape Recording Club. JOHN WEIR.

"Do-it-Yourself" Amplifier

THE first of a new series of Cossor kits, Model 562K, comprises a three-watt, two pentode amplifier to feed two loudspeakers, a 10×6in elliptical and a 4in tweeter; the same equipment being used in the factory-made 562 record player. The sensitivity is 240mV with a signal to hum and noise ratio of 45dB. The frequency response is 2dB down at 50c/s and 13kc/s with the treble cut control turned to minimum. Detailed assembly instructions are given, and most of the components are already soldered into position on a printed circuit board. The price of a complete kit is £9 15s.

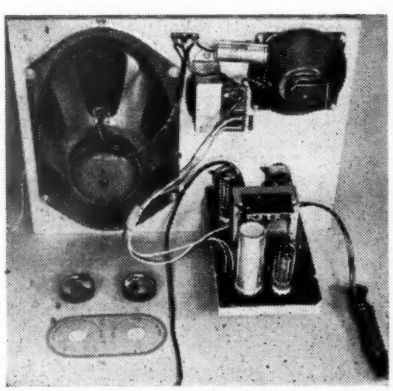

Completed Cossor 562K Amplifier

Technical Notebook

Solid "Electrolytic Tank" was described by Rowe and Martin at the I.E.E. Microwave Valve Convention. Instead of filling the volume round the metal electrode analogues with a liquid electrolyte, a solid conductor is used. The main advantage of using a solid is that, since there are no polarization effects, d.c. fields can be used instead of a.c. fields to measure the equipotentials between the electrode analogues, and errors due to a.c. pick-up are avoided. Another advantage is that the conductivity is less liable to vary with time. The solid is made by mixing conducting amorphous graphite (40 per cent by weight) and insulating gypsum plaster, these proportions giving the desired volume resistivity of about 10^5ohm-cm. Errors due to imperfect mixing can be kept below 2 per cent.

Modified Bifilar-T Traps.—The bifilar-T trap shown in the upper diagram (full lines) is widely used in television receivers to secure adequate sound rejection. This is obtained by making the sound i.f. fall in its "rejection notch" (lower diagram, full line). The network may also be used at audio frequencies for such purposes as harmonic rejection in fixed-frequency measuring instruments, and some practical results are described by A. Hendry and A. G. McIntosh in the July, 1958, issue of *Electronic & Radio Engineer*. The authors show how the basic network may be modified, e.g., by adding the capacitors shown dotted in the upper diagram, to produce a number of variant frequency responses such as low-pass (frequency of maximum response on low side of rejection notch) and symmetrical characteristics (dotted line, lower diagram). The insertion of such networks into negative-feedback loops can produce sharp band-pass responses.

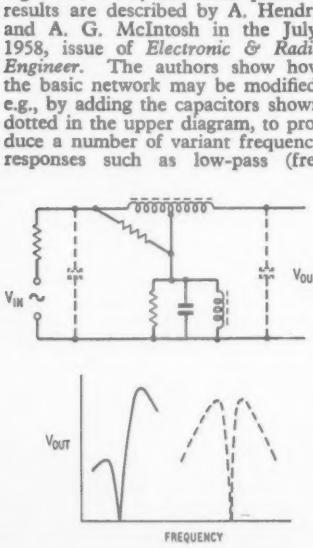

Two-State Indicator Tube for computer circuits introduced by Mullard is notable for its high sensitivity and low power requirements, making it suitable for transistor and other circuits where only small signal voltages are available. It is essentially a triode valve in which the anode serves as a fluorescent screen, giving a blue-green glow about 20 sq mm in area. Working with an anode voltage of 50V, the tube light output can be switched from maximum (anode current 0.5mA) to minimum (anode current less than 5μA) with a grid voltage swing of only 3V. The DM160, as the tube is designated, is very small, being mounted in a 5-mm diameter bulb with flying-lead connections.

Semiconductors at R.R.E.: Indium antimonide is used as the sensitive element in an infra-red-seeking guided missile, but for "good definition" and high sensitivity the sensitive area must be very small. The element actually takes the form of a strip less than 5×10^{-4}in thick, this thickness being achieved by electro-etching (the reverse of electroplating). Another process in semiconductor preparation demonstrated recently at the Royal Radar Establishment is the zone refining of silicon. Molten germanium is sufficiently non-reactive to allow this process to be carried out in a boat-shaped crucible which is passed through an r.f. field; but unfortunately silicon is so reactive at its melting point that this is impossible. Another feature of molten silicon is that it has a very high surface tension—several times that of mercury. This allows a rod of silicon to be passed vertically through an r.f. heating coil, in a vacuum, and as long as the molten zone does not exceed 1cm in length the rod remains in one piece. The rod is revolved and gradually drawn through the field, by pushing from below and pulling from above, so that a bent rod (provided it is not bent to such a degree that it cannot enter the vacuum chamber) is straightened, and, by "seeding" the leading end of the rod with a small crystal, the whole rod can be made into one single crystal structure.

—100°F Primary Cells.—*Electronic News* for 17th March reports that the Yardney Electric Corporation have produced a primary cell efficient down to temperatures as low as −100°F. The cell uses a silver chloride cathode, a calcium anode and acetonitrile as the electrolyte solvent. The efficiency of the cell is 4 watt hours/pound at −100°F and 18 watt hours/pound at 75°F with an e.m.f. of 2.55V.

Potentiometer-like Attenuator usable up to 3000Mc/s is made by the German firm Wandel and Golterman. The input is taken as usual to one end of the track, but, unlike a normal potentiometer, the earth connection is taken to the whole of the side of the track opposite to the wiped portion. This arrangement

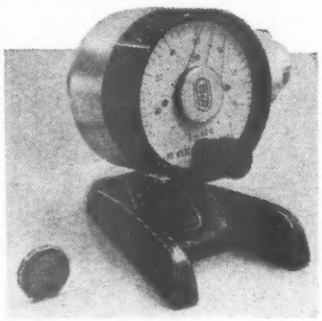

produces a resistively loaded line in which the series resistance is provided by the track length and the shunt resistance by the track width between the wiped and earthed sides. The output is taken from the tapping on this line made by the sliding contact. The output impedance would be incorrect near the ends of the line, so the sliding contact is prevented from reaching right to these ends. Thus there is a minimum insertion loss of 10dB in this attenuator. The maximum possible attenuation is 70dB, and the accuracy ±0.2dB. In this country the attenuator is available from Solartron.

Doppler Radar Using Transistors.—The Doppler navigational radar put into service with the R.A.F. in 1954 consists of four electronics units and weighs over 100 lb. Subsequent development for civil and military use has reduced this weight and has produced a smaller aerial system. Another version, using transistors as far as possible, is now under development at the Royal Radar Establishment. This consists of only two units, and will weigh considerably less than 100 lb.

CLIX B8F (4 X 150A) insulated valveholder designed for forced air cooling, with P.T.F.E. body moulding and chimney to direct flow over anode area. Cat. No. VH88-801.

The answer — in P.T.F.E. P.T.F.E. is a material with a number of unique properties. In many ways it is the answer to an electronic designer's prayer—high insulation resistance, low dielectric losses, wide temperature range and zero moisture absorption. But from the production angle it is tough, stubborn and thoroughly unco-operative. You have to know it for a long time before you can get it to do what you want.

We have the advantage of having grown up with P.T.F.E. and its associated problems, and our intimate knowledge of electronics puts us in a unique position for advising set designers and manufacturers on new applications of the material. We have more extensive P.T.F.E. fabricating experience, and we manufacture P.T.F.E. components in both smaller and larger sizes than anyone else in the country. Tough though it is, we have mastered the art of forming it into all the component parts you are likely to want, or we can supply it in blanks of all shapes, thicknesses and sizes for your own machine shops. And if necessary we are ready to help you with a lot of hard-earned know-how on the subject.

SIEMENS EDISWAN

P.T.F.E. COMPONENTS AND MACHINING BLANKS

SIEMENS EDISON SWAN LIMITED *An A.E.I. Company,*

155 Charing Cross Road, London, W.C.2 · Telephone: GERrard 8660. · Grams: Sieswan, Westcent, London

CXC 17/7

F

FREE— AN IMPORTANT BOOK

about YOUR CAREER • HOBBY...

...SPARE TIME WORK, etc....

...IN ANY OF THESE SUBJECTS:—

Accountancy
Advertising
Aeronautical Eng.
A.R.B. Licences
Art (Fashion Illustrating, Humorous)
Automobile Eng.
Banking
Book-keeping
Building
Business Management
Carpentry
Chemistry
City & Guilds Exams.
Civil Service
Commercial Subjects
Commercial Art
Computers
Customs Officer
Draughtsmanship
Economics
Electrical Eng.
Electrical Installations
Electronics
Electronic Draughtsmanship
Eng. Drawing
Export
General Certificate of Education
Heating & Ventilating Eng.
'Hi-Fi' Equipment
High Speed Oil Engines
Industrial Admin.
Jig & Tool Design
Journalism
Languages
Management
Maintenance Eng.
Mathematics
M.C.A. Licences
Mechanical Eng.
Metallurgy
Motor Eng.
Painting & Decorating
Photography
P.M.G. Certs.
Police
Production Eng.
Production Planning
Radar
Radio
Radio Amateurs (C. & G. Licence)
Radio & Television Servicing
Refrigeration
Sales Management
Sanitary Eng.
Salesmanship
Secretaryship
Servo Mechanisms
Shorthand & Typing
Short Story Writing
Short Wave Radio
Sound Recording
Telecommunications
Television
Time & Motion Study
Transistors
Tracing
Welding
Workshop Practice
Works Management
and many others

NEW PRACTICAL DO-IT-YOURSELF
YOU CAN MAKE & SAVE MONEY IN:—
RADIO & T/V BUILDING & SERVICING
ELECTRICAL APPLIANCE REPAIR
CHEMISTRY • PHOTOGRAPHY
HI-FI EQUIPMENT, ETC.
All the above special courses include practical equipment as part of the training.

Also courses for GENERAL CERTIFICATE OF EDUCATION, A.M.I.H.&V.E., A.M.S.E., A.M.Brit.I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.Ae.S., A.M.I.P.E., A.M.I.I.A., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Examinations, R.T.E.B. Servicing Certificates, R.S.A. Certificates, etc.

- Personal and Individual Tuition given by named tutors
- All equipment yours to keep
- Courses for Beginner or Advanced student

EMI INSTITUTES

E.M.I. Institutes is associated with:
"HIS MASTER'S VOICE", Columbia, etc.

POST TODAY

To:— E.M.I. INSTITUTES, Dept. 127K, LONDON, W.4

Please send, without any obligation, your free Book to:—

NAME _____ AGE _____ (if under 21)

ADDRESS _____

_____

Subject(s) of interest _____ With* / Without } equipment

(We do not employ travellers or representatives) *Delete as required.

AUG./58 IC.118

The only Home Study College run by a World-wide industrial organisation

PHOTOCELLS

By "CATHODE RAY"

Including Some Recent Semiconductor Devices

WE are all familiar with valves and perhaps transistors, but my guess is that only a minority of us habitually handle even one of the many varieties of photocell. Probably most of that minority are owners of photographic exposure meters. Yet in spite of the fact that so few people ever see them, photocells are used in a staggeringly large number and variety of ways. If I were to do no more than mention them by name I doubt whether it would leave me room for anything else, so I won't start. But partly because there are so many uses there are many different kinds of photocell, and because they are seldom seen most of us are probably rather vague about them. It isn't my intention to say much about their construction or methods of use, but to follow up our recent ventures into electronic theory by seeing how the chief kinds work.

If you followed the series from the beginning you may remember that the photo-electric effect played a very important part in triggering off the modern ideas about matter. It was discovered that when light is shone on certain metals they emit electrons, and (contrary to what nineteenth-century physics led one to expect) the force with which the electrons are emitted increases with the frequency rather than the intensity of the light. This was, however, quite in keeping with the revolutionary quantum theory that had just been introduced to a sceptical world by Planck. It is now accepted that light consists of something like small particles, called photons, each having an amount of energy equal to the frequency f of the light in c/s multiplied by a constant, h (Planck's constant), equal to 4.15×10^{-15} if one's unit of energy is the electron-volt (eV).

The obvious query on this is what, if light consists of particles and not waves, is f the frequency of? Well, we went into this to some extent in the March issue, and I can only repeat that both light and electrons do in fact have some of the properties both of waves and of particles, and if you don't like that idea you must, I am afraid, lump it.

Fig. 1 Response curve of antimony-cæsium photo-emissive cathode.

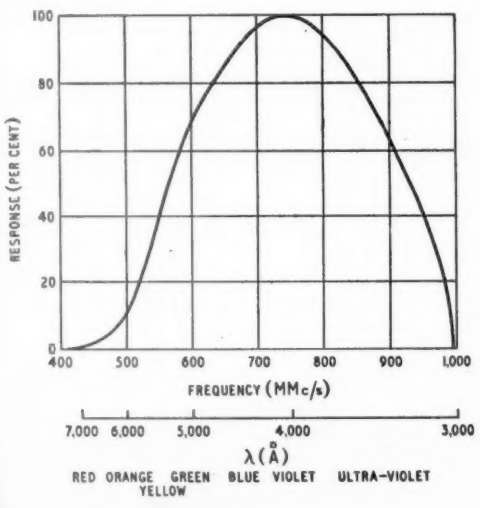

As we found in the June issue, metals and other solids have vast numbers of valency electrons circulating throughout them energetically, even at the absolute zero of temperature (0°K). Additional energy, usually amounting to several eV, is needed by any of these electrons to enable it to break surface and get clear—to be emitted, as we say. This quantity of energy is known as the work function, denoted by ϕ. One way of increasing the energy of the electrons is by means of heat. This is the method adopted in valves and cathode-ray tubes. Another method is to shed light on the cathode surface. Either way, the amount of energy imparted per electron must be at least equal to ϕ.

Fig. 2 Circuit for examining current/voltage characteristic of photo-emissive cell just above and below zero voltage.

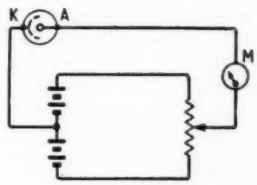

If the energy is derived from light, we know it is in packets of size hf. Since h is known, the lowest frequency needed to obtain emission from any metal follows. The ϕ for tungsten, for example, is 4.5eV, so the minimum f is $\phi/h^*=4.5/(4.13\times10^{-15})$ c/s= 1,090 MMc/s.

The frequency of light runs from about 400 MMc/s at the red end to a little over 800 MMc/s at the violet, so no visible light is effective with tungsten; ultra-violet is needed. By contrast, the ϕ for cæsium is only 1.8eV, so practically the whole range of visible light has sufficient energy to overcome it.

It might seem, then, a simple matter to choose a metal suitable for emitting electrons when illuminated by radiation of any particular range of frequency. In practice it is much less simple, because the effective ϕ depends very largely on the condition of the surface. The thinnest possible coating of impurity or tarnish, for example, may quite alter its emissive properties, for better or worse. Details can be found in any good book on photocells.

*I have just been looking up some books on this, and several of them give the equation for minimum frequency as $hf \times e\phi$ instead of $hf \times m$ Not one of these explains how hf (which is energy) can be equal to ϕ (which is energy) *multiplied by electric charge*. Anybody checking this equation by seeing whether the dimensions were the same on both sides would conclude that it was wrong. The explanation is that if the two sides are not in the same system of units a constant must be introduced to make them so. If hf is in conventional units, ϕ (usually in electron-volts) must be brought into the same system by multiplying by the number of conventional units of energy equal to one eV of energy. But to represent this by e, which stands for the amount of negative electric charge of one electron, is as muddling as making a change from British to metric units in an equation by introducing a factor l, denoting the length of an inch in metres.

In valves, heat is used to make the cathodes yield a constant emission for control by the other electrodes. Light is not a convenient alternative to this. The purpose of photo-emission is to detect or measure the light. And so we have the innumerable applications in television cameras, sound films, photometers, burglar alarms, etc., etc.

We have seen how to calculate the *minimum* frequency for emission from a surface of given φ; how about the maximum frequency? The surplus energy imparted by light of higher frequency than the minimum appears as kinetic energy of the emitted electrons. So if white light is shone on cæsium, the red part of it causes electrons merely to stagger out, with no spare energy, while the violet part, having double the frequency, makes them emerge with an energy of about 1.8eV; that it to say, with the speed they

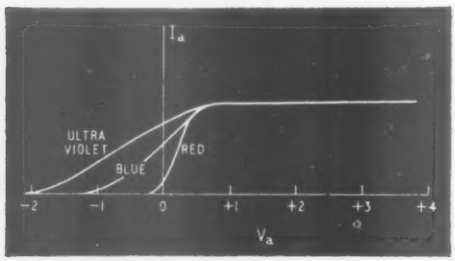

Fig. 3 How the current/voltage characteristic is influenced by colour of light.

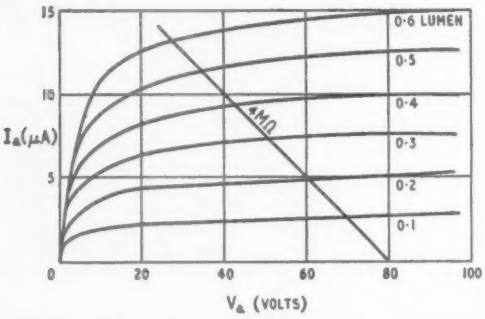

Fig. 4 The used part of a vacuum photocell's characteristic curve sheet resembles a pentode's.

would be given by a positive e.m.f. of 1.8V†. Of course, this speed is not necessarily at right-angles to the surface, so even when the light used is monochromatic—which means that it is all concentrated on one frequency—the speeds of emission directly away from the surface vary over a range from zero to the maximum as just calculated.

Under suitable conditions there is hardly any top limit to the maximum frequency that causes emission, and enormous velocities can be imparted to the emerging electrons; but ordinary photocells are enclosed in glass bulbs, which cut off most of the ultra-violet frequencies. If a cell is needed specifically for that range, a quartz window is fitted to admit it. There are other things affecting the band of frequencies for which the cell is effective; for example, surfaces absorb or reflect certain frequencies selectively. Fig. 1 shows a typical colour response curve for an antimony-cæsium cathode.

The fact that light frequencies higher than the minimum make electrons come out with speeds that can be reckoned in eV means that those electrons can land on another electrode *against* an e.m.f. up to that limit. Fig. 2 shows an arrangement for applying a controllable voltage to what we will call (by analogy with a valve) an anode, though it can be made either positive or negative. K is the photocathode, and the two electrodes are enclosed in the usual glass bulb so that the air between them can be removed. Although what is reckoned to be a high vacuum leaves about as many air molecules in every cubic centimetre as the entire population of the United States, they are so small that practically all the electrons get through without obstruction.

Let us suppose that we illuminate the cathode with various monochromatic lights, and that the cell has the characteristic shown in Fig. 1. Then a red light will just make a few electrons emerge with almost no speed, so a zero or slightly positive voltage will be needed at the anode to attract them there and make them show a deflection on the microammeter M. A blue light will bring some of them out with a velocity corresponding to a frequency difference of about 240 MMc/s, or say 1eV. They will just be able to reach the anode if it is made 1V *negative*. Making the anode gradually less negative brings in more and more of the emitted electrons—those emerging other than directly towards the anode—until finally, when all are gathered in, even a highly positive potential cannot increase the number. With near ultra-violet light, some electrons have even higher velocities, and a still more negative voltage is needed to ensure that none reaches the anode.

If the brightness of the three lights is adjusted to be effectively the same at the cathode, the results of these experiments will be as in Fig. 3. Increasing the brightness would proportionately increase the number of electrons emitted, so the current readings would all be multiplied everywhere by that factor. But the "starting voltage" for any one colour would be the same as before.

When a current flows *against* an e.m.f., as indicated by the left-hand region of Fig. 3, it possesses energy, which can be utilized. Suppose the battery and potential divider in Fig. 2 is abolished and simply a resistor is connected between K and A. Then the electrons flowing through it will set up a p.d. across it, making the anode negative. The cell will in effect be a generator driving current through the resistor. This corresponds exactly with the current that flows through a resistor between anode and cathode of an ordinary diode, the energy in that case coming from heating of the cathode instead of light shining on it. The same thing is familiar in other types of valve, where some grid current flows even when the grid is slightly negative.

Although there are rumours that direct conversion of heat to electrical energy in this way may become a practical source of power, the efficiency would seem too low to be attractive; and the power available from an ordinary emissive photocell is even more insignificant. The usual way of using the cell is to apply something of the order of +100V to the anode through a high load resistance, the relation-

†For voltages lower than about 10,000 (so that the relativity correction is negligible) the velocity is $594\sqrt{V}$ km/sec, so with V = 1.8 it is 800 km/s or 1,800,000 m.p.h.

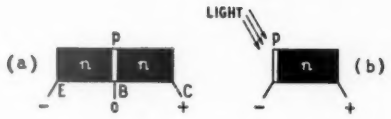

Fig. 5 An n-p-n transistor (a) and the corresponding photo-transistor (b).

ship between voltage drop across this resistance and brightness of light being very similar to that between load voltage and grid voltage in a pentode —see Fig. 4. The voltage drop is used as a measure of the light, or for actuating something by light.

I must just mention that the anode current can be multiplied considerably if a small amount of inert gas is admitted to the tube. The characteristics of these tubes are similar to Fig. 4 up to about 20V; above that, the electrons get up enough speed to knock electrons out of the gas atoms (ionize them, to use the technical term) and these swell the crowd. Which type is the better to use depends on the circumstances. In general, the vacuum type is used for measurement (quantitative) and the gas type for detection (qualitative).

We must press on, for we have covered only the first of the three points in the sermon—photo-*emissive* cells. As we have seen, one could also classify these as photo-*voltaic*, in that they are capable of generating an e.m.f. directly from the power of light, but as it is only to a very limited and insignificant extent one does not. Before coming finally to the cells which are photo-voltaic enough to be so used, let us take a look at the photo-*conductive* class. If you wanted to be awkward you might point out that the emissive type could also be regarded as photo-conductive—and in its normal mode of use, too—but for convenience the term is confined to solid conductors.

Selenium is the substance everyone thinks of here, because its light-sensitive properties were discovered as long ago as 1873, and for most of the time since it has remained supreme. But recently there has been considerable development of other semiconductors, notably compounds of lead and thallium with sulphur, selenium and tellurium. What is likely to interest us most is that still more recently transistor technique has become involved.

Semiconductors, you may remember, are substances in which there is a small energy gap between the energy band filled with valency electrons and a conduction band into which they have to be raised if the material is to conduct at all. The smallness of the gap means that the energy of heat at ordinary temperatures is sufficient to raise a small but significant proportion to the conduction band. In transistors and most other semiconductor devices this heat conduction is just a nuisance, because it is a sort of leakage, not under the control of the input signal. The useful current carriers, introduced by impurities, are under control. Light is another form of energy, and more effective than heat because of its higher frequency. That is why semiconductors tend to conduct better in the light than the dark. It is also why transistors are enclosed in opaque containers, but where control by light is desired they can be modified accordingly; hence the photo-transistor.

In general, a photo-transistor has one electrode

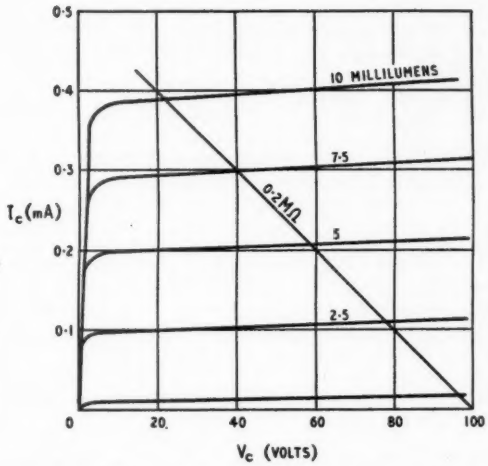

Fig. 6 The characteristic curves of a photo-transistor closely resemble those of a transistor triode.

fewer than the corresponding signal transistor, because the current carriers are introduced directly by the impact of light instead of from the usual emitter. Fig. 5(a) shows an *n-p-n* junction transistor in which the emitter functions as the source of free electrons, thanks to the donor impurity therein. Their flow into the base—whence they are snapped up by the positive collector voltage—is controlled by the signal voltage between emitter and base. Alternatively, electrons already in the base can be freed by the direct impact of light, as in Fig. 5(b). The characteristic curves (Fig. 6) are of exactly the same type as for the transistor triode, except for light taking the place of base voltage as the controlling parameter.

It is not essential to have a junction; the resistance of a simple strip of germanium goes down when it is exposed to light. The semiconductor compounds mentioned are also used simply as light-variable resistors. Some are remarkably sensitive and some respond to a very wide spectrum, embracing ultra-violet, visible and infra-red. At ordinary temperatures the current carriers released by light have to compete with those released by heat, so for extreme sensitivity they are cooled. A lead sulphide cell cooled by liquid air, for example, is sensitive to 10^{-13} watts per sq cm. Without this refinement, or any means of concentrating or directing the radiation, the Mullard 615V lead sulphide cell is stated to detect the heat from an ordinary soldering iron at 100 yards.

Lastly, photo-voltaic cells, which generate their

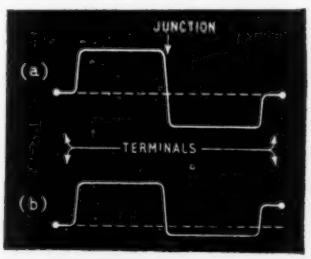

Fig. 7 Potential diagrams of a junction photo-transistor, (a) in the dark, and (b) illuminated.

own power. We noted in passing that emissive cells qualify also as photo-voltaic, but so slightly as to be of no practical value in that role. Semi-conductor junctions (*n-p*), as all treatises on them explain, develop a difference of potential between the two sides of the junction. Nearly all the said treatises fail to explain why no trace of it can be found when even a highly sensitive voltmeter is connected to the terminals. The reason, after one wrong guess, was given last month as the counteracting p.d.'s of the metal-to-semiconductor junctions at the terminals. But just as heating one of the junctions between different metals in a complete circuit upsets the balance and sends a thermo-electric current around the circuit, so the impact of light on a suitable junction enables it to act as a current generator. This is shown very simply in Fig. 7, where (a) is the balanced condition in the dark (or equal illumination throughout), whereby there is no p.d. between the terminals. The quite large p.d. at the junction, you remember, is caused by the superfluity of electrons in the *n* material and holes in the *p* material; these diffuse across the boundary, the electrons charging the *p* side negative and the holes charging the *n* side positive. The process ceases when this p.d. just balances the diffusive tendency. Heat—or light—dilutes the effect by creating hole-and-electron pairs in either or both regions. Neither electrons nor holes will diffuse into regions where there are already plenty of their own kind, and so the p.d. tends to be lower, as in Fig. 7(b), with the result that a net p.d. appears between the terminals.

If you like the Fermi level idea you may prefer to think of the thing on that basis. You remember that making pure semiconductor material into *p* or *n* displaces the Fermi level from the middle of the energy gap downwards or upwards respectively. So where the two kinds are in contact a p.d. is created as in Fig. 8(a). Heating the material tends to bring the Fermi level back to the middle again, the two opposite kinds of impurity conduction being (as it were) swamped by the increased intrinsic conduction. The p.d. is thereby reduced as shown at (b).

Light, if it could get to all the material represented, would have a similar effect. Since these materials are not particularly transparent, it is as much as one can do to illuminate a thin section at or about the junction. A transition from decidedly *p* or *n* type to near-intrinsic conduction at the junction due to strong illumination there can be represented by a shifting of the Fermi level in the gap, as shown at (c). The drop in p.d. as compared with (a) appears again.

Fig. 8 Fermi diagrams of a p-n junction, (a) normally, (b) heated throughout, and (c) exposed to light at the junction.

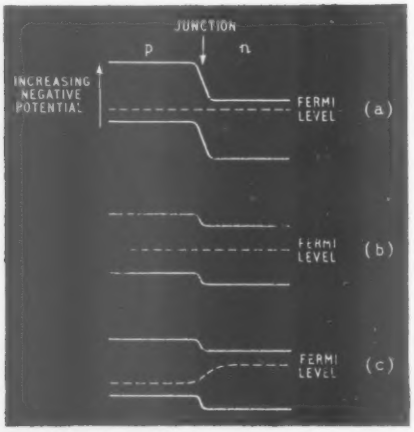

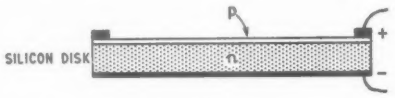

Fig. 9 Section of junction photo-voltaic cell used in Bell Telephone tests.

Selenium, although somewhat outmoded for photo-conductive cells, is a favourite material for the photo-voltaic kind, and electric exposure meters usually consist of a suitable metal-to-selenium junction feeding a microammeter. These instruments are taken for granted now, but a year or two ago some excitement was created by tests carried out by the Bell Telephone Laboratories, in which a special battery of photo-voltaic cells mounted on a rural telephone pole provided the power for a repeater station from sunlight alone. On a bright day the power developed was 10 watts—more than was needed by the repeater, so that there was a surplus to charge an ordinary battery to keep things going at night and during dull days. (Whether there would be enough surplus to ensure continuous operation in this country seems open to doubt!)

Fig. 9 gives some idea of the construction of the cells used. The semiconductor is silicon (presumably germanium would have rather an excessive intrinsic conductivity at the temperature it could reach in full American sunlight). Most of it is *n*-type due to arsenic "impurity," but an extremely thin layer of *p* is formed on one surface by diffusion of boron. The junction is only 0.0001in below the surface. In bright sunlight, the e.m.f. generated was about 0.5V; polarity as marked in Fig. 9. As many as 432 cells were used for the test, mounted in a flat aluminium case with glass lid. The efficiency was about 10%, which was a considerable advance on conventional photocells. Since it is estimated that in two days the earth receives more energy from sunlight than could be provided by all its known reserves of fuel, you may begin to wonder why we are bothering about nuclear power stations. There are, of course, many snags in solar energy, chiefly financial (capital costs, and so forth). But for special applications, such as this telephone idea, it has interesting possibilities.

One of these special applications has been demonstrated more recently, also by the U.S.A., giving their earth satellites at least one advantage over the first two sputniks,‡ which went dead (together with the dog) as soon as their batteries ran out. One of the American satellite's radio transmitters is energized by photo-voltaic cells, and since the sun at that altitude is not only unobscured by clouds but also by the atmosphere the radiation is much more intense and (except when eclipsed by the earth) continuous.

‡ Since writing, Sputnik III has gone up, energized partly by solar batteries.

Wide-Band Oscilloscope

By G. H. LEONARD*, B.Sc.

THE techniques used in oscilloscope Y amplifiers have made considerable advances during the past few years and instruments are commercially available having direct coupled amplifiers with a 3dB bandwidth of the order of 30Mc/s together with a rise time of the order of 10-15mμsec and a high sensitivity. These instruments are usually complex, making use of very accurate multivalve timebases, calibrators, etc., and the latest distributed p.d.a. tubes. They are excellent multi-purpose instruments but are very expensive.

Being faced with requirements for an oscilloscope having a rapid rise-time (with negligible overshoot) and wide bandwidth, it became apparent to the writer that provided certain limitations were accepted the distributed amplifier normally found in expensive instruments could be dispensed with. Using modern valves with a high figure of merit in conjunction with low anode loads, and cathode followers to reduce the effects of input capacitance, the design of a wide-band amplifier having a suitable gain appeared to present few problems, provided a.c. coupling were accepted together with considerable restriction of the usable Y deflection.

MODIFYING AN EXISTING COMMERCIAL INSTRUMENT

The use of a.c. coupling was not considered to be a serious drawback; the occasions when one is interested in examining rise-time and d.c. level together are, in the writer's experience, comparatively rare. When they do arise, it is frequently possible to make a separate observation of the d.c. level by the use of a simple chopper consisting of a pair of resistors and a high-speed relay energized from a 6.3-V, 50-c/s, supply to obtain a "double-beam" presentation of d.c. level. With this in mind, it was decided that the l.f. response of any amplifier must be such as to give negligible droop on a 50-c/s square wave.

Vertical Deflection

The minimum acceptable height of display is very much open to debate. For design purposes a minimum display of one centimetre for short pulses of either polarity (with the mean d.c. level roughly corresponding to the undeflected trace) was considered sufficient provided an adequate synchronizing signal could be obtained. This presupposed a display of 2cm for a sine wave or other symmetrical phenomena. To obtain such a display on a 4EP1 cathode-ray tube (commonly used in reasonably priced oscilloscopes) a peak-to-peak voltage swing of approximately 20V must be applied across the Y plates if the final anode voltage is 1kV and the p.d.a. voltage 2kV. This implies an output swing of 10 volts peak-to-peak from each half of a push-pull output stage, which is within the capabilities of a wide-band amplifier pentode with a high figure of merit, such as the Mullard E180F, even if the anode load is as low as 680 ohms, provided that negative feedback is used to retain good linearity.

With these facts in mind, it was decided to modify an existing oscilloscope to incorporate a wide-band amplifier. After examining the alternatives and contacting the manufacturer as to the h.t. current available for the Y amplifier, a Telequipment 720 was chosen.

The most important stages in a wide-band oscilloscope amplifier are the final paraphase output stage and the preceding stage, as it is here that large signals must be handled with reasonable linearity. It is therefore proposed to examine the design considerations for these stages in some detail. The effective input capacitance of each Y plate of the 4EP1 is 6pF, which consists of 3pF to the earthy electrodes plus the inter-plate capacitance, 1.5pF, which must be multiplied by 2 to allow for the anti-phase voltage applied to the other plate. Add to this a minimum of 4pF for strays, and a rough calculation shows that even with a resistive source impedance of 500ohms the 3dB point would be about 30Mc/s.

Since the cut-off of other stages would also have some effect, this frequency is too low and a lower source impedance must be obtained. This can be obtained by using a cathode follower, but it must be remembered that for large outputs the cathode CR must be kept sufficiently short for the C to be able to discharge through the R more rapidly than the fastest negative-going transient to be handled, otherwise the cathode will be unable to follow, the valve will cut off, and the output impedance will rise to the value of the cathode load. Again taking 500 ohms and 10pF, we have a time constant of 5mμsec which should be short enough. The mutual conductance of an E180F is 16.5 as an amplifier, but if the screen current is considered a higher figure is obtained. Calling this 18, we have that the output impedance of the stage is approximately $1/18k\Omega$ or 55 ohms, which is low enough to ensure that up to the frequency where the cathode ceases to follow, the drop in output will be small.

It is quite common practice in modern oscilloscope amplifiers to utilize a cathode-coupled pair, d.c. coupled to the Y plates, for the output stage, the Y shift potential being applied to the "earthy" grid. This arrangement ensures that the full grid base of the valves can be utilized when asymmetrical pulses are examined. Such a stage also has considerable gain, the push-pull (anode to anode) out-

* Ultra Electric.

put being equal in amplitude to the output which would be obtained from one valve operating as a simple amplifier with the same anode load. At first sight, it would therefore appear that the ideal arrangement is a cathode-coupled pair d.c. coupled to a pair of cathode followers which are d.c. coupled to the Y plates; any shift bias voltage, applied when examining asymmetrical waveforms, would bias the cathode followers to a suitable operating point to fully utilize their grid bases.

This arrangement suffers, however, from the following disadvantages. First, great care must be taken in the design in order to ensure that no valves are over-run if the Y shift potentiometer is left at one end of its travel, so that a "safe" design must have a restricted shift range which will in turn restrict the asymmetrical handling capacity. Secondly, an extra h.t. supply must be provided so that the cathode followers may be directly coupled to the preceding anodes whose potential is virtually h.t.+ if low loads are used. Thirdly, the stage requires four valves. Finally, the input impedance is not very high. This last point applies to both resistive and capacitive components. Since the cathode of the input valve has an a.c. voltage approximately equal to half of the input and in phase with it, the apparent input capacitance of the valve is halved, but as the grid is normally returned to a steady d.c. potential there is no feedback effect on the resistive component.

Phase Splitter Output

An alternative arrangement, which was the one chosen, is the "split anode load" phase splitter, which has effectively equal anode and cathode loads with a.c. coupling to the Y plates. This circuit, V5 in Fig. 1, gives anti-phase outputs at anode and cathode which are substantially equal to the input so that the stage gain is approximately two. Since the anode load, R_{25}, is kept low the output impedance at the cathode is substantially that of a similar cathode follower so that another valve is eliminated. The input capacitance is low and as the grid leak, R_{27}, is tapped into the cathode load the input resistance is high. This means that a smaller coupling capacitor can be used for the same l.f. response, reducing strays and thereby improving the h.f. response of the preceding stage. The handling capacity for symmetrical inputs is the same as for the cathode coupled pair, but for asymmetrical inputs, since the standing bias is not variable, it is limited by the grid swing available in each direction.

At first sight, it might appear that the anode of the stage could be coupled to a Y plate without interposing a cathode follower and that the stage would then be perfectly cathode compensated, the anode and cathode time constants being equal. In practice, however, these ideal conditions are not met. As the screen current increases the cathode current swing, the anode resistor must be larger than the cathode resistor to obtain equal outputs. Also the anode capacitance increases the anode time constant. The input capacitance of the cathode follower V6 is only about 2pF so that with the strays assumed as before to be 4pF and the anode capacitance of the valve (3pF) we have 9pF. This appears of the right order for ideal compensation.

The values derived above and earlier in the text are of course very approximate, being based on estimates of the stray capacitances. In practice, it was found that the stage was slightly over-compensated and it was necessary to add a small capacitance at the anode to eliminate a small overshoot.

The amplifier preceding the output stage, V4, is designed to give an output which is sufficient to fully load it without introducing distortion and for this reason the anode load, R_{20}, is higher than would at first seem desirable.

The undecoupled cathode resistor R_{23} helps, of course, in linearising the stage, introducing 6dB of negative feedback. Nevertheless, the theoretical stage gain is 6. Experiments were made with a view to applying cathode compensation to this stage, but in the layout used the improvement in rise-time which could be obtained without introducing overshoot was negligible.

As the input capacitance of the stage is relatively high, being of the order of 5pF, a cathode follower, V3, is used to isolate it from the preceding amplifier.

(*Continued on page 397*)

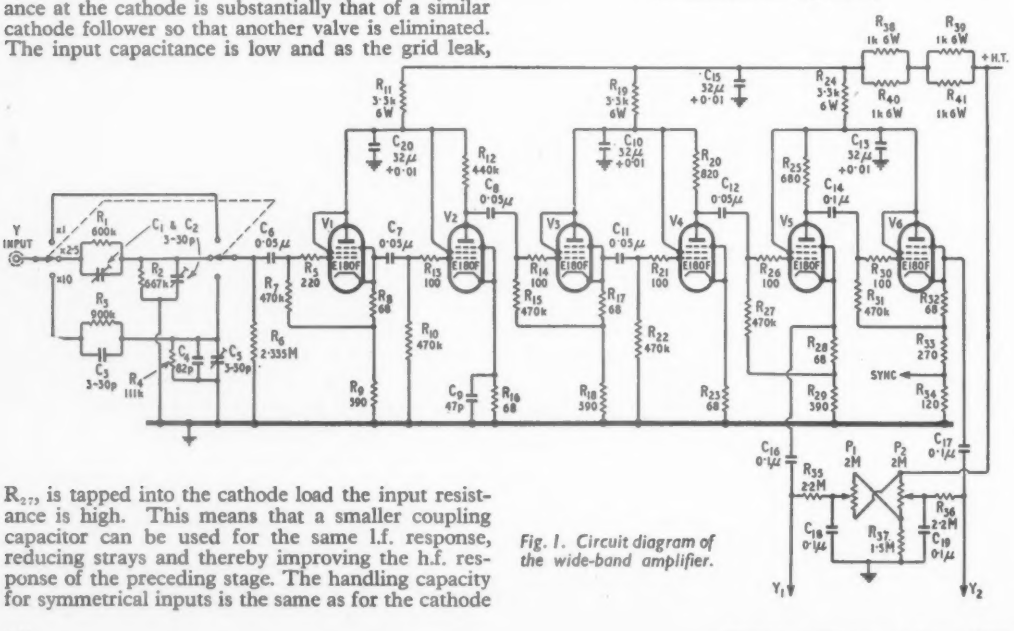

Fig. 1. Circuit diagram of the wide-band amplifier.

Vortexion quality equipment

Model W.V.B.

Our specialised MONITOR HEAD MODEL W.V.B. has an additional head and amplifier which enables this recorder to perform a number of useful functions. The most important of these is to monitor the recorded tape a fraction of a second after it is made, and if necessary compare it by throwing a switch, with the signal before it is recorded. This allows the recording engineer to make certain that he has made a first class recording before the artists leave the studio, without the necessity of waiting while another run through is made.

Additional items may be recorded one on top of another while listening to the first, since a switch is provided for the erase, and the bias, which also acts as a partial erase, can be lowered slightly, and its new value checked on the meter. In a similar manner the original signal may be fed back and recorded, resulting in an echo, the time constant of which is controlled by the speed of the tape and the distance apart of the heads.

VORTEXION RECORDERS use a synchronous capstan motor to ensure accurate recording and play back speed.

Many years of steady development have enabled us to still further improve the Vortexion W.V.A. and W.V.B. recorders which are now fitted with clock type position indicators.

All components which could contribute to noise or reliability are carefully measured and selected individually before incorporation, resulting in an exceedingly low background noise and distortion with frequency response within ± 1.5 db 50-10,000 c/s and ± 3 db 40-12,000 c/s.

★The meter fitted for reading signal level will also read bias voltage to enable a level response to be obtained under all circumstances. A control is provided for bias adjustment to compensate low mains or ageing valves.

★A lower bias lifts the treble response and increases distortion. A high bias attenuates the treble and reduces distortion. The normal setting is inscribed for each instrument.

★The distortion of the recording amplifier under recording conditions is too low to be accurately measured and is negligible.

★A heavy mu-metal shielded microphone transformer is built in for 15-30 ohms balanced and screened line, and requires only 7 micro-volts approximately to fully load. This is equivalent to 20ft. from a ribbon microphone and the cable may be extended 440 yds. without appreciable loss.

★The 0.5 megohm input is fully loaded by 18 millivolts and is suitable for crystal P.U.s, microphone or radio inputs.

★A power plug is provided for a radio feeder unit, etc. Variable bass and treble controls are fitted for control of the play back signal.

★The power output is 4 watts heavily damped by negative feedback and an oval internal speaker is built in for monitoring purposes.

★The play back amplifier may be used as a microphone or gramophone amplifier separately or whilst recording is being made.

★The unit may be left running on record or play back, even with 1,750ft. reels, with the lid closed.

FOUR CHANNEL ELECTRONIC MIXER

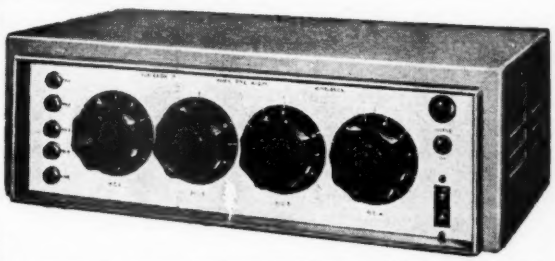

This is a studio quality electronic mixer suitable for any climate. The controls are hermetically sealed, and great care and selection of components to make certain reliable low noise operation, and individual screens prevent break through. The built-in power transformer is screened and potted, and all the microphone transformers are individually potted in selected heavy gauge mumetal boxes. Front or rear inputs and outputs may be obtained to order. The normal output is .5 volt.

The 3-CHANNEL MIXER and PEAK PROGRAMME METER is similar to the above but has the additional meter fitted calibrated in 2db steps from −20 db to +12 relative to l.m.w.—600 ohm. The meter is fed by the full P.P.M. 1 second time delay circuit which includes a stabiliser valve, to ensure accurate gain and calibration. The standard output is screened primary and l.m.w.—600 ohm balanced or unbalanced by switch. Inputs and outputs may be at the front or rear, and rack panel mounting is available at the same price.

Full details and prices of the above on request

VORTEXION LIMITED, 257-263, The Broadway, Wimbledon, London, S.W.19

Telephones: LIBerty 2814 and 6242-3 **Telegrams: "Vortexion, Wimble, London."**

WESTON
PORTABLE
INSTRUMENTS

Weston Portable Instruments include D.C. moving coil, A.C. rectifier and H.F. thermocouple types, and instruments of the A.C./D.C. moving iron type; high grade dynamometer models are also available.

Illustrated above is the Model S.82—a permanent magnet, moving coil instrument in the Portable range. This is primarily a Precision Grade instrument but can also be supplied with Industrial Grade accuracy. Details of this Model, together with others in this series, are available on request.

SINGLE PHASE AND POLYPHASE
WATTHOUR METERS
SYNCHRONOUS TIME SWITCHES
SYNCHRONOUS MOTORS
AND MOTOR UNITS

SANGAMO WESTON

PANEL & SWITCHBOARD INSTRUMENTS
D.C.Moving Coil,A.C. Rectifier,H.F.Thermocouple
A.C./D.C. Moving Iron
PORTABLE INSTRUMENTS
D.C.Moving Coil, A.C. Rectifier,H.F.Thermocouple
A.C./D.C. Moving Iron, A.C./D.C. Dynamometer
LABORATORY STANDARD INSTRUMENTS
D.C. Moving Coil, A.C./D.C. Dynamometer
CURRENT TRANSFORMERS . FREQUENCY METERS . ALL-PURPOSE TEST SETS AIRCRAFT INSTRUMENTS . RATIOMETERS TACHOMETERS . WESTON STANDARD CELLS . ELECTRICAL THERMOMETERS "PHOTRONIC" PHOTO ELECTRIC CELLS PHOTOMETERS

SANGAMO WESTON LIMITED
ENFIELD · MIDDLESEX
Telephone: ENField 3434 (6 lines) & 1242 (6 lines) *Grams*: Sanwest, Enfield

Scottish Factory: Port Glasgow, Renfrewshire
Port Glasgow 41151
Branches: London, CHAncery 4971
Glasgow, Central 6208; Manchester, Central 7904
Newcastle upon Tyne, Newcastle 26867
Leeds, Leeds 30867; Liverpool, Central 0230
Wolverhampton, Wolverhampton 21912
Nottingham, Nottingham 42403
Bristol, Bristol 21781
Southampton, Sol'ton 23328
Brighton, Brighton 28497

SW/28

Train for a wonderful future in ELECTRONICS...

Every day the demand for the expert in electronics grows. Radio, television, radar and the whole field of computers and automation are rapidly expanding and the trained specialist assures for himself a well-paid career in this quickly developing profession. Here is your opportunity to enter for :—

4 YEAR COURSE ELECTRONICS ENGINEERING — intended for young men who are capable of training into future team leaders in scientific applications. Entrance standard G.C.E. Advanced level in Mathematics and Physics. Syllabus covers B.Sc. and City and Guilds' Full Technological Certificate in Telecommunications Engineering. This course is recognised by the Institution of Electrical Engineers. The next course commences on the 17th September, 1958.

3 YEAR COURSE TELECOMMUNICATIONS — Entrance standard G.C.E. Ordinary level or equivalent. This course trains students to become Assistant Development Engineers. It covers the City and Guilds' Full Technological Certificate in Telecommunications Engineering. It also includes theoretical and practical instruction on Computers (Digital and Analogue), Process Control and Automation. The next course commences on the 9th September, 1958.

SCHOLARSHIPS

A number of Scholarships will be awarded for each course. Full details may be obtained on application.

The E.M.I. College of Electronics. Dept. 127, 10, Pembridge Square, London, W.2. Tel: BAYswater 5131/2

The College is part of the E.M.I. Group . . . Britain's foremost electronic engineers . . . Pioneers of the world's first public television service.

THE E.M.I. COLLEGE OF ELECTRONICS

EMI

IA44

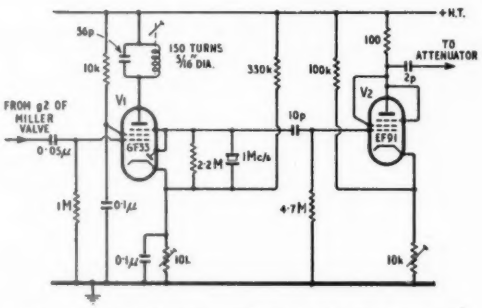

Fig. 2. Time calibration oscillator for the timebase, using a 6F33 and an EF91

The cathode CR of this valve, and the input cathode follower, is unlikely to introduce any distortion as the voltages handled are smaller.

The first amplifier, V2, is designed to give some gain (approx. 3) without noticeably affecting the frequency response, while the input cathode follower, V1, presents a high impedance to the attenuator or the circuit under test.

The various decoupling components shown in the circuit serve to reduce the h.t. voltage to 180 volts, the normal voltage for the E180F, and also give a small measure of anode compensation so that the 50-c/s square-wave response is adequate.

The input circuit and attenuator deserve special mention, being the only high impedance circuits associated with the amplifier. With the modern tendency to employ synthetic resin-bonded fibre switch panels at 200Mc/s the need for low-loss materials is easily overlooked. It was found, however, that an attenuator built on standard wafers introduced sufficient loss at higher frequencies to completely spoil the rise-time of the instrument. Only when a ceramic wafer switch was used and the anchoring points for the input capacitor were mounted on Polythene was the attenuator satisfactory. Similar considerations applied to a high-impedance probe, and in view of the cost of design and manufacture of this item the input impedance of the instrument was arranged to be similar to the well known Tektronix instruments for which probes can be purchased. To facilitate the use of this probe, capacitors are provided across both series and parallel elements of the attenuator so that the input capacitance is independent of the attenuator setting.

The Telequipment oscilloscope modified has available a 1-V peak-to-peak calibrating signal and a graticule of 6-mm squares. When the amplifier was built it was found that the maximum deflection obtainable was approximately 4 squares and it was felt desirable to increase this to 5 squares (the attenuator includes a $\times 2.5$ position) and also to provide a fine gain control for setting up. Since the inclusion of such a control in the amplifier was liable to introduce long leads, variable time constants or other complications likely to lead to either a poorer rise-time or instability, the e.h.t. circuit was examined. It was found possible to insert a variable resistor in an a.c. circuit so as to reduce the final anode potential of the c.r. tube without unduly affecting the p.d.a. voltage so that sufficient variation in sensitivity could be obtained. Space was found on the front panel for a "Set e.h.t." control, which is normally set up, together with the focus and astigmatism, at the start of any measurements.

Unfortunately, adjustment of the e.h.t. also affects the sensitivity of the X plates, which means that the calibration of the timebase is affected. The oscilloscope incorporated a sweep speed control, intended as a semi-preset, mounted at the rear of the instrument; this was moved to the front panel. The time calibration oscillator circuit had been removed with the original Y amplifier but room was found to mount a small sub-chassis on which was mounted the circuit shown in Fig. 2. This consists of a short suppressor grid base pentode, V1, with the anode and suppressor arranged as a crystal oscillator, the grid being fed from the unblanking circuit so that the oscillations are keyed on at the start of the sweep and a locked display obtained. The second valve, V2, is a clipper so biased that it only passes current on the peaks of the sine wave and hence produces short pulses at the anode. To save controls, the front panel space being limited, the time calibration and voltage calibration circuits are connected to spare positions on the attenuator switch. This also avoids the need for a second low-loss switch.

High Frequency Sync

The need for a further facility became apparent when the amplitude response of the amplifier, Fig. 3, was being plotted. Many signal generators of quite reputable make do not give a pure sine wave output, so that great care must be taken in comparing the peak-to-peak voltage displayed on an oscilloscope with any meter indicating peak or r.m.s. Examination of the brightness of the display with quite low timebase speeds gave some indication of the presence of distortion, but at frequencies above 3Mc/s a locked display of the actual waveform was very difficult to obtain. To improve the timebase performance an extra (high speed) position was incorporated on the "time multiplier" switch; this position gives approximately 10 times increase in sweep speed of the timebase with the risk that the rated grid

Fig. 3. Frequency response of the wide-band oscilloscope.

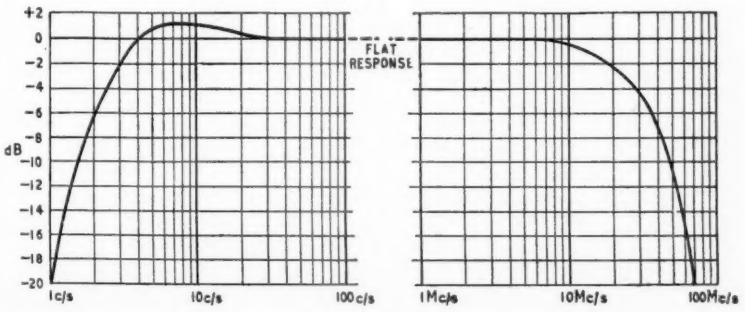

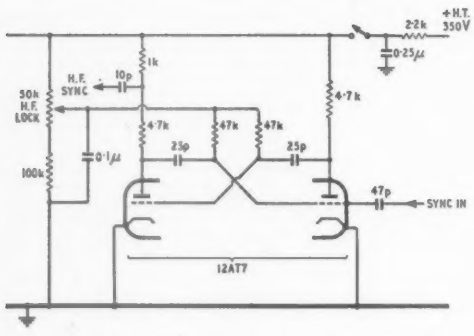

Fig. 4. Multivibrator for improving synchronization of the timebase at high frequencies.

current of the associated valve will be exceeded.

To overcome the limitations of the triggering circuits, which have a reduced performance at high frequencies, the arrangement shown in Fig. 4 is used. An "H.F. Sync" position is provided on the sync selector switch which feeds the output of the sync amplifier to the multivibrator, the output of which is switched to the timebase. The "H.F. Lock" control is adjusted to obtain a suitable division ratio, the multivibrator frequency (of the order of 1Mc/s) being within the limits at which the timebase will trigger. With this arrangement, it has been found possible to obtain a locked presentation of 20-Mc/s sine waves.

The instrument has obvious limitations in respect of brilliance etc. but nevertheless has many uses; the amplitude response being useful up to 40Mc/s, it has, for example, been found possible to use it to check television i.f. amplifiers for amplitude non-linearity under actual signal conditions with the a.g.c. in operation. It is also invaluable for pulse work, the Y amplifier rise and fall times being of the order of 15mμsec.

The writer wishes to acknowledge the part played by F. Woodrow and J. Mosely, who assisted in the development of the instrument.

Colour Receiver Development

IN last month's issue (p. 323) we published a picture of an experimental 21-inch colour television receiver for N.T.S.C. type signals developed at the G.E.C. Research Laboratories. As stated in the caption, the main feature of this set is its small size, which is obtained mainly by the use of a.c./d.c. technique for the power supplies. There are, however, several other interesting features and refinements in the circuit. In general the aim has been to provide accurate registration of the three images on the shadow-mask tube; adequate bandwidth and definition with correctly shaped frequency response characteristics in both luminance and chrominance channels, together with full d.c. maintenance; and stable and noise-free reference signal generation from the colour sync burst.

On the signal side, sound rejection and sound i.f. take-off conform to usual monochrome practice, but in the vision circuits two separate crystal detectors are used to provide isolation between the luminance and chrominance channels. This arrangement enables a high definition luminance signal to be maintained, and when this is fed to the ferrite-loaded delay line (for correct phasing of luminance and chrominance) small reflections in the line are prevented from disturbing the smooth and symmetrical chrominance channel frequency response.

The luminance signal is amplified by two video stages in a "bootstrap" circuit and is ultimately fed in the correct drive ratios to the three cathodes of the c.r. tube. Master brightness is controlled by a bias arrangement in one of the video stages, and the d.c. component of the signal is maintained to within about 1dB.

Two chrominance amplifiers with a 6dB bandwidth of ±500kc/s supply two "clamping" triodes for high-level demodulation along the red and green difference axes, R-Y and G-Y. After filtering, these difference signals are fed to the red and green grids of the tube, and also to a matrix amplifier which forms the B-Y signal for the blue grid of the tube. A reference frequency amplifier provides the two appropriately phased reference signals for the triode demodulators.

The continuous reference signal required for synchronous demodulation is obtained from an LC oscillator which is frequency and phase locked by a two-mode automatic phase control loop, or d.c. quadri-correlator, so that both fast pull-in and good noise performance are achieved. One of the two detectors in the automatic phase control loop provides a d.c. voltage only when a burst signal is present and when the oscillator is phase locked. Since this is a synchronous detector it provides an accurate indication of the presence of a burst even under adverse signal-to-noise conditions, and is used as a colour "killer" control for switching off the chrominance channel automatically when a burst signal is absent. The output of this detector is also fed as an automatic chrominance control signal to bias the chrominance amplifier from which the burst output is taken.

The colour burst is separated from the chrominance waveform and amplified before being applied to the automatic phase control detectors. The separation is carried out by a gating circuit which switches on the burst amplifier only during the burst period of about 4μsec. In order to be quite independent of line timebase synchronization, the gating circuit operates from the back edge of the line sync pulses appearing in the sync separator output.

The c.r. tube e.h.t. supply of 23kV at 1mA is obtained directly from the line flyback without voltage doubling, and a triode shunt regulator is used to stabilize the supply and thereby minimize the effect of e.h.t. changes on the convergence of the three electron beams. Passive convergence circuits, fed from the line and frame timebases, supply the appropriate current waveforms to the dynamic convergence coils mounted round the neck of the tube. Direct currents are also applied to these coils for static convergence adjustments.

AWARD OF I.E.E. PREMIUMS

TWENTY-ONE of the twenty-eight major premiums awarded by the Institution of Electrical Engineers for contributions read during 1957 are for papers on radio and electronic subjects.

The Institution Premium (£50) is awarded posthumously to Dr. E. C. S. Megaw for "Fundamental radio scatter-propagation theory".

The Kelvin Premium (£25) goes to Dr. G. H. Metson for "The conductivity of oxide cathodes".

G. G. Gouriet receives the Blumlein-Browne-Willans Premium (£20) for his contribution "Bandwidth compression of a television signal".

R. G. Medhurst and his three co-authors G. F. Small, H. D. Hyamson, and Muriel Hodgkinson share the Fahie Premium (£15) for their four papers covering various aspects of frequency-modulated systems.

The Coopers Hill War Memorial Prize and Medal (£20), which is awarded triennially in turn by the I.E.E., the School of Military Engineering, Chatham, and the School of Forestry, Oxford, goes this year to L. R. F. Harris, for his paper "Time sharing as a basis for electronic telephone switching".

The premier award of the Radio and Telecommunication Section, the Duddell Premium (£20), is shared by Professor A. L. Cullen and Dr. H. A. French for their paper "An instrument for the absolute measurement of low-level microwave power in the 3-cm band".

Professor H. E. M. Barlow and H. G. Effemey share the £15 Ambrose Fleming Premium for "Propagation characteristics of low-loss tubular waveguides".

Eleven £10 Premiums have been awarded this year for Radio Section papers. A number of them go to authors of papers read at the Ferrites Convention.

Two of the three premiums of the Measurement and Control Section are for papers on digital computers. Dr. T. Kilburn, Dr. G. R. Hoffman and R. E. Hayes share the Silvanus Thompson Premium (£20) for "An accurate electroluminescent graphical-output unit for a digital computer", and Dr. M. V. Wilkes, W. Renwick and Dr. D. J. Wheeler receive the Mather Premium (£15) for "The design of the control unit of an electronic digital computer". The third Measurement Section Premium (£10) goes to Dr. G. B. B. Chaplin and A. R. Owens for their papers on transistor d.c. amplifiers.

EXHIBITIONS AND CONFERENCES

FURTHER details of the exhibitions and conferences listed below are obtainable from the addresses given in brackets. British manufacturers can obtain information regarding exhibiting at overseas shows from the Board of Trade, Export Publicity and Fairs Branch, Lacon House, Theobalds Road, London, W.C.1.

UNITED KINGDOM

National Radio Show, Earls Court, London, S.W.5.....Aug. 27-Sept. 6
(Radio Industry Council, 56 Russell Sq., London, W.C.1.)

Farnborough Air Show .....Sept. 1-7
(Society of British Aircraft Constructors, 29 King St., London, S.W.1.)

Autumn Audio Fair, Grand Hotel, Harrogate .....Oct. 24-26
(Audio Fairs, Ltd., 42 Manchester Street, London, W.1.)

Convention of Scientific Instrument Manufacturers, Majestic Hotel, Harrogate .....Nov 6-9
(S.I.M.A., 20 Queen Anne St., London, W.1.)

Symposium on Mechanization of Thought Processes, N.P.L., Teddington, Middx. (National Physical Laboratory, Teddington.) Nov. 24-26

Radio Hobbies Exhibition, Royal Horticultural Society's Old Hall, London, S.W.1. (P. A. Thorogood, 35 Gibbs Green, Edgware, Middx.) Nov. 26-29

Electronic Computer Exhibition and Business Symposium, Olympia, London, W.14. Nov. 28-Dec. 4
(Electronic Engineering Association, 11 Green St., London, W.1.)

OVERSEAS

International Conference on Semi-conductors, Rochester, N.Y., U.S.A. ....Aug. 18-23
(G.E.C. Research Lab., P.O. Box 1088, Schenectady, N.Y., U.S.A.)

Western Electronic Show and Convention, Los Angeles, U.S.A. ..... Aug. 19-22
(Wescon, 1435 South La Cienega Boulevard, Los Angeles 35, Cal., U.S.A.)

Swiss Radio, Television and Recording Show, Zurich, Switzerland.....Aug. 28-Sept. 2
(W. Von Liliencron, 15 Strassburg Strasse, Zurich.)

International Analogy Computation Meeting, Strasbourg, France .....Sept. 1-9
(F. H. Raymond, 138 Boulevard de Verdun, Courbevoie (Seine).)

International Congress on Cybernetics, Namur, Belgium .....Sept. 3-10
(International Assoc. for Cybernetics, 13 rue Basse-Marcelle, Namur.)

Instrument-Automation Conference and Show, Philadelphia, U.S.A. .....Sept. 15-19
(Instrument Society of America, 313 Sixth Ave., Pittsburgh 22, Pa.)

International Symposium on Nuclear Electronics, Paris, France .....Sept. 16-20
(Société des Radioélectriciens, 10 av. Pierre-Larousse, Malakoff (Seine).)

International Radio-Television-Electronics Fair, Amsterdam, Netherlands..Sept. 22-29
(H. J. Kazemier, Emmalaan 20, Amsterdam Z.)

Irish Radio and Television Show, Mansion House, Dublin, Eire .....Sept. 23-27
(*Irish Radio & Electrical Journal*, 14-15, Dame Street, Dublin, Eire.)

British Components Exhibition, Stockholm, Sweden.....Sept. 29-Oct. 3
(R.E.C.M.F., 21 Tothill Street, London, S.W.1.)

I.R.E. Canadian Convention and Exposition, Exhibition Park, Toronto.....Oct. 8-10
(Grant Smedmor, 1819 Yonge Street, Toronto 7, Canada.)

National Electronics Conference, Chicago, U.S.A.....Oct. 13-15
(N.E.C., 84, East Randolph St., Chicago, Ill., U.S.A.)

International Radio and Telecommunications Fair, Ljubljana, Yugoslavia..Oct. 31-Nov. 9
(Gospodarsko Razstavisce, Titova 48, Ljubljana.)

Conference on Magnetism and Magnetic Materials, Philadelphia, Pa., U.S.A. Nov. 17-20
(C. J. Kriessman, Remington Rand Univac, 1900 W. Allegheny Ave., Philadelphia.)

Sound Perfect

When planning your Sound System you can rely on TRIX for speakers and microphones.

The new Sound Columns give a marked directional flat beam effect, with striking improvement in acoustic efficiency and economy in installation.

Both the microphones shown have wide frequency range and are also available with switches.

Write now for latest detailed literature.

TRIX

TRIX ELECTRICAL CO. LTD.
Maple Place, London, W.1
Telephone MUSeum 5817

RANDOM RADIATIONS

By "DIALLIST"

Repaired C.R.T.s

MY best thanks to the numerous readers who have kindly written to tell me of their experiences with repaired c.r. tubes. Without exception, their reports are favourable—provided that the work is expertly done by a well-equipped firm. A good many of those who wrote are wireless and television dealers. One said that he has been having tubes repaired during the past three years by the firm whose methods and equipment were described recently in *Wireless World*. "In that time," he wrote, "I have had all makes repaired and have received wonderful service from the tubes. In my opinion they are as good as new ones and so far as I know most of those I had repaired so much as three years ago are still going strong." Another wrote that the only trouble he had ever had concerned a tube which developed a cathode-heater short within six months. "But that," he said, "was put right without question under the guarantee and is still giving good service after 12 months' use." Well, you can hardly say fairer than that, can you? With c.r.t.s costing what they do, the call for re-gunning services is bound to increase. My only fear is that mushroom firms without the necessary equipment or knowledge will spring up with the idea of making money while the going's good.

A Cathode-Grid "Short" Tip

A Scottish dealer sends me an interesting tip for coping with cathode-grid shorts. "Except in the case of triode c.r.t.s," he writes, "the fault can be successfully overcome by strapping the grid permanently to the cathode." The boost h.t. supply is then disconnected from the first anode, to which the lead previously going to the grid is connected. This done, the first anode is used as a control grid and the tube, now converted into a triode, works, he claims, quite satisfactorily. Some adjustment of the focusing and ion-trap magnet and of the brilliance control will probably be found necessary. "When this has been done the picture is very nearly as good as it was before the short developed." I can't claim to have tried out the suggestion, for I don't possess a c.r.t. with a cathode-heater short. But it's certainly an ingenious idea, and I'd be glad to hear from anyone else who has put it into practice with success.

Colour Television

THE B.B.C.'s report on its colour television tests carried out up to the spring of last year shows that on the whole these have been very satisfactory and that results are promising. Myself, I hope that when a colour TV service comes it will break away completely from the 405-line, or 625-line standards, and won't bother its head about compatibility. My idea is that colour television should take place in, say, Band V and that the black-and-white pictures with the 405-line standard should continue to use Bands I and III. If the same programmes were broadcast in colour as in black and white, there'd be no hardship to anyone. Existing receivers could continue to be used in Bands I and III until their owners felt inclined (or could afford) to go in for colour sets. In Band V a standard of the order of 1,000 lines could be adopted and then we'd have some really fine colour pictures. With the smaller rooms of modern homes an increase—a big increase—in the number of lines would be a very great advantage. It's often not easy to sit far enough from a 17-in screen (to say nothing of a larger one) to get rid of lininess; and it seems that the man-in-the-street doesn't care about spot wobble or spot astigmatism. If only more of our folk could see the beautiful French 819-line pictures, with their freedom from lininess even on 21-in and 24-in screens, I'm sure there'd be a demand that when colour comes its transmissions should be of an equally high order of definition.

Why Valves?

PROFOUND as is my respect for W. T. Cocking's erudition in the realm of electronics, I must join issue with him when he accuses me of falling into "the common error of supposing that the word 'valve' means only a one-way device." *Pace* W. T. C., the idea couldn't be too common, for it really isn't an error. This he would have found had he consulted a large reference book such as the Shorter (not the Concise) Oxford English Dictionary, which runs to 2,494 large pages. Coming from the Latin *valva* (one leaf of a double door), it is quoted as having been used to denote a sluice. After the discovery of the circulation of the blood the name "valve" was given to "a membrane or fold in veins, arteries or the heart, which close to prevent any reflux of the blood." Similar arrangements, again called valves, were at one time believed to

ASSOCIATED ILIFFE TECHNICAL BOOKS

"WIRELESS WORLD" PUBLICATIONS

	Net Price	By Post
LOW-COST HIGH-QUALITY AMPLIFIER. P. J. Baxandall, B.Sc.(Eng.)	3/6	4/-
INTRODUCTION TO VALVES. R. W. Hallows, M.A.(Cantab.) and H. K. Milward, B.Sc.(Lond.), A.M.I.E.E.	8/6	9/4
ABACS OR NOMOGRAMS. A. Giet. Translated from the French by H. D. Phippen and J. W. Head	35/-	36/-
TELEVISION RECEIVING EQUIPMENT. W. T. Cocking, M.I.E.E. 4th Edition	30/-	31/9
TRANSISTOR A.F. AMPLIFIERS. D. D. Jones, M.Sc., D.I.C., and R. A. Hilbourne, B.Sc.	21/-	21/10
LONG-WAVE AND MEDIUM-WAVE PROPAGATION. H. E. Farrow, Grad. I.E.E.	4/6	4/10
RADIO LABORATORY HANDBOOK. M. G. Scroggie, B.Sc., M.I.E.E. 6th Edition	25/-	26/9
BASIC MATHEMATICS FOR RADIO AND ELECTRONICS. F. M. Colebrook, B.Sc., D.I.C., A.C.G.I. Revised and enlarged by J. W. Head, M.A.(Cantab.). 3rd Edition	17/6	18/6
FOUNDATIONS OF WIRELESS. M. G. Scroggie, B.Sc., M.I.E.E. 7th Edition	15/-	16/4

A complete list of books is available on application

Obtainable from all leading booksellers or from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1

exist in plants to prevent a backward flow of the sap. In mechanical uses the dictionary defines the word as "a device of the nature of a flap, lid, plug, etc., applied to a pipe or aperture to control the passage of air, steam, water and the like, usually acting automatically by yielding to pressure in one direction only." I can't offhand think of any true valve, anatomical, hydraulic, pneumatic or mechanical which doesn't serve as a one-way controller.

Inadequate

But my chief objection to the use of "valve" to denote a "bottle" containing three or more electrodes is that it is almost as inadequate as the French "lampe" or the American "tube." Surely the outstanding feature of triodes, pentodes and so on is their ability to amplify. It is on this account that simple tubes can also be made to act as oscillators. I'd like to see a name adopted which did more than refer to just the unidirectional current-controlling powers of one of the most useful inventions that Man has ever made. The Fleming diode was called a valve because, like the crystal detector (though this doesn't entirely prevent reflux), it allowed current to flow in one direction only. The name was passed on to Lee de Forest's triode and its successors and, despite its hopeless inadequacy, it has stuck. Can't we find a worthier and more descriptive name? Or has its use now become so firmly rooted that nothing will change it? I'm rather afraid that that's the case.

The Doppler Cop

THE new Marconi radar speed checking equipment, which makes use of the Doppler Effect, is most ingenious and if it becomes widely adopted by the police, I can foresee that some of our "sporty boy" motorists will have to watch their speedometers while driving on roads where there's a speed limit. PETA (portable electronic traffic analyser) uses a very narrow horizontal beam. It can give separate readings on vehicles as little as eight feet apart and can be made to lock automatically on to any selected target. Accuracy of better than ±1 m.p.h. is claimed. PETA has other possible uses besides aiding the traffic cop. A camera attachment will soon be available and an analyser unit. Using these gadgets it will be possible to record the speed and traffic density at any point of a road at such periods as may be desired.

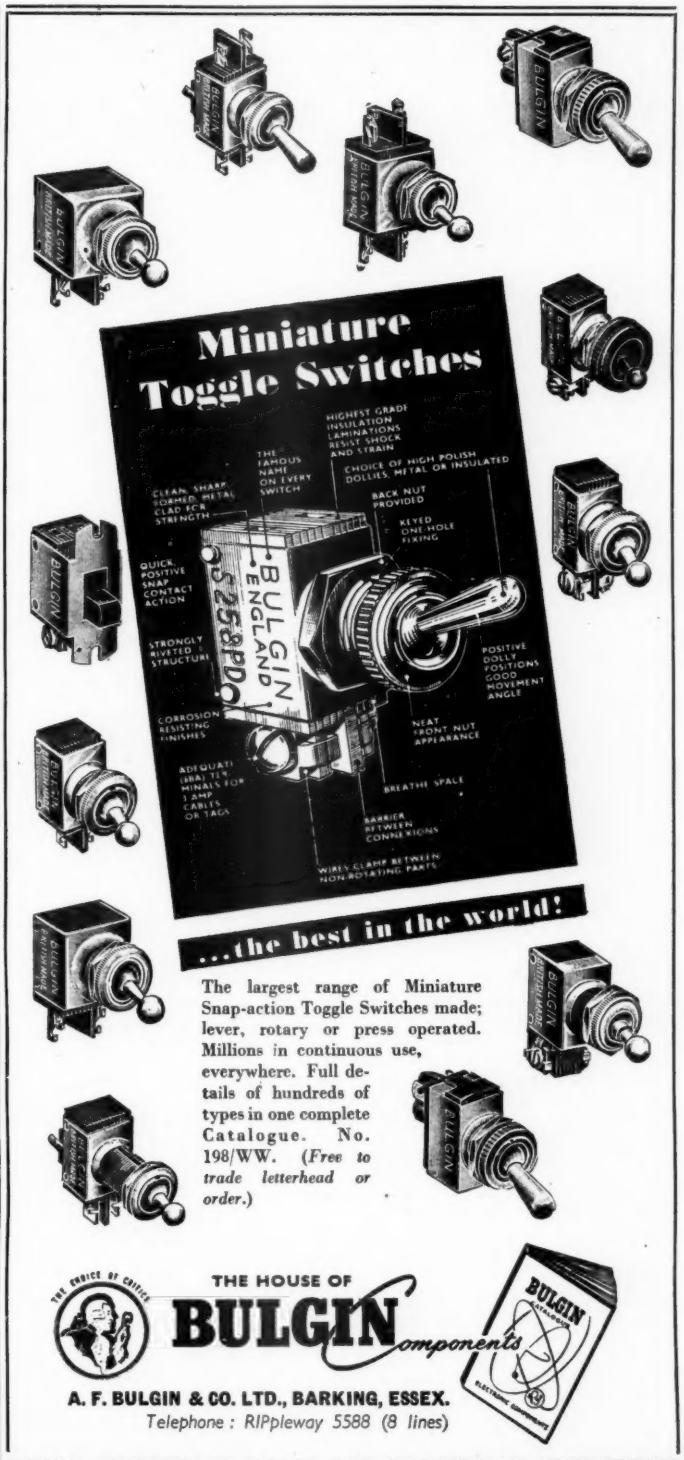
Miniature
Toggle Switches
THE FAMOUS NAME ON EVERY SWITCH
HIGHEST GRADE INSULATION LAMINATIONS RESIST SHOCK AND STRAIN
CHOICE OF HIGH POLISH DOLLIES, METAL OR INSULATED
CLEAN, SHARP FORMED METAL CLAD FOR STRENGTH
BACK NUT PROVIDED
KEYED ONE HOLE FIXING
QUICK POSITIVE SNAP CONTACT ACTION
STRONGLY RIVETED STRUCTURE
BULGIN ENGLAND S25PDO
POSITIVE DOLLY POSITIONS GOOD MOVEMENT ANGLE
CORROSION RESISTING FINISHES
NEAT FRONT NUT APPEARANCE
ADEQUATI (BRASS) TERMINALS FOR 3 AMP. CABLES OR TAGS
BREATHE SPACE
BARRIER BETWEEN CONNECTIONS
WIRES CLAMP BETWEEN NON-ROTATING PARTS
...the best in the world!
The largest range of Miniature Snap-action Toggle Switches made; lever, rotary or press operated. Millions in continuous use, everywhere. Full details of hundreds of types in one complete Catalogue. No. 198/WW. (Free to trade letterhead or order.)
THE CHOICE OF CRITICS
THE HOUSE OF
BULGIN components
A. F. BULGIN & CO. LTD., BARKING, ESSEX.
Telephone: RIPpleway 5588 (8 lines)
MANUFACTURERS OF RADIO AND ELECTRONIC COMPONENTS

UNBIASED

By FREE GRID

The Debagged Wavelengths

IN an article in the July issue describing a wavemeter for use on the "ultra-shorts," H. B. Dent calls attention to the fact that he designed a similar instrument 23 years ago which was also for "ultra-shorts," but this arbitrary expression then meant an order of wavelengths 10 times longer than it does today.

It would not surprise me if he designed another such instrument 23 years hence but I very much doubt whether the "ultra-shorts" of those future days will be only a mere 10 times shorter than they are now. We seem to be rushing down the slippery slope of wavelength shortness so rapidly nowadays that in 23 years' time the "ultra-shorts" will be so short that they may well be called the debagged wavelengths.

Thus in 1981, the five metres of 1935, which became the five decimetres of 1958, will not have become five centimetres nor yet five millimetres. As I see it, the techniques of radio communications in 1981 will have changed so radically that wavelengths will have descended far below that part of the spectrum occupied by heat and light and we shall be measuring our wireless wavelengths in micro-Angstrom units.

It is all very well for so-called experts to point out to me that such wavelengths would be impracticable for use in radio communication. I seem to remember hearing the same thing about 100-metre wavelengths in 1920 or thereabouts.

Outward Bound

SCIENCE fiction has been with us for a very long time even if we go back only to the days of Jules Verne. Since the end of the last war the writing of it has become a major industry, especially in the U.S.A.

I have often thought of trying my hand at it myself as it seems to be very remunerative, but unfortunately for me it needs a quality in which I am singularly deficient, namely, a very lively imagination. Also, judging by the efforts of certain American science-fiction writers, it does not seem to be necessary to stick too closely to the rules of science, and that would go against the grain with me.

Naturally, our own science of electronics and wave propagation plays a large part in the type of literature under discussion; in fact it plays the major part, and that is the only excuse I have for discussing science fiction in these columns.

Many writers of science-fiction stories use a very large canvas in that a recurrent theme is a journey to a distant planet or star by space ship. There are even stories in which a journey is being made to a very distant star which it would take many centuries to reach, so that provision has to be made on the space ship for generation after generation to be born and die of old age during the period of travel. Despite this, the thought never seems to have occurred to the writers of these stories, as it has to me, that the whole cosmos of stars, including our own solar systems with its inhabited earth, is merely a cluster of giant space ships which started on its journey many thousands of millions of years ago. For evidence it is only necessary to study the writings of the late Sir James Jeans—to say nothing of Mr. Fred Hoyle—about the expanding universe.

Apparently all the stellar systems, including our own, are receding from each other at high speed which suggests to my mind that they are flying fragments of a cosmic explosion. What does this suggest but a cosmic accident which occurred long ago when the universe was indeed one body as its name implies, and not merely the mass of fleeing fragments it is to-day?

Probably the inhabitants of the original universe reached a very high degree of scientific knowledge but a moment's carelessness on the part of a trigger-happy physicist, showing his blonde around the laboratory, led to a nuclear explosion of unparalleled intensity and the fragments are still flying asunder. Only in recent æons has life started to reappear on some fragments, including the earth.

When, how and where will the journey end? What a subject for a science-fiction writer!

Stereo or Anti-Stereo?

IT is getting increasingly difficult to know whether we are coming or going in the matter of stereophonic reproduction. No sooner do I tell you (July issue) that, if we are to believe the best authority, stereo will be impracticable in my humble living-room owing to the large amount of space required, than a well-known manufacturer leads me to believe the opposite.

Pye Group Records have done this by bringing out an arrangement whereby the public can listen to stereo discs in the necessarily confined space of a record dealer's listening booth. I have seen a photograph of it complete with its two loudspeakers, but unfortunately it is not to be sold to the public despite the fact that it ought to sell like hot cakes.

I have not yet had an opportunity of testing this arrangement on a dealer's premises, but a superficial examination of the photo I have seen might lead an untutored ignoramus like myself to suppose that it tended to blend the sound rather than the opposite, somewhat in the same manner as did those famous male-voice quartets of Victorian days.

Anti-stereophonists in 1889.

Maybe most of you are too young to have heard one of these anti-stereophonic quartets and so I have tried in the accompanying sketch to show how they *looked*. With regard to how they *sounded* I can only say it was the very reverse of stereophonic. Their object was to blend the sound or, as a musician would say, to obtain a good ensemble, a very important thing in harmony.

I'm sure this new close-quarters stereo listening arrangement isn't like that and I am looking forward to hearing a demonstration.

Mechanizing Art

IT IS reported in the press that at the National Gallery in Washington visitors who want to know something about the pictures they are looking at can hire a pocket wireless set with earphones which enables them to pick up a commentary made by the Director of the Gallery or one of his assistants.

This is a praiseworthy effort but there is nothing new in the basic idea. Well over twenty years ago I reported in these columns (27.12.35) that I had been in a picture gallery in Prague in which a commentary was given on any picture by a concealed loudspeaker immediately a visitor stopped in front of it. The commentary was a recorded one, the mechanism was set in motion by a visitor cutting an invisible ray as he took his stance in front of the picture.

This American idea is an improvement in many ways but no mention is made of the provision of recorded commentaries in several languages using a separate channel for each language. I suggested an improvement of this kind in my original pre-war note on the Prague installation.

NEW

LEAK

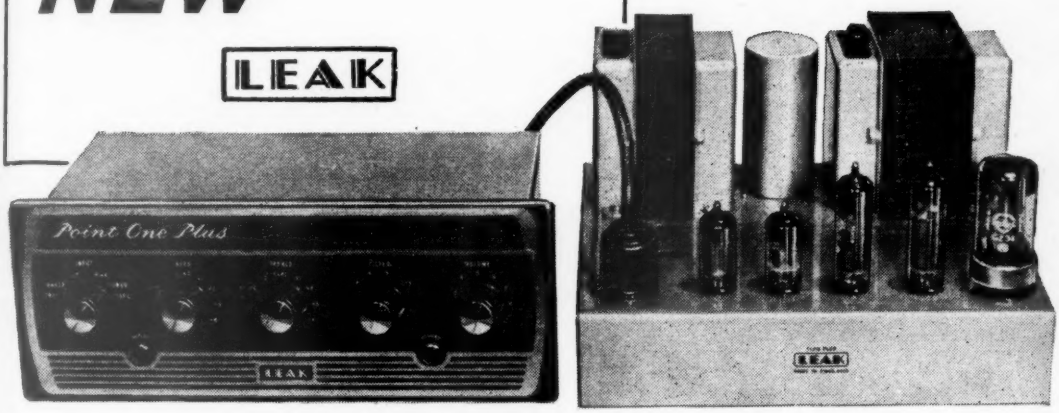

"Point One Plus" Pre-amplifier TL/12 Plus Power Amplifier

★

Make this THE HEART of your Hi-Fi EQUIPMENT

Styled by the world-famous designers
RICHARD LONSDALE-HANDS ASSOCIATES

Designed by HAROLD J. LEAK to give OPTIMUM RESULTS from:—

Any pick-up available in the world.
Any tape recorder/reproducer available in the world.
Any radio tuner available in the world.
Any dynamic microphone available in the world.

★

30 GNS
COMPLETE

A price made possible only by WORLD-WIDE SALES

The Point One Plus pre-amplifier and TL/12 Plus amplifier, when used with the best available complementary equipment, give to the music-lover a quality of reproduction unsurpassed by *any* equipment at *any* price. Even when the complementary equipment falls below that of the best obtainable, the use of these amplifiers will enable one to obtain very marked improvements in reproduction.

The new Point One Plus and TL/12 Plus were exhibited and demonstrated at the New York Audio Fair and received enthusiastic consumer acceptance resulting in initial orders for one thousand one hundred and fifty sets.

LEAK amplifiers have been the choice of the B.B.C. (over 500 delivered), the South African Broadcasting Corporation (600), I.T.V. and many other Commonwealth and overseas broadcasting and TV systems, who use them for transmitting and/or monitoring (quality checking) the broadcasts to which you listen. Also, many of the gramophone records you buy are cut via LEAK amplifiers. This acceptance by professional audio engineers has led to a demand for LEAK equipment from music-lovers throughout the world.
It is appropriate here to mention one of the basic principles of LEAK design. From long experience and by extreme attention to design details during development work on the pre-production models, we enable our craftsmen to achieve a high output per man-hour. The labour costs thus saved offset the increased costs incurred for high-grade materials, components and finishes, and this together with quantity production (made possible only by a world-wide market) explains how quality products may be sold at reasonable prices.

LEAK *The First Name in High Fidelity*

H. J. LEAK & CO. LTD., BRUNEL ROAD, WESTWAY FACTORY ESTATE, LONDON, W.3, ENGLAND

Telegrams: Sinusoidal, Ealux, London
Telephone: SHEpherds Bush 1173/4/5 Cables: Sinusoidal, London

Please send details of

- ☐ *FM Tuner*
- ☐ *Amplifiers*
- ☐ *Gram. pickup*
- ☐ *Name and address of my nearest Hi-Fi dealer*

Name .....

Address .....

.....

WW/8/58

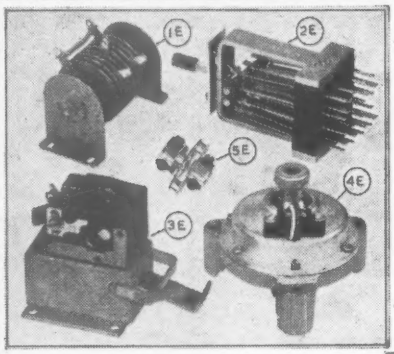

1E. Rectifier 36 v. ½ amp. for energising relays etc., **8/6.**

2E. Key Switch Muirhead 4 change up, 4 change down reference No. C-404-C, **12/6.**

3E. Cabinet safety switch double pole 15 amp. Switches off as door opens, **8/6.**

4E. Electrical brake disc type, for stopping lathes, coil winders etc. Operates on approximately 100MA, **25/-.**

5E. Flexible spindle coupler/insulator for ¼in. spindles, **2/6.**

6E. Instrument type slow motion drive with locking device, **8/6** complete.

7E. Chrome plated instrument handles, **8/-** pair.

8E Bakelite connection strip 16 way, **3/6.**

9E. Indicator lamp for panel mounting, **2/9.**

10E. Ganged wire wound pot value 25K ohms and 25K ohms, **6/-.**

11E. Bakelite mount for 2in. plug-in meter **6/-.**

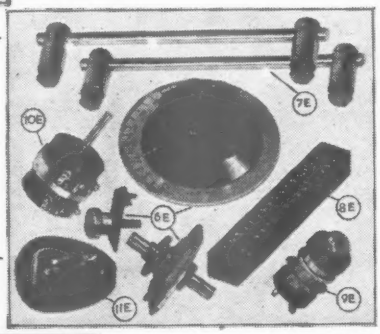

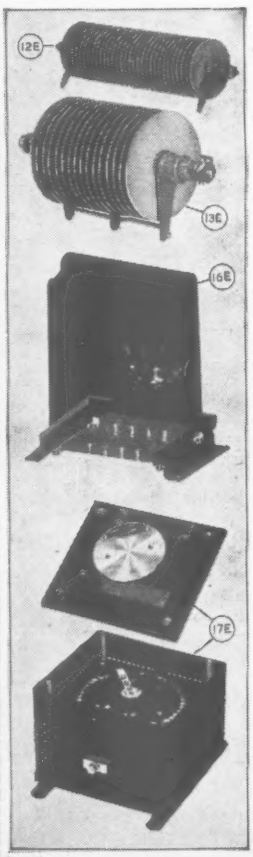

12E. Selenium Rectifier 500 v. ½ amp. half wave easily rebuilt into full wave or multiple type—contain 31-45 mm. discs, **10/-** each.

13E. Selenium Rectifier 36 v. 6 amp. full wave, easily rebuilt will make four 12 v. 3 amp. full wave charging rectifiers, **17/6.**

14E. Instrument transformer primary 230 v. secondaries: 6.3 at 3/4 amp. and 2 of 85 v. at 10 mA. **8/6**, plus 1/6 p. & p.

16E. Parmeko Audio transformer 4,000 ohms centre tapped primary, 100 ohm secondary **17/6** plus 2/6 carriage and insurance.

17E. Dimmer or Regulator
Total resistance 1,000 ohms maximum current of .59 amps. This is a beautiful unit which uses a 32 position stud switch, resistance is divided into 31 sections each approx. 30 ohms. In ventilated metal case, size approx. 7in. × 7in. × 5½in. with wall mounting brackets and large control knob, **15/-** plus 2/6 post and insurance.

18E. Remote Control Contactor
Double pole, rated for 30 amps. D.C. but suitable for much higher current on A.C. magnetic arch blowouts and asbestos arch shields. Coil wound for 230 v. D.C. but take turns off and it will be suitable for A.C. or if you prefer, work off A.C. with rectifier. Many applications such as remote switching of motors, banks of lamps, banks of heaters, etc., etc. Energising coil can be operated off Thermostat, Toggle Switch, Push Button or our vacuum delay switch. Size overall is 10in. x 8in. x 4½in. Original cost probably over **£5**, our price **27/6** each plus 3/6 carriage and insurance.

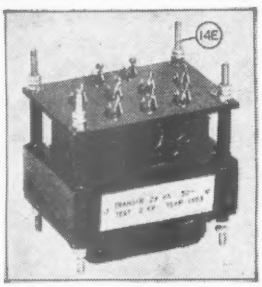

15E. Instrument switch multi contact, **12/6.**

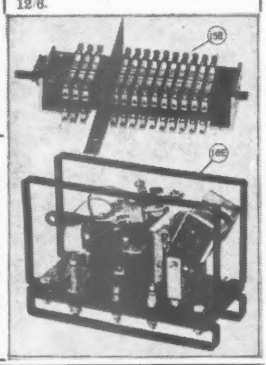

We wish to remind customers that with the new postage rates the minimum postage on a parcel is now 1/6. Orders for lightweight items which total over **£3** will be sent post free, otherwise sufficient must be included to cover postage. Also where a postage and insurance figure is specifically mentioned then this must be included regardless, as these items have to be sent separately.

Summer Sale

7 Valve 5 Waveband Superhet Chassis. H.F. stage and magic eye. Unused but may be slightly soiled and need servicing—less valves, power pack and tuning scale. Contains really fine coil pack which alone would cost twice what we are asking for the whole unit. Price with circuit diagram **£2/15/-.** Carriage and insurance 7/6.

4 Valve Superhet Chassis. Long and medium wave complete with valves but not scale. Unused but slightly soiled and may need servicing (no data available), **29/6,** plus insurance 3/6.

10 Valve Superhet. 1½ metre ex Government but unused, complete with valves, easily converted for Band III, **39/6** carriage and packing 7/6.

Isolation Transformer 150 watt, mains in, isolated mains out, makes servicing safe. **29/6.**

Filament Transformer. 6.3 volt 3/4 amps., tapped primary, **8/6.**

Transistor. Suitable A.F. or low R.F., new tested, O.K. most circuits, **6/6.**

Midget Output Transformer. Standard pentode matching, **4/6.**

Midget Output Transformer special for battery sets, pentode matching, **4/6.**

14in. T.V. Cabinet by famous maker, cost over £4 to make, new and perfect, **15/-,** carriage 4/6.

Metal Rectifier, 250 v. 60-80 milliamps, ideal for mains set or instrument or to replace that expensive valve, **4/6.**

Constructors' Parcel, 5 valve superhet, chassis, 15 x 15 x 2 with three waveband glass scale, pulleys, drive head etc., **9/6,** plus post and insurance 1/6.

Toggle Switch, standard metal body type with round dolly, fixing ring and on/off indicating plate, **1/3** or **12/-** doz.

Weymouth Coil Pack, long, medium and two short, **19/6.**

Thin Paxolin Panels, size 8in. x 5in., 2/6 dozen.

Midget I.F. Coils. 465k/c. but with feed back winding for economy circuits, **6/6** pair.

Mains Transformer standard 230 v., input, 250-0-250 at 80 mA., 6.3 v. at 5 mA., **12/6.**

Out of Season Bargain. Enough waterproof heating element to make an average size blanket, normally sold at 15/-, price complete with illustrated data **9/6.**

50 Assorted Resistors, well mixed and useful values ¼ and ½ watt, **5/-** for 50.

Ditto but 1 watt, **6/6** for 50.

.1 mfd. 350, small tubular metal cased condensers made by Dubilier, **2/6** dozen.

Loudspeaker 8in. energised field, **9/6,** carriage 3/6.

Welding Transformer 12 v.-50 amp. continuous rating, intermittent rating for spot welding, exceeds 2,000 amps., **45/-,** carriage and packing 5/-.

Metal Rectifier equivalent of RM5 250 mA. 250 v. **12/6.**

Cathode Ray Tube VCR517 **7/6,** carriage etc. 3/6.

Thermal Delay Vacuum Relay with book of interesting circuits, **6/6.**

Connecting Wire P.V.C. covering all colours, sale price **2/6** 100ft. coil or 5 coils different colours **10/-** lot.

6ft. unbreakable Mains Lead. Type of lead fitted to electric razors, makes fine lead for test meters and any other devices where subject to continuous bending. Twin figure eight construction, soft cream P.V.C. covered. Normally costs 2/- per yard, we offer three leads for 2/-.

Auto Transformer. Totally enclosed, primary 200/250 v., secondary 110/120 v. rated 200/250, **27/6,** carr. & ins. 2/6.

Screened Cable. Rubber covered flexible with metal brading, ideal for microphone or gramophone extension. **4d.** per yd. **30/-** per 100 yds.

Cabinet with Chassis Bargain

is a fine walnut veneered table receiver cabinet complete with metal chassis, three colour glass scale, back plate and scale mounts, as illustrated but less knobs. Offered at less than the price of the cabinet, namely **39/6** plus 5/- carriage and insurance.

Medresco Hearing Aid

As supplied by National Health, completely overhauled and in good working order with six months' guarantee. Only **£2/15/-** plus 2/6 post and ins. Complete with earphone and *new* ear plug but not batteries, these can be supplied as an extra for 5/- per set.

Instructions showing how to convert to pocket radio available free if requested.

Now Two Models Turret Tuner

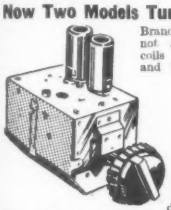

Brand new stock not surplus, with coils for Band I and III, complete with valves. Model I.—I.F. output 33/38 mc/s. Series heaters. Model II.—I.F. output 16 - 19 mc/s. Parallel heaters with circuit diagram, **79/6**.

With knobs 3/6 extra, post and ins. 2/6.

Yours for 10/- down and 17 weekly payments of 10/- or cash price £8.10.0

The latest, most up-to-date Record Player made by the famous B.S.R. Company. Using Hi-Fi Crystal Pick Up and fitted with every modern device. Definitely a record changer which will give years of trouble-free music. Not surplus but the current model. Price **£8/10/-** or **10/-** deposit and 17 weekly payments of **10/-**, carriage and insurance 5/-.

Sub-Miniature Electrolytics

These are extremely small—for instance, 1 mfd. is only approx. ¼in. long by a little over ¼in. diameter. Mainly developed for transistor receivers, price **2/9** each. Special quotes for quantities. The following values available but additional types are being added almost weekly. 1 mfd. 18 v., 1¼ mfd. 6 v., 2.5 mfd. 6 v., 6 mfd. 6 v., 5 mfd. 12½ v., 8 mfd. 6 v., 10 mfd. 6 v., 16 mfd. 12 v., 25 mfd. 6 v., 25 mfd. 25 v., 32 mfd. 3 v.

TV Masks

Latest type grey crystallate

14in., **10/-**, 17in., **12/-**.

Plus 1/- Post.

Short Wave Communications Receiver R.208 for 10/- Deposit and 14 weekly payments of 10/-, or Cash Price £6/19/6.

This is a super short-wave receiver covering 5-30 metres (10-60 Mc/s). Uses 6 valves. Has R.F. stage, 2 I.F. stages, B.F.O., etc. Muirhead instrument drive, two internal power packs, mains and battery vibrator pack. Complete with own P.M. speaker. Provision for phones and speaker muting. Complete in metal transit case; size approx. 24 × 18 × 12in.; weight 70lb. Suitable A.C. mains 100-250 and 6 volt battery. In perfect condition, practically unused. Tested before despatch and guaranteed. Handbook free with each. Price **£6/19/6**, carriage and insurance 15/-. Or **10/-** deposit plus 15/- carriage and ins. then 14 weekly payments of **10/-** each.

Famous Transmitter Virtually Given Away

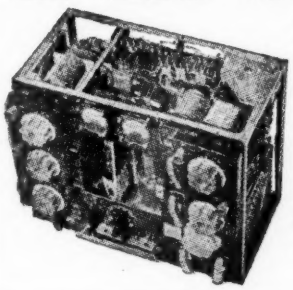

The famous R1154M—unused but slightly soiled and not tested. Covers 200-500 Kc/s, 3-5.5 mc/s. and 5.5-10 mc/s. Has unique "click stop" mechanism (7 stops) and permits selected frequency to be held, returned to, etc. Hartley oscillator, power amplifier, keying and speech. Wonderful breakdown value meters, relays, switches. Complete with valves—real bargain at **29/6**, plus 10/- carriage.

THIS MONTH'S SNIP

Multi-Purpose Mains Transformer

Heavy duty construction, must have cost at least £3 to make. Offered at a snip price of **14/6**.

Specification:—

Primary	Standard 230 v.; 50 c.p.s. screen to sep. terminal.
Secondary 1.	660 v.-200 mA. centre tapped.
Secondary 2.	80 v.-100 mA.
Secondary 3.	23 v.-750 mA.
Secondary 4.	7 v.-5 amp. centre tapped.
Secondary 5.	5 v.-3 amp.

In addition to the above secondaries there is a window space which will allow extra L.T. windings to be put on. The winding ratio is 2½ turns per volt. Weight of transformer is 12 lb., size approximately 6in. × 4¼in. × 4¼in. Connections all brought out to terminals on bakelite panel. We have only 500 of these, so order at once to avoid disappointment. Non-callers add 3/6 postage please.

Super Sensitive (2,000 O.P.V.) Multimeter Kit

17 ranges including D.C. volts to 1,000 volts, A.C. to 1,000 volts, D.C. milliamps to 500, ohms to 2 meg., capacity and inductance. All the essential parts including metal case, selected resistors, wire for shunts, selected switches, calibrated scale and instructions, **32/6**, plus 2/6 post and insurance.

Tabby Equipment complete

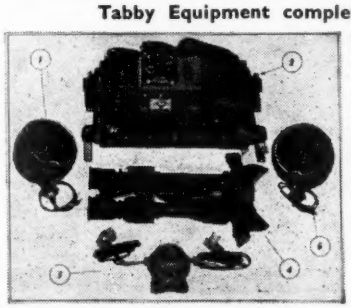

Complete equipment for seeing in the dark, as fitted to Army vehicles for night driving, etc. Complete working equipment comprises: 2 Infra Red Radiators, adjustable binoculars, powerpack for 6 or 12 volts, control units and interconnection cables. Original cost probably around £100. Unused and in perfect order—**£10** plus 10/- carriage and insurance. Mains power pack 44 extra.

Like all AVO mtters it is a very fine instrument; it has a sensitivity of 10,000 ohms per volt and 19 most useful ranges as follows:—D.C. volts 0-1,000 (seven ranges). A.C. volts 0-1,000 (five ranges). D.C. Current 0-1 amp. (5 ranges), resistance 0-2 mega. (2 ranges) (complete with test leads). Immediate delivery. **Cash** price **£9/10/-** or **10/-** deposit and 19 weekly payments of **10/-**.

FREE GIFT.—All purchasers of the above item this month will receive the M.M. Range Extender Scale and data which adds: capacity 0.1 m.r. in two ranges—inductance 0-100 henrys, etc., etc.

Charging Switchboard

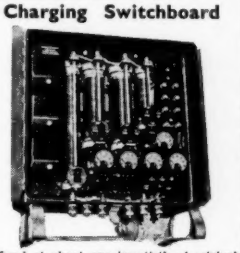

Offered at about one twentieth of original cost. This is an ex Government switchboard. It contains three reverse current relays, one voltmeter, one main ammeter, two secondary ammeters and three variable resistors for controlling circuits. These are original cases. Price **£2/15/-**. Carr. 10/-.

Band III Converter

Suitable Wales, London, Midlands, North, Scotland, etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers, and resistors. (Metal case available as an extra). Price only **19/6**, plus 2/6 post and insurance. Data free with parts or available separately **1/6**.

Unused and Boxed Valves

American list, others in stock. Send us your enquiry or order C.O.D.

1A4	9/-	6C4	6/6	6TH8	12/-
1A6	9/-	6C6	6/6	6U5	8/6
1D6	12/6	6C8	5/-	6V6	9/6
1C5	12/6	6D6	6/6	6X5	7/6
1D7	9/-	6F5	9/6	6Z5	15/-
1F6	12/6	6F6	7/6	7A7	9/6
1H5	10/-	6F8	9/6	7C7	9/6
1LD5	3/6	6G6	7/6	7V7	9/6
1T4	7/6	6H6	2/6	7Y4	8/6
1R5	7/6	6J5	5/-	25Y5	10/-
1S5	7/6	6J7	6/-	25Z4	9/6
1T5	8/-	6K6	7/-	25Z6	10/6
2A5	12/6	6L5	9/-	27	10/-
2A6	12/6	6L6	9/-	28D7	3/6
2A7	12/6	6L7	10/6	36	10/-
2X2	4/6	6N7	8/6	39/44	10/-
3A4	7/-	6P8	9/-	41	9/6
3D6	7/-	6Q6	9/-	42	8/-
3B4	8/-	6Q7	9/-	43	10/-
3V4	9/-	6R7	9/-	57	10/-
5Y3	8/-	58A7	8/-	58	10/-
5R4	9/6	68C7	9/-	71	9/6
5U4	8/-	68H7	6/-	75	12/6
5Z3	15/-	68J7	8/6	78	8/6
5Z4	9/6	68K7	6/-	84	8/6
6A7	12/6	68L7	8/-	89	12/-
6A8	10/-	68N7	7/6	807	6/6
6B4	5/-	68Q7	9/-	1625	10/6
6B8	4/-	68S7	9/-	954	3/6

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66 Grove Road Eastbourne, marked Department 2.

42-46, Windmill Hill, Ruislip, Middx. Phone: RUISLIP 5780. Half day, Wednesday.

66, Grove Road, Eastbourne, Sussex. Half day, Saturday.

29, Stroud Green Rd., Finsbury Park, N.4. Phone: ARChway 1049. Half day, Thursday.

226, London Road, Croydon. Phone: CRO 6558. Half day, Wednesday.

XUM

CLYNE RADIO LTD.

162, HOLLOWAY ROAD, LONDON, N.7

NORth 6295/6/7

ALSO AT :—18, TOTTENHAM COURT ROAD, LONDON, W.1.

MUSeum 5929/0095

(50 yards only from Tottenham Court Road Tube)

All post orders and correspondence to 162, HOLLOWAY ROAD, LONDON, N.7

TRANSISTORS !!!

SURPLUS—P.N.P.

RED SPOT (Audio/Experimental Applications) ..... 7/6 ea.
WHITE SPOT, R.F. up to 2.5 Mc/s. ..... 15/- ea.

STANDARD—

BRIMAR
T.S.1. ..... 18/- ea.

MULLARD
OC16 Power 3 watt ..... 60/- ea.
OC45 R.F. up to 6 Mc/s. ..... 35/- ea.
OC70 ..... 21/- ea.
OC71 ..... 24/- ea.
OC72, matched pair 60/-

PYE
V6/R2 R.F. up to 4 Mc/s. ..... 24/- ea.

(ALL POST FREE)

COLLARO MK. IV TAPE TRANSCRIPTOR LIMITED STOCKS ONLY

Subject to being unsold. £25. Plus 7/6 C. & r. Pre-amplifier and power pack for use with the above deck is also available in limited quantity at £31. Plus 3/6 P. & P. Wired to transcriptor £1/10/- extra. H.P. or credit sale terms available.

PORTABLE GRAM AMPLIFIERS

RC1.A AMPLIFIER. A small high-quality gramophone amplifier employing the latest circuitry and highly efficient miniature valves. Very neat chassis finished in bronze stove enamel. Size (overall) 5½ × 4 × 5in. Valve. 6X5, ECL82. Output 3 watts max. Controls. Volume. Tone/On/Off. For use on AC mains 200/250 v. Price £3/19/6 plus 2/- P. & P.

RC2A. Small PRINTED CIRCUIT single-valve high-gain amplifier for the smaller type of portable. Employs latest type ECL82 valve. Further details on request. Price only 59/6 plus 2/- P. & P.

RC3A. A superior quality 3-valve amplifier employing EZ80, EL84 and ECC83. With separate bass and treble controls. Further details on request. Price £3/19/6 plus 2/6 P. & P.

RC4.A (STALLION). This is supplied complete with high flux 8in. P.M. Speaker and Baffle. Incorporating three octal type valves 6Q7, 6V6 and 6X5, this robust and well-made unit is ideal for use in the larger type of record player and is equally suitable for use in conjunction with a radio feeder unit. Separate bass and treble controls are provided: also provision is made for an extension speaker and mains supplies to gram. motor. Output approx. 4 watts. Size overall 13in. × 4in. × 9in. high. For use on A.C. mains 100/200/250 v. Set of 3 engraved knobs in cream or brown 4/- extra.

PRICE £5/19/6 plus 2/6 P. & P. H.P. terms £2/19/6 deposit and four monthly payments of 16/6.
Fits our portable cabinet "G" at 85/- without modification.

MULLARD 3-3 HI-FI AMPLIFIER to Mullard spec. Assembled tested, fully guaranteed. £8/8/- plus 3/6 P. & P. Leaflet on request.

MULLARD 510 HIGH FIDELITY AMPLIFIER

We are proud to be able to offer our printed circuit version of this excellent amplifier, with ULTRA-LINEAR PUSH-PULL output stage, giving an exceptionally high quality output of 10 watts (max.). Built-in Controls are provided for independent bass and treble Tone correction to suit all types of signal input. Will match all crystal or high impedance magnetic pick-up heads, F.M., A.M. or A.M./F.M. tuners or tape recorder output. All required components of best quality to Mullard Spec. are offered at a special inclusive price of £9/9/- plus 3/6 P. & P. Instruction Book, containing full constructional details, theoretical, practical wiring diagrams, itemised price list available separately at 3/6, post free.

SURPLUS METER BARGAINS

We have large stocks of meters from 50 microamp to 200 v. and will be pleased to forward a complete list upon receipt of 3d. stamp.
METER RECTIFIERS 1 m/a. and 5 m/a. each at 6/6. Brand new.

"R.E.P. MINI-7"

POCKET TRANSISTOR PORTABLE

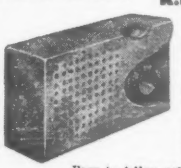

AT LAST! A pocket-sized SUPERHET Transistor portable for medium and long-wave reception THAT REALLY WORKS, and at a price YOU can afford. The "R.E.P. MINI-7" utilises 2 White Spot, 4 Red Spot and 1 R.F. Transistor specially selected to our specification by leading manufacturer. Push-Pull output. Powered by two 3-volt miniature transistor batteries. Attractive plastic case, finished in dove grey and scarlet. Size only 5¼in. × 3¼in. × 1⅝in. Incorporates Hi-Grade 2½in. P.M. Loudspeaker, Ferrite Slab Aerial, also drilled and eyelet ted Paxolin Chassis. Easy to follow practical and theoretical diagrams and itemised price list available separately at 1/6 post free. All necessary components at special inclusive price £10/10/-. Medium wave only £9/19/6, plus 2/6 P. & P.

AM/FM CHASSIS SPECIAL!!!

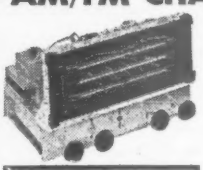

This is an ideal chassis to modernise existing equipment or as a basis for a new "up-to-the-minute" radiogram, and is highly recommended. Overall dimensions: 9¾in. deep × 12in. wide × 7¾in. high. Dial 11¼in. × 4¼in. Price: (whilst stocks last)

£18 . 19 . 6 Plus 5/- C. & P.

TERMS AVAILABLE

(By leading Manufacturer)

A favourable purchase enables us to offer this wonderful Type H.3. AM/FM Chassis at a greatly reduced price. NOTE these outstanding features:—

★Extremely sensitive F.M. Tuner section enabling first class reception in both Fringe and Local areas.
★Simple and positive tuning with the aid of the latest type indicator and special logging scale.
★Exceptionally stable and free from drift.
★Three waveband reception: Long, Medium and F.M.
★Negative Feedback over Audio Stages providing first rate quality.
★Pick-up, extension speaker, tape outlet and gram motor sockets.
★Built-in Ferrite Rod Aerial for AM. Bands.
★Valve line-up: BC085, ECH81, EF89, EABC80, EL84, EM81, EZ80.

SPECIAL PURCHASE AC/DC CHASSIS MANUFACTURER'S SURPLUS

Owing to favourable purchase we can offer strictly limited quantity of these handsome chassis. AC/DC 200/250 v. for Medium and Long Waves, plus gram position. Incorporates own frame aerial. Valve line up: U107, N108, DH107, W107 and X109. Overall chassis size 12 × 5½ × 7¼in. high. Attractive bronze dial with gold and cream lettering. Dial size 11½ × 4¼in. Scale length 7¾in. Logging scale provided. Price £7/19/6 only, tax paid, plus 3/6 P. & P. H.P. terms. £4 deposit plus four monthly payments of £2/-.

The "New Look RAMBLER"

SUPERHET BATTERY PORTABLE

Your summer holiday will not be complete without our most popular All-dry Battery Portable Superhet, now available with a new cabinet of even more attractive appearance. Finished in two-tone RED/GREY "Lionide," it is washable and unscratchable. The standard cream plastic top panel, engraved in red and green, complete the overall "air of quality." This receiver has everything: quality, sensitivity, economy and ample volume. Employs a high quality 5in. loudspeaker and the following popular readily obtainable miniature valves: 3V4, 1R5, 1S5, 1T4.

All necessary components, including cabinet can be supplied, ex-stock, at the original Special Inclusive Price of £7/7/- plus 2/6 p. and p. (less batteries). Uses all-dry 1.5 v. 1.t. (1/6), 90 v. h.t. (10/-). Easy-to-follow instruction booklet containing practical and theoretical diagrams and itemised price list available separately at 1/6 post free.

NOTE! Optional extra! Latest Ultra-low consumption "96" Range Valves and simple modification data can be supplied with the "RAMBLER" at 8/6 extra.

4-SPEED CHANGERS

B.S.R. MONARCH. Mixer Autochange in cream and gold £7/19/6, plus P. & P. 3/6. Limited Stocks.

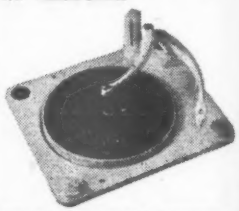

THE LATEST COLLARO "CONQUEST" 4-speed autochanger in cream with Studio "O" insert, £7/19/6, plus P. & P. 3/6.

SINGLE UNITS

COLLARO AC 3/554. Three-speed single player for AC mains 200/250 v. Cream finish, complete with turnover crystal pick-up incorporating the well-known high output "T" type head. Strictly limited quantity at £5/19/6 plus 3/6 P. & P.

COLLARO 4-SPEED single record unit with separate pick-up and HGP59 crystal cartridge. Brand new, few only, £4/19/6 plus 3/6 P. & P.

CABINETS TO SUIT ALL TYPES OF EQUIPMENT. Prices from 45/-. Send stamp for illustrated list.

DULCI

All Dulci products available ex stock. Illustrated leaflets and H.P. or Credit terms available. Demonstrations at both branches.

OUR NEW TRANSISTOR/RECEIVER (To Build Yourself)

This receiver, covering medium waveband, which can be assembled in about 1 hour, will give amazing volume and tonal quality when used in conjunction with a good aerial and earth. Incorporating PNP Transistor and Germanium Diode. For headphone reception. Included with the kit of parts is a handsome plastic case in black and white, measuring 4½ × 2½ × 1⅝in. This case accommodates the complete receiver, including battery.

PRICE OF ALL NECESSARY COMPONENTS 25/- plus 1/3 P. & P.
Lightweight high resistance headphones can be supplied separately at 15/- pair. If, however, all items purchased together they will be supplied at a SPECIAL INCLUSIVE PRICE OF 37/6 plus 1/6 P. & P. Optional extra. 100ft. coil single 7/36 coloured P.V.C. covered wire suitable for both aerial and earth, 2/6 only.

Our advantageous H.P. and Credit Sale terms are available on any single item over £5. Your enquiries invited.

If not stated, please add postage on orders under £1. Cash with order or C.O.D. (charges extra).

Open: Tottenham Court Road: 9 a.m. to 6 p.m. Mon. to Fri., Sat. 1 p.m. Holloway Road: 9 a.m. to 6 p.m. daily. Thurs. 1 p.m., Sat. 5.30 p.m.

★ TO BUILD YOURSELF ★

ALL PARTS AVAILABLE SEPARATELY

WE ARE THE EXPERTS IN THIS FIELD AND CARRY THE MOST COMPREHENSIVE STOCKS IN THE COUNTRY

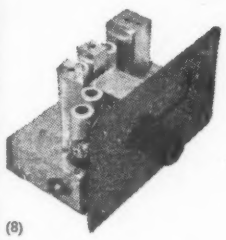
(8)

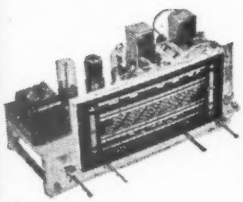
(6)

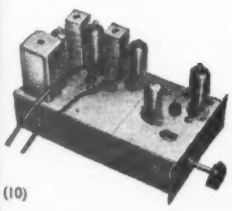
(10)

(4)

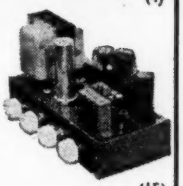
(15)

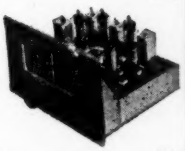
(11)

(5)

	All required components at special inclusive price	P. & P.	Instruction Book and itemised price list available separately
(1) New Look " RAMBLER " all dry portable	£7 7 0	2/6	1/6
(2) " RAMBLER " Mains Unit (suitable for most portables)	£2 7 6	1/6	9d.
(3) " ECONOMY FOUR " T.R.F. Mains Receiver	£5 10 0	2/6	1/6
(4) " FAMILY FOUR " (our new T.R.F. Receiver)	£4 19 6	2/6	1/6
(5) " SUPERIOR FOUR " (Four valve mains receiver)	£6 9 6	2/6	1/6
(6) GRAM Chassis 5-valve Superhet	£8 8 0	2/6	1/6
(7) T.S.L. F.M. Tuner (self powered)	£10 19 6	3/6	2/6
(8) Standard JASON F.M. Tuner	£6 15 0	2/6	2/–
(9) Fringe area JASON F.M. Tuner	£7 15 0	2/6	2/–
(10) JASON " MERCURY " Switch tuned F.M. feeder	£9 19 6	2/6	2/–
(11) OSRAM 912 Printed circuit F.M. Tuner	£8 8 0	2/6	2/6
(12) JASON " ARGONAUT " AM/FM Chassis	£16 5 0	2/6	2/–
(13) JASON " ARGONAUT " AM/FM Tuner	£13 19 6	3/6	2/–
(14) F.M. Power pack (suitable for most tuners)	£1 17 6	1/6	1/–
(15) R.C. 3/4 watt amplifier (with Bass, Middle & Treble controls)	£4 5 0	2/6	1/–
(16) 2-amp. Battery Charger	£1 18 6	2/6	3d.
(17) R.C. Transistor/Crystal Receiver (with 'Phones)	£1 17 6	1/3	3d.
(18) R.E.P. 1-valve Battery Receiver " "	£2 2 0	2/–	9d.
(19) " CRY-BABY " ALARM (Baby Alarm)	£3 12 6	2/6	1/–
(20) " R.E.P. MINI-7 " Transistor Portable (see opp.)	£9 19 6	2/6	1/6
(21) MULLARD 510 Amplifier (Printed circuit) Ultra Linear version	£9 9 0	3/6	3/6
(22) ???			

The following are also available assembled and tested:—
(2) " RAMBLER " Mains Unit, **£3/5/-**; (7) T.S.L. F.M. Tuner, **£13/15/-**; (14) F.M. Power Pack, **52/6**; (15) R.C. 3/4 watt Amplifier, **£5/5/-**; (16) 2-amp. Battery charger, **45/-**; (19) " CRY-BABY " Alarm, **89/6**; Instruction Books which contain full description, easy-to-follow practical wiring diagrams, theoretical diagrams, itemised price lists, etc., are supplied free of charge with all parcels but may be purchased separately if required.

NOTE: (2) The " RAMBLER " Mains Unit is suitable for use with MOST all-dry portables.

No. 38 TRANSMITTER/RECEIVER

(popular Walkie-Talkie). We have been most fortunate in obtaining a further supply of these complete stations comprising TX/RX unit, headphones, microphone, aerial, junction box, battery satchel and full operating instructions. Range: approx. 5 miles. Frequency coverage 7.4-9 mc/s. ABSOLUTELY BRAND NEW, **65/-**. Export enquiries invited.

VALVES. We have perhaps the most up-to-date valve stocks in the trade. A stamp will bring complete list of brand new imported valve types, fully guaranteed, P.T. paid. Also all usual surplus types available such as **6V6GT**, etc.

SPECIAL PURCHASE from MINISTRY BRAND NEW No. 17 Mk. II TRANSMITTER/RECEIVER.

Built into strong wooden cabinet 15in. × 14in. × 9in. Complete with headphones and microphone. Range 5-8 miles with simple aerial. Frequency coverage 44-61 mc/s. (6-7 metres). Uses standard 120 v. H.T. and 2-volt L.T. batteries. Complete with full operating instructions, **59/6**.

N.B.—All our T.R.F. circuits include specially wound Denco "Max Q" coils on polystyrene formers. Our High "Q" coils are supplied for our "RAMBLER" Superhet Portable.

LIMITED SUPPLIES OF THIS FINE AND POPULAR CABINET

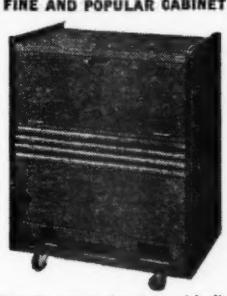

Instantly recognised as being of leading High Quality manufacturer's stock, this trolley-type cabinet is finished in polished dark walnut. Can easily be adapted to accommodate tape recorder, amplifier, radiogram, etc., etc. External measurements: 24½in. × 16in. × 29in. The whole is mounted upon "easy run" castors. Subject to being unsold **£5/19/6**, plus **15/- C. & P.**

No. 18 TRANSMITTER/RECEIVER UNIT

We have just taken delivery of a quantity of these fine units, brand new and complete. This is a very good portable, self-contained transmitter/receiver designed for short range telephony and C.W. Range: approx. 5 miles. Frequency coverage 6 mc/s.-9 mc/s. All accessories supplied, i.e., Headphone, Mike, Morse Key, Aerial, comprehensive instruction book with circuit diagram. Valve line-up: 3 A.R.P.12, 2 AR8, 1 ATP4. Weight approx. 22lb. Dimensions (overall): 8in. × 10in. × 17in. **UNREPEATABLE at 99/6 plus 7/6 C. & P.**

TRANSFORMER SPECIAL.

Superior quality half shrouded drop thro' Mains Transformer. Input 200/250 v. Output 350-0-350 v. 80 mA.; 6.3 v. 3 amps. 5 v. 2 amps. Ex-equipment but guaranteed O.K. Only **9/6** plus **1/- P. & P.**

BARGAIN CORNER

RP25 UNIT. 40-50 mc/s. Brand new **10/6**.
RP26 UNIT. 50-60 mc/s. Brand new **22/6**.
Postage and Packing 2/-.

6 VOLT VIBRATOR PACK. Ex-W.D. Output 140 v. at 30 mA. Fully smoothed. Size only 6½in. × 5in. × 2½in. New condition **12/6**. Plus 1/6 P. & P.

12 VOLT VIBRATOR PACK. Mallory. Output 150 v. 40 mA. Complete with Synchronous Vibrator. Brand new **12/6**. Plus 1/6 P. & P.

6½in. GOOD QUALITY EXTENSION LOUDSPEAKER in attractive Bakelite Cabinet (Black or Brown). Complete with input socket and two wander plugs. Slightly shop soiled. Guaranteed working order. **ONLY 27/6** plus 1/6 P. & P.

WIRING WIRE. 5 coils 10 yards each in different colours contained in cellophane bag, **5/-** bag plus 9d. postage.

CONTINUITY TESTER. Comprising well made polished wooden carrying case 8½in. × 6½in. × 3½in., with hinged lid and web carrying strap, 50 mA. 2½in. flush round meter (unscaled), mounted on paxolin panel with 10 ohm. wire wound "zero set" pot, complete with leads, heavy duty test prod, and battery compartment. Ideal for conversion to multi-range test meter. In new condition. Only **17/6** plus 1/6 P. & P.

SET OF 10 HI-GRADE TWIST DRILLS. Brand new. All useful sizes from approx. 3/16in. to 1/32in. in cellophane packet. **6/-** a set, plus 9d. P. & P. (Ex-W.D.).

12in. BAKER/SELHURST LOUDSPEAKERS. 15 ohm, 15 watt, 30-14,000 cps. Few only. Brand new. **£4/10/-** plus **3/6** P. & P.

CLYNE RADIO LTD.

162 Holloway Road, London, N.7.
and at
18 Tottenham Court Road, London, W.1.

G.W. SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

CR.100 SPARES KITS

Complete set of new valves 2 X66, 2 U50, 2 DH63, 2 KT63, 6 KTW61. Also set of resistors, condensers, pots, toggle switch and output transformer. Supplied new and boxed 59/6 each. P/P. 4/6.

CRYSTAL MICROPHONE INSERTS. Only 4/6 each. P/P. 6d.

300FT. COPPER AERIAL WIRE, 3/6 reel. P/P. 1/-.

CV967 1 INCH C.R. TUBES. Suitable for oscilloscopes, brand new 25/- each. P/P. 1/6.

AVO BATTERY ELIMINATOR POWER PACKS. Operation 200/250 volts A.C. Output 1.4 volts at 300 ma. and 67 volts at 10 ma. Stabilised by VS70, whole unit fully fused. Size 8½ × 5 × 3½in. Ideal for personal battery sets, etc., supplied brand new in maker's cartons, 39/6 each. P/P. 2/6.

AR.88 WAVECHANGE SWITCHES. Brand new, 17/6. P/P. 2/6.

P/O TELEPHONE HANDSETS. Std. type. Brand new, 12/6. P/P. 1/3.

R.1155 "N" TYPE SLOW MOTION DRIVES. Brand new, 12/6. P/P. 1/-.

METER BARGAINS.

50 Microamp. D.C. M/C, flush sq., 6in.	119/6
50 Microamp. D.C. M/C, flush rd. 2½in.	59/6
50 Microamp. D.C. M/C proj. rd. 2½in.	49/6
100 Microamp. D.C. M/C, flush rd. 2½in.	42/6
500 Microamp. D.C. M/C, flush rd., 2in.	15/6
500/0/500 Microamp. D.C. M/C, proj. rd. 2½in.	19/6
1 Milliamp. D.C. M/C, flush rd. 2½in.	25/-
10 Milliamp. D.C. M/C, flush rd. 2½in.	9/6
30 Milliamp. D.C. M/C, flush rd. 2½in.	9/6
200 Milliamp. D.C. M/C, flush rd. 2½in.	9/6
1.5 Amp. A.C./D.C. M/I flush rd. 2in.	8/6
7.5 Amp. D.C. M/I, proj. rd. 3½in.	10/6
30 Amp. D.C. M/C, flush rd., 2½in.	9/6
15 Volt D.C. M/C, flush rd. 1½in.	10/6
15 Volt A.C. M/I, flush rd. 2½in.	9/6
25 Volt D.C. M/C, proj. rd. 2in.	8/6
120 Volt D.C. M/C, flush rd. 3½in.	32/6
300 Volt A.C. M/I, flush rd. 2½in.	25/-
300 Volt A.C. M/C, rectifier, flush rd. 2½in.	25/-
500 Volt A.C. M/I, flush rd., 2½in.	25/-

ALL BRAND NEW AND TESTED.

ROTARY TRANSFORMERS. American type. 2 models, either 6 or 12 volt D.C. input. Output 250 volts 80 ma. 22/6 each. P/P. 3/6.

MUIRHEAD PRECISION STUD SWITCHES. 24 positions, 4 banks. Heavy duty contacts. New, boxed, 17/6 each. P/P. 1/6. Ditto 2 banks, 10/6. P/P. 1/-.

2 VOLT 3 A.H. ACCUMULATORS. Exide, unfilled, 2/- each. P/P. 1/-. 12 for 21/-. P/P. 4/6.

AMERICAN GEARED MOTORS. American 24 volt D.C. motor with built-in precision gearbox giving twin outputs 20 r.p.m. and 6 r.p.m. Will also operate on 12 v. giving reduced outputs. Size 7 × 1¾in. Shaft dia. ¼in. Supplied brand new only. P/P. 3/-. **19/6** each.

MARCONI TF-144G STANDARD SIGNAL GENERATORS. 85 kc/s. to 25 mc/s. Reconditioned as new, with test certificate. £45 each. Carriage £1.

MARCONI SIGNAL GENERATORS TF-517.
SPECIAL OFFER
Frequency coverage 10 to 18 mc/s. 33 to 58 mc/s. and 150 to 300 mc/s. Operation 200/250 volt A.C. Supplied in good working order, only £12/10/- each. P/P. £1.

TRANSFORMERS

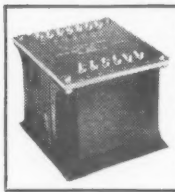

PARMEKO TABLE TOP TRANSFORMERS. Input 230 v. 50 cycles. Output 620/550/375/0/375/550/620 volts 250 ma. Also 2-5 volt 3 amp. windings. Size: 6½ × 6½ × 5½in. Brand new only 45/- each. P/P. 5/-.

RCA ET.4336 PLATE TRANSFORMERS. Special release, brand new in original maker's transit cases. Primary tapped 200 to 250 volts 50 cycles. Secondary 2,000/0/2,000 volts 400 ma., tapped 1,500/0/1,500 volts. Price £12/10/- each. P/P. £1.

A.C. MAINS VOLTAGE REGULATOR TRANSFORMERS. Input 230 volts. Output variable from 185 to 250 volts at a max. rating of 24 amps. Ideal for laboratory use, etc., supplied as new. £15 each. P/P. 10/-.

HEAVY DUTY MAINS ISOLATING TRANSFORMERS. Specifications: Primary 230 volts 3 amps. Secondary 230 volts 3 amps (service rating, OK 5 amps.). Ideal for laboratory or workshop use. Supplied brand new in original transit cases. £6/10/- each. P/P. 10/-.

ADVANCE CONSTANT VOLTAGE TRANSFORMERS. Input 190 to 260 volts. A.C. 50 cycles. Output constant at 230 volts. Max. rating 150 watts. Supplied brand new in original crates. £8/10/- each. P/P. 5/-.

AUTO TRANSFORMERS.
Midget 105/115/120/210/230/240 v. 20 watt, 9/-. P/P. 1/-. Small shrouded American, 110/230 v. 50 watt, 12/6. P/P. 1/6. Service type, 110/230 v. 100 watt, 15/6. P/P. 2/-. General purpose. 110/230 v. 150 watt, 21/-. P/P. 2/6 **Heavy Duty** 110/230 v. 750 watt, 69/6. P/P. 5/-.

HEAVY DUTY L.T. TRANSFORMERS. Type 1. Primary tapped 110/200/250 volts. Secondary 55 volts tapped 50 volts 10 amps. Brand new, 72/6 each. P/P. 4/6. Type 2, Primary 200/250 volts. Secondary tapped 3, 6, 9, 12, 24 or 36 volts 5 amps., 35/- each. P/P. 4/6.

FERRANTI POTTED FILAMENT TRANSFORMERS. Hermetically sealed, ceramic terminations. All new and boxed. Type 1,200/250 v. input. Output 6.3 v. CT. 5.6 a., tapped 5 v. 6.3 v. CT. 4.8 a. tapped 4 v. 6.3 v. CT. 1 a. tapped 4 v., 19/6 each. Type 2. Input 200/250 v. Outputs, 6.3 v. CT. 3.3 a. tapped 5 v. 6.3 v. CT. 1 a. tapped 4 v. 6.3 v. CT. .9 a. 6.3 v. CT. .6 a., 15/6 each. P/P. 2/- each type.

PARMEKO TRANSFORMERS. Input 230 volts. Output 350/0/350 volts 150 ma. 6.3 v. 4 a. 5 v. 4 a. Brand new, 32/6. P/P. 3/6. Also 350/310/0/310/350 volts 220 ma. 6.3 v. 5 a., 2 × 6.3 v. 3 a., 2 × 6.3 v. 1 a., 5 v. 3 a., potted, 49/6. P/P. 5/6.

HOOVER H.T. IIa ROTARY TRANSFORMER. Midget type. Input 12 v. D.C. Output 310 v. 30 ma. Brand New and Boxed. 22/6 each. P/P. 2/-.

U.S.A. PRECISION SERIES TEST-METERS

20,000 Ω/volt D.C., Resistance	Volts	1,000 Ω/volt A.C./D.C. Current
6,000Ω	A.C./D.C.	50 Microamp
600,000Ω	3 v.	300 Microamp
60 Megohm	12 v.	3 m/a.
	60 v.	30 m/a.
	300 v.	120 m/a.
	600 v.	600 m/a.
	1,200 v.	12 amp.
	6,000 v.	

Output +34 to −12 db.
Housed in wooden carrying case. Supplied in good working order with leads and prods, £9/19/6 each. P. & P. 4/-.

LEACH AERIAL CHANGEOVER RELAYS. 12 volt D.C., double pole, transmitter type. New boxed, 7/6 each. P/P. 9d.

AMERICAN SUPER LIGHTWEIGHT HEADPHONES. Res. 50 ohms. Fitted with rubber earmoulds to fit inside the ear, extremely good quality, ideal for communication receivers, etc. New and boxed. 15/- pair. P/P. 1/-.

EDDYSTONE MAINS POWER PACKS. Supplied brand new and unused. Mains input 200/250 volts. Output 175 volts 60 ma. and 12 v. 2.5 a. Double choke and condenser smoothed. 5Z4 rectifier. Housed in grey metal case. Only 32/6 each. P/P. 3/6.

BARGAIN GRAM. MOTORS. Garrard centre-drive motors complete with turntables 200/250 volts A.C. Adjustable mechanically from 0 to 45 r.p.m. Only 22/6 each. P/P. 3/-.

6-VOLT VIBRATOR POWER PACKS. Output 120 volts 30 ma. Fully smoothed, uses standard 4-pin Mallory vibrator. New and boxed. 12/6 each. P/P. 2/6.

JOHNSON TX. CONDENSERS. 500 PF variables. Brand new, boxed, 15/6 each. P/P. 1/-. New, boxed, Johnson variable inductances, 22/6. P/P. 2/6.

POTTED "C" CORE CHOKES. Brand new Parmeko 20 Henry 90 ma. 10/6 each. P.P. 1/6.

W.1191 WAVEMETERS.
Portable precision battery operated frequency check meters, coverage 100 kc/s. to 20 mc/s. Supplied complete with all valves, and 1 mc/s. Xtal and calibration charts. £5/19/6 each. P/P. 6/-.

SMOOTHING CHOKE BARGAINS. 10H, 60 ma., 4/6; 15H, 60 ma., 5/6; 8H, 100 ma., 8/6; 9H, 100 ma., 7/6; 10H, 100 ma., 8/6; 5H, 200 ma., 5/6; 20H, 120 ma., 10/6; 50H, 120 ma., 15/6; swinging choke 3.6-4.2 H, 250 ma., 10/6; 3H, 100 ma. 6/6; 20H, 50ma., 7/6; 16H, 120 ma., 10/6; 100H, 30 ma., 10/6. P/P. 1/- to 2/6.

RCA OUTPUT TRANSFORMERS.
Completely potted. Centre-tapped primary, 8,000 ohms. Secondary tapped 3, 7.5, 15 or 600 ohms. Separate feedback winding. 15 watts rating. Suitable for 6L6, EL84, etc., unused, 27/6 each. P/P. 2/-.

EX NAVY SOUND-POWERED TELEPHONES. This type requires no batteries to operate and can be fitted in moments to give complete inter-communication between two points. Hand generator calling. Only 45/- each. P/P. 4/6.

ALKALINE NIFE ACCUMULATORS

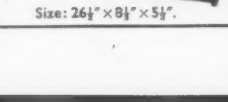

Size: 26½" × 8½" × 5½".

Banks of 10 cells giving 12 volts 45 A.H. Unused in wooden crates. £5/10/- each. P.P. 7/6.

COSSOR BEAM OSCILLOSCOPE TYPE 339

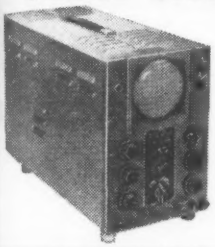

Operation 110/200/250 volts A.C. 120 watts. Time Base 10 positions. 6 cps. to 250,000 cps. Amplifier 10 cps. to 2,000,000 cps. Sensitivity, Y1.Y2.3.1 v. D.C. 1.1 v. rms. X. 2.25 v. D.C. .8 v. rms.

Supplied in good working order, complete with handbook and circuit. **£27/10/-** each. P/P. £1.

AMERICAN MULTI-RANGE TESTMETERS

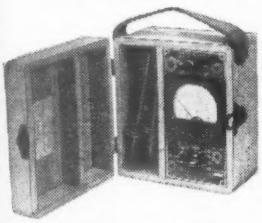

1,000 ohms per volt, 400 microamp basic movement.

A.C. VOLTS	D.C VOLTS
2.5 v	2.5 v.
10 v.	10 v.
50 v.	50 v.
250 v.	250 v.
1,000 v.	1,000 v.
5,000 v.	5,000 v.

D.C. CURRENT	RESIST'CE.
1 ma.	500 ohms
10 ma.	100 K. ohms
100 ma.	1 meg. ohms
1 amp.	DECIBELS —10 to +69

ALL BRAND NEW. COMPLETE WITH INTERNAL BATTERY, TEST PRODS AND INSTRUCTIONS. **£5/19/6** EACH. P/P. 3/-.

EVERSHED AND VIGNOLES WEE-MEGGERS 500 VOLTS

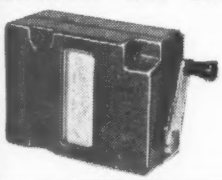

Special release, brand new and unused, complete with leather carrying case, only **£12/10/-** each. P/P. 2/6.

Also available secondhand models, but perfect working order complete with leather case, **£8/10/-** each. P/P. 2/6.

R.1155 COMMUNICATION RECEIVERS MODEL "N"

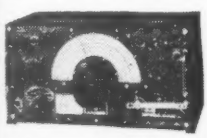

Incorporating the trawler band. Frequency coverage: 200-250 kc/s., 600-1,500 kc/s. 1.5-3 mc/s. 3-7.5 mc/s. and 7.5-18 mc/s. Supplied in perfect working order, aerial tested, with illustrated leaflet, **£12/19/6** each. P/P. 7/6. Standard models available but fitted with improved dial drive as above model, **£8/19/6** each. Combined A.C. mains power packs and output stage available. 85/- each. P/P. 3/6.

WESTON MODEL 772 TESTMETER

A.C. VOLTS	D.C. CURRENT	A.C. CURRENT
2.5 v.	100 micro/a.	500 ma.
10 v.	1 ma.	1 amp.
50 v.	10 ma.	5 amp.
250 v.	50 ma.	RESIST-ANCE
1,000 v.	100 ma.	100 ohms.
D.C. VOLTS	500 ma.	1,000 ohms
2.5 v.	OUTPUT METER	100K. ohms
10 v.		10 MEG. ohms
50 v.		
250 v.		
1,000 v.		

Supplied in perfect working order complete with rexine carrying case, internal batteries and instructions. **£10/10/-** each. P/P. 4/-.

UNIVERSAL AVOMETER MODEL "D"

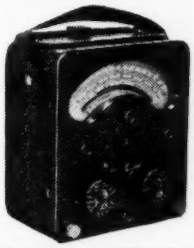

D.C. VOLTS	A.C. VOLTS	D.C. Current	A.C. Current
150 mv.	7.5 v.	15 ma.	75 ma.
300 mv.	15 v.	30 ma.	150 ma.
1.5 v.	75 v.	150 ma.	750 ma.
3 v.	150 v.	300 ma.	1.5 amp.
15 v.	300 v.	1.5 amp.	7.5 amp.
30 v.	600 v.	3 amp.	15 amp.
150 v.	750 v.	15 amp.	Resist-ance
300 v.	1,500 v.	30 amp.	1,000Ω
750 v.			10,000Ω
1,500 v.			

Supplied reconditioned as new, with internal battery, instructions and leads **£8/19/6** each. P/P. 4/-.

G.E.C. SELECTEST MULTI-RANGE TESTMETER

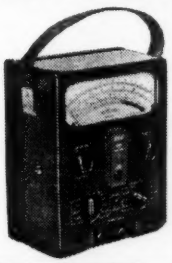

D.C. VOLTS	A.C. VOLTS	D.C. Current	A.C. Current
150 mv.	7.5 v.	1.5 ma.	75 ma.
300 mv.	15 v.	3 ma.	150 ma.
1.5 v.	75 v.	15 ma.	750 ma.
3 v.	150 v.	30 ma.	1.5 amp.
15 v.	300 v.	150 ma.	7.5 amp.
30 v.	600 v.	300 ma.	15 amp.
150 v.	750 v.	1.5 amp.	Resistance
300 v.	1,500 v.	3 amp.	10k. ohms
750 v.		15 amp.	100k. ohms
1,500 v.		30 amp.	1 meg. ohm

Incorporates overload trip and special safety interlocking switches. Supplied in perfect condition with leads, **£9/19/6** each. P/P. 4/-.

UNIVERSAL AVOMINOR TESTMETERS

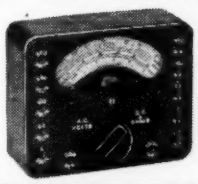

Small, compact, accurate instrument. Resistance measurements from 0 to 20 k. ohms, D.C. volts from 0 to 500 v. A.C. volts from 0 to 500 v. D.C. current from 0 to 500 ma. Supplied in perfect working order, complete with leather case and leads. **£5/10/-** each. P/P. 2/6.

EVERSHED AND VIGNOLES MEGGER OHMMETERS

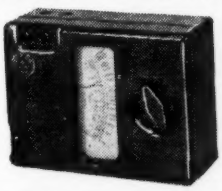

Ranges 0 to 1,000 ohms and 0 to 200k. ohms. Ideal for all continuity and polarity tests. Supplied brand new, boxed with all leads and instructions, **59/6** each. P/P. 2/-.

PORTABLE PRECISION VOLTMETERS

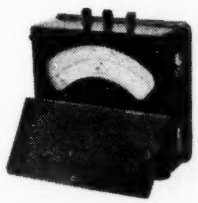

Brand new and boxed instruments by famous manufacturer. Housed in polished teak case. Moving iron movement reading A.C. or D.C. volts on 2 ranges. 0-160 v. and 0-320 v. 8in. mirror scale. Accuracy within 2%. Supplied at a fraction of original cost. Only **£5/19/6** each. P/P. 3/6.

G.W. SMITH & CO (RADIO) LIMITED
Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

XUM

LASKY'S RADIO

SAVE POUNDS! ORDER BY POST IF YOU CANNOT CALL

TURRET TUNERS
All types in stock—Cyldon, Brayhead, Telenge, Valradio, etc., from
79/6
Describe your set for quotation. We have what you need.

BAND III CONVERTERS
All types in stock at prices from 99/6. Few only left. WOLSEY 13-Channel (List £9/19/6)
£5 . 19 . 6
Post 3/6.

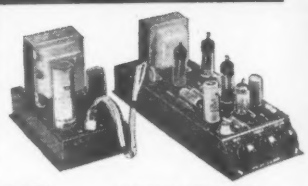

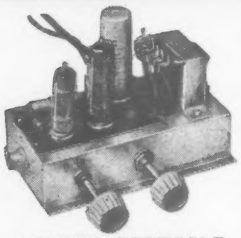

LASKY'S PORTABLE GRAM AMPLIFIER KIT

2 watts. Note small dimensions, approx. 6¾in. × 3¾in. max., height 5in. Uses EL84 output and 6X4 rectifier, double-wound transformer, tone control, output transformer, etc. Built on a T.C.C. PRINTED CIRCUIT.

COMPLETE KIT, including valves, printed circuit, full instructions, less Speaker. **49/6**
Carr. 2/6.
7in. × 4in. Elliptical Speaker, if required, 19/6 extra.

LASKY'S 4-WATT PORTABLE GRAM AMPLIFIER

Will suit any crystal or magnetic pick-up. Uses 3 valves: EL84 output, L63 and EZ80 rect.

COMPLETE with 3 valves and knobs. Carr. 5/-. **79/6**

Details and circuit diagram post free.

STOP PRESS BARGAIN

A.M. / F.M. SUPERHET RADIOGRAM CHASSIS

By famous manufacturer. Magic eye indicator, 6 valves, incorporates Gorler F.M. tuning unit. Brand new, perfect and fully guaranteed. Limited number only. Size: 12" × 7½" × 7½" high.

Listed at 22 Gns.

LASKY'S PRICE **£17.19.6**
Carr. and pkg. 12/6.

ALMOST HALF PRICE!

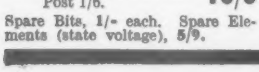

SOLON SOLDERING IRONS
Ex-Govt. new and unused. Pencil bit, 65 w., 230-250 v. A.C./D.C. List 27/6.

LASKY'S PRICE **16/6**
Post 1/6.

Spare Bits, 1/- each. Spare Elements (state voltage), 5/9.

LONDON'S HI-FI SPECIALISTS!

Visit our Tottenham Court Road address for selective Demonstrations of the latest Hi-Fi Equipment.

AMPLIFIERS. QUAD, ROGERS, LEAK, RCA, PAMPHONIC, DULCI, W/B, ARMSTRONG A10 Mk. II.

SPEAKERS. WHARFEDALE, GOODMANS, LOWTHER, G.E.C., LORENZ, PHILIPS.

PICK-UPS. COLLARO, GARRARD, CONNOISSEUR, LEAK, B/J, ORTOPHONE, GOLDRING.

TRANSCRIPTION TURNTABLES. COLLARO, GARRARD, LENCO, CONNOISSEUR.

TAPE RECORDERS. GRUNDIG, ELIZABETHAN, BRENELL, TRUVOX, SOUND VORTEXION, FERROGRAPH, MAGNAVOX, HARTING

CABINETS. WIDE SELECTION INCLUDING THE NEW G-PLAN CONTEMPORARY CABINETS.

SUPER BARGAIN! famous make HI-FI AMPLIFIER

New and Unused

LISTED AT 13 GNS

LASKY'S PRICE

7 GNS.

Post & Packing 5s.

For mains 200/250 v. A.C.

- ★ 4 valves: 2 EF86, 1 EL84 and EZ80.
- ★ Overall Freq. Response 20 to 35,000 c.p.s. Flat approx. ±1dB.
- ★ Hum level better than 65dB below full input.
- ★ Output 4 watts max. with choice of 3 or 15 ohm imp. by means of switch.
- ★ Separate bass and treble controls and 4-position input selector switch.

CABINET AVAILABLE. 11¾ × 6¾ × 7¼in. deep, polished medium oak veneer. Price, if purchased with Amplifier, 30/-.

HI-FI BARGAIN!

GOODMANS AXIOM 12" SPEAKERS

15 watt. Dual cone. Secondhand but thoroughly reconditioned and re-coned by makers

SPECIAL PRICE

£7.19.6

Post 7/6. Fully guaranteed (equiv. to Axiom 50, Mk. II).

SPECIAL OFFER OF MAGNETIC RECORDING TAPE

Famous make. P.V.C. base on latest type plastic spools. Not surplus but brand new, perfect and boxed. SATISFACTION OR MONEY REFUNDED.

STANDARD	Lasky's Price
1,200ft. on 7in. spool. List 35/-	21/-
850ft. on 5¾in. Continental spool. List 28/-	16/6
600ft. on 5in. spool. List 21/-	12/6
300ft. on 4in. spool. List 10/6	7/11
LONG PLAY	
1,200ft. on 5¾in. Continental spool. List 35/-	22/6
850ft. on 5in. spool. List 28/-	16/6
225ft. on 3in. spool. List 8/6	6/6

Post: 1 spool, 1/6.
Orders over 70/- post free.

MULLARD 510 AMPLIFIER KIT WITH T.C.C. PRINTED CIRCUIT

All specified components and your choice of transformers and chokes by Partridge, Haddon, W/B, Ellison or Gilson.

COMPLETE KIT of parts and printed circuit as low as **£9.9.0**
Details on request.
Book 3/6 post free. Printed Circuit separately 22/6. Also available built ready for use. Price according to transformers used.

MICROPHONE BARGAIN

ACOS type 33/1. Crystal hand or table Microphone.

Incorporates specially designed acoustic filter. Flat response 30-7,000 c.p.s. Omnidirectional. Suitable for tape recording, public address, etc. Attractive dark brown plastic case. Brand new in maker's cartons. List 50/-.

LASKY'S PRICE **29/6**
Post 1/6.

SUB-MIN CRYSTAL MICROPHONE INSERTS

ACOS type MIC.17. Size approx. ⅜in. square, 7/32in. thick. Brand new and boxed. Each 4/6. Post 1/-.

TAPE RECORDER AMPLIFIERS

Mains 200/250 v. A.C. 6 watts output. For use with low impedance Tape Heads. 4 valves: EZ41 rect., EL41 output, EF40 and ECC81. Tone, volume and record/play back controls. Neon level indicator. Microphone and gram inputs. Can be used as a straight amplifier. Circuit diagram supplied.

LASKY'S PRICE **£6 . 19 . 6**
Complete with valves. Post & Pkg. 5/-.
Full details on request.

TAPE DECKS

SPECIAL OFFER OF COLLARO TAPE TRANSCRIPTOR, Mk. III, fitted with digital counter. Limited quantity only. List £22, Lasky's Price **£17/19/6.**
Carr. 21/-

COLLARO TAPE PRE-AMPLIFIER, fitted and wired. **£21.**
COLLARO TAPE TRANSCRIPTOR, Mk. IIII, **£25.**
LANE DECK **£18/10/-.**
WEARITE DECKS **£35** and **£40**
Carr. extra.

ANOTHER LASKY BARGAIN

DUAL CONCENTRIC SPEAKERS (15in.)

Famous make. High Fidelity. 25 watts, 15 ohms imp., full freq. range 20 c.p.s. to 17,000 c.p.s., resonance 20 c.p.s. Complete with crossover unit. List £27/4/6.

LASKY'S PRICE **£16 . 19 . 6**
Carr. 7/6 plus 30/- for wood packing case (returnable).

RADIO · TELEVISION · HI-FI · ELECTRONICS · RECORDERS

LASKY'S RADIO

4-SPEED MIXER AUTO-CHANGERS

COLLARO RC.456. Incorporating auto and manual control. Complete with Studio crystal p.u. and sapphire stylus. List £13/17/-. LASKY'S PRICE **£7 . 19 . 6** Post 3/6.

B.S.R. type UA8 with latest B.S.R. ful-fi, P.U. £6.19.6. Post paid.

Garrard 12, MK. II, £9.19.6.
Garrard 121, MK. II, £10.19.6.

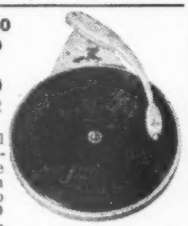

COLLARO 4-SPEED SINGLE RECORD PLAYER

Model 4/564 complete with Studio T or O p.u. crystal cartridge and styli. Automatic stop. LASKY'S PRICE Carr. 3/6. **£6.19.6**

Garrard 4SPD..... £7.19.6

Collaro "Junior" 4-spd. motor and p.u. with HGP50 cartridge. Post 2/6. **90/-**
Motor only 59/6, post 2/6.
Pick-up only 29/6, post 2/6.

Delivery from stock of the **COLLARO 4-speed Transcription Turntable**
4T200/PX £19/10/-
Less pick-up £14/18/-. Carr. paid.

PICK-UP CARTRIDGES
GARRARD MAGNETIC t/o, p.u. Cartridges. Type TOM/2, less than half price. **30/-**
ACOS turnover, complete with l.p. and standard styli. List £2/1/7. LASKY'S PRICE Post 1/-. **18/-**

20,000 VALVES IN STOCK
Brand new surplus and imported valves, also full stocks of B.V.A. valves and C.R. Tubes. List free.

TRANSISTORS
R.F. P.N.P. Junction Type suitable for medium and low freq. oscillators freq. changers and I.F. amplifiers (1.5 to 8 Mc/s). **21/-**
(Double spot—yellow and red.)
AUDIO P.N.P. Junction Type suitable for high gain and low freq. amplifiers, and for output stages up to 250 milliwatts. (Double spot—yellow and green.) **10/-**
Post free.

All types of MULLARD, B.T.H., BRIMAR and GOLTOP Transistors. Also all sub-min. components.

SPECIAL PURCHASE PLESSEY P.M. SPEAKERS
5in. round or 7 × 4in. elliptical. Brand new.
LASKY'S PRICE **14/6** Post 1/6

MOVING COIL P.M. SPEAKERS
2½in. **17/6**. 3in. and 3½in. **19/6**. 5in. **16/6**. 6½in. **17/6**. 8in. **21/-**. 10in. **29/6**. 12in. **29/6**. 6½in. with transformer **21/-**. 7 × 4in. **19/6**. 10 × 7in. Elliptical **32/6**.

TRUVOX "SENIOR" SPEAKER DRIVING UNIT (Pressure Type)
Power handling cap. 15 watts peak. With 12in. cinema horn reproduces down to 17 c.p.s. List £7/15/-. Carr. 5/-. LASKY'S PRICE **59/6**

LASKY'S TRANSISTOR SUPERHET TUNER
For construction on Printed Circuit. Size 3⅞ × 3½in. Uses 3 R.F. transistors, 1 germanium diode, 3 I.F. transformers. Ferrite rod aerial. Operates from 6 v. battery and 1.5 v. cell.
Can be built for **£5 . 12 . 9**
Post 3/6.
Full details on request.

LASKY'S TRANSISTOR AMPLIFIER KIT
200 milliwatts. Output impedance 5 ohms. Operates from 6 v. battery. Miniature size. 3½in. × 3½in. height can be under 1in. COMPLETE KIT including 4 Transistors. PRINTED CIRCUIT full instructions. Post 3/6. Full details on request. **79/6**

TELETRON "COMPANION"
3-TRANSISTOR POCKET RADIO, T.R.F. circuit covering med. and long waves, with balanced armature output. Ferrite aerial. Size: 4½ × 3 × 1in. **89/6**
CAN BE BUILT FOR ONLY
Full instructions and price list 6d. post free.

LASKY'S FULLY TRANSISTORISED PORTABLE FOR HOME CONSTRUCTION

Note these star features:—
★ Printed circuit. 6½in. × 2½in.
★ 200 milliwatts p.p. output.
★ Uses 7 Transistors and 1 germanium diode.
★ Ferrite rod aerial.
★ Fully tunable.
★ 6 v. operation. Very low consumption.
★ Choice of 7in. × 4in. elliptical or 3½in. P.M. Speaker.
★ Choice of cabinet.

Circuit diagram and full building instructions supplied.
Full data and building instructions available separately, 1/6 post free.

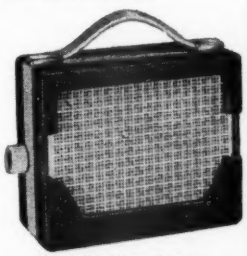

CAN BE BUILT FOR
£9 . 19 . 6 Post & Pkg. 3/6

LASKY'S F.M. TUNER
PRINTED CIRCUIT VERSION OF G.E.C. 912 "F.M. PLUS" TUNER FOR HOME CONSTRUCTION
Uses 5 valves; 2 germanium diodes and brand new T.C.C. condensers. The PRINTED CIRCUIT ensures that the I.F. and R.F. amplifiers are extremely stable at maximum gain and results are consistent on all tuners.
CAN BE BUILT FOR (including valves) **£7.19.6**
Post Free.
G.E.C. FM TUNER BOOK plus our full data and Shopping List, 2/6 post free.
All parts available separately.
ALIGNMENT SERVICE available.

JASON F.M. TUNER
Special Parcel containing data book, chassis front panel, dial, drive, tuning condenser full sets of coils, I.F.s, ratio detector, etc. Post 2/6. **68/9**
DATA BOOK with price list, 2/-. This tuner can be built for £6/15/-, post 3/6. Also in stock **JASON "ARGONAUT" AM/FM TUNER** and **JASON "MERCURY"** switched. Tuner. Data Books 2/- each post free.

LASKY'S NEW MIDGET T.R.F.

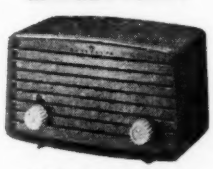

CAN BE BUILT FOR ONLY 99/6
Post & Pkg. 5/-.

Handsome contemporary design case, overall size 8½in. wide, 4½in. deep, 5in. high. 2 latest double-purpose valves EBF89 and ECL80, contact cooled rectifier. For A.C. mains 200-250 v. Med. and long wave, 5in. P.M. speaker. Plastic cabinet in cream, pastel green, pink, blue. FULL DATA, instructions circuit diagram, shopping list 1/6. All components available separately.
CABINET only, as illus., 14/-. plus 4/6 post and pkg.

BUILD THIS 4-VALVE S/HET PORTABLE

FOR ONLY £7/7/- plus 3/6 carr. and pkg., you can build this med. and long wave Portable using all brand new components and valves, only batteries extra. Printed circuit, circuit diagram and full instructions supplied.

Circuit diagram and full data 1/6 post free.

FOR ONLY £9/9/- plus 3/6 carr. and pkg. you can build this job as a mains and battery Portable using our specially designed build-it-yourself Power Unit for 200-250 v. A.C.

ALL TYPES F.M. TUNERS
DULCI, QUAD, LEAK, ROGERS, PAMPHONIC, etc., in stock.

DULCI HI-FI CHASSIS TUNERS AND AMPLIFIERS
Full range in stock.

The new PULLIN "100" MULTI-RANGE TEST SET.
Built on printed circuit. 21 basic self-contained ranges AC/DC voltage, current and resistance, 10,000 ohms per volt (A.C. and D.C.). Basic movement, 100 microamps. Complete with leads **£12.7.6**
Post & pkg., 4/6.
Credit sales terms: 30/- deposit and 8 payments of 30/-.

MOVING COIL METERS
SPECIAL OFFER. Brand new Grade 1, 3in. flush panel mounted, calibrated in decibels.

0-100 micro/A	0-200	0-500
39/6	35/-	29/6

Also, 0-1 m/A., 25/-. 0-30 m/A. 15/-.

2½in. round projecting. 0-750 m/A., 15/-. Post per meter, 2/6.

H.P. TERMS AND CREDIT SALES AVAILABLE
LASKY'S (HARROW ROAD) LTD.

42 TOTTENHAM COURT ROAD, W.1.
Nearest Station Goodge Street
MUSeum 2605.

370 HARROW ROAD, PADDINGTON, W.9.
(Opposite Paddington Hospital)
LAD 4075 and GUN 1979

Open all day Saturday. Early closing Thursday (both addresses)

LASKY'S RADIO

ALL MAIL ORDERS TO HARROW ROAD PLEASE

Stern's "fidelity" TAPE RECORDERS

THEY INCORPORATE . . .
- Choice of the latest COLLARO or TRUVOX Tape Decks.
- The model HF/TR2 " fidelity " AMPLIFIER.
- ROLA/CELESTION 10in. x 6 P.M. Speaker.
- 1,200ft. reel EMI Tape.
- ACOS Crystal Microphone.

THIS POPULAR RECORDER IS OFFERED INCORPORATING EITHER

★ **The NEW MK. IV COLLARO TRANSCRIPTOR DECK or**

★ **The latest TRUVOX MK. IV DECK**

● **You WON'T BUY better value. Truly "Hi-Fi" RECORDINGS are obtainable.**

PRICE INCORPORATING COLLARO DECK, £49.10.0
CREDIT SALE. Deposit £12/8/- and 9 monthly payments of £4/10/8.
H.P TERMS. Deposit £24/15/- and 12 monthly payments of £2/5/11.

PRICE WITH TRUVOX DECK INCORPORATING REV. COUNTER, £52.10.0
CREDIT SALE. Deposit £13/2/6 and 9 monthly payments of £4/16/3.
H.P. TERMS. Deposit £26/3/- and 12 monthly payments of £2/8/8.
(Plus £1/10/- carriage and insurance, of which £1 is refunded on return of Packing Case.)

STERN'S TAPE PRE-AMPLIFIER and ERASE UNIT

Please send S.A.E. with any enquiry.

Provides the "Link" between the HIGH-QUALITY AMPLIFIER and TAPE DECK.

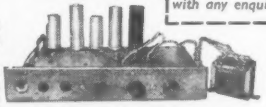

MODEL HF/TR1P . . . A completely assembled Pre-Amplifier with own Power Supply. Can be supplied correctly matched for use with Truvox or Collaro Decks, and incorporates Recording Level Indicator and Monitoring facilities.

PRICE **£11.10.0** (plus 5/- carr and insurance)

A COMPLETE KIT OF PARTS TO BUILD
The "fidelity" TAPE AMPLIFIER Model HF/TR2 including a separate small POWER SUPPLY UNIT

FOR ONLY **£12.0.0** (Plus 5/- carr. and ins.)

Designed to meet the requirements of the enthusiasts for High Fidelity reproduction. It is based on the very successful design, completed by the Mullard Technicians and only new high-grade Components including MULLARD Valves are incorporated. **THE ASSEMBLY MANUAL PRACTICAL DIAGRAMS, etc., are available for 9/9**

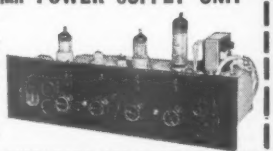

WE ALSO SUPPLY THE HF/TR2 ASSEMBLED AND READY FOR USE FOR £16 (Plus 6/- carr. & ins.). **H.P. TERMS:** Deposit £8 and 9 monthly payments of £1. **CREDIT TERMS:** Deposit £4 and 9 monthly payments of £1/9/4.

HOME CONSTRUCTORS

BUILD YOUR OWN RECORDER — WE MAKE SPECIALLY REDUCED PRICES FOR COMBINED ORDERS — and have the following in STOCK.

★ **The NEW COLLARO MK. IV TAPE DECK £24/-/-**

★ **The TRUVOX Mk. IV Tape Deck £27/6/-.** ★ **The TRUVOX MK. IV DECK with Rev. Counter £30/9/-.**

SPECIAL REDUCED PRICES - WE OFFER

(a) The **HF/TR2 AMPLIFIER** and **UNIT**, fully assembled, with the TRUVOX MK IV TAPE DECK for £38 10 0
ALTERNATIVELY Amplifier and P/Unit KIT OF PARTS..... £35 0 0

(b) The **HF/TR2 AMPLIFIER** and **UNIT** fully assembled, with the TRUVOX TAPE DECK incorporating PRECISION REV. COUNTER £41 10 0
ALTERNATIVELY the Amplifier and P/Unit KIT OF PARTS.. £38 0 0

(c) The **HF/TR2 AMPLIFIER** and **UNIT**, fully assembled, with the **MKIV COLLARO TRANSCRIPTOR**..... £36 0 0
ALTERNATIVELY the Amplifier and P/Unit as a KIT OF PARTS £32 10 0
(Plus 12/6 Carr. and Insurance.)

ADD TAPE TO YOUR EXISTING AMPLIFIER

(a) The Model **HF/TR1P TAPE PRE-AMPLIFIER** together with the TRUVOX MK IV TAPE DECK £35 0 0

(b) ALTERNATIVELY as in (a) above but Truvox Deck incorporating PRECISION REV. COUNTER £38 0 0

(c) The model **HF/TR1P TAPE PRE-AMPLIFIER** together with the MKIV COLLARO TRANSCRIPTOR Tape Deck £32 10 0

PLEASE INCLUDE 12/6 to cover cost of Carriage and Insurance.

HIRE PURCHASE and CREDIT SALE TERMS are available on all equipment (excluding Kits of Parts). Send S.A.E. for details.
NOTE . . . The Deck switches of the Transcriptor have to be "wired-up." We will complete this wiring, for use with either the HF/TR2 or the HF/TR1P for an extra charge of £1
We have a few only Collaro Mk. III Transcriptor Tape Decks . . . offered at £17/19/6 (Carriage and Insurance 10/- extra).

TO COMPLETE THE RECORDER . . . WE OFFER

The Portable Carrying Case . . . Acos
Crystal Mike . . . Rola 10" × 6" P.M.
SPEAKER . . . 1,200ft. Plastic Tape

ALL FOR **£9.0.0** (plus 7/6 Carr. & ins.)

RECORD PLAYERS

THE VERY LATEST MODELS ARE IN STOCK

MANY AT REDUCED PRICES ! ! ! !

TRANSCRIPTION UNITS—AUTOCHANGERS SINGLE RECORD PLAYERS

Send S.A.E. for ILLUSTRATED STOCK LIST

A FEW CASH BARGAINS
ALL ARE BRAND NEW UNITS

● The latest 15 S.t Monarch 4-speed mixer Autochanger — entirely complete with crystal pick-up **£7.19.6**

● The latest Collaro 4-speed Auto-changer — complete with the Studio "O" Pick-up **£7.19.6** Also available with the low gain Studio "P" pick-up for **£8/15/-.**

● The latest Collaro 4-speed Single Record Player complete with Studio "O" Pick-up **£6.19.6**

● The Collaro Junior 4-speed Single Record Player complete with separate Pick-up **£4.10.0**
(This high output crystal pick-up is available separately for **£1/12/6.**)

(Carriage and insurance on above units 5/- extra.)

STERN'S "fidelity" F.M. TUNING UNIT

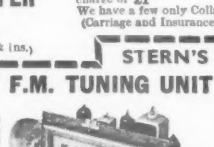

A 5-Valve Tuner incorporating the latest **Mullard Permeability Tuned Unit.** Price assembled less Power Supply.

£14.10.0

(Plus 7/6 carr. and ins.)

TERMS: (a) **H.P.** Deposit **£7/5/-** and 9 monthly payments of **18/4.**
(b) **Credit** Deposit **£3/12/6** and 9 monthly payments of **£1/6/7.** Provides " Hi-Fi " reproduction with any make of Amplifier and many Radio Receivers. It incorporates:
● The latest Valve line-up—ECC85 2 type EF85. EF91 and EM80. ● A " Magic Eye " Indicator. ● Power consumption is 1.7 amps. at 6.3 volts and 25 m/s at 250 volts

STERN'S "fidelity" COMBINED A.M. and F.M. TUNING UNIT

This is IDENTICAL to the Stern's F.M. Tuner illustrated above, but in addition incorporates the MEDIUM WAVE-BAND and thereby also provides a selection of foreign stations. **PRICE £18.18.0** (Plus 7/6 carr. and ins.).

TERMS:—(a) **H.P.** Deposit **£9/9/-** and 10 monthly payments of **£1/1/-**; (b) Credit Deposit **£4/15/-** and 9 monthly payments of **£1/14/7. Send S.A.E.** if further details required

HOME CONSTRUCTORS . . . You can build
(a) The " fidelity " F.M. TUNING UNIT FOR **£10.0.0**
(b) The "fidelity" AM/FM TUNING UNIT for **£13.10.0**

The COMPLETE ASSEMBLY DIAGRAMS and INSTRUCTIONS CAN BE OBTAINED FOR 1/6 each.

SPECIAL CASH ONLY OFFER ! !

This very attractive **PORTABLE AMPLIFIER CASE** together with a good quality **GRAM AMPLIFIER** and a matched **P.M. SPEAKER, ALL FOR ONLY £8.7.6**

(plus 7/6 carr. & ins.). The Amplifier consists of a 2 Stage design incorporating the 3 modern BVA valves and has separate BASS and TREBLE CONTROLS. The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Grey colour Rexine—WE ALSO SUPPLY SEPARATELY:—

(a) The 2-Stage (plus Rectifier) **AMPLIFIER**	£4	2	6
(b) The **PORTABLE CARRYING CASE**	£3	17	6
(c) **6½in. P.M. SPEAKER**		18	9

(Carriage and insurance 4/- extra.)

We also have a smaller **PORTABLE CASE Ideal for Record Players.** PRICE ONLY **£3/3/-** (plus carriage and ins.)

Open Monday to Friday 9 a.m.—6 p.m.
Saturdays 9 a.m.—1 p.m.

STERN RADIO LTD.

THE 1958 NEW LOOK

MULLARD DESIGNS FOR THE HOME CONSTRUCTOR

AMPLIFIERS PRE-AMPLIFIERS

COMPLETE KITS OF PARTS FOR THE "HI-FI" ENTHUSIAST
Designed by MULLARD—Presented by US strictly to their specification

THE VERY POPULAR MULLARD "5-10" MAIN AMPLIFIER

Undoubtedly the most successful amplifier yet designed and used in conjunction with the new Mullard Pre-Amplifier, an undistorted power output of up to 10 watts is obtained. Thoroughly recommended to the "Hi-Fi" enthusiast who contemplates a very high quality home installation. In addition the versatility of the equipment makes it quite suitable for use in small halls, etc. We supply complete to MULLARD'S SPECIFICATION with specified valves and components and including the latest PARMEKO Ultra linear Output transformer and the Parmeko mains transformer which has power available to drive Radio Tuning Unit.

Price for COMPLETE KIT OF PARTS..... **£10.0.0**
Alternatively we supply ASSEMBLED and TESTED **£11.10.0**
(Carriage and insurance 5/- extra).

We also offer this "5-10" incorporating the latest PARTRIDGE ULTRA-LINEAR OUTPUT TRANSFORMER for £1/6/- extra.

SPECIAL PRICE REDUCTIONS—WE OFFER

(a) THE COMPLETE KIT of PARTS to build both the "3-3" MAIN AMPLIFIER and the 2-stage PRE-AMPLIFIER-CONTROL UNIT **£12.10.0**

(b) THE COMPLETE KIT or PARTS to build both the "5-10" MAIN AMPLIFIER and the 2-STAGE PRE-AMPLIFIER-CONTROL UNIT **£15.15.0**

ALL PRICES QUOTED FOR THE "5-10" ARE SUBJECT TO £1/6/- EXTRA IF THE PARTRIDGE TRANSF. IS REQUIRED.

When ordering please include an extra 7/6 to cover the cost of carriage and insurance

MULLARD'S NEW 2-STAGE PRE-AMPLIFIER-TONE CONTROL UNIT

A completely new design employing two EF86 valves, and in particular designed to operate with the Mullard range of Power Amplifiers, but also perfectly suitable for other makes. Briefly it incorporates:—

- Equalisation for the latest R.I.A.A. characteristics.
- Input for variable reluctance. Magnetic Pick-ups.
- Input for Crystal Pick-ups.
- Input for Tape replay.
  - (a) Direct from High Impedance Tape Head.
  - (b) From a Tape Amplifier or Pre-Amplifier.
- Sensitive Microphone Channel.
- Wide range BASS and TREBLE Controls
- Attractive Perspex front control panel.
- Our Kit is strictly to MULLARD'S SPECIFICATION.

Price, COMPLETE KIT OF PARTS..... **£6.6.0**
Alternatively we supply ASSEMBLED and TESTED **£8.0.0**
(Carriage and Insurance 5/- extra.)

Only NEW HIGH GRADE Components and Mullard Valves are supplied with these kits—we DO NOT use "Surplus or Cheap" components.

Please enclose S.A.E. if ILLUSTRATED and DESCRIPTIVE LEAFLETS are required . . . alternatively the COMPLETE ASSEMBLY MANUALS containing component Price Lists and practical Drawings etc. are available at 1/6 each.

(a) THE "3-3" and the 2-STAGE PRE-AMPLIFIER both ASSEMBLED and TESTED..... **£15.0.0**

CREDIT TERMS: DEPOSIT £3/15/- and 9 monthly payments of £1/7/6.
H.P. TERMS: DEP. £7/10/- & 9 monthly payments of 19/-.

(b) THE "5-10" and the 2-STAGE PRE-AMPLIFIER both ASSEMBLED and TESTED **£18.18.0**

CREDIT TERMS: DEPOSIT £4/15/- and 9 monthly payments of £1/14/7.
H.P. TERMS: DEP. £9/9/- & 12 monthly payments of 17/6.

THE NEW MULLARD "3-3" MAIN AMPLIFIER

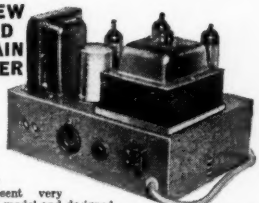

Based entirely on the present very popular "3-2" model and designed to operate in conjunction with the new 2-stage PRE-AMPLIFIER (shown here) thus providing all the facilities associated with the more expensive "Hi-Fi" equipment. We recommend it as the IDEAL SMALL HOME INSTALLATION where very high quality is desired at the lower volume level (up to 3 watts).

We supply completely to MULLARD'S SPECIFICATION INCLUDING the latest PARMEKO Output Transformer specified Valves and Components. Has Power available to drive a Radio Tuning Unit.

Price for COMPLETE KIT of PARTS **£7.0.0**
Alternatively we supply ASSEMBLED and TESTED **£8.0.0**
(Carriage and Insurance 5/- extra.)

THE NEW COMPLETE MULLARD "3-3"

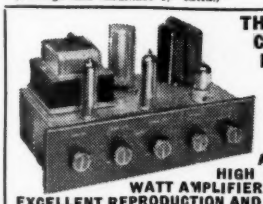

A VERY HIGH QUALITY 3 WATT AMPLIFIER PROVIDING EXCELLENT REPRODUCTION AND HAVING AN ATTRACTIVE ENGRAVED PERSPEX FRONT PANEL.

Price for COMPLETE KIT OF PARTS.... **£7.10.0**
(plus 6/6 carriage and insurance.)
Alternatively supplied ASSEMBLED and FULLY TESTED..... **£8.19.6**
(plus 6/6 carriage and insurance.)

The complete specification is available for 1/6.

Developed from the very popular 3-valve 3-watt Amplifier designed in the Mullard Laboratories. Our kit is complete to the Mullard specification, including supply of specified components, valves and PARMEKO OUTPUT TRANSFORMER. We also include switched inputs for 78 and L.P. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available.

THE NEW COMPLETE MULLARD "5-10" AMPLIFIER

We offer this popular and very successful design COMPLETE to MULLARD'S SPECIFICATION, but incorporating some improvements in the general layout. HIGH QUALITY REPRODUCTION up to a maximum of 10 watts output. The CONTROL UNIT is separate and completely enclosed; it is normally fitted to the Main Amplifier Chassis as shown in the illustration but, if it is desired to use the unit remote from the Main Chassis, it can be quite easily detached and used up to 2 yards distance. We incorporate SPECIFIED COMPONENTS and NEW MULLARD VALVES. We also give the purchaser the choice of two of the best ULTRA-LINEAR OUTPUT TRANSFORMERS made—first the latest by PARMEKO LTD., and also the latest by PARTRIDGE (£1/6/- extra) which is generally recognised as the best U/L Output Transformer made today and ensures maximum undistorted output and the widest frequency range. We also supply the PARMEKO MAINS TRANSFORMER, and this has extra power available to supply a Radio Tuning Unit amounting to 200 volts at m/a and a separate heater winding giving 6.3 volts 2½ amps.

Price COMPLETE KIT OF PARTS (PARMEKO TRANSFORMER) **£11.10.0**
Alternatively we supply ASSEMBLED and TESTED..... **£13.10.0**
Credit Sale: Dep. £3/7/6 and 9 monthly payments of £1/4/11. H.P. Terms: Dep. £6/15/- and 8 monthly payments of 19/3.
Send S.A.E. for ILLUSTRATED LEAFLET or 1/6 for the COMPLETE ASSEMBLY MANUAL.

HOME CONSTRUCTORS

BUILD YOUR OWN "Hi-Fi" LOUDSPEAKER SYSTEM

WITH W-B's WELL-KNOWN RANGE OF READY-TO-ASSEMBLE CABINETS. ALL ARE BEAUTIFULLY MADE AND FINISHED AND VERY EASILY ASSEMBLED. ONLY A SCREWDRIVER IS REQUIRED, THEY ARE PACKED FLAT IN CARTONS AND COMPLETE WITH SCREWS.

Send S.A.E. for illustrated leaflet—it contains a selection of 10 CABINETS including models to accommodate Amplifiers, Pre-amplifiers, Tuning Unit, Record Player, etc. Prices from £5/10/-. THE W.B. STENTORIAN "Hi-Fi" P.M. Speakers are also in Stock.

A COMPLETE KIT OF PARTS, STERN'S 8-10 WATT AMPLIFIER

Has power supply available for Radio Tuning Unit.
Price of COMPLETE KIT OF PARTS (plus 5/- carr. & ins.) **£7.10.0**
WE ALSO OFFER IT ASSEMBLED and READY FOR USE for (plus 5/- carr. & ins.). **£9.10.0**

This amplifier has proved one of the most popular models yet offered to the HOME CONSTRUCTOR. It provides really excellent reproduction up to 8 watts, employing 6V6's in push-pull and incorporating negative feedback. Provides for the use of both 3 and 15 ohm Speakers. The complete SPECIFICATIONS and BUILDING INSTRUCTIONS ARE AVAILABLE for 1/6.

A Selection of RADIOGRAM CHASSIS enabling "MODERNISATION" of that OLD RADIOGRAM

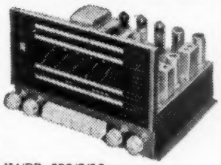

ALL ARE THE LATEST AM/FM DESIGN

- The Dulci Model H.3 **£20/17/-**
- The Dulci Model H.4 **£24/6/6.**
- The Dulci Model H4/PP **£29/3/10.**
- The ARMSTRONG PB.409 **£29/8/-.**
- The ARMSTRONG AF105 **£37.**

We also have the latest FM or combined AM/FM RADIO TUNING UNITS.

- THE Dulci FM Tuner incorporating Power Supply **£17/10/3.**
- The NEW DULCI AM/FM, TUNER model H4T/2 incorporating own Power Supply **£34/19/-.**
- JASON "MERCURY" SWITCHED F.M. TUNER (a) KIT OF PARTS **£9/19/6.** (b) Assembled and Tested **£14/10/-.**

The Above are just a few examples—we have others—Send S.A.E. for full data on any chassis.
Credit Sale and H.P. Terms are available.

"FRUSTRATED EXPORT ORDER"

The Cossor Model 527/X 4 Valve "All-dry" Battery Set.
Offered For **£6.15.0**
Plus 5/- carr. & ins.

Consists of a 4 valve Superhet Receiver covering Medium Waveband 197-575 metres, and two Short Wavebands 13.6 to 135 metres. The new low consumption valves are incorporated and the whole is accommodated in an attractive robustly made case. Battery required is 90 volts and 1.4 volts (price 19/6) and is external to case.

Please enclose S.A.E. with all enquiries

109-115 FLEET ST. LONDON E.C.4

Phone: FLEet Street 5812-3-4.

SEND FOR LEAFLET OF EASY TO ASSEMBLE CABINETS FOR HI-FI EQUIPMENT. AVAILABLE CASH OR CREDIT.

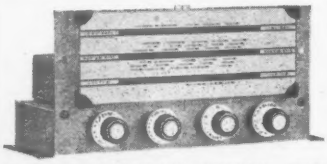

AM/FM RADIOGRAM CHASSIS, HIGH QUALITY. PUSH PULL. 6-8 WATTS OUTPUT

Current manufacture. 12 months' guarantee. For 200-250 v. mains. Covers L. and M. Wavebands plus F.M. Includes 8 latest type miniature B.V.A. valves. Only **22 gns.** plus 7/6 carr. Or deposit £2/12/- and 9 monthly payments of £2/12/-. Guaranteed 12 months.

AM/FM RADIOGRAM

29½ GNS.

By leading manufacturer. Brand new, cartoned, 4 wavebands including V.H.F. Auto-changer at 3 speeds, Hi-Fi pick-up with duo point sapphire stylus. For 200-250 v. 50 c.p.s. A.C. mains. Limited stocks at a fraction of listed price. Only 29½ gns. Or Deposit £6/19/6 and 9 monthly payments of 3 gns. Carr. 10/-.

THE SKY FOUR T.R.F. RECEIVER

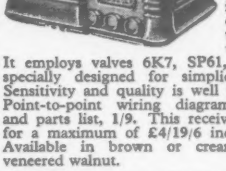

A design of a 3 valve 200-250 v. A.C. Mains L. & M. wave T.R.F. receiver with selenium rectifier. For inclusion in cabinet illustrated or walnut veneered type. It employs valves 6K7, SP61, 6F6G, and is specially designed for simplicity in wiring. Sensitivity and quality is well up to standard. Point-to-point wiring diagrams, instructions and parts list, 1/9. This receiver can be built for a maximum of £4/19/6 including cabinet. Available in brown or cream bakelite, or veneered walnut.

R.T.C. 12in. "SUPER HI-FI 25" LOUDSPEAKER UNIT

With mechanical damping device. A 25 watt 15 ohm precision built moving coil unit with 17,600 line Alcomax magnet. Frequency range 25–20,000 c.p.s. Designed to provide lifelike reproduction in large halls, theatres, cinemas, etc. Only **12 gns.** Or Deposit 28/9 and 9 monthly payments of 28/9.

AI2 12 Watt HIGH FIDELITY AMPLIFIER with SEPARATE PRE-AMPLIFIER. Ready for use **14 GNS.** Carr. 10/-.

Valve line-up ECC83, EF86, ECC83, EL84, EL84, EZ81. Frequency response ±3 d.b. 30-20,000 c.p.s. Sensitivity 4 m.v. at 'mike' input; 30 m.v. L.P. Gram., 27 m.v. 78 r.p.m. Gram.; 75 m.v. Radio. Filter 9 Kc/s and 5 Kc/s. Turnover. 4 position equalisation (tone compensation) switch and separate input sockets. Separate Bass and Treble controls. Bass +9 d.b. to −9 d.b. Treble +9 d.b. to −9 d.b. Pre-amp. size 11 x 4½ x 2¾in. Front plate 12 x 3½in. Main amplifier 9 x 7 x 6in. Chassis finished stoved gold/bronze. For operation on 200-250 v. 50 c.p.s. A.C. mains. Power supply at 4-pin socket available for Radio Tuner. H.T. 250 v. 35 ma. L.T. 6.3 v. 1.5 a. This unit is designed for use with high quality ancilliary equipment to provide sound realism in the home.

COLLARO RC54 3 SPEED MIXER AUTO-CHANGER

Fitted studio pick-up with turnover head. Brand new cartoned but for 110 v. 50 c.p.s. A.C. mains. So that the unit can be operated from normal 200-250 v. A.C. mains we are supplying free with every changer a suitable auto-transformer with input and output voltages clearly marked. Limited number only. £6/19/6. Carr. 5/6.

COLLARO 4-SPEED AUTO-CHANGERS

With studio pick-up with turnover head, BRAND NEW. Cartoned latest model. For 200-250 v. A.C. mains. Very limited number Conquest £8/19/6. Continental 9 **gns.** Carr. 5/6.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

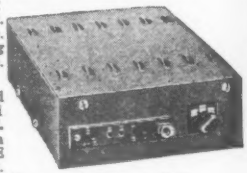

Type BM1. An all dry battery eliminator. Size 5½ × 4½ × 2in. approx. Completely replaces batteries supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s. is available. **Suitable for all battery portable receivers requiring 1.4 v. and 90 v.** This includes latest low consumption types. Complete kit with diagram 39/9 or ready for use 46/9.

Type BM2. Size 8 × 5½ × 2¾in. Supplies 120 v., 90 v., and 60 v. 40 mA. and 2 v. 0.4 a. to 1 amp. fully smoothed **THEREBY COMPLETELY REPLACING BOTH H.T. BATTERIES AND L.T. 2 v. ACCUMULATORS** when connected to A.C. mains supply 200-250 v. 50 c/s. SUITABLE FOR ALL BATTERY RECEIVERS normally using 2 v. accumulator. Complete kit with diagrams and instructions, 49/9, or ready for use, 59/6.

R.S.C. TRANSFORMERS

FULLY GUARANTEED. INTERLEAVED AND IMPREGNATED

MAINS TRANSFORMERS

Primaries 200-230-250 v. 50 c/s.

FULLY SHROUDED UPRIGHT MOUNTING

250-0-250 v. 60 mA., 6.3 v. 2 a., 5 v. 2 a.	17/6
250-0-250 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a.	23/9
250-0-250 v. 100 mA., 6.3 v. 6 a., 5 v. 3 a., for R1355 conversion	31/-
300-0-300 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a.	25/9
350-0-350 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a.	25/9
300-0-300 v. 130 mA., 6.3 v. 4 a., c.t., 6.3 v. 1 a., suitable for Mullard 510 Amplifier	33/9
375-0-375 v. 150 mA., 6.3 v. 4 a., 5 v. 2 a.	29/9
350-0-350 v. 150 mA., 6.3 v. 4 a., 5 v. 3 a.	33/9
350-0-350 v. 150 mA., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a.	33/9
425-0-425 v. 200 mA., 6.3 v. 4 a., c.t., 6.3 v. 4 a., c.t., 5 v. 3 a., suitable Williamson Amplifier, etc.	49/9

TOP SHROUDED DROP-THROUGH TYPE

260-0-260 v. 70 mA., 6.3 v. 2 a., 5 v. 2 a.	16/9
350-0-350 v. 80 mA., 6.3 v. 2 a., 5 v. 2 a.	18/9
250-0-250 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a.	22/9
300-0-300 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a.	23/9
350-0-350 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a.	23/9
350-0-350 v. 150 mA., 6.3 v. 4 a., 5 v. 3 a.	29/9

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s.

120 v. 40 mA., 5-0-5 v. 1 a.	14/9
90 v. 15 mA., 6-0-6 v. 250 mA.	9/11

FILAMENT TRANSFORMERS

Primaries 200-250 v. 50 c/s.

6.3 v. 1.5 a.	5/9	6.3 v. 3 a.	8/11
6.3 v. 2 a.	7/6	6.3 v. 6 a.	17/6
0-4-6.3 v. 2 a.	7/9	12 v. 3 a. or 12 v. 1 a.	7/9
25 v. 1.5 a.	17/6		

CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s. Primaries: 0-9-15 v. 1½ a., 11/9; 0-9-15 v. 3 a., 16/9; 0-9-15 v. 5 a., 19/9; 0-9-15 v. 6 a., 23/9.

OUTPUT TRANSFORMERS

Midget Battery Pentode 66:1 for 3S4, etc.	3/6
Small Pentode 5,000Ω to 3 Ω	3/9
Standard Pentode, 5,000 Ω to 3 Ω	4/6
Standard Pentode, 8,000 Ω to 3 Ω	4/9
Push-pull 8 watts 6V6 to 5 ohms	8/9
Push-pull 10-12 watts 6V6 to 3 Ω or 15 Ω	15/9
Push-pull 10-12 watts to match 6V6 to 3-5-8 or 15 Ω	16/9
Push-pull EL84 to 3 or 15 ohms	16/9
Push-pull 15-18 watts, sectionally wound, 6L6, KT66, etc., to 3 or 15 ohms	21/9
Push-pull 20 watt high-quality sectionally wound, 6L6, KT66, etc. to 3 or 15 Ω	47/9

SMOOTHING CHOKES

250 mA., 5 H., 100 ohms	11/9
150 mA., 7-10 H., 250 ohms	11/9
100 mA., 10 H., 200 ohms	8/9
80 mA., 10 H., 350 ohms	5/6
60 mA., 10 H., 400 ohms	4/11
1 amp. 0 5 ohm. L.T. type	6/6

SELENIUM RECTIFIERS

L.T. Types	
2/6 v. ½ a.h.w.	1/9
6/12 v. ½ a.h.w.	2/9
F.W. Bridge	
6/12 v. 1 a.	4/11
6/12 v. 2 a.	9/9
6/12 v. 3 a.	11/9
6/12 v. 4 a.	14/9
6/12 v. 6 a.	19/9
6/12 v. 10 a.	25/9
H.T. Type H.W.	
120 v. 40 mA.	3/9
250 v. 50 mA.	5/9
250 v. 80 mA.	7/9
350 v. 60 mA.	7/9
250 v. 250 mA.	10/9

BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250v. 50 c/s. Guaranteed 12 months

ASSEMBLED CHARGERS

6 v. 1 a.	19/9
6/12 v. 1 a.	27/9
6 v. 2 a.	29/9
6/12 v. 2 a.	38/9
6/12 v. 4 a.	56/9

Above ready for use with mains and output leads. Cases well ventilated and finished in stoved blue hammer. Carr. and packing 3/6.

BATTERY CHARGER KITS

Consisting of Mains Transformer F.W. Bridge. Metal Rectifier, well ventilated steel case. Fuses, Fuse-holders, Grommets, panels and circuit. Carr. 2/6 extra.

6 v. or 12 v. 1 amp.	22/9
6 v. 2 amps.	25/9
6 v. or 12 v. 2 amps.	31/6
6 v. or 12 v. 4 amps.	53/9

BATTERY CHARGER KIT Consisting of F.W. Bridge Rectifier 6/12 v. 5 a. Mains Trans. 0-9-15 v. 6 a. output, and ammeter. Only 49/9. Post 3/-.

ASSEMBLED CHARGER

6 v. or 12 v. 2 amps. Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case, finished attractive hammer blue. Ready for use with mains and output leads. Double Fused. Only **49/9** Carr. 3/6.

Assembled 6v. or 12v. 4 amps.

Fitted Ammeter and variable charge selector. Also selector plug for 6 v. or 12 v. charging. Double fused. Well ventilated steel case with blue hammer finish. **75/-** Ready for use with mains and output leads. Carr. 3/9. Or Deposit 30/- and four monthly payments 13/-.

R.S.C. A10 ULTRA LINEAR 30 WATT AMPLIFIER

HIGH FIDELITY PUSH-PULL UNIT EMPLOYING SIX VALVES. EF86, EF86, ECC83, 807, 807, GZ34. Tone Control Pre-amp. stages are incorporated. Sensitivity is extremely high. Only 12 millivolts minimum input is required for full output. **THIS ENSURES THE SUITABILITY OF ANY TYPE OR MAKE OF MICROPHONE OR PICK-UP.** Separate Bass and Treble controls give both "lift" and "cut" with ample tone correction for long playing records. An extra input with associated vol. control is provided so that two separate inputs such as "mike" and gram., etc., etc., can be simultaneously applied for mixing purposes. **AN OUTPUT SOCKET WITH PLUG IS INCLUDED FOR SUPPLY OF 300 v. 20 mA. and 6.3 v. 1.5 a. FOR A RADIO FEEDER UNIT.** Price in kit form with easy-to-follow wiring diagrams. Cover as illustrated 18/9 extra. Only **11 Gns.** carr. 10/-. Or Factory built with 12 months' guarantee £13/19/6. **TERMS ON GARRISON THEATRES, etc., etc. We can supply Microphones, ASSEMBLED UNITS. DEPOSIT 36/9** and 9 monthly payments of 31/9. **Speakers, etc., at keen cash prices or on terms with amplifiers. EXPORT ENQUIRIES INVITED**

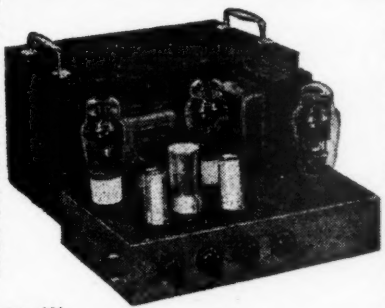

Type 807 output valves are used with High Quality Sectionally wound output transformer specially designed for Ultra Linear operation. Negative feedback of 20 D.B. in main loop. **CERTIFIED PERFORMANCE FIGURES ARE EQUAL TO MOST EXPENSIVE UNITS AVAILABLE.** Frequency response ± 3 D.B., 30-20,000 c/s., Tone Controls ± 12 D.B. at 50 c/cs., + 12 D.B. to − 6 D.B. at 12,000 c/cs., Hum and noise 70 D.B. down. Good quality reliable components used. Chassis finish blue hammer. Overall size 12×9×9in. approx. Power consumption 150 watts. For A.C. mains 200-230-250 v. 50 c/cs. Outputs for 3 and 15 ohm speakers. **EQUALLY SUITABLE FOR THE CONNOISSEUR OR FOR LARGE HALLS, CLUBS, or OUTSIDE FUNCTIONS. IDEAL FOR USE WITH MUSICAL INSTRUMENTS SUCH AS STRING BASS, ELECTRONIC ORGAN, GUITAR, etc. FOR DANCE BANDS,** etc., etc.

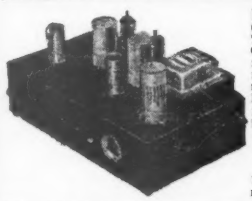

LINEAR LT/45 HIGH QUALITY TAPE DECK AMPLIFIER COMPLETE with POWER PACK and OSC. STAGE. Suitable for Collaro, Lane, Truvox, Aspden, Brennell, etc., etc. State make of Deck when ordering. Chassis size 12-7-3in. Overall size 12-7-6¼in. For 200-250 v. 50 c/cs. A.C. mains. Output for standard 2-3 ohm speaker. Only 15 millivolts input required for full recording. Only 2 millivolts minimum output required from recording head. Magic Eye recording level indicator. Provision for feeding P.A. amplifier. Negative feed-back equalisation. Linear frequency response ±3 D.B. 50-11,000 c/cs. Facilities for recordings at 15in., 7½in. or 3¾in. per second. Automatic equalisation at the turn of a knob. When switching from record to playback position automatic demagnetisation of heads is assured. Separate gain and output controls. Valves type ECC83, ECC83, EL84, EZ80, EM34. Output 4 watts. Unit supplied with maker's 12 months' guarantee. We know of no other make which represents the same exceptional value. Leaflet 6d.

12 Ready for use **GNS.** Carr. 7/6

COLLARO JUNIOR 4 SPEED RECORD PLAYER with separate pick-up having dual point sapphire stylus. Brand new, cartoned. For 200-250 v. A.C. mains only. Only **4 GNS.** Post 3/6.

LG3 MINIATURE 3 WATT GRAM. AMPLIFIER For 200-250 v. 50 c.p.s. A.C. Mains. Overall size only 6½×4½×2½in. Fitted vol. and Tone Control with mains switch. Designed for use with any kind of single player or record changing unit. Output for 2-3 ohms speaker. Guaranteed 12 months. Only **55/9**

R.S.C. A5 4-5 WATT HIGH GAIN AMPLIFIER

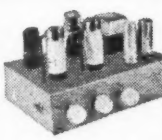

A highly sensitive 4-valve quality amplifier for the home, small club etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity pick-up heads in addition to all other types of pick-ups and practically all mikes. Separate Bass and Treble controls are provided. These give full long playing record equalisation. Hum level is negligible being 71 D.B. down. 15 D.B. of negative feedback is used. H.T. of 300 v. 26 mA. and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit or Tape Deck pre-amplifier. For A.C. mains input of 200-230-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with the blue hammer finish, and point-to-point wiring diagrams and instructions. Exceptions value at only **24/15/-** or assembled ready for use **25/-** extra, plus 3/6 carriage. Or Deposit **22/-** and five monthly payments of **22/-** for assembled unit.

R.S.C. A7 3-4 WATT QUALITY AMPLIFIER A highly sensitive 4-valve amplifier using negative feedback and having an excellent frequency response. Pre-amplifier and Tone Control stages are incorporated with separate Bass and Treble controls giving full tone compensation for long playing records. Suitable for any kind of pick-up including latest high fidelity types. H.T. of 250 v. 20 mA. and L.T. 6.3 v. 1 a., available for supply of Radio Feeder Unit etc. ONLY 40 millivolts input required for full output. Fully isolated chassis with baseplate. For A.C mains 200-250 v. 50 cycles. Output for 2-3 ohms speaker. Complete kit of parts, point-to-point wiring diagrams and instructions. Only **23/15/-**, carr. 3/6 or factory built **25/-** extra.

SENSATIONAL OFFER

STAAR GALAXY 4-SPEED MIXER AUTO-CHANGERS

A precision manufactured unit with unique fingertip control. Pick-up fitted with dual sapphire tipped stylus. A very compact changer in attractive duo-tone finish. For A.C. mains 110—250v. Brand new, cartoned. **£4/19/6.** *Post 4/6.*

ACOS HIGH FIDELITY PICK-UPS. GP54 with HGP59/62 cartridge. Dual point sapphire stylus. Cream finish. A fortunate purchase enables us to offer these at approx. half price. Only **29/11**

LINEAR "DIATONIC" 10-WATT HIGH FIDELITY AMPLIFIER. Incorporating pre-amp. For A.C. mains input 200-230-250 v. 50 c.p.s. A compact attractively finished unit with two separately controlled inputs and outputs for 3 and 15 ohms speakers. Separate Bass and Treble controls. Five latest type miniature Mullard valves. Only **12 Gns.** Send S.A.E. for leaflet and credit terms.

LINEAR L45 MINIATURE 4/5 W. QUALITY AMPLIFIER. Suitable for use with Garrard, B.S.R. or any other record playing unit and most microphones. Total negative feedback 12 D.B. Separate Bass and Treble controls. For A.C. mains input of 200-250 v. 50 c.p.s. Output for 2/3 ohm speaker. Three miniature Mullard valves used. Size only 6×5×5¼in. high. Chassis fully isolated from mains. Guaranteed 12 months. Only **£5/19/6.** Or Deposit **22/-**, and five monthly payments of **22/-**. Send S.A.E. for leaflet.

PLESSEY DUAL CONCENTRIC 12in. P.M. SPEAKERS

(15 ohms), consisting of a high quality 12in. speaker of orthodox design supporting a small elliptical speaker ready wired with choke and condensers to act as tweeter. This high fidelity unit is highly recommended for use with our A11 or any similar amplifier. Rating is 10 watts. Gauss 12,000 lines. Price only **£5/17/6.** Or Deposit **13/-** and nine monthly payments of **13/-.**

A11 ULTRA LINEAR 12-14 WATT AMPLIFIER

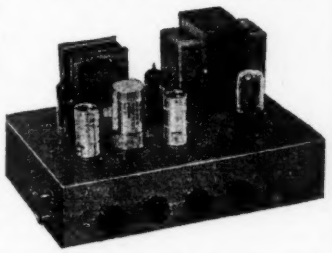

NEW 1958 DESIGN HIGH-FIDELITY PUSH-PULL AMPLIFIER WITH "BUILT-IN" TONE CONTROL PRE-AMP. STAGES

Two input sockets with associated controls allow mixing of "mike" and gram. as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, 5Y3. High Quality sectionally wound output transformer specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut." Frequency response ±3 DB 30-30,000 c/cs. 8ix negative feedback loops. Hum level 60 DB down **ONLY 23** millivolts INPUT required for **FULL OUTPUT.** Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs. For **STANDARD** or **LONG PLAYING RECORDS.** For **MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS** etc., **OUTPUT SOCKET** with plug provides 300 v. 30 m.a. and 6.3 v. 1.5 a. For supply of a **RADIO FEEDER UNIT.** Size approx. 12-9-7in. For A.C. mains 200-230-250 v. 50 c/cs. Output for 3 and 15 ohms speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied.

Only **8 GNS.** Or factory built **45/-** extra. Carr. 10/-. If required louvred metal cover with 2 carrying handles can be supplied for **18/9. TERMS ON ASSEMBLED UNITS. DEPOSIT 25/6** and nine monthly payments of **25/6.** Send S.A.E. for Illustrated leaflet detailing. Ready-to-assemble Cabinets, Speakers, Microphones, etc., with cash and credit terms.

W.B. "STENTORIAN" HIGH FIDELITY P.M. SPEAKERS

HF1012, 10 watts 15 ohm (or 3 ohm) speech coil. Where a really good quality speaker at a low price is required, we highly recommended this unit with an amazing performance. £4/10/9. Please state whether 3 ohm or 15 ohm required.

P.M. SPEAKERS

2-3 ohm 2½in. Rola **17/9.** 5in. Goodmans **17/9.** 7×4in. Elliptical **19/9.** 6½in. Rola, **19/9.** 8in. Rola, **19/9.** 8in. Goodmans **21/9.** 10in. R.A., **28/9.** 10×6in. Elliptical Goodmans **29/9.** 12in. Plessey **29/11.** 12in. Plessey 3 ohms, 10 watts, 12,000 lines, **59/6.**

SUPERHET RADIO FEEDER UNIT

Design of a high quality Radio Tuner Unit (specially suitable for use with any of our Amplifiers). A Triode Heptode F/changer is used. Pentode I.F. and double Diode Second Detector, delayed A.V.C. is arranged so that A.V.C. distortion is avoided. The W.Ch. 8w. incorporates Gram. position. Controls are Tuning, W. Ch. and Vol. Output will load most Amplifiers requiring 500 mV input depending on Ae location. Only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size of unit approx. 9-6-7in. high. Send S.A.E. for illustrated leaflet. Total building cost is **£4/15/-.** Point-to-point wiring diagrams and instructions, **2/6.**

Radio Supply Co. (LEEDS) LTD.

Personal Shoppers to **MAUDE ST.** (Opposite Parish Church School) **LEEDS, 2.**
Mail Orders to **29-31, Moorfield Road, LEEDS, 12.**

Terms: C.W.O. or C.O.D. No. C.O.D. under £1. Postage 1/9 extra on all orders under £2. 2/9 extra under £5 unless carriage charge stated. Full Price List 6d. Trade List 5d. Open to Callers: 9 a.m. to 5.30 p.m. Saturday until 1 p.m. S.A.E. please with all enquiries.

RADIO SUPPLY CO. (LEEDS) LTD.

(Dept. D) Maude Street, (Opposite Parish Church School) Leeds, 2.

FOR TERMS SEE DISPLAYED ADVERT PAGE 123

CO-AXIAL CABLE. 75 ohms, ¼in., 8d. yard. Twin screened feeder 11d. yard.

ELECTROLYTICS (current production) Not Ex-Govt.

Tubular Types		Can Types	
8 mfd. 450 v.	1/9	16μF 450 v.	2/9
8 mfd. 500 v.	2/6	32μF 350 v.	2/11
16μF 350 v.	1/11	32 mfd. 450 v.	4/9
16μF 450 v.	2/9	100 mfd. 450 v.	4/9
16μF 500 v.	3/9	8-8μF 450 v.	2/11
25μF 25 v.	1/3	8-16μF 450 v.	3/11
50μF 12 v.	1/3	16-16μF 450 v.	3/11
50 mfd. 25 v.	1/9	32-32μF 350 v.	4/9
50μF 50 v.	1/9	32-32μF 450 v.	5/9
100 mfd. 12 v.	1/9	100-100 mfd. 350 v.	5/9
100 mfd. 25 v.	2/3	150 mfd. 450 v.	5/9
3,000 mfd. 6 v.	3/9	100-200 mfd. 275 v.	6/11
6,000 mfd. 6 v.	3/11		

VOLUME CONTROLS with long spindles, all values, less switch, 2/9; with S.P. switch, 3/9.

EX GOVT. STEP UP/STEP DOWN TRANSFORMERS. Double wound 80/100 watts. 10-0-100-200-220-240 v. to 5-0-75-115-125-135 v. or Reverse. Only 12/9 plus 2/9 post 10-0-100-200-220-240 v. to 9-0-110-122-136-148 v. or Reverse. 300 watts, 35/9, plus 7/6 carr.

EX GOVT. METAL BLOCK PAPER CONDENSERS

8 mfd. 500 v... 4/6 10 mfd. 500 v. 3/9

EX GOVT. VIBRATOR UNITS. 12 v. input, 280 v. output. Suitable for Car Radio, etc. 16/6.

VIBRATORS, oak and Wearite, synchronous 7 pin, 2 v. 7/9, 6 v. 8/9.

JUNCTION TRANSISTORS. R.F. type 17/6, A.F. 7/9.

INSTRUMENT KNOBS. Black 1¼in. diam. Standard type 1/- each. 9/- doz. 90/- gross.

BAKELITE FUSE HOLDERS. Panel mtg. 4/6 doz.

RE-ENTRANT SPEAKERS. Tannoy 8 watt, 7.5 ohms, 25/- each.

LINEAR 50 WATT HIGH FIDELITY AMPLIFIER Sensitivity 25 millivolts for full output. Completely enclosed in well ventilated case with carrying handles. Suitable for any kind of Microphone or pick-up. Output matchings for 3 ohm and 15 ohm speakers. Brand New, cartoned. Guaranteed 12 months. For 200-250 v. 50 c.p.s. A.C. mains. Only 19 gns. Carr. 15/-. Or Deposit 3 gns. and 9 monthly payments of 42/3.

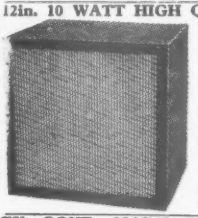

12in. 10 WATT HIGH QUALITY LOUDSPEAKERS IN POLISHED WALNUT FINISHED CABINET. Gauss 12,000 lines Speech coil 3 ohms or 15 ohms. Only £4/19/6, Carr. 5/-. Terms: Deposit 11/- and 9 monthly payments of 11/-.

EX GOVT. MAINS TRANSFORMERS All 200-250 v. 50 c/s input.

250-0-250 v. 60 mA., 6.3 v. 3 a., 6.3 v. 1 a. Potted 4½-3½-3in. 11/9

Pr. 0-110-200-230-250 v., 275-0-275 v. 100 mA., 6.3 v. 7 a., 5 v. 3 a. 21/9

230-0-230 v. 80 mA. 12.6 v. 1.5 a., 5 v. 2 a. 11/9

250-0-250 v. 150 mA. 5 v. 3 a. 16/9

350-0-350 v. 160 mA. 6.3 v. 5 a., 5 v. 3 a. 27/9

400-0-400 v. 250 mA. 5 v. 2 a., 5 v. 2 a. 18/9

450-0-450 v. 150 mA. 6.3 v. 5 a., 6.3 v. 1 a., 5 v. 3 a. 29/9

450-0-450 v. 250 mA. 6.3 v. 3 a., 6.3 v. 1 a., 5 v. 6 a. 49/9

12.5 v. 3 a., 5 v. 3 a. 12/9

0-24-26-28 v. 15 amp. A.C. conservative Gov. rating (marked with D.C. rating after rectification) 69/9. Carr. 10/-.

0-10-20-25 v. 24 a. (Gov. rating) 79/6. Carr. 15/-.

EXTENSION SPEAKERS Limited number in handsome Walnut veneered cabinets. 2-3 ohm speech coils. 6½in. 29/9. 8in. 35/9.

MANUFACTURERS' SURPLUS TRANSFORMERS. Primary 230-250 v. Drop through type 325-0-325 v. 100 mA., 6.3 v. 2.5 a., 5 v. 2 a. 17/9. Post 2/9.

EX GOVT. SMOOTHING CHOKES

250 mA., 20 H., 150 ohms	19/6
200 mA., 3 H., 50 ohms	9/9
150 mA., 10 H., 50 ohms	10/11
120 mA., 12 H., 100 ohms	9/9
100 mA., 10 H., 100 ohms	6/9
100 mA., 5 H., 100 ohms, tropicalised	3/11
80 mA., 20 H., 900 ohms	6/9

EX GOVT. CASES. Well ventilated, black crackle finished, undrilled cover. Size 14 × 10 × 8½in. high. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/9 post. Size 13½in. × 8in. × 6½in. with undrilled perforated cover finished in stoved grey enamel, 7/9, plus 2/9 post.

SPECIAL OFFERS. Small 2 gangs .0005 mfd., 4/9. Electrolytics 32-32-32 mfd. 250 v., 2/9 each or in lots of six, 2/3 each.

BRAND NEW LUCAS MOTOR CYCLE BATTERIES. 6 v. 22 A.H. (In sealed cartons.) Limited number available singly, at only 39/6 each. Carr. 3/6. Or 75/- pair. Carr. 5/-.

INSULATED STAPLES ¼in. Boxes of 100. Only 1/- each. 10/6 doz. £5/10/- gross.

THE "TRANSISTOR–8"

COMBINED CAR-RADIO/PORTABLE

PUSH-PULL SUPERHET

This Portable 8 Transistor Superhet is tunable for both Medium and Long Waves and is comparable in performance to any equivalent Commercial Transistor Set.
Simplified construction enables this set to be built easily and quickly into an attractive lightweight cabinet supplied.

TEN STAR FEATURES

- ★ 8 Specially selected Transistors
- ★ 250 Milliwatts Output Push Pull
- ★ Medium and Long Waves
- ★ Internal Ferrite Rod Aerial
- ★ 7 × 4 Elliptical Speaker
- ★ Drilled Plastic Chassis of 8½ × 2½in.
- ★ Point to Point wiring and practical layout
- ★ Economical. Powered by 7½ v. battery
- ★ Highly sensitive fix
- ★ Ideal car radio

Car Radio Conversion Components, 8/- extra.
320 MW version 40/- extra.

We can supply these items including Cabinet for £11/10/-. All parts sold separately. Send for FREE circuit diagrams, assembly data, illustrations and instructions, and full shopping list.

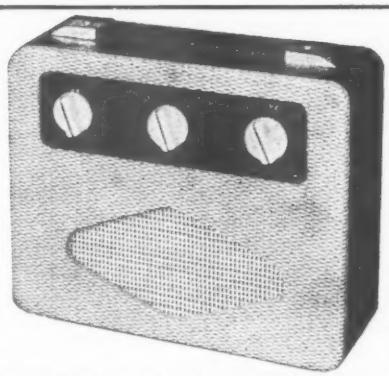

CALL AND HEAR DEMONSTRATION MODEL

MINI–7 POCKET TRANSISTOR PORTABLE

HIGHLY SELECTIVE ! *WELL RECOMMENDED !*

Size 5⅛in. × 3⅛in. × 1 1/16in.

MAY BE BUILT FOR ONLY **£9/19/6**

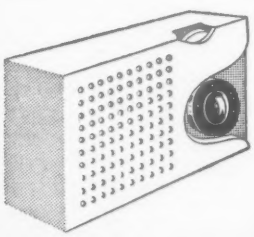

SPECIAL FEATURES

- ★ 7-selected Transistors
- ★ Push-Pull Output
- ★ Ferrite Rod Aerial
- ★ Drilled Chassis
- ★ Practical Layout
- ★ Medium Waves
- ★ Long Wave 10/6 extra
- ★ Attractive Plastic Case

This superhet is superior in performance to most commercial transistor sets and costs less than half the price.

All components as specified can be supplied at an inclusive price of ..... **£9/19/6** P. & P. 2/6.

Send 1/6 for instruction booklet and prices.

HENRY'S RADIO LTD., 5, HARROW RD., EDGWARE RD., W.2 PAD. 1008/9

NOW! Even Easier To Build!
Punched pascolin chassis with brackets for battery and ferrite aerial now supplied at no extra cost. Also included, a resistor colour code chart free.

"EAVESDROPPER" THREE TRANSISTOR POCKET RADIO

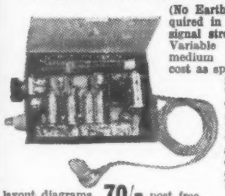

(No Earth or Aerial required in areas of good signal strength.) Variable tuning on medium waves. Total cost as specified, including Transistors, Transformers, Coils, Condensers and Battery, etc., with circuit and plastic case. All items sold separately. Full practical layout diagrams, **70/-** post free.

With balanced armature earpiece. **73/6**
With Min. Hearing Aid **86/-**

MINI-TWO TWO TRANSISTOR MINIATURE POCKET RADIO

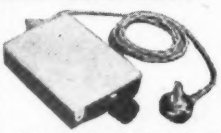

The smallest Transistor set offered on the market. Variable tuning. Drilled chassis, plastic case 3 × 2 × 1in., Miniature Hearing Aid, 2 Transistors and all components including 3 volt battery, circuits and full practical layout diagrams. All components sold separately. Total cost **47/6** complete.

"HOMELIGHT" TWO TRANSISTOR PERSONAL PORTABLE

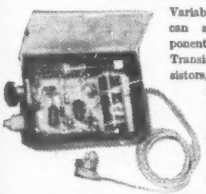

Variable tuning. We can supply all components, including two Transistors, Diode, Resistors, Condensers, Miniature Hearing Aid, Plastic case, Practical layout, drilled chassis and battery for **50/-** All items sold separately.

TRANSISTOR PUSH-PULL AUDIO AMPLIFIER
(200 Milliwatts Output)

Complete kit of parts including four Transistors and all Components with Circuit and Plastic Case (less Speaker)
69/6 P.P. 2/6.

TRANSISTORS PNP
JUNCTION TYPE

Red Spot 800 kc/s. Audio Amp. 7/6 each.
Red Green Audio Amp. 7/6 each.
White Spot, 2.5 Mc/s. Osc./mixer, I.F. Amp. 15/- each.
Red Yellow 1.5 to 8 Mc/s. R.F. and I.F.Amp 15/- each.
XA102 8 Mc/s. Osc./mixer, 40/- each.
XB102 Audio Amplifier, 500 kc/s. 21/- each.
XC101 Matched pairs for up to 350 mW. 60/- pair.

FULL TRADE DISCOUNTS.
Transistor Holders 9d. each; 8/- doz.

TRANSISTOR SIGNAL TRACER. Complete Kit with 2 Transistors, Components, Phones and Circuit and plastic case ... **37/6**

TRANSISTOR SQUARE WAVE GENERATOR. Complete Kit with 2 Transistors, Components, Circuit and plastic case **20/-**

Sputnik Special
SHORT-WAVE COMMUNICATION RECEIVER
10-60 Mc/s (5-30 Metres)
RECEPTION SET TYPE 208

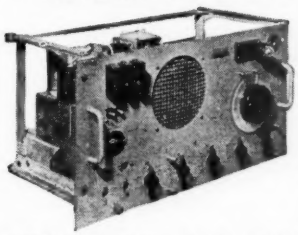

Containing 6 valves, 2-6K8G, 2-EF39, 7Q6G and 6V6G, Metal rectifiers, built-in mains pack and 6 v. Vibrator pack, built-in 6½in. speaker. Muirhead slow motion drive, B.F.O. and R.F. stage. 2 Mc/s I.F. freq. Provision for 'phones and muting and 600 ohm line.

Input 100/250 v. A.C. 6 v. Vibrator pack supplied for battery operation.

£6/19/6 Carr. 15/6.

In new condition and air tested.
BE PREPARED TO LISTEN TO THE SATELLITES

R.F. WATTMETER TS/87/AP
3 position 0-10/15/30 watts
Complete with photo-cell, 2 spare lamps and leads, with transit case.
BRAND NEW £10/10/-. P.P. 7/6.

TEST EQUIPMENT

PIRANI HIGH-VACUUM TEST EQUIPMENT
with calibrator and galvo.
£33/10/-
SEND FOR BOOKLET

FERRANTI TEST VAC
High Speed Vacuum Tester 200/250 A.C. supply
£10/10/-

500 v. EVERSHED WEE-MEGGERS
New condition, with leather case £8 19 6
Brand new, with leather case £12 10 0
100 v., new condition, with leather case £6 0 0

TRIPLETT AC/DC POCKET TEST-METER TYPE 666H

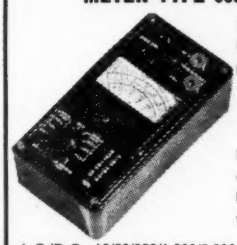

15 ranges
1,000 ohms per volt

In new condition with Prods and Internal battery.

A.C./D.C. 10/50/250/1,000/5,000 volts.
Milliamps 0-10/100/500.
Ohms 0-300/250,000.

£5/10/-

OTHER TYPES OF MULTI-METERS INCLUDING AVOS IN STOCK.

U.S.A. TESTMETER TYPE "834-S"
AC/DC 15—RANGES F.S.D. 1,000 O.P.V.
AC/DC Volts 12/60/300/600v./1,200/6,000v.
Milliamps 1.2/12/60/600 mA. **£6/19/6**
ohms 0-5,000/5 meg.
Complete in wooden carrying case with leads and internal batteries.

SIGNAL GENERATORS
All wave and pattern generators in stock.

CALIBRATED WAVEMETER 44-60 Mc/s. 10/-.

BC-906-D FREQUENCY METER. Range 150-235 Mc/s. 45/-.

QUARTZ CRYSTALS
100 Kc/s. to 27 Mc/s. From 5/- each. Send for complete list of frequencies.

"373" MINIATURE IF STRIP 9.72 M/cs

The ideal F.M. conversion unit as described in "P.W." April/May, 1957. Complete with 6 valves, three EF91's, two EF92's and one EB91. I.F.T.'s etc., in absolutely new condition. With circuit and conversion data.

12/6 (less valves) **42/6** (with valves)
Postage and packing 2/6 (either type).
FM AT ITS CHEAPEST!

JUST ARRIVED!
NEW BOXED VALVES
EQUIVALENT TO FOLLOWING TYPES

AC/SG	DDT4	MVS/PENB	SP4(5)	VP4(5)
AC/SGVM	FC4	MVS/PEN(5)	S4VB	VMP4G
AC/PEN	GU50	MS/PEN(5)	SP4(7)	W42
AC/VPI(7)	H30	MS/PEN(7)	TDD4	ID5
AC/VPI(5)	MHD4	MX40	URIC	7D5
AC/VP2	MKT4	PEN4VA	UMS4	7D6
AC/HLDD	MS4B	PEN36C	UP4(7)	41MPG
CYIC	MVS/PEN(7)	PP36	UP4B	

10/- Each

PX25 12/6 each. PX25A 12/6 each. AZ31 12/6 each.
SEND FOR FREE COMPLETE VALVE LIST.

Send 3d.—28-PAGE CATALOGUE CONTAINING BARGAINS IN VALVES, COMPONENTS AND METERS

HENRY'S RADIO LTD.
5, HARROW ROAD, PADDINGTON, W.2
(Opposite Edgware Road Station) PAD. 1008/9

RELAYS P.O. TYPE 3000.

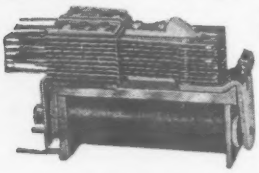

BUILT TO YOUR SPECIFICATION
QUICK DELIVERY KEEN PRICES
CONTACTS UP TO 8 CHANGEOVER

MINIATURE RELAYS

Siemens High Speed. Sealed
2.2Ω+ 2.2Ω 1 C O H96A 17/6
1700Ω+ 1700Ω 1 C O H96E 25/-

S.T.C. Sealed
700Ω 1 make HD 4186ED 19/6
700Ω 2 Change over 4184GD 19/6
2700Ω 2 Change Over 4184GE 22/6

G.E.C. Sealed
2Ω 2 make SM5H1 19/6
180Ω 2 make 2 B. SM5H9 22/6
670Ω 2 make 2 B. SM5H12 25/-
2500Ω 1 C. O. SM5N18 25/-

T.M.C. Carpenter Relays
330Ω+1040Ω B421 75/-
850Ω+2680Ω 5M32A 45/-
300Ω+ 700Ω 5XA24 45/-

All available from stock.

KEY SWITCHES

PROMPT DELIVERY ALL TYPES UP TO 4co/8co

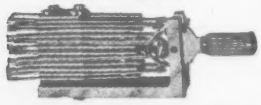

HIGH GRADE INSTRUMENTS FOR RESEARCH LABS, SCHOOLS, etc.

WHEATSTONE BRIDGE, by H. W. Sullivan Ltd., Cat. No. WY0242, 5 decades, with rotary switch ratio arm adjustments. Complete with Galvo and spare suspension, Lamp stand and Scale, Contact and Testing Keys, Resistance for Galvo. Complete in 3 fitted cases..... **£125**

TEST SET Reading Absolute Volts and Amps. D.C., by Elliott Bros., First Grade, B.S.89. 5in. Mirror scale with 150 divisions. 6 ranges of volts, 0/.075 to 0/750. 4 ranges of Amps. 0/1.5 to 0/600. Brand new, complete with all shunts and leads..... **£35**

AMMETERS 0/3 Moving Coil D.C., 6in. Flush Round with a fine open scale with divisions of 50 MA, B.S.S. 89..... **90/-**

VOLTMETERS, 0/300 Moving Iron, A.C., 6in. Flush Round..... **110/-**

AMMETERS, 0/50 or 0/100 Moving Iron, A.C., 6in. Flush Round... **90/-**

VOLTMETERS, 0/300, Moving Iron, A.C., 2½in. Flush Round..... **25/-**

AMMETERS, 0/3, Moving Iron, A.C., 3in. Scale, Portable Type..... **45/-**

MICROAMMETER, 250 F.S.D., 3½in. Flush Round, Sangamo Model S37. Sealed for valve voltmeter, circuit available free..... **55/-**

BRIDGE MEGGER TESTERS No. 1. 1,000 volts 100 megohms with Resistance Box. Brand new. **£75** (less than half price).

"WEE MEGGERS," 500 volts, in leather case, **£12/10/-.**

MEGGERS Series 2. 500 volts 100 megohms, **£25.**

AVO TEST BRIDGES. 220/240 volt A.C. Measures capacities from 5 pf to 50 mfd and resistances from 5 ohms to 50 megohms. Valve voltmeter range 0.1 to 15 volts, and condenser leakage test. BRAND NEW. Full working instructions supplied with instrument. **£9/19/6.** Post 3/-.

Stock list of meters available

SIGNAL GENERATOR TYPE 52A. Input 230 volt 50 cycles, complete with leads, dummy antenna. Brand new in transit case. 6 to 52 Mc/s inclusive in 4 bands with calibration charts. Coarse and fine attenuators. Int. and ext. mod. Output 0.5 volt to 100 mv impedance 70 and 100Ω. **£10.** Cge. 10/-.

BATTERY CHARGERS

Input 200/250 volts A.C., 50 cycles. Output 10 amps., 22 volts D.C. Controlled by two 4-position switches for fine and coarse control which enables 6 to 24 volt batts. to be charged. Made by G.E.C. Brand new with 0/12 ammeter. Fused A.C. and D.C. **£17/10/-,** carriage 20/-.

MIDGET NIFE BATTERIES, 1.2 volts, 3 amps., 3½ × 2⅜ × 1in., **5/-** each, **48/-** doz.

NIFE BATTERIES. Practically indestructible. 1.2 volts, 75 amp. Alkaline filled. Any voltage can be built up. Brand new, **25/-** each, carriage 5/-.

SELENIUM METAL RECTIFIERS for battery charging, etc. Full Wave Bridge. 12 volt 1 amp **8/6.** 24 volt **13/-.** 12 volt 2 amp **13/6.** 24 volt **24/-.** 12 volt 3 amp **16/6.** 24 volt **28/-.** 12 volt 4 amp **20/-.** 24 volt **36/-.** Suitable mains transformers for 12 volt 2 amp **24/-,** 4 amp **29/6,** 24 volt 3 amp **25/-.** Post 2/6.

VENTAXIA EXTRACTION FANS 230 volt A.C. 6in. blades. Ideal for ventilating kitchens, etc. Easy to fix. Silent running. **130/-,** post 3/-. Larger types also in stock suitable for cafes, hotel kitchens. XPELAIR, 7½in. blades, with baffle outlet, **190/-,** cge. 5/-.

CONDENSERS. 1 mfd 10,000 volts. T.C.C. **45/-.** 0.1 mfd 31,000 volts. S.T.C. **75/-.**

AIR BLOWER. 230 volt A.C. 15in. fan. Volume of free air at max. R.P.M. is 1,250 cu. ft. min. and 900 at max. efficiency. Brand new. **£25,** cge. 20/-.

FANS, INDUSTRIAL TYPE. 230/240 volt A.C. 16in. blades. In housing with adjustable louvres and filter. Brand new. **£19/10/-.**

SOLENOIDS. 12 volt D.C., with 3½in. lever. Very powerful. Ideal for remote control, model railways, etc. **5/-** each. Post 1/6.

TYPE UNIT containing 26 of the above solenoids complete with letters and useful moving parts. Brand new. **£7/15/-.** Cge. 15/-.

SWITCHES. 1 hole fixing, 3 amp. 250 volt. Single pole changeover, **1/6** each, **12/-** doz., **£37/10/-** per 1,000.

VOLTAGE REGULATORS. Input 230 v. A.C., 21 amp. Output 57.5 v. to 228 in 16 steps with current limiting reactor. **£12/10/-** each, carriage 15/-.

L. WILKINSON (CROYDON) LTD.

19, LANSDOWNE ROAD, CROYDON
Phone: CRO 0839 **Telegrams: "WILCO" CROYDON**

EDDY'S (NOTTM.) LTD.

DEPT. WW
172 ALFRETON ROAD, NOTTINGHAM

ACOS MIKE INSERTS. 4/11 each. High Quality can be used for Tape Recorders, Baby Alarms, Musical Instruments, etc. Post and packing 8d. each.

ACOS CRYSTAL TURNOVER PICK-UPS (2 Sapphire Stylii). 29/11 each. Post 2/6 extra.

MAP CASES. 2/11 each plus 6d. extra post, etc. Ideal for the motorist, Service Sheet holders and Job Cards, etc.

ACOS CRYSTAL MIKES. List price £2/10/-. OUR PRICE 29/11. New and boxed. Postage and packing 3/- extra.

ALL ABOVE ARE NEW AND GUARANTEED

1D5	10/6	6V6G	5/11	35W4	7/6	EF40	13/11
1R5	7/11	6X4	4/6	35Z4G	7/6	EF41	9/6
1S5	7/3	6X5GT	4/6	807	4/11	EF42	12/6
1T4	7/3	7B7	8/6	807(A)	5/11	EF80	8/6
3Q4	9/-	7C5	8/-	954	1/6	EF85	8/6
3Q5GT	9/6	7C6	8/-	955	3/11	EF91	4/11
3S4	8/-	7H7	8/-	956	2/11	EY51	12/6
3V4	8/6	7S7	9/11	AZ31	12/11	EY86	15/-
5U4G	6/6	7Y4	7/11	CY31	12/11	PCC84	9/-
5Y3G	8/6	10F9	11/6	DAF96	9/6	PCF80	12/6
5Z4G	9/11	12AH7	7/6	DF96	9/6	PCL83	15/6
6AG5	6/6	12AH8	9/11	DK96	9/6	PEN36C	14/6
6AQ5	7/6	12AT6	8/9	DL96	9/6	PL33	12/11
6B8G	2/11	12J7GT	11/6	DM70	7/11	PL81	16/-
6BA6	6/6	12K7G	7/6	EABC80	8/6	PL82	9/6
6BJ6	7/6	12Q7G	7/6	EB91	5/11	PL83	9/3
6F1	13/11	12SH7	5/6	EBC41	9/6	PY81	8/6
6F13	13/-	12SJ7	7/6	EBF80	9/6	PY82	9/6
6F15	13/-	12SN7GT	17/6	ECC81	8/-	TDD4	12/6
6J5G	2/11	12SK7	7/6	ECC82	8/-	UAF42	10/6
6K7G	2/11	14S7	14/6	ECC83	8/11	UCH42	8/11
6K8G	7/11	25A6G	12/11	ECC84	8/11	UF41	8/-
6L18	11/6	25L6GT	9/11	ECC85	8/11	UF42	14/6
6Q7G	8/11	25Z4G	9/11	ECH35	10/11	UL41	9/6
6SN7GT	5/11	35A5	10/6	ECH42	9/11	UY41	7/6
6SK7GT	7/11	35L6GT	9/11	ECL80	13/6		

Any parcel insured against damage in transit for only 6d. per order. All uninsured parcels at customer's risk.

SURPLUS, NEW AND GUARANTEED VALVES
All tested before despatch. Cash with order or C.O.D. only.

Postage and packing 6d. per valve extra.
Over £3 Free.
S.A.E. with all enquiries.

LYONS RADIO LTD.

8 MFD. CONDENSERS. 500 v. D.C. wkg., paper. Overall size: 5½in. high × 3in. × 1¼in. PRICE each **5/6,** post up to 3 for 2/- then plus 6d. each

UNISELECTORS. 6 banks of 26 contacts traversed by 2 sets of wipers (3 wipers only per set) set at 180 degrees being in effect 3 bank 52 contact. 5 ohm coil to operate from 12 v. D.C. As new. PRICE **25/-,** post free.

UNIVERSAL MEASURING BRIDGES. Ex Govt. by Mullards. Measure 0.1 ohms to 10 Megohms and 10 pfd. to 10 mfd. Can also be used to calculate power factor, for percentage tolerance and, with the use of external standards, inductance measurement. Operate from 100 to 250 v. 50 cps. A.C. mains. Supplied in good condition and working order with instructions. PRICE ONLY **£7,** post 3/6.

WEE MEGGERS. Ex-Govt. by Eversheds, 100 v. test in brand new condition. PRICE ONLY **85/-,** post 3/6.

V.F.O. UNITS. Frequency range 1.5 to 20 Mc/s. Ex Air Min. units of very high grade manufacture enabling a setting accuracy to within a few hundred cycles to be achieved. More fully described in May issue of W.W. PRICE ONLY **£7/10/-.** Carriage 12/6.

LOUD-HAILER SPEAKERS. Handle up to 8 watts, with output transformer, speech coil 7 ohms. Mounted in wood case approx. 9 × 8 × 7in. Ex Govt. by Tannoy. PRICE ONLY **17/6,** post 3/6.

6 v. VIBRATORS. Standard 4-pin UX. non-synchronous type. PRICE **8/6,** post 9d.

3 GOLDHAWK RD., (Dept. M.W.), SHEPHERD'S BUSH, LONDON, W.12
Telephone: Shepherd s Bush 1729

POLYTHENE

INSULATORS, END CAPS, PLUGS, ETC.

for

T.V. AERIALS

Standard Articles or Special Mouldings

AMPLEX APPLIANCES (KENT) LTD.

19 DARTMOUTH ROAD, HAYES, BROMLEY, KENT
(RAVensbourne 5531)
All export enquiries to
ANGLO NETHERLAND TECHNICAL EXCHANGE LTD., 3, TOWER HILL, LONDON, E.C.3.

Best Buy at Britain's

SELENIUM BRIDGE RECTIFIERS. Funnel cooled. A.C. input 45 v. RMS. D.C. output 30 v. 10 amps. BRAND NEW. Boxed. 45/-. Post 3/6.

ADMIRALTY HT TRANSFORMERS. Pri. 230 v. 50 c/s. Secs. 620-550-375-0-375-550-620 v. (620 and 550 v. 200 m/Amps., 375 v. 250 m/Amps.), plus two 5 v. 3 Amp. rectifier windings. Total rating 278 VA. Upright mtg. Wt. 25 lb. Made 1953. **BRAND NEW.** Original boxes. 45/-. Carr. 5/-.

MAINS ISOLATING TRANSFORMERS (Vortexion). Fully-shrouded. For testing A.C./D.C. sets in safety. 230 v. input. Output 230 v. 100 watts, 22/6. Post 2/6

DUAL PURPOSE TRANSFORMERS (Gresham). Pri. 230/250 v. Secs., 240-0-240 v. 1.5 amps., 5 v. 12.5 amps., 5 v. 1.75 amps. Ideal for ISOLATING TRANSFORMER, to obtain TWO 240 v. 360 watt lines. Potted, oil-filled, 7 x 7½ x 10½in. high. Wt. 50 lb. **BRAND NEW.** £3/10/-. Carr. 10/-

AR77 MAINS TRANSFORMERS. Fully shrouded, drop-through 3¾in. x 3¼in. Primary 110/125/150/210/240 v. 50-60 c/s. Secs., 325-0-325 v. 100 m/amp., 6.3 v., 3.5 amp., and 5 v. 2 amp. **BRAND NEW** ex-U.S.A., 29/6.

AR88 MAINS TRANSFORMERS Input 110-240 v. Output 345-0-345 v., 125 m/amps., 6.4 v. 4.5 amps., 5 v. 2 amps. 4¾ x 4½ x 5¼in. high. Wt. 12 lb. Potted. Tag ends. RCA. BRAND NEW. Boxed. 29/6, post 3/6.

VIBRATOR PACKS. Input 6 v. D.C. Output approx. 100 v. D.C. at 30 m/amps., fully smoothed and R.F. filtered. Size 6½ x 5 x 2in. Fitted with Mallory 629C vibrator. **BRAND NEW.** Boxed. 12/6. **ANOTHER,** but 200 v. D.C. 100 m/amps. With OZ4 valve and vibrator. **BRAND NEW.** Boxed. 25/-.

MINIATURE STC RELAYS. 250 ohms coil. DP C/O (double silver contacts). 1¼ x ⅝ x ¾in. Wt. one oz. 6 v. operation. 7/6.

U.S.A. RELAYS. 25 ohms coil operates from 3 volts. 4 pole C/Over and 1 make. Brand new. Boxed. 8/6 post paid.

MARCONI TF.340 OUTPUT METERS. Perfect working order. £29/10/-.

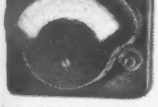

SANGAMO-WESTON VOLTMETERS S61. Dual range 0-5 and 0-100 v. D.C FSD 1 m/A. 3in. scale. Recent manufacture. Ideal for schools. Complete in super quality canvas carrying case, with test prods and leads. **BRAND NEW.** Boxed. 27/6. Post 2/6.

CR100 SPARES KITS

Contents: 15 valves, 2 of U50, DH63, KT63. X66, and seven KTW61 or KTW62. Output transformer, Resistors, Condensers, Potentiometers, FK screws, pilot lamps, drive cord, etc., etc. **ALL BRAND NEW. 59/6.** Post 4/6.

AMERICAN METERS. Triplett 100 microamp., 4in. meters, scaled as multimeter, exactly as used in Combination Tester. Brand new, boxed, **79/6.** Post 1/6.
Triplett 100 microamp, 3in. square, flush mtg. Scaled as output meter, 1.5 and 0-6 volts A.C. Rectifier not fitted. Brand new, boxed, **42/6.** Post 1/-. Westinghouse 0-5 Milliamp D.C., flush mtg., circular, 2in. blank black scale. Brand new, boxed, **8/6.** Post 1/-.

AMERICAN MULTIMETERS

A good general purpose portable meter by Precision, U.S.A. Basic, FSD 400 micro-Amps. Ranges: A.C. and D.C. volts 0 to 12, 60, 300, 600, 1,200 and 6,000; D.C. milli-Amps. 0 to 1.2, 12, 60 and 600 Ohms. 0 to 5 K. 500 K. and 5 Meg.; —10 to +16 dB. In polished wooden case with carrying handle and compartment for leads, etc. Size 7½ × 7½ × 5½in. Complete with batteries, tested and guaranteed. **£8/19/6.** Post 2/6.

ADMIRALTY POWER UNITS. Equivalent to AM234. Input 200-250 v. 50 c/s. A.C. mains. Outputs 240 v. D.C. 125 m/amps. and 6.3 v. A.C. 6 amps. Dual purpose 24in. panel mounted 300 v. meter reads input and H.T. volts. Double smoothing with paper capacitors. Standard 19in. rack mounting. **BRAND NEW. 79/6.** Carr. 7/6.

MEGGERS

Evershed and Vignoles Wee Meggers. 500 volts. Complete in leather case, with leads and instruction booklet. **BRAND NEW. £12/10/-.** Ditto as new. **£8/19/6.** Ditto, but 100 volts. **BRAND NEW £6/10/-.**
E. & V. SERIES 2 MEGGERS, 500 volts. 0-100 Megohms. In leather case. First class condition. **ONLY £16.**
INSULATION TESTERS by Record Electric. 500 volts. 0-50 Megohms. Tested and guaranteed. **ONLY £8/10/-.**

MINIATURE 373 IF STRIPS. For FM tuner described in "Practical Wireless." Complete with 3 of EF91, 2 of EL92 and 1 of EB91. A fresh release enables us to offer these once again **BRAND NEW.** Complete reprint of conversion instructions and circuit supplied free. 42/6. OR less valves, **12/6.** Post, either, 2/6.

MARCONI SIGNAL GENERATORS

85 Kc/s. to 25 Mc/s. A.C. mains operation. In fair condition and working order. TF144F, **£45.** TF144G, **£50.**

HRO SENIOR MODELS

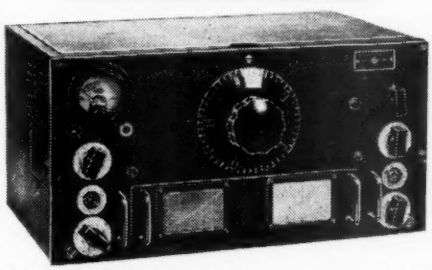

Complete with valves, 9 general coverage plug-in coilsets 50 Kc/s. to 30 Mc/s., instruction booklet, and circuit, but less external power supply unit.
Table models, as new condition, **21 GNS.** Rack Mounting, **18 GNS.** Packing and carriage 22/- extra.
Send S.A.E. for further details.

METER BARGAINS

RANGE	TYPE	SIZE		PRICE
50 Microamp.	D.C. M/C	2½in.	Flush Circ., scaled 0-100	59/6
100 Microamp.	D.C. M/C	2½in.	Flush Circ.	42/6
100 Microamp.	D.C. M/C	2½in.	Flush Circ., scaled "Mega."	39/6
500 Microamp.	D.C. M/C	2in.	Flush Circ. Ex 19 Set	12/6
1 Milliamp.	D.C. M/C	2in.	Flush Square. Fe/NFe.1954	22/6
1 Milliamp.	D.C. M/C	2½in.	Flush Circ. Made 1954	35/-
1 Milliamp.	D.C. M/C	3½in.	Flush Circ.	35/-
1 Milliamp	D.C. M/C	6in.	Flush Circ. Scaled 0-12 v.	79/6
200 Milliamp.	D.C. M/C	2½in.	Flush Circular	10/6
1 amp. Thermocouple		2½in.	Projecting Circular	6/9
1 Amp. Thermocouple		2½in.	Flush Circular	7/6
4 Amp. Thermocouple		2in.	Flush Square	6/9
15 Volts	A.C. M/I	2½in.	Flush Circular	8/6
300 Volts	A.C. M/I	6in.	Flush circular. Made 1955	79/6
300 Volts	A.C. M/I	2½in.	Flush Circular	25/-
500 Volts	A.C. M/I	2½in	Flush Circular	25/-
40 Amperes	D.C. M/C	2in.	Flush Circular	7/6

METER RECTIFIERS. Full wave bridge. Brand new, Salford 1 mA., **6/6.** 5 mA., **6/6.** STC 2 mA., **5/6.**

CHARLES BRITAIN (Radio) Ltd.

11 UPPER SAINT MARTIN'S LANE LONDON, W.C.2. *TEMple Bar 0545*

One Minute from Leicester Sq. Station (up Cranbourn St.)
Shop Hours: 9-6 p.m. (9-1 p.m. Thursday) *Open all day Saturday*

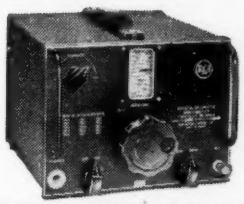

RCA TE-149 HETERODYNE WAVEMETERS. Employs V-cut 1 Mc/s. crystal (0.005%). Overall accuracy better than 0.02%. Dial DIRECTLY calibrated every 1 Kc/s. from 2.5-5 Mc/s. Useful harmonics up to 20 Mc/s. Provision for fitting internal dry batteries. As new in original transit case. £ /19/6. Carr. 5/6.

AVOMETER MODEL D. 34 ranges. Large size AVO. For full details see previous adverts. Thoroughly overhauled. Complete with batteries and instructions. **£8/19/6,** post 4/-.

SANGAMO-WESTON ANALYSER E772. A useful multi-range meter in Rexine covered carrying case. Thoroughly overhauled and in perfect working order. For full details see previous adverts. 10 Gns., carr. 4/-.

TRIPLETT COMBINATION TESTERS. Valve tester and multimeter combined. 10,000 ohms per volt. Complete with batteries, instructions, and tested ready for use on A.C. mains. **BRAND NEW. £14/19/6,** carr. 7/6. See illustrated advert. p. 140 May W.W.

MULLARD C. & R. BRIDGES. 0.1 ohm. to 10 Megohms in 4 ranges; 10 pFd. to 10 mFd. in 3 ranges; Calibrate, Open Bridge, and % range. For 100-250 V. A.C. mains. Tested and guaranteed. **£7/10/-.** Post 3/6.

TRIPLETT MULTIMETERS

25 Ranges: 0 to 5, 25 100, 250, 1,000, and 5 kV. D.C. (20,000OPV); 0 to 5, 25, 100, 250 and 1,000 v. A.C. (1,000 OPV); 0-to 50 microA, 1, 10, 100 and 500 mA. 1 and 5 amps. D.C.; 0 to ½, 1, 5 and 10 amps. A.C.; 0 to 1,000, 100 K, and 10 megohms. Square meter, size 4 x 4in. Contained in 11¼ x 8 x 5¼in. wooden case, weight 10lb. Supplied complete with instruction book, batteries, leads and special high voltage leads. **BRAND NEW** ready for use and fully guaranteed. **15 gns.** Post 5/-.

TRANSMITTER TYPE 36. A complete 50 Watt transmitter for phone or CW. Covers 10-40 Mc/s. Tested and ready to plug into A.C. mains. **£12/10/-,** carr. 30/- Eng. and Wales. For full details see previous adverts. or send S.A.E.

MONITOR TYPE 61. 3½in. C.R. Tube. A.C. mains power pack. Very modern design. Ideal for conversion to Oscilloscope, full data supplied. Condition as new. **£8/19/6,** carr. 15/-.

CRYSTALS. 200 Kc/s. American GEC, 10/- each. 100 Kc/s. RCA bars, **15/-.**

R1155 RECEIVERS. Model "B" with latest type SM drive. In good condition and perfect working order. Realigned and air-tested. S.A.E for details of power packs, etc. **£7/19/6.** Carr. 10/6.

MARCONI LOOP AERIAL type 696. A small, compact, enclosed loop. On swivel mount with degree scale. **BRAND NEW. 69/6.** Post 2/6. Ideal for R1155, etc.

FERRANTI VOLTMETERS N5. 0-300 volts, 25-100 c/s. Moving iron, 6in. scale. Fl. mtg. Hermetically sealed, grade IN. Made 1955. BRAND NEW. Boxed. **79/6,** post 3/6.

G

SIGNAL GENERATOR

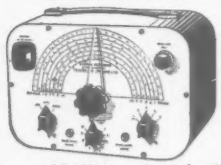

Coverage 100 Kc/s.-100 Mc/s. on fundamentals and 100 Mc/s. to 200 Mc/s. on harmonics. Metal case 10in. × 6½in. × 5½in. grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250 v. Internal Modulation of 400 c.p.s. to a depth of 30%: Modulated or unmodulated R.F., output continuously variable 100 millivolts, C.W. and mod. switch, variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.

£6/19/6 Or 25/- deposit and 6 monthly payments of **21/6**. Post & Packing 5/- extra.

SIGNAL GENERATOR

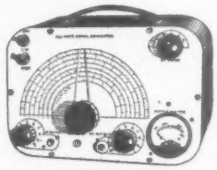

Coverage 120 Kc/s.—280 Kc/s., 300 Kc/s. —900 Kc/s., 900 Kc/s.—2.75 Mc/s., 2.75 Mc/s.—8.5 Mc/s., 8 Mc/s.—28 Mc/s., 16 Mc/s.—56 Mc/s., 24 Mc/s.—84 Mc/s. Metal case 10in. × 6¼in. × 4¼in. Size of scale, 6¼in. × 2¼in. 2 valves and rectifier A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated R.F., output continuously variable 100 millivolts, C.W. and mod-switch variable A.F. output and moving coil output meter. Grey hammer finish case and white panel.
Accuracy plus or minus 2%.

£4/19/6
Or 25/- deposit and 4 monthly payments **21/6**. P. & P. 5/- extra.

SIGNAL & PATTERN GENERATOR

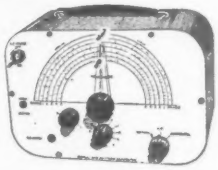

£6/19/6 P. & P. 5/-
Or 25/- deposit. P. & P. 5/- and 6 monthly payments of **21/6**.
Coverage 7.6 Mc/s.-210 Mc/s. in five bands, all on fundamentals, slow motion tuning audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ±1%. A.C. mains 200-230 v.

PORTABLE AMPLIFIER

Size 6¼in. long, 5in. high, 2¼in. deep. Will suit any type of crystal pick-up. Output approx. 2 watts. Incorporating ECC83 double triode, Cossor 142BT output pentode and contact-cooled rectifier. Fully isolated mains transformer for 220/250 A.C. mains. Base, treble and volume controls. **49/6** Plus P. & P. 3/6

5" SPEAKER WITH O.P. TRANSFORMER

purchased with the above **18/6**. Plus P. & P. 1/6.

B.S.R. MONARCH 4-SPEED AUTOMATIC CHANGER

CURRENT MODEL. Will take 7in., 10in. or 12in. records mixed. Turnover crystal head. A.C. mains 200/250 v.

£6/19/6 Plus Post & Packing 5/-.

COMPLETELY BUILT 8-WATT AMPLIFIER

A.C. mains 110/250 v. Size 10½in. × 6¼in. × 2½in. Incorporating 6 valves, H.F. pen., 2 triodes, 2 output pens., and rectifier. For use with all makes and types of pick-up and mike. Negative feed back. Two inputs, mike and gram., and controls for same. Separate controls for Bass and Treble lift. For use with 8in. or L.P. records, musical instruments such as Guitars etc. Complete with 8in. speaker and ready for use. **£4/9/6** Plus P. & P. 5/-.

COLLARO MIXER 4-SPEED AUTOMATIC CHANGER

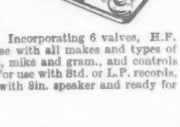

Model 457. Type "O" Pick-up, size 12in. × 13¼in. Minimum clearance above baseboard 5in., below 2¾in. 10 records. A.C. mains 200/250 v. Turnover crystal head. BRAND NEW. Fully guaranteed (suitable for use with above amplifier). 25/- deposit plus P. & P. 5/- and 7 monthly payments of 25/-.
Cash **£8/19/6** Plus P. & P. 5/-.

AC/DC POCKET MULTI-METER KIT

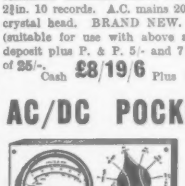

Comprising 2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps, 0-10, 0-100. Ohms range, 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero setting), toggle switch, resistors and rectifier. Basic movement 2 mA. In grey hammer finish case.

19/6 Plus P. & P. 1/6 Built and tested 7/6 extra.
Point to point wiring diagram 1/- free with kit.

RADIO AND T.V. COMPONENTS (ACTON) LTD.

23 ACTON HIGH STREET, LONDON, W.3

GOODS NOT DESPATCHED OUTSIDE U.K. *ALL ENQUIRIES S.A.E.*

COMMUNICATIONS RECEIVER R.107

Just purchased from the Ministry of Supply, this magnificent 9 valve 3 Waveband receiver gives world-wide reception over a coverage of 1.2–17.0 Mc/s. (18–250 metres), taking in several important Amateur Bands, Shipping Band and part of the Medium waveband, including the B.B.C. Light Programme. The sensitivity is 1 micro-volt on C.W. and 2–6 micro-volts on R.T. The controls include a Bandwidth Switch ("Wide" or "Narrow"), choice of AVC and BFO, Audio Filter, RF Gain, Aerial Trimmer. Has built-in Output Stage with Internal Speaker, which can be switched out to use Headphones. Uses normal International Octal Valves. Incorporates A.C. Mains Power Unit for 100–250 volts and Vibrator Pack for 12 volts D.C. In grey metal case size 24 × 13 × 17in. These sets are used, but in first-class condition, thoroughly checked and aerial tested before despatch. Complete, ready to switch on. ONLY **£8/19/6** (carriage 20/- England and Wales, rest of U.K. extra). S.A.E. for leaflet.

MARCONI SIGNAL GENERATOR TF-517-F/1. Special offer of these Laboratory Signal Generators. Cover 10–18 Mc/s., 33–58 Mc/s and 150–300 Mc/s. In good used condition, with charts. Checked before despatch. Complete with power pack for normal A.C. mains. ONLY £12/10/-. (carriage, etc., 20/-).

MARCONI SIGNAL GENERATOR TF144G. Frequency coverage 85 kc/s. to 25 Mc/s. and known as a Laboratory Standard. For normal A.C. mains and complete with all leads. Reconditioned AS NEW. ONLY **£65.**

TCS TRANSMITTERS

The renowned American TCS Model designed by the Collins Company for static or mobile use. Covers 1.5–12.0 Mc/s. in 3 bands and is complete with 7 valves, employing 2 of 1625 in P.A. Stage, 1 each of 1625 in Buffer and Modulator Stages, and 3 of 12A6 in Oscillator Stage. Provision for VFO or Crystal Control. 4 Crystal positions. Radio Telephone or Radio Telegraph. Has Plate and Aerial Current Meters. Power requirements 12 v. L.T. and 400 v. H.T. In black crackle case, size 11 × 13 × 11in., condition BRAND NEW and UNUSED ONLY **£12/10/-** (carriage, etc., 15/-). The double Dynamotor Power Unit, Type 21881B for 12-volt operation, delivering 400 v. for Transmitter and 225 v. for Receiver is available at **£12/10/-** (carriage, etc., 15/-).

MUIRHEAD SLOW-MOTION DRIVES. A really precision product of this famous maker. 3in. in diameter and fitted to removable white back-plate marked 0–180. Overall diameter 4in. BRAND NEW IN MAKERS' CARTONS. ONLY **10/6** (post 1/6).

MAINS ISOLATING TRANSFORMER. Manufactured by Vortexion. Fully shrouded. Will provide true 1:1 Ratio from nominal 230 v. Primary. Rated at 100 watts. BRAND NEW. ONLY **22/6** (post 2/6).

12 VOLTS AMERICAN DYNAMOTOR. Delivers 220 volts at 100 mills. Size 5½ × 3¼in. diameter. Ideal for running Radio or Electric Shaver, etc., from car battery. BRAND NEW. ONLY **32/6.**

EHT TRANSFORMERS. 5.5 kV (Rect.) with 2 v. 1 a., **79/6.** 7 kV (Rect.) with 2 v. 1 a., **89/6.** 2.5 kV (Rect.) with 2-0-2 v. 1.1 a., 2-0-2 v. 2 a. (for VCR 97 tube, etc.), **42/6** (postage 2/- per trans.).

ROLA 6½in. P.M. SPEAKER. Mounted in grey crackled metal cabinet. 9 × 9 × 4¾in. and with volume control. BRAND NEW AND UNUSED. ONLY **27/6.**

1 MA METERS, 2¾in. circular, rim fixing, 2½in. barrel, 50 divisions, scale marked .2-.4 etc. BRAND NEW IN MAKERS' CARTONS. ONLY **25/-.**

6 v. VIBRATOR PACKS. Output approx. 130 v. at 30 mA., fully filtered and smoothed. Complete. ONLY **12/6.**

R1155 SUPER SLOW-MOTION TUNING ASSEMBLY. As used on all late model 1155s. Easily fitted to "A" sets, etc. ONLY **12/6.**

POCKET VOLTMETERS. Not ex-Govt. Read 0–15 v. and 0–300 v. A.C. or D.C. BRAND NEW and UNUSED. ONLY **18/6.**

SPECIAL MAINS TRANSFORMER OFFER. Normal 230 v. A.C. Primary. Secondaries 330–0–330 v. 100 mA. 4 v. 3 amps. Ex-W.D. BRAND NEW AND UNUSED. ONLY **15/-** (postage etc., 2/6).

12-WAY SCREENED CABLE. In 10ft. lengths, fitted with plugs, originally made for use with the 19 Set. UNUSED. ONLY **17/6** per lead.

CRYSTALS. British Standard 2-pin 500 kc/s., **15/-.** Miniature 200 kc/s. and 465 kc/s. **10/-** each.

Cash with order please, and print name and address clearly.
PLEASE ADD POSTAGE OR CARRIAGE COSTS ON **ALL** ITEMS.

HARRIS ELECTRONICS (LONDON) LTD.

RADIO CORNER, 138 GRAY'S INN ROAD, LONDON, W.C.1

Phone: TERMINUS 7937

Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.

RUSH TO RELDA

WE OFFER THE FINEST SELECTION OF EQUIPMENT

TEST METERS

MODEL AN/20 MICRO TESTER is a magnificent 18-range universal multi-test meter. High sensitivity type (5,000 ohms per volt on all ranges) and has accurate linear scales for the lower A.C. voltage ranges. Pocket size and complete with test leads. Ranges: 0 to 2.5, 10, 50, 250 and 1,000 v. D.C.; 0 to 2.5, 10, 50, 250 and 1,000 v. A.C.; 0 to 1, 100, 1,000 mA. D.C.; 0 to 15 K, 1.5 megohms; 0, +13, +27 Db (0 Db=6 MW into 500 ohms). Brand new £9/9/-.

MODEL AN/27 TEST METER. An accurate, high sensitivity (5,000 ohms per volt on all ranges), 27-range A.C./D.C. instrument. Housed in a leatherette covered case with tool storage provision, complete with leads. Ranges: 0 to 2.5, 10, 100, 250, 500 and 2.5 KV D.C.; 0 to 2.5, 10, 100, 250, 500, 2.5 KV A.C.; 0 to .25, 2.5, 25, 250, 500 mA. D.C.; 0 to 1 and 5 amperes D.C.; 0 to 2.5 K, 25 K, 250 K and 2.5 megohms; 0, +20, +28, +34 Db (0 Db=6 mW into 500 ohms). Brand new £15/15/-.

R.F. UNITS Type 25, 40/50 Mc/s with circuit 8/6. P. & P. 3/6d.

INDICATOR UNIT 277. Consisting of one inch C.R. tube type VCR522, 6 valves:—4-EF50, 2-VR92. Incorporates Focus, Brightness and Gain controls. Size 7 x 10 x 5in. Manufactured by Cossor. Only 65/-. P. & P. 3/6.

GELOSO V.F.O. UNITS. Type 101 covering 80, 40, 20, 15 and 10 metres, single end output, using 1-6J5, 1-6AU6, 1-6V6. Complete with calibrated dial and escutcheon. Less valves £7/12/6. P. & P. 2/6.

HEADPHONES — BRAND NEW. High resistance 4,000 ohms 11/6. P.&P. 1/6. Low resistance 120 ohms 6/6. P.&P. 1/6.

MICROPHONES — BRAND NEW. Throat, magnetic, 4/6; Throat, carbon, 3/6; No. 8 carbon with switch, 6/6; No. 7 moving coil, 8/6.

COMPLETE HEADPHONE AND MICROPHONE ASSEMBLY. Consisting of padded headphones and No. 7 moving coil hand microphone with cord and plug. Brand new. Price 10/-. P.&P. 3/6.

TELEPHONE HANDSET. Brand new. 12/6. P. & P. 1/-.

AMERICAN MIDGET ACCUMULATORS. 36 volts, lead acid type 2/6 each. P. & P. 1/-.

LUMINOUS MAGNETIC MARCHING COMPASS. Pocket size. Brand new with instructions. ONLY 12/6. P. & P. 1/-.

866A VALVES. New and boxed, 13/6. P. & P. 1/6.

COMMUNICATION RECEIVER RA 1B. Covers 150 kc/s-15 Mc/s in 6 bands, 12 or 24 operation. S.A.E. for details.

HOOVER ROTARY TRANSFORMER. 11.5 v. input, 490 v. output and 6 v. input 230 v. output at 65 mA. 27/6

I.F. TRANSFORMERS. 465 kc/s. 7/6 pair. P. & P. 1/-.

MALLORY JACK PLUGS. 2 contact. 3/6 or 4 for 10/-.

200 WATT AUTO TRANSFORMERS. 125-230 volts. 40/-. P. & P. 3/6.

AMERICAN ROTARY CONVERTORS.

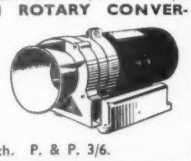

With cooling Fan. Input 12 v. D.C. Output 250 v. at 90 mA. Completely suppressed. Only 17/6 each. P. & P. 3/6.

OSCILLOSCOPE

MONITOR, TYPE 61. A First-Grade Synchroscope designed for D.C. Pulse and R.F. Envelope investigation, and employs a 3½in. CRT type VCR138A. R.F. Frequency 180/220 Mc/s approx.; and is tuneable in that range. Has internal 500 kc/s. Calibrating Oscillator on Y Plates. Existing Time Base Speeds are 50 cycles, 20 Micro-seconds fast, and 1,000 Micro-seconds slow. Mains Power Pack 115 v. and 230 v. Is an excellent general purpose Oscilloscope. Size 10½in. x 12½in x 19in deep **£10.10.0** Carr. 10/-.

WHEATSTONE BRIDGE

Consisting of four stud switches: 0-10 ohms, 0-100 ohms 0-INF. Galvanometer centre zero F.S.D. 2.5 mA. Ranges easily extended. Housed in oak cabinet 16 x 7½ x 6in. Worth £20. Complete with instructions **40/-** P.&P. 4/-.

RELDA MAINS TRANSFORMERS

(Fully Guaranteed)

Interleaved and impregnated. Primaries 200-230-250 v. 50 c/s

250-0-250 v. 80 mA., 6.3 v. 3.5 a., 4 v. 4 a.; 0-4-5 v. 2 a.	22/6
350-0-350 v. 80 mA., 6.3 v. 3.5 a.; 4 v. 4 a.; 0-4-5 v. 2 a....	22/6
250-0-250 v. 100 mA., 6.3 v. 3.5 a.; 5 v. 2 a.	25/6
300-0-300 v. 100 mA., 6.3 v. 3.5 a.; 5 v. 2 a.	25/6
6.3 v. 2.75 a. Filament transformers	7/6
0-12-15-20-24-30 v. 2 a. Filament transformers	20/6
0-5-11-17 v. 4 amps. Battery charger type	22/6

2-way TELEPHONE KIT

Install your own intercom.!!! with this brand new kit consisting of 2 " press to talk " hand telephones, long-life battery, 100ft. of flex and simple wiring details. Ideal for garage, office, workshop, factory, farm, camping, and home. Will give endless hours of pleasure and has proved reliable under all conditions. Complet kit sent for only **25/-** P. & P. 3/6.

3CM TEST SET 205

Consisting of wavemeter, tunable generator and oscillator. Wavemeter calibrated from .5 to 3.5 cm., input 12 v. Complete test set. Carr. 20/-. **£7.10.0**

S.T.C. RECTIFIER UNIT

Input 100-250 v. A.C. Output 110-115 v. D.C. at 700 mA. Provision for adjustment of 3 and 12 volts either side of mean voltage. **55/-** Carr. 5/-.

No. 18 TRANS/RECEIVER

A portable, self-contained Transmitter/Receiver for Telephone and C.W. Range approx. 10 miles. Frequency 6-9 Mc/s. (50-33.3 metres) Valve line-up: 3 ARP-12, 2 AR-8, 1 ATP4. Complete with aerial, H.T. and L.T. meter Weight 20lb., size 8 x 10 x 17in. Only **60/-** Carr. 10/-.

813 VALVES U.S.A. 70/-

NO. 19 SET ATTACHMENTS

Supply units	30/-
Variometers	20/-
Headphone and microphone assembly	13/6
Morse key assembly	4/6
12ft. aerial.....	12/6
Control box, single	5/6
Control box, double	8/6
Test meter	19/-
Circuit and instruction book	2/6

PLESSEY SPEAKERS

7in. x 4in. elliptical 3 ohms 18/6, post paid. 5in. circular 3 ohms 17/6, post paid.

COMMUNICATION RECEIVER R1155. This magnificent receiver covers 5 ranges: 75-200 kc/s, 200-500 kc/s., 600-1,500 kc/s., 3-7.5 mc/s., 7.5-18.5 mc/s. Fully tested before despatch. Complete with circuit and instruction booklet, £8/10/-, carriage 10/-.

INFRA RED MONOCULAR. Ideal fo. night viewing, etc. Complete with push-button power unit and focus lenses. Brand new in beautiful leather carrying case. Originally cost Govt. £40. OUR PRICE 25/-. P. & P. 3/6.

R.T.-7/APN-1 ALTIMETER TRANSCEIVER. Complete with 14 valves: 3-12SJ7, 4-12SH7, 2-12H6-1-VR150, 2-9004, 2-955. Famous Wobbulator Unit. Dynamotor. Relays 3,500 ohms and 6,500 ohms A.F. amplifier. Receiver section covers 400-450 mc/s. Transmitter sweeps 418 to 462 mc/s. Ideal for model control work, etc. Only 35/-. Carriage 10/-.

AMERICAN GEARED MOTOR. 24 v. D.C. with built-in precision gear box. No. 1 drive 24 R.P.M. No. 2 drive 6 R.P.M. On 12 v. No. 1 drive 16 R.P.M. No. 2 drive 4 R.P.M. Overall size of motor and gearbox 7½ x 3½ x 3in., weight 2lb. Brand new. 17/6. P. & P. 3/-.

PACKARD-BELL PRE-AMPLIFIER. Complete with 1-28D7, 1-6SL7GT, miniature relay, push pull input and output transformers, miniature 8-way plug and socket, switch and jack plug. Size 5in. x 3½in. x 4in. Complete with circuit. 17/6. P. & P 2/6.

No. 46 TRANSMITTER/RECEIVER. for R/T and M.C.W. for frequencies between 3.6-9.1 Mc/s. Fixed crystal controlled. Weight 9lb. Size 6½in x 12in. x 4in. Complete with 6 valves and circuit. Less crystals and coil unit 50/-.

METERS. 500 micro-amp. 2in. circular, calibrated 0-15 and 0-600 volts, 17/6. P. & P. 1/6. 0-1 mA. 2in. square 22/6. P. & P. 1/6. 1 amp. H.F. 2in. circular 5/6. P. & P. 1/-.

ARMOUR RECORDING WIRE. U.S.A. top quality on original reels, length 3,700 yds. 10/-. P. & P. 1/6.

RELAYS. 6,500 ohms and 3,500 ohms. 8/- pair Post paid.

COLVERN WIRE WOUND POTENTIOMETER. 25 watts 50k and 100k. Price 6/- each

MUIRHEAD VERNIER SLOW MOTION DRIVES. Scaled 0-180 deg. Ratio 25 to 1. 3in. dia 10/6. P.P. 1/6.

DIPOLE AERIAL No. 4A. 52ft. hard drawn 7/22 copper wire with centre insulator, fitted with feeder sockets. Both ends have 3 link insulators and slotted wire adaptors. Brand new. Price 9/-. P. & P. 2/-.

LEAD ACID ACCUMULATORS (unspillable). 2 volts 16 A.H. Ideal for 6 volts and 12 volts supply. Brand new original cartons. Size 4in. x 7in. x 2in. **5/6** Each P.P. 1/6. 3 for 15/-. P.P. 3/6; 6 for 27/6. P.P 5/-.

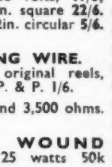

Relda Radio Ltd.

87, TOTTENHAM CT. RD., LONDON, W.1.
32A, COPTIC STREET, LONDON, W.C.1.

All post orders and correspondence to (Dept. " W ") 32A, Coptic Street, London, W.C.1. MUSeum 9607

AERIALS

STANDARD TELEPHONE HAND SET

No. 6. With sound powered earpiece and Carbon mike. Press to talk. BRAND NEW with cord and plug. Can be used as sound powered telephone system by connecting 1.5v cell in series. ONLY **12/6** each. P. & P. 2/6.

AMERICAN MINIATURE MICRO SWITCHES. On/off or off/on, mains 1 amp. Size 1 1/16" × ½" × ½". Ideal for furniture manufacturers. Fraction of original cost. **2/6** each or **25/-** per dozen.

MICROPHONES

All types available. All Brand New.

No. 8 (*as illustrated*). Blue Carbon Insert. Complete with cord and plug. ONLY **5/-**. Post paid.

No. 3C. Refillable Carbon Insert. Finished in Red and Black Bakelite with flat front. Cord, plug, and canvas neckband. **5/-**, post paid.

AMERICAN No. 7 MOVING COIL MICROPHONES. Tested. ONLY **6/6** each.

3-PIECE 12FT. SETS FOR ONLY 7/6. Incorporating copper plated bottom, middle and solid top aerial sections. P. & P. 2/6.

1 FOOT SECTIONS. Can be extended as required. Only **6d.** each or **5/-** per dozen.

F. ROD AERIALS. Bottom sections 4 feet Copper Plated. Can be used to form Beam Antenna or complete Aerial Masts, **2/3** each. 6 for **12/-**. Please add carriage.

PORTABLE BATTERY OPERATED FIELD OR FACTORY SWITCHBOARD

Simple to operate ten line telephone switchboard. Ideal for mobile operations. Field Days, Sports events, etc., etc. This universal switchboard can keep ten extensions in constant touch by turn of a handle. Only requires batteries for immediate use. Send us your requirements for quotation.

HEADPHONES

TYPE D.L.R.5. Single earpiece with cord, plug and canvas headband. ONLY **4/-**. P. & P. 1/6.

LOW IMPEDANCE PADDED HEADPHONES with metal headband (as illustrated). **7/-** per pair. P. & P. 2/-.

HIGH RESISTANCE EARPIECES. 1,000 Ω. Brand new. **3/6** each.

C.L.R.3 LOW RESISTANCE. Complete with cord and plug. Brand new. Only **5/-** each.

Please send us your enquiries for all types of Microphones and Headphones, we can offer the keenest prices in the country.
EXPORT ENQUIRIES A SPECIALITY

ATTACHMENTS FOR WIRELESS SET No. 19

Variometers **18/6**, Morse Key assembly **4/6**. 12ft. Aerial **7/6**, 12 volt Power Unit (Dynamotor & Vib. pack) **30/-**. Control boxes, single **5/6**, double **8/6**.

ALL 19 SET CONNECTORS NOW IN STOCK.
Send details of your requirements.

ACCUMULATORS

LEAD ACID (unspillable), 2 volts 16 A.H. Ideal for 6 volts and 12 volts supply. Brand new original cartons. Size 4in. x 7in. x 2in. **5/6** each. P.P. 1/6; 3 for **15/-**. P.P. 3/6; 6 for **27/6**. P.P. 5/-.

COMPLETE No. 1 HEADGEAR

BRAND NEW

consists of low impedance padded headphones and No. 7 hand microphone with moving coil insert. For use with Army No. 19 set and all other Army Transreceivers

Price **10/-**.

P. & P. 3/6.

B. ADLER & SONS (Radio) Ltd.

KING'S HEAD YARD, COPTIC ST., LONDON, W.C.1 Tel.: MUSeum 9606

RADIO CLEARANCE LTD.

TRADE ENQUIRIES INVITED

27, TOTTENHAM COURT RD., LONDON, W.1.

The oldest Component Specialists in the trade

Telephone : MUSEUM 9188
EST. 30 YRS

ELECTROLYTIC CONDENSERS—WE HOLD THE LARGEST STOCK OF ELECTROLYTICS IN ENGLAND
All Electrolytics and other components as advertised last month are still available.
TO AVOID DELAY ALL ORDERS MUST INCLUDE AN ADEQUATE AMOUNT TO COVER POSTAGE AND PACKING

SUB MINIATURE ELECTROLYTIC CONDENSERS
2 MFD., 6 MFD., 8 MFD., 10 MFD. ¼in. × ⅞in. 3 v. or **6 v. 16 MFD.** and **30 MFD.** ⅞in. × ¼in. **2/9** each.

MINIATURE BIAS CONDENSERS
25 MFD. 25 v. **50 MFD.** 12 v. **50 MFD.** 25 v. ¾in. × ¾in. **1/6** each.
25 MFD. 50 v. ¾in. × 1¼in. **1/9** each.

SUB MINIATURE METALLISED PAPER CONDENSERS
¼in. × ¼in. 100 v. working.
.005 MFD., .0022 MFD., .002 MFD., .001 MFD. 9d. each.
.01 MFD., .02 MFD. Price **9d.** each. **.04 MFD. 10d.** each.

DISC CERAMIC CONDENSERS 500 v. Wkg.
.001 MFD., .0025 MFD., .002 MFD., .003 MFD., .005 MFD. 6d. each. **.01 MFD. 9d.** each.

HIGH VOLTAGE MICAS
100 pF., 140 pF., 5 kV., 300 pF., 8 kV. 9d. each. **100 pF 12 kV. 1/-. 1,000 pF Visconol 20 kV. 5/6** each.

VARIABLE GANG-CONDENSERS
Twin Gang. 20 pF. Ideal for F.M. 2in. × 1¼in. × 1in. **2/-** each.
Twin Gang. .0005 MFD. 2¼in. × 2in. × 1¼in. Spindle ⅛in., **4/-** each.
Min. Twin Gang. .0005 MFD. 2¼in. × 1¼in. × 1¼in. Spindle ¼in., **5/6** each.
Min. Twin Gang. .0005 MFD. 2¼in. × 1¼in. × 1¼in. Spindle ¼in. with trimmers, **6/6** each.

METALLISED PAPER TUBULARS
T.C.C. .02 MFD. 350 v.w. **8d.** Dubilier, **.05 MFD.** 350 v.w. **8d.** Hunts. **.05 MFD.** 500 v.w. **9d.** Dubilier **.1 MFD.** 150 v. **6d.** **.1 MFD.** 500 v.w. **9d.**

SWITCHES ROTARY
Size 1 1/16 in. dia. 2in. spindles. Price **2/11** each.
1 pole 10 way. 1 pole 12 way. 2 pole 2 way. 2 pole 3 way. 2 pole 4 way. 2 pole 5 way. 2 pole 6 way. 3 pole 3 way. 3 pole 4 way. 4 pole 3 way.

WIRE WOUND RESISTORS
5 watt size ⅝in. × 1¼in. **10d.** each
7 Ω., 7.5 Ω., 8 Ω., 10 Ω., 12 Ω., 27 Ω., 30 Ω., 33 Ω., 34 Ω., 36 Ω., 39 Ω., 41 Ω., 43 Ω., 45 Ω., 47 Ω., 50 Ω., 51 Ω., 54 Ω., 55 Ω., 56 Ω., 60 Ω., 64 Ω., 66 Ω., 67 Ω., 68 Ω., 70 Ω., 75 Ω., 80 Ω., 82 Ω., 110 Ω., 136 Ω., 160 Ω., 170 Ω., 180 Ω., 250 Ω., 300 Ω., 320 Ω., 330 Ω., 470 Ω., 500 Ω., 560 Ω., 600 Ω., 620 Ω., 800 Ω., 820 Ω., 940 Ω., 1 K., 1.1 K., 1.3 K., 1.4 K., 1.6 K., 1.7 K., 1.8 K., 2 K., 2.2 K., 2.4 K., 2.5 K., 2.7 K., 3.3 K., 4.5 K., 4.7 K., 5 K., 5.2 K., 5.6 K., 5.9 K., 6 K., 6.2 K., 6.5 K., 6.8 K., 7 K., 8.5 K.
6 watt size. ⅝in. × 1¼in. **1/-** each.
47 Ω., 100 Ω., 250 Ω., 260 Ω., 300 Ω., 350 Ω., 470 Ω., 500 Ω., 560 Ω., 680 Ω., 1 K., 1.6 K., 1.8 K., 1.9 K., 2 K., 2.7 K., 3 K., 4.3 K., 4.7 K., 5.1 K., 5.6 K., 6.2 K., 6.4 K., 6.8 K., 11 K., 13 K., 14.5 K.
7 watt size. ⅝in. × 1¼in. **1/-** each.
10 Ω., 12 Ω., 29 Ω., 33 Ω., 45 Ω., 50 Ω., 55 Ω., 57 Ω., 60 Ω., 120 Ω., 270 Ω., 330 Ω., 470 Ω., 600 Ω., 620 Ω., 680 Ω., 800 Ω. 820 Ω., 1.8 K., 3 K., 3.3 K., 3.7 K., 3.8 K., 4.3 K., 4.7 K., 5 K., 7 K., 11 K., 12.5 K., 13 K., 14 K., 17 K.

HIGH STABILITY RESISTORS
1¼ watt, ½ watt, ¾ watt, 1 watt, 1%, 2%, 5%. Price 1% **10d.** 2% **8d.** 5% **6d.** Please send lists first.

T.V. COMPONENTS
34 Mc/s. I.F. Transformers. Size ¾ × ¾ × 2½. **1/6.**
38 Mc/s. I.F. Transformers. Size ¾ × ¾ × 2½. **2/-.**
Frame Output Transformers. Wide angle, **6/-** each.
Focus Magnets. Adjustable for 14in. tetrode, **6/-** each.
Choke. 2 Henries. 250 m/a. 30 Ω res., **3/11** each.
Choke. 1.9 Henries. 230 m/a., **2/11** each.
Choke. 1.3 Henries. 150 m/a., **2/6** each.

PRE-SET TRIMMERS T.V. TYPE
With knurled knob and 6 BA fixing. 750 pF., 1,000 pF., **1/6** each.

VALVE HOLDERS
4 pin Brit. Pax. 2d. each. **4 pin U.X. Amp. 7d.** each. **5 pin Brit. Pax. 2d.** each. **7 pin Brit. Pax. 3d.** each. **7 pin Brit. Amp. 4d.** each. **7 pin Brit. Cer. 4d.** each. **Int. Octal Pax. 3d.** each. **Int. Octal Amp. 8d.** each. **Mazda Octal Pax. 3d.** each. **Loctals Amp. 6d.** each. **B7G Pax. 6d.** each. **B7G P.T.F.E. 8d.** each. **B7G Cer.** with saddle and valve retaining spring **1/-** each. **B7G Cer.** with skirt **10d.** each. **B3A Pax. 4d.** each. **B8A Amp. 6d.** each. **B8A Cer. 8d.** each. **B9A Pax. 6d.** each. **B9A Amp. 8d.** each. **B9A Amp.** with skirt **10d.** each. **B9A Cer. 10d.** each. **B9A Cer.** with saddle and valve retaining spring **1/-** each. **B9A** ceramic with skirt **1/-** each. **B9A** printed circuit **1/-**.

POTENTIOMETERS CARBON
Less Switch. Dia. 1in., 2½in. spindles **5 K., 10 K., 25 K., 50 K., 100 K., 250 K., 500 K., 1 Meg., 2 Meg. 2/6** each.
With D.P. Switch Dia., 1in., 2½in. spindles, **5 K., 10 K., 25 K., 50 K., 100 K., 250 K., 500 K., 1 Meg., 2 Meg. 4/6** each.
T.V. pre-set Controls with knurled knob and 6 BA fixing dia., **25 K., 50 K., 100 K., 250 K., 500 K. 1/3** each.
25 K., wire wound, **1/6** each.

METAL RECTIFIERS
G.E.C. 250 v. 250 m/a. T.V. Price **10/-** each.
Westinghouse. 16 RD. 2.2.8.1. **7/-** each.
Westectors W.X.6, **1/-** each.

METERS
0-50 m/a. 2in. square, **7/6** each.
350 m/a. Thermo Couple, 2in. round plug mounting. **2/6** each.

CHOKES
Parmeko Smoothing 3/9 Hy. 100 mA., 6/6. R.F. Type, 2 or 3 pie. **4d.** each. **L.T. Type. 4d.** and **6d. H.F. T/V Type 3d. V.H.F. Type, 6d. Mains Hash Twin Type, 2/-. Vibrator Hash Type, 1/-.**

ALL ARTICLES ADVERTISED ARE BRAND NEW AND CARRY OUR USUAL GUARANTEE.
PLEASE STATE IF THE NEAREST VALUE COMPONENT WILL SUIT, SHOULD THE ONE ORDERED BE OUT OF STOCK.
WE HAVE MANY OTHER ITEMS FAR TOO NUMEROUS TO LIST, WHY NOT PAY US A VISIT WHEN IN TOWN ? IT WILL PAY YOU
TERMS OF BUSINESS. CASH WITH ORDER. STAMPED ADDRESSED ENVELOPES WITH ALL ENQUIRIES PLEASE. All Orders received, despatched the same day.

C.R.T. ISOLATION TRANSFORMERS

For Cathode Ray Tubes having Heater/Cathode short circuit and for C.R. Tubes with falling emission.
Type A. Low leakage windings. Optional Boost 25% and 50%. Tapped mains primaries.

2 volt	12/6 each
4 volt	12/6 each with Tag
6.3 volt	12/6 each Panel and
10.5 volt	12/6 each Solder Tags
13.3 volt	12/6 each

Type B. Mains input. Low Capacity. Multi Output 3, 4, 6.3, 7.3, 10 and 13 volts. Optional boost 25% and 50%. This transformer is suitable for all Cathode Ray Tubes. 21/- each.
Type C. Low capacity quality transformer for use with 2 volt Tubes with falling emission. Mains input. Output 2-2½-2½-3 volts at 2 amps. 17/6 each.

RESISTORS. All preferred values. 20% 10 ohms to 10 meg., ½ w. 4d.; 1 w., 4d.; 1 w., 6d.; 2 w., 1/-.
HIGH STABILITY. ½ w., 1%, 2/-. All preferred values 100 ohms to 10 meg. Ditto 5%, 9d., 10%, 6d.

WIRE-WOUND RESISTORS

5 watt	1/3
10 watt	1/6
15 watt	2/-

25 ohms—10,000 ohms
15,000 ohms—50,000 ohms 5 w., 1/9; 10 w..... 2/3
WIRE-WOUND POTS. 3 WATT LAB. COLVERN, ETC. Pre-set Min. T.V. Type Knurled Slotted knob. All values 25 ohms to 30 K. 3/- ea. 50 K., 4/-. Ditto Carbon Track 50 K. to 2 Meg., 3/-.
Standard size Pots., 2½in. Spindle High Grade. All Values 100 ohms to 50 K., 5/6; 100 K., 6/6.
W/W EXT. SPEAKER CONTROL 10Ω, 3/-.
O/P TRANSFORMERS. Heavy Duty 50 mA., 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Hyrrade Push-pull 7 watts, 15/6. MULLARD "510" 6k or 8k 30/-.
L.F. CHOKES 15/10H 60/65 ma., 5/-. 10H 85 ma. 10/6. 10H 150 ma. 14/-. 5H 250 ma. 16/6.

MAINS TRANSFORMERS

STANDARD. 250-0-250, 80 mA., 6.3 v. tapped 4 v. 4 a. Rectifier 6.3 v., 5 v. or 4 v., ditto 350-0-350	22/6
MINIATURE. 200 v. 20 mA., 6.3 v. 1 a	10/6
MIDGET. 220 v. 45 mA., 6.3 v. 2 a.	15/6
SMALL. 220-0-220, 50 mA., 6.3 v. 3 a.	17/6
STANDARD. 250-0-250, 65 mA., 6.3 v. 3.5 a.	17/6

HEATER TRANS. Tapped 200/250 v. 6.3 v. 1½ amp., 7/6.
ALADDIN FORMERS and cores. ½in. 8d.; ⅝in. 10d. 0.3in. FORMERS 5237/8 and Case TV1/2. ½in. sq. × ½in. and ⅜in. sq. × 1¼in., 2/- complete with cores.
SLOW MOTION DRIVES. Epicyclic ratio 6 : 1, 2/3.
TYANA. Midget Soldering Iron. 200/220 v. or 230/250 v., 16/9. SOLON INSTRUMENT IRON. 25 w., 24/-.
MAINS DROPPERS. 3 × 1½in. Three Adj. Sliders, .3 amp. 750 ohms, 4/3. .5 amp., 1,000 ohms, 4/3.
LINE CORD. .3 amp., 60 ohms, per foot, 2 amp., 100 ohms per foot, 2 way, 6d. per foot, 3 way, 7d. per foot.

CRYSTAL MIKE INSERT by Acos

Precision engineered. Size only ¾ × ⅝in. Bargain Price 6/6. No transformer required.

MIKE TRANSF. 50 : 1, 3/9 ea.; 100 : 1, Potted, 10/6.
LOUDSPEAKERS P.M. 3 OHM. 2½in. square, 17/6.
5in. R.A., 17/6. 7in. × 4in. Goodmans 21/-
3½in. Square Elac., 21/-. 8in. Plessey, 19/6.
6½in. Goodmans, 18/6. 10in. R.A., 30/-.
4in. ELAC TWEETERS, 25/-. 12in. Plessey, 30/-.
8in. M.E. 2.5 k. field tapped O.P. transformer, 24/6.
15 ohm Plessey 10 wt. 12in. with Tweeter, 97/6.

I.F. TRANSFORMERS 7/6 pair

465 kc/s slug tuning miniature can 2½ × 1 × 1in. High Q and good band width. By Pye Radio. Data sheet supplied.
Wearite M800 I.F. Miniature 465 kc/s. 12/6 pair.
Wearite 550 I.F. Standard 465 kc/s. 12/6 pair.

CRYSTAL DIODE G.E.C. 2/-. GEX34, 4/-. 49 Circuits, 3/-.
H.R. HEADPHONES. 4,000 ohms, brand new. 16/6 pair.
SWITCH CLEANER Fluid, squirt spout, 4/3 tin.
TWIN GANG CONDENSERS. 365 p.f. Miniature, 1⅛in. × 1⅛in. × 1¼in., 10/-. .0005 Standard with trimmers, 9/-; less trimmers, 8/-. Midget, 7/6; Single 50 p.f., 2/6; 100 pf., 2/-. Solid Dielectric 100, 250, 500 pf., 3/6.
VALVE HOLDERS. Pax int. Oct., 4d. EF50, EA50, 6d. B12A, CRT, 1/3. Eng. and Amer. 4, 5, 6, 7 and 9 pin, 1/-. MOULDED Mazda and Int. Oct., 6d., B7G, B8A, B8G, B9A., 9d. B7G with can, 1/6. VCR97, 2/6. B9A with can, 2/6.
CERAMIC, EF50, B7G, B9A Oct., 1/-. B7G with can, 1/9.
SPEAKER FRET. Gold Cloth 17in. × 25in., 5/-. 25in. × 38in., 10/-. Expanded metal, Silver 13in. × 9½in., 2/-.
Tygan 54in. wide, 10/- ft. ¶27in. wide, 5/- ft. Samples.
WAVECHANGE SWITCHES.
1 p. 2-way, 3 p. 2-way, short spindle 2/6
1 p. 4-way 2 wafer, short spindle 6/6
3 p. 6-way, 4 p. 2-way, 4 p. 3-way, long spindle 3/6
1 p. 6-way, 1 p. 12-way, long spindle 3/6
Wave change "MAKITA." 1 wafer 8/6; 2 wafer 12/6; 3 wafer 16/-; 4 wafer 19/6; 5 wafer 23/-; 6 wafer 26/6.
TOGGLE SWITCHES. S.P., 2/-; D.P. 3/6; D.P.D.T., 4/-.
NORSE KEYS, good quality 2/6. Buzzers 3/6.

TRANSISTORS
PRODUCT OF WELL-KNOWN MANUFACTURER
JUNCTION TYPE P.N.P.

AUDIO suitable for high gain and low frequency amplifiers, and for output stages giving up to 250 milliwatts. PRICE **10/-**
Data supplied.
Equivalents OC71, OC72 T83, Red Spot
R.F. suitable for medium and low frequency oscillators, frequency changers and I.F. amplifiers. Frequency 2.5 Mc/s. minimum. PRICE **21/-**
Equivalent OC44, XA 102, Blue Spot, White Spot.

1958 RADIOGRAM CHASSIS

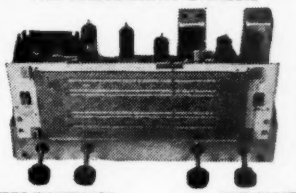

THREE WAVEBANDS
S.W. 16 m.—50 m.
M.W. 200 m.—550 m.
L.W. 800 m.—2,000 m.
FIVE VALVES
LATEST MULLARD ECH42, EF41, EBC41, EL41, EZ40
12 month Guarantee. A.C. 200/250 v., 4-way switch. Short-Medium-Long-Gram. A.V.C. and Negative feedback 4.2 watts. Chassis 13½in. × 8½in. × 2½in. Glass Dial 10 × 4½in. horizontal or vertical available. 2 Pilot Lamps. Four Knobs, Walnut or Ivory, aligned and calibrated. Chassis isolated from mains.

BRAND NEW £10.10.0 Carr. 4/6.
Less 10% cash with order.
TERMS: Deposit £5/5/- and 6 monthly payments of £1.
MATCHED SPEAKERS 8in., 17/6: 10in. 25/-: 12in. 30/-

★ GARRARD 4-SPEED RECORD CHANGERS RC120/H MKII MODELS ★
Brand new and fully guaranteed 12 months

AUDIO PERFECTION

Designed to play 16, 33, 45, 78 r.p.m. Records. 7in., 10in., 12in. Lightweight Xtal pick-up, GC2 head, two separate sapphire styli, for Standard and L.P.
OUR PRICE **£10.15.0** each. Post Free.
Terms: Deposit £6 and 6 monthly payments of £1.

MAKE A GARRARD RECORD PLAYER

★ **AUDIO PERFECTION** ★

Amplifier Player Cabinet, 18 × 13½ × 8½in., with ready-cut motor board	63/-
2-valve 2-stage Amplifier, 6½in. speaker. 2 controls, volume and tone, 3 watts	72/6
3-valve 3-stage Amplifier, 6½in. speaker. 3 controls, volume, bass and treble, 4 watts	95/-

GARRARD 4-SPEED SINGLE RECORD PLAYER 4SP

£8 **AUDIO PERFECTION** POST FREE

Designed to play 16, 33, 45, 78 r.p.m. Records, 7in., 10in., 12in. Lightweight Xtal pick-up, GC2 turnover head, two separate sapphire styli, Standard and L.P.

EXCEPTIONAL OPPORTUNITY

COLLARO 4-speed MODEL 4/564 Single Player, heavyweight turntable and lightweight Studio O Pick-up with turnover Xtal mounted on baseplate. Autostop fitted. **OUR PRICE 6gns.** Carr. 4/-
Amplifier Player Cabinets, 45/-.

BUILD THIS REPRODUCER BARGAIN SPECIAL SINGLE PLAYER KIT
Ready for immediate assembly.

4-speed Collaro "Junior" Unit	£4 12 6
Handsome portable case, 17½ × 13½ × 7in.	£2 5 0
Ready-built 3 watt amplifier with two valves and loudspeaker	£3 12 6

or **£9.15.0** complete kit post free.

COSSOR COMPANION
SUPERHET BATTERY MODEL 527/X

S.W.1 13.6 to 43 metres, S.W.2 42.8 to 136 metres, Medium 187 to 575 metres.
World-wide reception on three wavebands (H.T. 90 v., L.T. 1.5 v.), low consumption valves DK92, DF96 DAF96, DL96.
6in. ELLIPTICAL LOUDSPEAKER
The cabinet is attractively presented in maroon and beige with gold trimmings.
SIZE 9½ × 6½ × 4½in. Leaflet S.A.E.
OUR PRICE **£6.6.0** (Battery 16/6 extra)
Carriage and insurance 4/-.

THREE TRANSISTOR PRINTED CIRCUIT TELETRON COMPANION POCKET RADIO

Medium and Longwave, Internal Speaker, Local Station Receiver, only 4½ × 3 × 1½in. **Complete Kit 99/6.** Plans only 6d.

THE HI-GAIN BAND 3 PRE-AMP.

Cascode circuit using Valve ECC84. Complete kit 29/6 less power; or 49/6 with power pack kit. Plans only 1/6.

Volume Controls

Midget size
Long spindles. Guaranteed 1 year. All values 5 K. ohms to 2 Meg.

No Sw.	D.P.Sw.
3/-	4/9

Linear or Log Tracks

80 ohm CABLE Coaxial

Semi-air spaced Polythene insulated ⅛in. dia. Stranded core. Ideal Band III 9d. yd. Losses cut 50%.

FRINGE QUALITY
AIRSPACED.... 1/6 yd.

COAXIAL PLUGS 1/- DOUBLE SOCKET 1/3
SOCKETS 1/- OUTLET BOXES 4/6
BALANCED TWIN FEEDER per yd. 6d. 80Ω or 300Ω
TWIN SCREENED BALANCED FEEDER 1/6 yd., 80 ohm.
TRIMMERS, Ceramic, 30, 50, 70 pf., 9d. 100 pf., 150 pf. 1/3. 250 pf., 1/6. 600 pf., 750 pf., 1/9. Pitalinis, 1/- ea.

ALUMINIUM CHASSIS. 18 s.w.g. Plain, undrilled with 4 sides, riveted corners and latitice fixing holes, with 2in. sides. 7 × 4in., 4/6; 9 × 7in., 5/9; 11 × 7in., 6/9; 13 × 9in., 8/6; 14 × 11in., 10/6; 15 × 14in., 12/6; and 18 × 16 × 8in., 16/6.

BLACK CRACKLE PAINT. Air drying, 3/- tin.
P.V.C. CONN. WIRE, 8 colours, single or stranded, 9d. yd.
NEON MAINS TESTER SCREWDRIVERS, 5/-.
CORED SOLDER RADIOGRADE 3 yds. 9d. ½ lb. 2/6.

12/6 PURETONE RECORDING TAPE

1,200 ft. on standard fitting 7in. metal reels. Spare Reels 5½in. plastic, 3/-; 7in. plastic, 4/-.
SUPERIOR 1,200ft. Plastic Tape 21/- on 7in. plastic reels. Quality guaranteed.

SENTERCEL RECTIFIERS. E.H.T. TYPE FLY-BACK VOLTAGES. K3/25 2 kV., 5/-; K3/40 3.2 kV., 7/-; K3/45 3.6 kV., 7/6; K3/50 v. 4 kV., 8/-; K3/100 8 kV., 14/6. 50 c.p.s. Voltage 30% of above.
MAINS TYPE. RM1, 125 v., 60 mA., 5/-; RM2, 100 mA., 6/-; RM3, 120 mA., 8/-; RM4, 250 v. 275 mA., 16/-.
MINIATURE CONTACT COOLED RECTIFIERS. 250 v. 50 m/a., 7/6; 60 m/a., 8/6; 85 m/a., 9/6.
COILS. Wearite "P" type, 3/- each. Osmor Midget "Q" type adj. dust core, from 4/- each. All ranges.
TELETRON. L. and Med. T.R.F., with reaction, 3/6.
FERRITE ROD AERIALS. M.W., 8/9; M. and L., 12/6.
T.R.F. COILS A/HF 7/- pair. H.F. CHOKES, 2/6.

JASON F.M. TUNER COIL SET. 26/-. H.F. coil, aerial coil, Oscillator coil, two I.F. Transformers 10.7 Mc/s., Detector transformer and heater choke. Circuit and component book using four 6AM6, 2/-. Complete kit with Jason calibrated dial and valves, £6/15/-. Mercury Switched FM Tuner Kit, £9/19/6.

CONDENSERS. New stock. .001 mfd. 7 kV. T.C.C., 5/6. Ditto 20 kV., 9/6; 100 pf. to 500 pf. Micas, 6d.; Tubular 500 v. .001 to .01 mfd., 9d.; .05 .1 1/-; .25 1/6; .5 1/9; .1/350 v., 9d.; 0.1 mfd., 2,000 v., 3/6; 0.01 mfd., 2,000 v. 1/9.
CERAMIC CONDS. 500 v. .3 pf. to .01 mfd., 10d.
SILVER MICA CONDENSERS. 10% 5 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/3.
CLOSE TOLERANCE (±1pf.) 1.5 pf. to 47 pf., 1/6. DITTO 1% 50 pf. to 815 pf. 1/9; 1,000 pf. to 5,000 pf., 2/-.

NEW ELECTROLYTICS. FAMOUS MAKES.

TUBULAR		TUBULAR		CAN TYPES	
1/350 v.	2/-	100/25 v.	2/-	8+16/450 v.	5/-
2/450 v.	2/3	8+8/450 v.	4/6	16+16/450 v.	5/6
4/450 v.	2/3	16+16/500 v.	6/-	6,000 mfd. 6 v.	6/6
8/450 v.	2/3	CAN TYPES		32+32/350 v.	4/6
8/500 v.	2/9	Clips	3d.	32+32/500 v.	7/6
16/450 v.	3/6	16/500 v.	4/-	64+120/275 v.	7/6
16/500 v.	4/-	32/350 v.	4/-	60+100/350 v.	11/6
32/450 v.	5/6	100/275 v.	5/6	100+200/275 v.	12/6
25/25 v.	2/-	50+50/350 v.	7/-	1,000+1,000/6 v.	6/6
50/25 v.	2/-	500/12 v.	3/-		
50/50 v.	2/-	2500/3 v.	4/-		

FULL WAVE BRIDGE SELENIUM RECTIFIERS. 2, 6 or 12 v. 1½ amp., 8/9; 2 a., 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v. 1½ a., 15/6; 2 a., 17/6; 4 a., 22/6. Charger circuit free on request.

All boxed VALVES New & Guaranteed

1R5	8/6	6K8	8/6	EA50	1/6
1S5	8/6	6L6	10/6	EABC80	10/6
1T4	8/6	6Q7	10/6	EB91	6/6
2X2	2/6	6SA7	10/6	EBC33	8/6
3S4	8/6	6SJM	10/6	EBC41	10/6
3V4	8/6	6SN7	8/6	EBF80	10/6
5U4	8/6	6V6G	7/6	ECC84	12/6
5Y3	8/6	6V6GT	8/6	ECF80	11/6
5Z4	10/6	6X4	7/6	ECF82	11/6
6AM6	8/6	6X5	7/6	ECH42	10/6
6B8	5/6	787	10/6	ECL82	12/6
6BE6	7/6	12AH8	10/6	EF39	7/6
6BH6	10/6	12AT7	10/6	EF41	10/6
6BW6	10/6	12AU7	9/6	EF50	5/6
6CH6	10/6	12AX7	9/6	Equip.	
6D6	1/6	12BE6	9/6	EF50	8/6
6F6	7/6	12BH7	10/6	8-lvlr.	
6H6	3/6	12K7	8/6	EF80	10/6
6J5	6/6	12Q7	8/6	EF92	5/6
6J6	7/6	35Z4	9/6	EL32	5/6
6J7	8/6	80	10/6	EL84	10/6
6K6	6/6	807	6/6	EZ40	10/6
6K7	5/6	954	1/6	EZ80	9/6
				EZ81	11/6
				U118	1/6
				U22	12/6
				UBC41	10/6
				UCH42	10/6
				UF41	10/6
				UL41	10/6
				UY41	10/6
				X22	10/6
				X79	10/6

Our written guarantee with every purchase. Please address all Mail Orders correctly as below

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE RD., WEST CROYDON

OPEN ALL DAY—(Wed. 1 p.m.) CATALOGUE 6d.

TEL. THO 1665. Buses 133 or 68 pass door. S.R. Stn. Selhurst. P. & P. 1/-, £2 orders post free. C.O.D. Service 1/6. (Export C.W.O. post extra, no H.P.).

"AMPERIOR"

(Model 4/10 PA)

High impedance microphone and gram inputs with mixer circuit and common tone control.

Output 10 watts.

Valves: 6BR7, ECL82 (2), EZ81.

S.A.E. for full details. of Range—3 to 60 Watts.

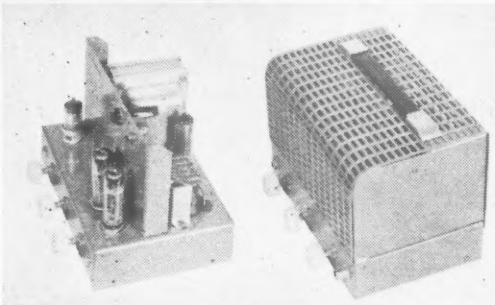

Drop over shroud complete with P.V.C. cushion sleeve handle.

OVERALL size 9×7×7½in.

£12/12/-. Carr. 9/-. C.W.O. or C.O.D.

Ultra Linear and Relay versions available.

Phone: KNOTTINGLEY 2081

E. K. ELECTRONICS, BROTHERTON, KNOTTINGLEY, YORKS.

TECHNICAL TRADING CO.

4-SPEED PLAYERS. (while they last)

WITH STAAR GALAXY AUTOCHANGERS, LIGHTWEIGHT DUAL SAPPHIRE TURNOVER P.U. A.C. 200/250 v. (Listed approx. £15). THIS YEAR'S BARGAIN. High finish case as illustrated. (Post 4/-). **£5.15**

4-SPEED PLAYERS. Above Changer, 3 Valve Amplifier, 7in. speaker in two-tone Portable Attache Case (worth £20). 13 GNS.

GALAXY SPARES. 1,000's available, reasonable prices. S.A.E. quotations.

GALAXY PICKUPS. Lightweight, one hole mounting, complete dual sapphire Xtal cartridges, all speeds. Power Point 19/6. Sonotone or Steig & Reuter 22/6. Acos GP65 25/-.

TRANSISTORS

RED SPOT (up to 800 Kc/s). Guaranteed 7/-
BLUE SPOT (up to 1.6 Mc/s.) Guaranteed 10/-
WHITE SPOT (up to 2.5 Mc/s.) Guaranteed 14/-

GUARANTEED T.V. TUBES! (EX EQUIPMENT)

12in. (MW31-74, CRM121, 3/31, etc.)..	£5	5	0
14in. (MW36-24, C14BM, 4/14, etc.) ..	£4	10	0
17in. (MW43-64, C17BM, 4/15, etc.) ..	£6	10	0
17in. (CRM171 only)	£6	0	0

(All guaranteed 6 months) (carr. & ins. 12/6)

GUARANTEED RADIO VALVES, BOXED, 24-HOUR SERVICE

5U4G	6/6	6L6G	8/-	12Q7GT	7/6	ECC84	10/6	PEN45	15/-
5Z4	9/-	6L7	6/-	25L6GT	8/6	ECC85	9/-	PCC84	9/-
6AC7	5/6	6SA7M	7/-	25Z5	9/6	ECF80	12/-	PCC85	11/6
6AS	9/-	6SG7M	5/6	35Z4GT	7/6	ECL80	13/6	PCF80	12/6
6AL5	5/6	6SJ7M	7/6	41	9/6	EG36	4/-	PEN25	5/-
6AM6	6/6	6SKGT	5/-	42	9/6	EF37	7/-	PL81	13/6
6BA6	6/6	6SN7GT	5/9	43	9/6	EF37A	8/-	PL82	9/-
6BE6	6/6	6U4GT	12/6	80	7/6	EF39	5/-	PL83	11/-
6C4	4/9	6V6G	6/-	83	7/6	EF50(BR)	3/6	PM12M	5/6
6C6	4/6	6V6GT	7/-	807(BR)	3/9	EF50(AM)	4/9	PY80	8/6
6D6	4/6	6V6M	7/-	807(AM)	5/6	EF80	11/-	PY81	8/6
6H6	2/-	6X4	6/-	EA50	1/6	EF85	7/-	PY82	8/6
6J5M	5/-	6X5GT	5/-	EB34	1/6	EF89	9/6	SP41B	9/6
6J56T	4/6	7B7	7/6	EB91	5/6	EF91	6/6	SP13C	11/-
6J5G	3/-	6C6	7/6	EBC33	7/-	EF95	8/6	SP41	2/6
6J6	4/6	12A7M	8/6	EC52	5/-	EL32	4/6	SP61	2/6
6J7G	5/-	12AT7	8/-	ECC31	9/6	EZ80	7/6	TDD4	15/-
6K7G	4/6	12AU7	6/6	ECC81	8/-	HVR2A	5/-	TH41	12/6
6K7M	6/-	12AX7	8/6	ECC82	6/6	KT44	12/6	U22	7/6
6K8G	7/6	12K7GT	6/6	ECC83	8/6	KTW63	6/-	U52	9/6
								VP41	9/6

SEND S.A.E. FOR SPECIAL LIST 500 ITEMS

All items less 5% and post free for a dozen or more

Postage 1/- in £1 (1/9 in £1 Speakers/Trans.). Min. 6d. No. C.O.D.

100 TELEVISION SET BARGAINS TO CALLERS AT:—

350/352, FRATTON ROAD, PORTSMOUTH

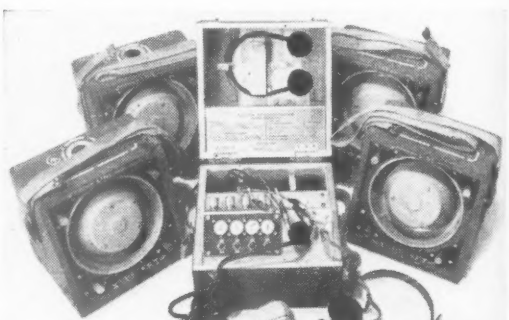

BEST EVER BUY!

EX MINISTRY OF SUPPLY

CANADIAN P.A. SYSTEM

Complete with Amplifier, 4 Speakers, Microphones, Headphones & all spares

6 or 12 volt D.C. Supply **£7.10** COMPLETE

NEW & UNUSED. PACKED IN WOODEN CASES. CARRIAGE EXTRA

For details of our full range of lines see January to July issues of Wireless World

DEPENDABLE RADIO SUPPLIES LTD.

12A TOTTENHAM STREET, LONDON, W.1

Phone LANgham 7391/2

ENGINEERS!

Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES." Full details of the easiest way to pass A.M.I.Mech.E., A.M.I.C.E., C. & G. (Electrical, etc.), General Cert., etc., on "NO PASS—NO FEE" terms and details of Courses in all branches of Engineering—Mechanical, Electrical, Civil, Auto, Aero, Radio, etc., Building etc. If you're earning less than £15 a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE

144 PAGES

Free!

B.I.E.T.

387 College House, 29-31, Wright's Lane, London, W.8.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

COVENTRY RADIO

COMPONENT SPECIALISTS SINCE 1925

We have now trebled the size of our premises in order to supply a larger range of Components, Amplifiers and HI-FI Equipment.

Send your enquiries to:

189-191, DUNSTABLE ROAD LUTON, BEDS.

New Telephone No.: LUTON 7388-9

PROVED

The finest method for cleaning records

Already over 200,000 enthusiastic users

THE "Dust Bug"

AUTOMATIC GRAMOPHONE RECORD CLEANER

PATENT APPLIED FOR

Price reduced to 17/6 (plus 7/- purchase tax)

from your local dealer or

CECIL E. WATTS

Consultant and Engineer (Sound Recording and Reproduction)

Darby House, SUNBURY-on-THAMES, MIDDX

VALVES
Guaranteed All Tested Before Dispatch

AC6PEN	6/6	KK32	23/-	UL41	10/6	6C6	5/-	6V6G	7/-	15D2	7/9
AC/THI	34/9	KLL32	8/6	UL44	27/10	6C8G	5/-	6V6GT	7/6	19BG6G	24/4
AC/P1 5 pin	12/6	KT24	5/-	UL46	24/4	6CD6G	31/4	6V6M	8/6	20D1	16/-
ATP4	3/6	KT33C	10/-	UL84	11/6	6CH6	7/6	6X4	7/6	20F2	27/10
AZ31	12/6	KT36	27/10	UU6	20/11	6D6	5/-	6X5G	7/-	20P1	27/10
CBL31	24/4	KT55	12/6	UU8	27/10	6F6G	7/6	6X5GT	7/-	20P3	24/4
CCH35	24/4	KT66	15/-	UU9	8/6	6F6M	7/6	6/30L2	12/6	20P5	20/11
CL33	20/2	KTW61	8/-	UY41	8/6	6F13	14/-	7B7	8/6	25A6G	11/6
CY31	17/5	KTW63	7/6	UY85	10/-	6F15	14/-	7C5	8/-	25L6GT	10/-
DAF96	10/6	KTZ41	6/6	VP2B	8/-	6G6G	4/6	7C6	8/-	25Y5G	9/9
DF96	10/6	ME91	7/6	VP13C	3/6	6H6	2/6	7D6	13/6	25Z4	9/6
DH63	9/-	MH41	7/9	VP23	6/6	6H6GT	2/6	7H7	9/-	25Z5	10/-
DK96	10/6	MSP4/5	12/6	VP41	8/6	6J5M	6/6	7Q7	9/-	25Z6	10/-
DL96	10/6	MSP4/7	12/6	VR105/30	8/-	6J6	6/-	7S7	9/6	30F5	11/6
DM70	8/6	N37	18/1	VR116	4/-	6J7G	6/6	7Y4	8/6	30FL1	11/6
EA50	1/6	N78	12/6	VR150/30	9/-	6J7M	9/-	8D2	2/9	30P4	21/7
EABC80	10/-	OZ4	5/6	VU120A	3/6	6K6GT	7/-	9D2	3/6	30P12	12/6
EAC91	7/6	P61	3/6	VU111	2/6	6K7G	5/-	10F1	27/10	30PL1	12/6
EAF42	10/6	PCC84	10/-	VU39 (MU12-14)	8/9	6K7M	6/9	12A6	6/6	35L6GT	9/6
EB34	2/-	PCF80	13/6	W77	8/6	6K8G	8/6	12AH8	11/6	35W4	8/6
EB41	9/6	PCF82	12/6	W729	13/6	6K8GT	10/-	12AT6	10/6	35Z4GT	8/-
EBC33	7/6	PCL82	12/-	X65	11/6	6K25	20/11	12AT7	9/-	35Z5GT	9/-
EBC41	10/-	PCL83	14/6	X78	22/3	6L6G	9/-	12AU6	10/6	42	8/-
EBF80	10/6	PL38	27/10	X79	11/6	6L7	7/6	12AU7	8/-	50C5	11/6
EBF89	18/1	PL81	16/-	Y63	9/-	6N7	7/6	12AX7	9/-	50CD6G	31/4
EBL21	24/4	PL82	8/6	Z309	9/6	6P28	27/10	12BA6	9/-	50L6GT	8/6
EBL31	24/4	PL83	11/6	Z359	9/6	6Q7G	9/-	12BE6	10/-	75	11/6
ECC40	12/6	PX25	12/6	Z759	9/6	6Q7GT	9/-	12H6GT	3/-	77	7/6
ECC84	10/3	PY80	9/-	1A3	3/6	6SA7GT	8/-	12J5GT	4/6	80	8/6
ECC85	9/6	PY81	10/-	1A5GT	6/-	6SG7	7/6	12J7GT	10/6	142BT	3/6
ECF80	13/6	PY82	9/-	1C2	11/6	6SH7	6/-	12K7GT	7/6	185BT	34/9
ECF82	13/6	PY83	10/-	1C5GT	12/6	6SJ7	8/6	12K8GT	13/6	210DDT	4/6
ECH21	24/4	PZ30	20/11	1D5	12/6	6SK7	6/-	12Q7GT	7/6	210VPT	3/6
ECH35	10/6	PEN4DD	27/10	1D6	12/6	6SL7GT	8/-	12SC7	1/6	807	6/6
ECH42	10/6	PEN4VA	15/-	1H5GT	10/6	6SN7GT	7/6	12SG7	7/6	954	2/-
ECH81	9/-	PEN25	5/-	1L5	6/6	6SQ7	9/3	12SH7	5/6	955	4/9
ECL80	13/6	PEN44	27/10	1LD5	3/6	6U4GT	14/-	12SJ7	8/-	956	3/6
ECL82	13/-	PEN45	27/10	1N5	10/6	6U5/6G5	8/6	12SK7	6/-	9001	5/6
EF22	8/6	PEN46	7/-	1R5	8/-	6U5G	8/6	12SL7	8/-	9003	5/6
EF36	6/-	PEN220A	4/-	1S4	10/6	6U7G	8/6	12SN7GT	17/6	9004	5/6
EF37A	12/-	PENA4	15/-	1S5	7/6			12S7Q	8/6	9006	5/6
EF39	6/6	QP21	7/6	1T4	7/6						
EF40	14/6	R16	27/10	1U5	7/6						
EF41	9/9	R19	13/6	2C26	1/6						
EF42	14/-	SP41	3/-	2X2	4/6						
EF50	4/-	SP61	3/-	3A4	7/-						
EF54	6/-	T41	24/4	3D6	5/-						
EF55	10/-	TH2	9/-	3Q4	9/-						
EF80	8/6	TP25	27/10	3Q5GT	9/6						
EF85	9/-	U10	10/6	3S4	8/-						
EF86	14/6	U14(DW4/500)	8/6	3V4	9/-						
EF89	10/-	U22	8/-	4D1	3/-						
EK32	8/6	U25	14/6	5R4GY	9/6						
EL32	5/6	U26	14/6	5U4G	8/-						
EL33	20/2	U36	13/6	5Y3G	8/-						
EL38	27/10	U37	27/10	5Y3GT	8/-						
EL41	11/-	U45	15/-	5Z4G	10/-						
EL42	12/-	U50	8/-	6A7	13/-						
EL81	10/6	U329	14/6	6A8G	10/-						
EL84	10/6	U403	17/5	6AC7	6/6						
EM34	10/6	U404	11/10	6AG5	5/6						
EM80	10/6	U801	31/4	6AK5	6/6						
EM81	11/6	UABC80	10/6	6AL5	6/6						
EY51	13/6	UAF42	10/6	6AM6	9/-						
EY86	13/6	UB41	9/6	6AQ5	7/6						
EZ40	9/-	UBC41	10/-	6AT6	8/6						
EZ41	10/-	UBF80	9/6	6AU6	10/6						
EZ80	8/9	UCC84	20/11	6B4	5/-						
EZ81	11/10	UCF80	23/-	6B8G	4/-						
EZ90	8/-	UCH42	10/6	6BA6	7/6						
E1148	2/-	UCH81	11/6	6BE6	8/-						
FC13	7/6	UCL82	23/-	6BG6G	24/4						
FW4/500	10/-	UCL83	25/9	6BH6	16/-						
GZ32	12/-	UF41	10/6	6BJ6	9/-						
H30	5/-	UF85	10/6	6BR7	11/6						
HL23DD	8/6	UF89	10/6	6BW6	8/6						
HL41	3/-			6BW7	10/-						
K40N	9/-			6C4	7/-						
KF35	8/6			6C5GT	6/6						

MAINS TRANSFORMERS

3-Way Mounting Type.

MT1
Primary 200-220-240 v. Secondaries 250-0-250 v. 80 m/A 0-6.3 v. 4 amp. 0.4 v. 2 amp. Both tapped at 4 v., **21/9** each.

MT2
Primary 200-220-240 v. Secondaries 350-0-350 v. 80 m/A 0-6.3 v. 4 amp. 0.5 v. 2 amp. Both tapped at 4 v., **21/9** each.

MT3
Primary 200-220-240 v. Secondary 30 v. 2 amps. Taps at 3 v., 4 v., 6 v., 8 v., 9 v., 10 v., 15 v., 18 v., 20v., 24 v., **21/9** each. Postage and Packing please add 2/- per transformer.

HEATER TRANSFORMERS. Primary 220/240 volts.

2 volt ½ amp.	5/-	5 volt 2 amp.	10/-
2 volt 3 amp.	8/3	6.3 volt ½ amp.	5/6
4 volt 1½ amp.	5/6	6.3 volt 1½ amp.	6/9
4 volt 3 amp.	10/-	6.3 volt 3 amp.	10/-
		12 volt ¾ amp.	5/7

OUTPUT TRANSFORMERS
5,000 ohms to 3 ohms. 40 m/A **4/6** each. 10,000 ohms to 3 ohms 30 m/A **4/6** each. 5,000 ohms to 3 ohms 60 m/A **5/-** each. Universal output Transformer 18 ratios available Optimum loads 3,000 ohms to 12,000 ohms, Speech Coil Impedance 2.5 ohms, 12.5 ohms and 15 ohms, current 40 m/A **5/9** each.

L.F. CHOKES (Clamp Construction). 20H, 250 ohms 60 m/A **6/-** each. 10H, 200 ohms 90 m/A **9/3** each.

TRANSFORMERS FOR BATTERY CHARGERS. Primary 220/240 volts. 6-12 v. 1 amp. **13/6** each. 6-12 v. 3 amp. **18/-** each. 6-12 v. 4 amp. **21/-** each.

CHASSIS
Aluminium undrilled with reinforced corner. Available in the following sizes —

6in. × 4in. × 2½in.	**4/6** each
8in. × 6in. × 2½in.	**6/3** each
10in. × 7in. × 2½in.	**7/3** each
12in. × 3in. × 2½in.	**5/9** each
12in. × 5in. × 2½in.	**6/9** each
12in. × 8in. × 2½in.	**8/6** each
14in. × 3in. × 2½in.	**6/-** each
14in. × 9in. × 2½in.	**12/-** each
16in. × 6in. × 2½in.	**8/6** each
16in. × 10in. × 2½in.	**14/-** each

All are four-sided—ideal for radio receivers—amplifiers—power packs, etc.

SMALL MAINS TRANSFORMER. Type TE6. Suitable for Television Convertors, etc. Specification Primary 230 v. 50 c/s. Secondary 1A 250 v. 40 m/A. Secondary 2·6.3 v. 1.5A. Clamp construction Overall size. 3.9in. x 2.4in. x 2in. over Windings. Fixing Centres 3.3in. Price **15/-**.

COMPLETE KIT OF PARTS FOR "MINI 7" £10/10/-.

COMPLETE KIT OF PARTS FOR 4 VALVE BATTERY PORTABLE £7/7/-.

COMPLETE KIT OF PARTS FOR ALPHA TRF SET £5/10/-.

COMPLETE KIT OF PARTS FOR TELETRON COMPANION £4/8/6.

RICHARD ALLAN
"BAFFLETTE"
EXTENSION SPEAKERS.

Attractive walnut finished cabinet on black plinth—expanded metal grill, fitted volume control, 8in. P.M. speaker 2-4 ohms. Large purchase from Relay Company of used units as above. Only require removal of matching transformer. All are in good working order.

Offered at a fraction of original cost.

25/6 each. POST PAID.

LOUDSPEAKERS—ELLIPTICAL TYPES

6in. × 4in. Plessey	19/6
7in. × 4in. Goodman	19/6
7in. × 5in. Goodman	19/6
8in. × 5in. Elac	25/6
10in. × 6in. Plessey	25/6

All brand new 2 to 3 ohms speech coil.

OUR NEW 1958/59 CATALOGUE

Fully illustrated and including all the latest components it is invaluable to Amateurs and Service Engineers.

Send 1/- in stamps today for your copy.

ACOS MICROPHONE
Manufacturer Discontinued Model.
MIC.33-1.
A crystal hand or desk microphone designed for the high quality public address and tape recording field, incorporating a specially designed acoustic filter giving a response flat from 30 to 7,000 c.p.s. The microphone is omni-directional and is housed in an attractive plastic case.
Listed 50/-.

OUR PRICE 29/6.

ALPHA RADIO SUPPLY CO.
103, LEEDS TERRACE, WINTOUN STREET, LEEDS, 7

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-.
For full terms of business see inside cover of our catalogue.
Personal Shoppers 9 a.m. to 5 p.m. Mon. to Friday. Saturday 10 a.m. to 1 p.m.

RADIO TRADERS LTD.

23 WARDOUR ST., LONDON, W.1. (Coventry Street end)

Phone No. :GERrard 3977/8 Grams: "Radiotrade"

STOCKISTS OF CARR FASTENER COMPONENTS

ALL POPULAR TYPES OF Cinch Reg'd. COMPONENTS SUPPLIED FROM STOCK

SPECIAL OFFER OF CURRENT MANUFACTURE ELECTROLYTIC CONDENSERS (tubular wire end P.V.C. sheathed). 8 mfd. 450 v., 2/6 each; 16 mfd. 450 v. 3/-; 32 mfd. 450 v. 4/-; 8 x 8 mfd. 450 v. 3/9; 8 x 16 mfd. 450 v. 4/-; 16 x 16 mfd. 450 v. 4/6; 32 x 32 mfd. 350 v. 5/-.

BIAS CONDENSERS. 2,500 mfd. 3 v. 3/6; 250 mfd. 25 v. 2/-; 100 mfd. 25 v. 1/6; 50 mfd. 12 v. 1/6; 25 mfd. 25 v. 1/6.

ELECTROLYTIC CONDENSERS. Manufacturers' surplus, in perfect condition. 100 mfd. x 200 mfd. 350 v. surge 5/6 each; 100 mfd. x 100 mfd. 425 v. surge 5/6 each; 150 mfd. 450 v. wkg. 5/6 each.

TRANSISTORS: Junction type Red Spot by well-known manufacturers 10/- each.

TRANSISTOR CONDENSERS: Miniature Electrolytic Capacitors. 32 mfd. 3 v., 25 mfd. 25 v., 25 mfd. 6 v., 16 mfd. 12 v., 8 mfd. 6 v., 5 mfd. 12 v., 2.5 mfd. 25 v. 1.6 mfd. 6 v., 1 mfd. 12 v. All these types of condensers are 3/6 each. SPECIAL DISCOUNTS FOR QUANTITIES.

AIR-SPACED TRIMMERS, 5, 10, 15, 20, 25, 50 and 75 of pre-set and spindle types 2/- each.....doz. 21/-

MIDGET MICA CONDENSERS. .0001, .0002, .0003, .0004, .0005 5/- per dozen.

200 Assorted Moulded Mica Condensers, popular value.....	£2 10 0
200 Assorted Silver Mica Condensers, popular values.....	£2 10 0
200 Assorted Carbon Resistors, ½, ¼ and 1 watt. Good selection	£1 10 0

PAXOLIN SHEET. 18 x 4½ x 1/16in. 1/6; 10 x 10 x 1/32in. 1/6; 20 x 20 x 1/32in. 3/-; 10 x 10 x 1/16in. 2/-; 20 x 10 x 1/16in. 4/-. Minimum P. & Pkg. 1/6.

MANUFACTURERS PLEASE NOTE. We hold large stocks of Nitrogol, Visconol and other block-type Condensers, your enquiries are invited.

W.W. RESISTORS. 5 watt 1/6; 10 watt 2/6; 15 watt 3/-; 20 watt 3/6. We carry stocks of resistors from 2 watts to 150 watts W.W. Your enquiries invited.

HIGH STABILITY RESISTORS. ½ watt 5% 6d.; ¼ watt 5% 9d.; 1 watt 5% 1/-. A few values in 1% and 2% still available. ALL ORDERS FOR RESISTORS C.O.D. PLEASE, AS WE CANNOT GUARANTEE TO STOCK ALL VALUES.

GROMMETS. 1 gross assorted ⅛in. to 1in..... 8/6

WESTECTORS. WX6, WX12, W4, 1/- each.....per doz. 9/-

SIGNAL LAMP HOLDERS. Panel mounting, complete with Adjustable Lamp Holder 2/- each.....per doz. 21/-

FUSEHOLDERS. B/Lee L.356 single hole 2/6 each; B/Lee L.1033/C4 double pole 3/6 each. SPECIAL PRICES FOR BULK QUANTITIES.

BARGAIN OFFER OF BATTERIES

4½ v. Heavy Duty Bell, bty. size 6½ x 4½ x 2½in.....	2/6+1/9 P.P.
72 v. H.T. 1.5 v. L.T., 6 x 5 x 1⅛in.....	2/6+1/9 P.P.
60 v. H.T. 1.5 v. L.T., 3½ x 3½ x 1½in.....	4/6+1/6 P.P.

All batteries are sealed, unused, and are tested prior to despatch.

WEARITE COILS. PA4, PO4, PA5, PO5, 1/3 each.....per doz. 12/-

4-WAY PUSH BUTTON UNITS. 2/6 each. Knobs for same, 3d. each.

POINTER KNOBS. Small black with white line 7/6 per doz. Small white with black line 8/- per doz. Both types ¼in. spindle. Large price reductions for 1,000 lots and over.

VALVE HOLDERS. Moulded B9A 7/6; B7G 6/-; Int. Oct. 9/-; Eng. Oct. 4/6. Valve holders fitted with lower can 1/6 per doz. extra.

SCREENING CANS for B7G and B9A 6/- per doz.

CO-AXIAL PLUGS, SOCKETS AND CONNECTORS

PYE TYPE. 10H/3911, 1/6 each; 10H/701, 1/6; 10H/628, 1/6; "Tee" con. 2/-. F. & E. Type: LS-I-PF, 2/- each; JP-I-250 c.c.t. 2/-; JS-I-BHF, 4/6; PL259 DE, 4/6. LARGE QUANTITIES AVA .ABLE. SPECIAL PRICES FOR 100 and 1,000 lots.

JONES PLUGS AND SOCKETS. 4 pin 2/6 pair; 6 pin 3/6 per pair; 8 pin 4/6 per pair; 12 pin 6/6 per pair. If cover required send 1/6 extra per cover.

WANDER PLUGS. Red and black.....doz. 2/-

PHILIPS TRIMMER TOOLS 1/- each.....doz. 10/6

CASH WITH ORDER OR C.O.D. ALL ORDERS DEPT. W.1

ALL ORDERS FOR LESS THAN £2 ADD POSTAGE

We invite your enquiries for items not listed.

Trade Counter open 9 to 6 Monday to Friday

Also 9 to 1 Saturdays. Callers welcomed

WHOLESALE MANUFACTURERS AND EXPORT ENQUIRIES INVITED

TRS

OFFER THE BEST FOR YOUR MONEY!

MULLARD "3–3" QUALITY AMPLIFIER

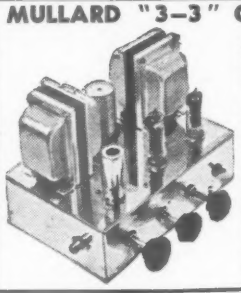

An ideal companion unit to the JASON Tuner. A really first-class 3-valve 3-watt Amplifier giving Hi-Fi quality at a reasonable cost. Mullard's latest circuit. Valve line-up: EF86, EL84, EZ80. H/duty mains trans. giving extra HT and LT for Tuner Unit addition.

Variable treble cut and bass boost controls, sensitivity 100 MV for 3-watt output. Frequency response + or − 1db, 40 c/s to 25 kc/s.

Complete amplifier wired and tested with quality sectionalised output transformer to Mullard specification

(less speaker) Carr. and ins. 4/6. **£8.8.0**

Wired Power O/Put Socket with Additional Smoothing for F.M. Tuner 10/6 extra.

JASON F.M. TUNER UNIT 87-105 mc/s

Designer Approved Kit of parts to build this modern highly successful unit, drilled chassis and superior type dial. Coils, cans and all quality components, etc., for only 5 gns., post free. Set of 4 spec. EF91 or equiv. valves 30/-, post free. Illustrated handbook with full details, 2/-, post free—**Free with Kit. 48-hr. Alignment Service** 7/6 and 2/- p. & p. **AND NOW—Jason "Mercury" Switched F.M. Tuner,** with A.F.C. Complete kit only 8¼ gns., plus 2/6 p. & p.
Set of 3 x E F 80 valves, special price 21/-.

ELECTROLYTICS ALL TYPES NEW STOCK

TUBULAR		CAN TYPES	
25/25v., 50/12v.	1/9	8+8/450v.	4/6
50/50 v. 4,500v.	2/-	8+16/450 v.	5/-
100/250 v.	1/9	8+16/500 v.	5/6
8/450 v.	2/3	16+16/450 v.	5/6
8/500 v.	2/9	16+16+8/350v	5/6
8+8/500 v.	4/6	32+32/350 v.	5/6
8+16/450 v.	5/-	32+32/275 v.	4/6
16/450 v. ..	3/6	50+50/350 v.	6/6
16+16/450 v.	5/6	60/350 v.	6/6
32/350 v. ..	4/-	60+250/275 v.	12/6
32/500 v. ..	5/-	64+120/275v.	11/6
32+32/350 v.	5/6	100+200/275v.	12/6
32+32/450 v.	6/6	100/270 v.	6/6

MIDGET TRANSISTOR TYPES. 2μF 4μF, 8μF, 6v. 3/6; 6μF, 10μF, 16μF, 3v., 3/6; 32μF, 1½v. 3/6.

CONDENSERS—Silver Mica. All pref. values, 2 pf. to 1,000 pf. 6d. each. Ditto ceramics 4d. each. Tubulars 450 v. T.C.C., etc. .001 mfd.-.01 and .1/350 v., 9d. each. 02-1.500 v. 1/- each. .25 Hunts. 1/6. 5 T.C.C., 1/9. .001 6kv. 5/6. .001 20kv. 9/6.

CLOSE TOLERANCE CONDENSERS 8/Mica. 10% Type. 5pf.—500 pf., each 1/-; 600 pf.—5,000 pf., each 1/3. 1% Type, 1.5 pf.—50 pf. (Tol. 1 pf.), 1/9; 56 pf.—500 pf. each 1/9; 575 pf.—5,000 pf., each 2/-

RESISTORS.—Pref. val. 10 ohms 10 M ohms.

CARBON		WIRE-WOUND	
20% Type, ½ w.	3d.	5 w.	25 ohms—1/3
½ w., 5d.; 1 w.,	6d.	10 w.	10,000 ohms 1/6
6 w.,	9d.	15 w.	2/-
10% Type, ½ w.	9d.	5 w.	15,000—33,000 ohms 1/9
5% Type, ½ w.,	1/-	10 w.	2/3
1% Hi-Stab, ½ w.	2/-		

WIRE-WOUND POTS

Pre-set Min. T.V. Type Knurled Slotted Knob. All values 25 ohms to 30 K., 3/- ea., 50 K. 4/-. Ditto Carbon Track, 50 K., to 2 Meg., 3/-.

3 w. LAB. COLVERN, etc. Standard Size Pots 2¼in. Spindle. High Grade. All Values. 100 ohms to 50 K., 5/6; 100 K., 6/6.

W/W EXT. SPEAKER CONTROL, 10Ω, 3/-.

SPEAKER FRET.—Expanded Bronze anodised metal 8 x 5in., 2/3; 12 x 8in., 3/-; 12 x 12in., 4/6; 12 x 16in., 6/-; 24 x 12in. 9/- etc. Preferred sizes only.

SENTERCEL RECTIFIERS. H.T. Type Fly-Back Voltages. K3/25 2 kV., 5/-; K3/40 3.2 kV. 6/9; K3/45 3.6 kV. 7/3; K3/50 4 kV., 7/9; K3/100 8 kV. 13/6; etc. **MAINS TYPES.**—RM1 125 v. 60 mA., 4/9; RM2 125 v. 100 mA. 5/6; RM3 125 v. 120 mA., 7/6; RM4 250 v. 250 mA., 16/-; RM4B type 270 mA. 17/6; RM5 250 v. 300 mA., 21/-.

TYGAN FRET (Murphy pattern). 12in. x 12in., 2/-; 12 x 18in., 3/-; 12 x 24in., 4/-, etc.

NEW BOXED VALVES ALL GUARANTEED

1R5, 1T4	7/6	EABC80	9/6
185, 1847	7/6	EB91	6/6
384 3V4	8/-	EBC41	9/6
5Z4	9/6	ECC83	10/6
6AT6	8/6	ECC84	12/6
6K7	6/6	ECF80	12/6
6K8	8/6	ECF82	12/6
6Q7	8/6	ECH42	10/6
6SN7	8/6	ECH81	10/6
6V6	7/6	ECL80	10/6
6X4	7/6	EF41	10/6
6X5	7/6	EF80	10/6
7C5	9/-	EF86	12/6
7Y4	8/6	EF91	8/6
DAF96	9/-	EL41	10/6
DF96	9/-	EL84	11/6
DK96	9/-	EY51	12/6
DL96	9/-	EY86	14/6
35L6	10/6	EZ40	8/6
EZ81	8/6	MU14	9/6
PCC84	10/6	PCF80	10/6
PCF82	10/6	PCL83	12/6
PL82	10/-	PL83	11/6
PY80	9/6	PY81	9/6
PY82	8/6	PY83	10/6
U22	8/6	U25	12/6
UBC41	9/6	UCH42	10/6
UF41	10/-	UL41	10/6
UY41	8/6		

SPECIAL PRICE PER SET

1R5, 1T4, 185, 184 or 384 or 3V4	27/6
DK96, DF96, DAF96, DL96	35/-
6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5	35/-

Vol. Controls Log ratios, 10,000 ohms—2 Megohms. Long spindles, 1 yr. guarantee. Midget Ediswan type, 1¼in. dia. No. Sw. 3/-; S.P. Sw., 4/-; D.P. Sw. 4/9. Linear Ratio, 10,000ohms—2Megohms. Less switch, 3/- each. **Coax plugs** 1/-. **Coax sockets,** 1/-. **Couplers** 1/3. **Outlet Boxes,** 4/6.

80 ohm CABLE COAX

STANDARD ¼in. diam. Polythene insulated. GRADE "A" ONLY.

8d. yd.

SPECIAL—Semi-air spaced polythene. 80 ohms **Coax.** ½in. dia. Standard core. Losses cut. 50% **9d. yd.**

IDEAL BAND 3

MAINS TRANSFORMERS.—Made in our own Workshops to Top Grade spec. Fully interleaved and Impregnated. **RADIO AND AMPLIFIER TYPE.**—250 v., 60 mA. F.W. sec. 5 v. or 6.3 v. 1 a., rect. 6.3 v. 2.5 a. sec. Htrs., 22/6, etc., **C.R.T., HTR. ISOLATION TYPE.**—Low leakage with or without 25% sec. boost voltage. Ratio 1 : 1 or 1.25, 2 v., 10/6; 4 v. 10/6; 6.3 v., 10/6; 13.3 v., 10/6. Ditto with mains primaries 200/250 v., 12/6.

SPECIAL TRANS.—Wound to your requirements.

LOUDSPEAKER.—P.M. 3 ohms 2½in. Elac, 17/6; 3in. Goodmans 18/6; 5in. Rola 16/6; 6in. Elac 18/6; 7 x 4in. Goodmans Elliptical 18/6; 8in. Rola 20/-; 10in. B. and A., 25/-; 10in. WB-HF1012 99/9; 12in. Pleasey 15 ohm with 6 x 4in. Tweeter and Cross Over Filter, 97/6.

ONLY A FEW ITEMS ARE LISTED FROM OUR COMPREHENSIVE STOCK.

TRS

RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK RD., THORNTON HEATH, SURREY

Phone: THO 2188. Hours 9 a.m.—6 p.m., 1 p.m. Wed. Open all day Saturday. By Thornton Heath Station.

Terms C.W.O. or C.O.D., Kindly make cheques, P.O.s, etc., payable to T.R.S. Post and Packing up to 1lb. 7d., 1lb. 1/1, 3lb. 1/6, 5lb. 2/-, 10lb. 2/9. Bargain Lists 9d.

Visit the City's new acoustically designed

HI-FI Centre

AMPLIFIERS BY:

VERDIK	GOODSELL
ARMSTRONG	QUAD
ROGERS	LEAK
DULCI	W.B., etc.

TUNER UNITS
AM/FM CHASSIS
RADIOGRAM CHASSIS
BY LEADING MAKERS

A COMPREHENSIVE RANGE of Hi-Fi speakers by **Goodmans, Wharfedale, W.B., G.E.C., Lorenz,** etc. Tweeter units by **Goodmans, Wharfedale, T.S.L., Elac,** etc.

AUTO-CHANGERS

BRAND NEW OFFER!

COLLARO 4-SPEED AUTO-CHANGERS

incorporating auto and manual control. Complete with Studio crystal p.u. and sapphire stylus.

Our price Plus 5/- post. **£7-19-6**

B.S.R. 4-speed Model T.U.8 Autochanger, plays 7in., 10in. and 12in. mixed records. Crystal T/O pick-up. £7/19/6. (Plus 5/- post and ins.)

GARRARD 4-SPEED SINGLE PLAYER UNIT with GC2 t/over cartridge for 78 and L.P. records. Our price **£7/10/-**, 4/6 post and ins.

4-SPEED COLLARO. 4/546 single player with Studio t/over pick-up. Limited number only. Our price **£6/19/6.** (Plus 3/6 post and pkg.)

COLLARO JNR. 4-speed motor and t/table with Acos crystal t/over cartridge. Our price £4/10/- complete. 3/6 post and ins.

GRAM. MOTOR AND T/TABLE only at £3/2/6. Post and ins. 2/6.

THE NEW B.S.R. 4-SPEED TU9 record player using the new B.S.R. ful-Fi crystal cartridge. Our price **£4/12/6.** (Plus 4/- post and ins.)

PICK-UP SNIP

Featherweight pick-up with HGP 59/1 t/over cartridge and pick-up rest **32/6**
Plus 1/6 post and ins.

NOW IN STOCK. Collaro 4-speed transcription turntable and pick-up. **£19/10/-.** Post and packing 7/6.

Brand New 5-valve RADIOGRAM CHASSIS complete with valves.

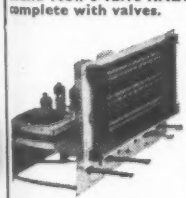

Superhet with long, medium and short wave bands. Pick-up and ex. speaker sockets. Our price **£9/10/-.** Plus 7/6 p. & ins.

THIS MONTH'S SNIP

LIMITED QUANTITY OF 9in. and 12in. MAGNETIC T.V. TUBES. BRAND NEW AND BOXED BY FAMOUS MAKER

SPECIFICATION 12in. TUBE
Will replace most MAZDA 12in. 2 v. Tubes. Flat face, white fluorescence triode, 2 v. heater, 1.5 A heater current, anode voltage 10 kv. OUR PRICE **£8/19/6** including mask. *9in. TUBE.* Round face, white fluorescence, 4 v. heater, 1 a. heater current, max. anode voltage 7 kv. OUR PRICE **£5/17/6.** Crating and carriage 11/6.

ANOTHER BARGAIN

Due to the popularity of this chassis, we have been able to reduce production costs and can now offer our 1958 AM/FM R/G Chassis at **19 gns.** complete.

Eight-valve AM/FM chassis with printed circuit FM tuner section. Illuminated dial; 4 waveband; coverage 1,000-2,000 metres, 200-550 metres, 15-50 metres, 88-100 Mc/s. Dimensions 13 x 9 x 6in.; Fully guaranteed. Exceptional value—only **19 gns.**, plus 7/6 post and ins.

ANOTHER SCOOP—50 ONLY. Brand new Collaro Mk. III Tape Transcriptor with digital counter. Price **15 gns.** Carriage and pkg. 12/6. Pre-amp. power pack for above deck, **£21**, plus 3/6 post and pkg.

3 NEW RECEIVERS FOR CONSTRUCTORS

1 valve 5 w. radio, 24-40 metres. All components, **35/-.**
Beginners' transistor pocket radio, miniature components, **35/-** complete.
Personal portable radio. All parts, complete, **35/-.**

STEREO!
WE ARE NOW DEMONSTRATING THE NEW STEREOPHONIC EQUIPMENT

ROGERS. New Stereo Control Unit for Hi-Fi stereo reproduction from tape, records and radio. Designed to match most R.D. Junior Units. Price **£18/10/-.**
The new B.J. Stereo Cartridge with diamond stylus, **£8/8/-.**
B.J. Tan II Arm for Cartridge, **£4/7/6.**
Brenell Mk. 5 Tape Recorder and Hi-Fi Speaker with all the latest features, **64 gns.** Mic. extra.
Stereo heads and amplifiers available for this recorder.

BRAND NEW HIGH-GRADE METERS By E. TURNER

1 M/Amp. DCO—10 Scale 2½in. diam....	50/-
100 M/Amp. DCO—100 mA 3-7/8in. diam.	50/-
100 Micro Amp. D.C. 0-2mA. 0-250 v. 3-7/8in. diam.....	85/-
500 V.D.C. 0-500 v. (1 KVPV) 3-7/8in. diam.	65/-
1000 V.D.C. 0-1000 v...(20 KVPV) 3-7/8in. diam.	95/-
300 V.A.C. 0-300 v. 3-7/8in. diam.	50/-

Post and packing 2/6.

BRAND NEW 0-1 AMP. 12in. SCALE R.F. METER
Thermocouple 5/-; 0-300v A.C., 2½in. scale, moving iron meter, 25/-. Post 2/6.

0-1 M/amp. meter, M/C flush mounting	17 6
0-100 amps. 50 c.p.s., 4½in. meter	£2 10 0
0-50 amps. moving iron 6in. meter ...	£3 10 0

All brand new and boxed. Post and ins. 1/6.

EXCEPTIONAL VALUE. New Triplett A.C./D.C. pocket Test Meter with test prods and clips. 15 ranges; 1000 ohms per volt; ohms 0-300/250,000; milliamps 0-10/100/500; A.C./D.C. 10/50/250/1,000/5,000 volts. Only **£5/10/-**, plus 2/6 post and pkg.

EXTRA SPECIAL OFFERS in SPEAKERS
12in. Plessey P.M. speaker, 3 ohm speech coil, **32/6** plus 2/6 post and ins.
10in. Rola P.M. speaker, 3 ohm speech coil. Astounding value. only **24/6** plus 2/6 post and ins.
4½in. Plessey P.M. speaker, 3 ohm speech coil, **14/9** plus 1/6 post.
2½in. **ROUND SPEAKER**
1½in. deep **16/6** plus 1/-.

SPECIAL OFFERS TO TRANSISTOR CONSTRUCTORS. New range of sub-miniature capacitors by well-known manufacturer. All a. 2/6 each.
1μF 18 v. 1.6 μF 6 v. 2.5 μF 6 v. 5 μF 12.5 v. 8 μF 6 v. 16μF 12.5 v. 25 μF 6 v. 32μF 3 v. 25μF 25 v. 80 μF 6 v.

TRANSISTORS. Junction type PNP. Red-spot audio freq. **6/6.** R.F. **18/-.**

All TELETRON and REPANCO transistor components in stock.

SENSITIVE GERMANIUM DIODES. 3 for 2/6. New GD3 diodes 2/6 each. Mullard OA81 diodes 6/-. Postage 6d.

SPECIAL NEWS

For all Constructors and Browsers. NOW OPEN our new "walk-around" Bargain Basement, exceptional sale offers of manufacturers' and Govt. surplus components and equipment. IT WILL PAY YOU TO PAY US A VISIT.

Electronics (FLEET ST.) Ltd

Dept. B,
152/3 FLEET ST., LONDON, E.C.4.
Telephone: FLE 2833
Business hours: weekdays 9-6, Saturdays 9-1.

CABINETS & ENCLOSURES

By STAMFORD.

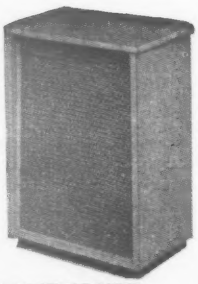

We are specialists in High-Fidelity enclosures built strictly to the specifications of the leading speaker manufacturers, and have pleasure in introducing an entirely new range of enclosures for the

COMPLETE WHARFEDALE RANGE
OPEN ALL DAY SATURDAY

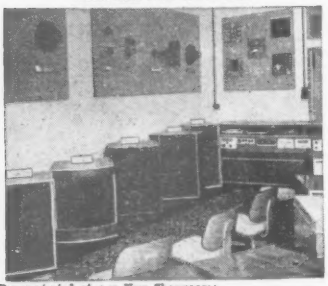

Demonstrated at our New Showroom:
Weymouth Terrace, (Off Hackney Road), London, E.2
Telephone: SHO 3003.
HOURS 9.30—5.30. 7 p.m. WEDNESDAY
COMPREHENSIVE DEMONSTRATIONS OF OUR NEW WHARFEDALE ENCLOSURES

Using Super 12 FS/AL; W 12/FS, 10in. Golden, 10in. Bronze and an entirely New and Very Attractive CORNER ENCLOSURE FOR THE WHARFEDALE 3-way system and embodying their patent Acoustic Filter. (Used with the approval of Messrs. Wharfedale Ltd.)

EACH ENCLOSURE is Hand-made throughout in superior ¾in. material, acoustically lined and quilted interior.

These cabinets are supplied in Oak, Walnut and Mahogany veneers finished to shade required. Delivery 12/6 in England and Wales, Scotland and N. Ireland 25/-.

Write for Catalogue of Equipment and cabinets for EQUIPMENT, RECORDS, SPEAKERS, PYE BLACK BOX, AND GOODMANS AXIOM ENCLOSURES. Satisfaction guaranteed or money refunded.

ANY CURRENTLY AVAILABLE EQUIPMENT OR SPEAKER CAN BE SUPPLIED, FITTED FREE OF CHARGE.

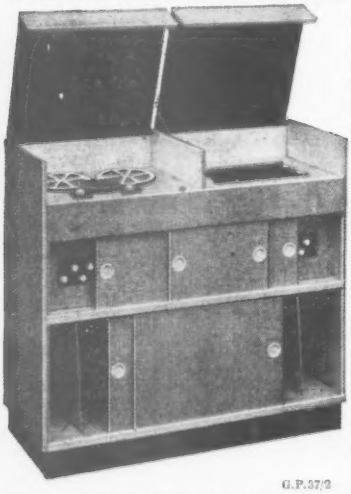

G.P.37/2

G.P.37/1. With taper legs in place of record storage: £22/11/6, or £3/4/- deposit and 9 payments of £2/6/5. G.P. 37/2. 3ft. 2in. Wide, 3ft. 3in. High, 17½in. Deep. £32, or £4/16/- deposit and 9 payments of £3/5/-.
Correspondence only:—

A. L. STAMFORD (Dept. C.4.)
20, College Parade, Salusbury Road, London, N.W.6

LONDON CENTRAL RADIO STORES

MIRROR GALVO'S. Instrument resistances, 190 ohm. External resistance 1,400 ohm. Sensitivity 2,200 M.M.S. NEW, in wooden transit box. Size 13×6×6in. £3/15/-.
ELLIOTT PEN RECORDERS. Decibel Meter 0-1mA. Suitable for measuring sound, atmospherics, etc. Price on request.
KING PIN INDOOR T.V. AERIALS. Band 3, Dipole 7/6. B.B.C. 13/6. Combined I.T.A./B.B.C. 16/-. Fully adjustable any angle. B.B.C./F.M. Radio 9/-. (All without co-axial cable).
DASHBOARD 8-DAY CLOCKS. Panel mounting, size 2½in. By well-known makers. £2/17/6.
VENNER 8-DAY CLOCKWORK TIME SWITCHES. 230 volts, 1 amp., 3½ × 2⅝ × 2½in., with key and connecting socket, 27/6.
HIGH-SPEED ELECTRO-MAGNETIC COUNTERS. Ex-Govt. 0-9,999, 25/50 v. D.C. Size 4 × 1 × 1in. Single coil, 2,300Ω. 18/6.
METAL RECTIFIERS. Ex-Govt., made by S.T.C., 250 v. 60 mA. Size 5⅛in. × 1in. dia. Unused. 7/6.
ELECTRO MAGNETIC COUNTERS. Ex-G.P.O., every one perfect, 400 and 500 ohm coil, counting to 9,999, operated from 25 v.-50 v. D.C., 4½in. long × 1½ × 1in. many industrial and domestic applications. 5/6.
0-1 MOVING COIL MILLIAMMETER. Overall dia. 3¼in. dial, 2½in. flush panel mounting. Guaranteed in perfect working order. 19/6.
DECIBEL METER. Moving coil, reading—30 to zero (0db=.775 v. (R.M.S.), overall dia. 4½in., dial 3in. £2/15/-.
MOVING COIL HAND MIKE. Type No. 7. 7/6.
UNISELECTOR SWITCHES. Have many applications including automatic tuning, circuit selection, etc. Operation on 24-50 v. Half wipe 6-bank. 12/6.
EX-G.P.O. DESK PHONES with a dial 0-9, in black bakelite case with handset attached. £2/10/-.
RELAYS. Type 3,000. 1,000 ohm coil, 2,000 ohm coil, 500 ohm coil, and 50 ohm coil. 7/6 each.
MILLIAMMETERS. 2in. dial. Reading 30-0-30, flush mounting. Ex-Govt. Not checked for accuracy. 6/-.
L.R. HEADPHONES. Lightweight. 7/6.
TUFNOL SHEETS. ¼in. thick, 47½in. × 47½in. £2, 23in. × 16in. 7/6, 16in. × 16in. 5/- per sheet.

All prices include carriage.

23 LISLE ST. (GER. 2969) **LONDON, W.C.2**
Closed Thursday 1 p.m. Open all day Saturday

NEW G.E.C., S.T.C. AND "WESTALITE" SELENIUM RECTIFIERS. Largest L.T. range in Gt. Britain. ONLY Makers' LATEST GOODS supplied NOT Surplus.

S.T. & C. E.H.T. K3/15, 5/ ; K3/45, 9/4; K3/50, 9/10; K3/100, 16/8; all post 4d extra.

BRIDGE CONNECTED FULLWAVE 17 v. 1 a., 13/4; 1.5 a. 26/6; 3 a., 30/6; 4 a., 38/-; 5 a., 38/6; all post 6d. 33 v. 1 a., 22/9; 1.5 a., 45/-; 3 a. 54/-; 5 a., 68/-; all post 1/6. 54 v. 1 a., 33/-; 1.5 a. 62/-; 2 a. 74/-; 3 a. 74/-; 5 a. 97/-; 72 v. 1 a. 42/-; 1.5 a. 78/-; 2 a. 95/-; 3 a. 95/-; 5 a. 124/-; 100 v. 1 a. 61/-; 1.5 a. 112/-; 2 a. 134/-; 3 a. 134/-; 5 a. 180/-, all post 2/-.

BRIDGE CONNECTED WITH 7¾in' SQUARE COOLING FINS 17 v. 6 a. 53/7; 10 a. 61/-; post 2/6.

BRIDGE CONNECTED HEAVY DUTY FUNNEL COOLED or 7¾in. SQUARE COOLING FINS. Both types, same price. 17 v. 20 a. 120/-; 30 a. 172/-; 50 a. 280/-; 33 v. 6 a. 89/-; 10 a. 102/-; 20 a. 202/6; 54 v. 6 a. 124/-; 10 a. 144/-; 72 v. 6 a. 160/-; 10 a. 186/-; 100 v. 6 a. 227/6; 10 a. 270/-; all post 3/-.

"WESTALITE" (BRIDGE) 12-15 v. D.C. 0.6 a. 12/-; 1.2 a. 30/-; 2 a. 32/6; 5 a. 37/6; 1.0 a. 64/6; 20 a. 117/6; 30 a. 171/-; 50 a. 278/-; 24 v. 1.2 a. 30/-; 5 a. 60/-; 10 a. 109/6; 20 a. 208/-; 36 v. 1.2 a. 47/6; 5 a. 82/6; 10 a. 154/6; 100 v. 1.2 a. 82/6; 2.5 a. 154/6; 5 a. 195/6; 10 a. 391/-; All post extra 1/6-3/6. E.H.T. Rects. 14D.134, 25/-; 36 E.H.T. 60 35/10, post 4d. 1 ma. AC/DC meter, rects. 14/6.

"G.E.C." (BRIDGE). 6 and 12 v. D.C. 1 a. 7/6; 1.5-2 a. 8/6; 2.5 a. 11/9; 3 a. 14/9; 4-5 a. 16/6; 6 a. 23/6; 10 a. 34/-; 14 a., 42/-; 24 v. 1 a. 12/6; 1.5 a. 14/3; 2 a. 15/6; 3 a. 26/-; 4 a. 29/6; 6 a. 36/6; 10 a. 75/-; other sizes. Post, under £1 add 1/- over £1 add 1/6.

Wholesale and Retail.

T. W. PEARCE
66 Great Percy Street, London, W.C.1
Off Pentonville Road. Between King's Cross and Angel

The FAMOUS R/T No. 22

W/S No. 22 is a complete R/T and W/T station, operating from 2-8 Mc/s. (37.5-150 metres). Set may be used on C.W., M.C.W., and R/T, with Break-in working possible on C.W., and M.C.W., complete with 500 Micro-amp. meter and 13 valves: 2 of AR8, 1 ARDD5, 5 of ARP 12, 1 of Arp 34, 1 of CV65, 3 of VT52. In excellent condition £5/19/6. Carr. 15/-.
12 v. vibrator type Power Supply Unit for above set, 22/6. Carr. 5/6. For price list of additional 22 set accessories send stamped addressed envelope.

WALKIE-TALKIE No. 38 MK. II

RIGHT IN PRICE AND SIZE—9×6×3½in.

Ideal for search parties, fire brigades, civil defence, building contractors, etc. Range approximately 5 miles, 7.4-9 Mc/s. Brand new condition. Complete with 5 valves, headphones, throat mic., junction box, aerials, harness signal satchel, spare set of valves and instruction card with illustrations. Operated from dry batteries H.T. 120/150 v., and L.T. 3 v. (not supplied). In brand new condition, our price £2/17/6 each, p. & p. 7/6.

RECEIVER-TRANSMITTER No. 18 Mk III
6-9 Mc/s., Rec. can be detached from Trans. Unit, built-in micro-amp-meter, complete with headphone and mic., aerial etc. In excellent condition. Our price 75/-, p. & p. 7/6.

MIDGET ROTARY TRANSFORMER

SIZE 1np. 11.5 v. Output 365/310 v. at 30 mA. Brand new and Trop. packed, 17/6 ea. p. & p. 1/6.

EX G.P.O. ELECTRO MAGNETIC COUNTERS, 5 × 1½ × 1¼in., 4 figures, various voltages D.C. 3/6 v. 18/24 v. 100/110 v. 200/230 v., 7/6 each, p. & p. 1/6.
INTERCOMMUNICATION HAND SETS, self-energised, similar to G.P.O. type, no electricity or batteries required, connect with 2-way bell wire, clear range of several hundred yards. Brand new, 32/6 per pair p. & p. 2/-.
HIGH SPEED RELAY, 2 bobbins, 1,000 ohms each 5/6, p. & p. 1/-.
U.S. HIGH SPEED RELAY, 300 ohms coil 2.65 v. adjustable contacts, 5/-, p. & p. 1/3.
HEADPHONES M/C, complete, 9/6 per set, p. & p. 1/6.
EX U.S. AERIAL, 9ft. spring loaded and fully collapsible, complete with cords and guys, ideal as aerial or fishing rod, brand new, 10/6, p. & p. 2/-.
AERIALS, 3 four foot "F" rods, bottom, centre and top (tapering) push-in-type sections, 10/6 per set, p. & p. 2/6. Matching aerial base 3/6, p. & p. 1/6.

BROADCASTER

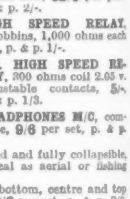

for talking, singing or announcing over your own radio, simply connect to your Radio pick-up . . . 2 Broadcasters will make a 2 station intercom. house phone. No electricity or battery required, just connect with 2-way wire. 12/6 ea., p. & p. 2/-.
M/C METER. 0-15 and 0-600 v. D.C. 2in. flush mounting ex equipment, 8/6, p. & p. 1/3.
METER. 2½in., 0-1 amp., projecting type thermo-couple, new and boxed, 6/6, P. & P. 1/3.
U.S. MIDGET MOTORS. 2×1¼in. Will operate from 6 v. to 24 v. D.C. 12/6 each, p. & p. 1/6.
DITTO. Will operate from 9 v. to 28 v. D.C., 12/6 each, p. & p. 1/6.

Special prices for bulk quantities.
Stockists of W/S No. 19 and spares.
TERMS C.W.O.

We specialise in Telephone and Z.A. Equipment and spare as used by Govt. Depts. and the Services. Trade and manufacturers' enquiries invited.

Postage and Carriage quoted, British Isles only.

FINSBURY TRADING CO.
12 STOKE NEWINGTON HIGH ST., LONDON, N.16. *Tel.: CLissold 7342*

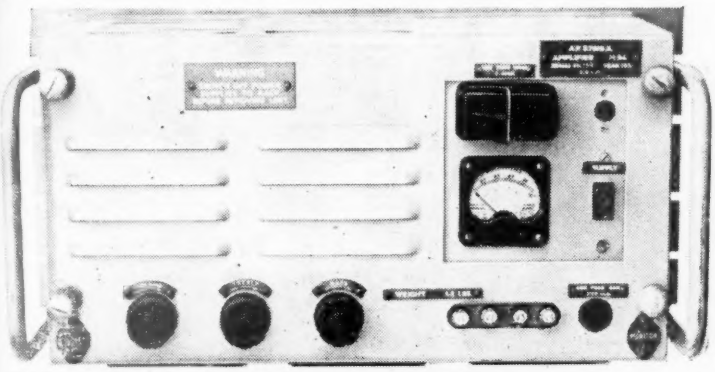

PUBLIC ADDRESS AMPLIFIERS

Two KT.66 giving 25 watts Push-Pull Output 110V–230V A.C. Mains. Ideal Factories, Fairgrounds, Sports Clubs etc. Built to most stringent Admiralty specification. Volume, Base and Treble Controls. Built in meter with switch for checking valves in operation. Paper block smoothing. Requires only 150 m-v high impedance input from gram or mike for full output. Tapped for 3.5–7–15 ohm Speakers and 600 ohm line.

BRAND NEW in original cases. **£12/17/6**. Carr. 12/6. Overall size approx. 17" × 17" × 8" Wt. 68lbs.

METERS BRAND NEW GUARANTEED PERFECT

Charging types.

2½ amp. D.C. M.I. 2in. fl. rnd.	7/6
5 amp. D.C. M.I. 2½in. fl. rnd.	11/6
7½ amp. D.C. M.I. 3½in. proj. rnd	12/6
9 amp. D.C. Hot Wire WR. 2½in. fl. rnd.	6/6

Voltmeters.

6 V. D.C. M.C. 2½in. proj. rnd.	8/6
12 V. D.C. M.C. 2½in. proj. rnd.	8/6
25 Volt D.C. M.C. 2in. fl. rnd.	7/6
30 Volt M.I. 3in. proj. rnd.	10/6
40 Volt M.C. 2in. fl. sq.	9/6
250 Volt A.C. rectified moving coil linear scale 3½in. fl. rnd.	35/-
300 Volt A.C. M.I. 2½in. fl. rnd.	22/-
400 Volt A.C. M.I. 4½in. fl. rnd.	35/-

Milliammeters

50 mA M.C. 2in. fl. sq.	7/6
30 mA M.C. 2½in. fl. rnd.	9/6
100 mA M.C. 2½in. fl. rnd.	9/6
500 mA M.C. 2½in. fl. rnd.	9/6
1 mA. M.C. 2½in. fl. rnd.	22/6
500 Microamp latest type Ernest Turner 2in. fl. rnd. with mounting ring and scaled 0-5	19/6
500 Microamp ex. equip. M.C. 2in. rnd. scaled 0-15 and 0-600 V.	14/6

Thermo-coupled

350 mA 2in. rnd. plug-in.	2/6
500 mA 2in. rnd. plug-in.	2/6
POSTAGE ON ALL METERS	1/-

U.S.A. PRECISION SERIES 834.S MULTIRANGE TESTERS for A.C. and D.C. volts, ohms and milliamps, basic movement 400 microamp., in wooden carrying case, complete with test prods, new batteries, guaranteed perfect. Price **£6/19/6**. P. & P. 2/6

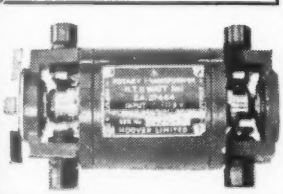

MIDGET ROTARY TRANSFORMERS 2½in. dia. x 4½in. Input 11.5 volt. Output 310/365 volt at 30 mA. Brand new. 17/6 each. P. & P. 1/6.

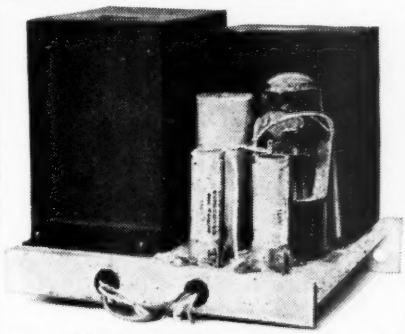

MAINS POWER SUPPLY UNITS, potted and sealed transformer and choke by famous maker. Mounted on metal chassis 6½ x 7½in. complete with 5Z4 rectifier valve and full smoothing. Input tapped 220-230-240 Volts. Output: 300 V D.C. at 100 mA.
6.3 V. A.C. at 4.5 amp.
6.3 V. A.C. at 2 amp.
Rectifier supply 5 V A.C. at 3 amp. Very conservatively rated. Price **42/6** plus P. & P. 3/6.

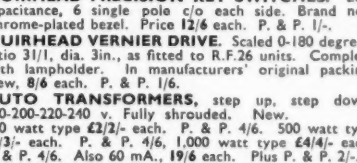

MUIRHEAD PRECISION KEY SWITCHES. Low capacitance, 6 single pole c/o each side. Brand new Chrome-plated bezel. Price **12/6** each. P. & P. 1/-.

MUIRHEAD VERNIER DRIVE. Scaled 0-180 degrees, ratio 31/1, dia. 3in., as fitted to R.F.26 units. Complete with lampholder. In manufacturers' original packing. New, **8/6** each. P. & P. 1/6.

AUTO TRANSFORMERS, step up, step down, 110-200-220-240 v. Fully shrouded. New. 300 watt type **£2/2/-** each. P. & P. 4/6. 500 watt type **£3/3/-** each. P. & P. 4/6, 1,000 watt type **£4/4/-** each. P. & P. 4/6. Also 60 mA., **19/6** each. Plus P. & P. 2/-.

Photo Multiplier. Type 931A, for Alfa counting, film scanning, spectography, etc., new. **£2/5/-** each. P. & P. 1/-.

AIRCRAFT CINE CAMERA G45B Mk. III, fully modified, fitted with f/3.5 triple anastigmatic lens, takes 25ft. of 16 mm. film, fitted with 24 v. motor. 16 exposures per sec. Mint condition, brand new, in maker's original packing. **£6/10/-** each. P. & P. paid.

MOVING COIL HEADSETS FINEST CANADIAN MAKE complete with moving coil No. 7 microphone, earpieces fitted with soft chamois leather. Ideal for No. 19 Sets and similar equipment. **BRAND NEW.** Price **12/6**. P. & P. 2/6.

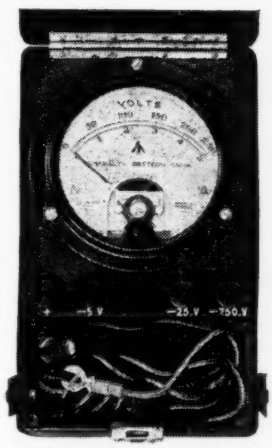

TRIPLE RANGE VOLTMETER, 0-5 25-250 V D.C. M/C 3½in. meter 3in. scale, mounted in bakelite carrying case 7½ x 4½ x 3in. complete with handle and test leads. **27/6** ea. P. & P. 2/-.

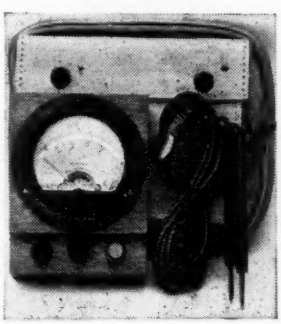

BRAND NEW BASIC 0-1 mA. MOVING COIL METERS. 3in. mirror scale 0-5 and 0-100 volt D.C., resistance 1,000 ohms per volt In wooden casing complete with test prods and beautiful leather case. **29/6** each. P & P. 2/-

U.S.A. 27-volt 4-Pole CHANGE-OVER RELAYS. Brand new and boxed. **5/6** each. P &. P. 6d.

VEEDER REVOLUTION COUNTER. 6 columns, fitted reduction drive, built inside small unit. New. **8/6** each. P. & P. 2/-.

ASK FOR EXPORT QUOTATIONS — WE ARE EXPERTS AT OVERSEAS PACKING & SHIPPING!

SERVICE TRADING Co.

PERSONAL CALLERS ONLY: **9 Little Newport Street, London, W.C.2.** *Tel: GER 0576*

ALL MAIL ORDERS: *(Early Closing Thursday)*
47-49 High Street, Kingston-on-Thames.
Telephone: KINgston 4585

CABINETS & ENCLOSURES

By STAMFORD.

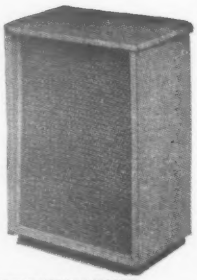

We are specialists in High-Fidelity enclosures built strictly to the specifications of the leading speaker manufacturers, and have pleasure in introducing an entirely new range of enclosures for the

COMPLETE WHARFEDALE RANGE
OPEN ALL DAY SATURDAY

Demonstrated at our New Showroom:
Weymouth Terrace, (Off Hackney Road), London, E.2
Telephone: SHO 5003.
HOURS 9.30—5.30. 7 p.m. WEDNESDAY
COMPREHENSIVE DEMONSTRATIONS OF OUR NEW WHARFEDALE ENCLOSURES

Using Super 12 FS/AL, W 12/PS, 10in. Golden, 10in. Bronze and an entirely New and Very Attractive CORNER ENCLOSURE FOR THE WHARFEDALE 3-way system and embodying their patent Acoustic Filter. (Used with the approval of Messrs. Wharfedale *Ltd.*)

EACH ENCLOSURE is Hand-made throughout in superior ¾in. material, acoustically lined and quilted interior.

These cabinets are supplied in Oak, Walnut and Mahogany veneers finished to shade required. Delivery 12/6 in England and Wales, Scotland and N. Ireland 25/-.

Write for Catalogue of Equipment and cabinets for EQUIPMENT, RECORDS, SPEAKERS, PYE BLACK BOX, AND GOODMANS AXIOM ENCLOSURES. Satisfaction guaranteed or money refunded.

ANY CURRENTLY AVAILABLE EQUIPMENT OR SPEAKER CAN BE SUPPLIED. FITTED FREE OF CHARGE.

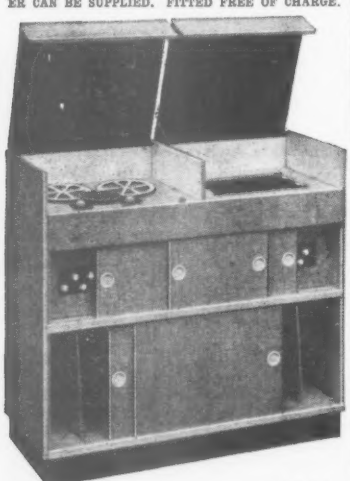

G.P.37/2

G.P.37/1. With taper legs in place of record storage. £22/11/6, or £3/4/- deposit and 9 payments of £2/6/5.
G.P. 37/2. 3ft. 2in. Wide, 3ft. 3in. High, 17¼in. Deep. £32, or £4/16/- deposit and 9 payments of £3/5/-.
Correspondence only:—

A. L. STAMFORD (Dept. C.4.)
20, College Parade, Salusbury Road, London, N.W.6

LONDON CENTRAL RADIO STORES

MIRROR GALVO'S. Instrument resistances, 190 ohm. External resistance 1,400 ohm. Sensitivity 2,200 M.M.S. NEW, in wooden transit box. Size 13×6×8in. £3/15/-.
ELLIOTT PEN RECORDERS. Decibel Meter 0-1mA. Suitable for measuring sound, atmospherics, etc. Price on request.
KING PIN INDOOR T.V. AERIALS. Band 3, Dipole 7/6. B.B.C. 13/6. Combined I.T.A./B.B.C. 16/-. Fully adjustable any angle. B.B.C./F.M. Radio 9/-. (All without co-axial cable).
DASHBOARD 8-DAY CLOCKS. Panel mounting, size 2¼in. By well-known makers. £2/17/6.
VENNER 8-DAY CLOCKWORK TIME SWITCHES. 230 volts, 1 amp., 3¼ × 2¼ × 2¼in., with key and connecting socket, 27/6.
HIGH-SPEED ELECTRO-MAGNETIC COUNTERS. Ex-Govt. 0-9,999, 25/50 v. D.C. Size 4 × 1 × 1in. Single coil, 2,300Ω. 18/6.
METAL RECTIFIERS. Ex-Govt., made by S.T.C., 250 v. 60 mA. Size 5¼in. × 1in. dia. Unused. 7/6.
ELECTRO MAGNETIC COUNTERS. Ex-G.P.O., every one perfect, 400 and 500 ohm coil, counting to 9,999, operated from 25 v.-50 v. D.C., 4¼in. long × 1¼ × 1in. many industrial and domestic applications. 5/6.
0-1 MOVING COIL MILLIAMMETER. Overall dia. 3¼in. dial, 2¼in. flush panel mounting. Guaranteed in perfect working order. 19/6.
DECIBEL METER. Moving coil, reading—30 to zero (0db=.775 v. (R.M.S.), overall dia. 4¼in., dial 3in. £2/15/-.
MOVING COIL HAND MIKE. Type No. 7. 7/6.
UNISELECTOR SWITCHES. Have many applications including automatic tuning, circuit selection, etc. Operation on 24-50 v. Half wipe 6-bank. 12/6.
EX-G.P.O. DESK PHONES with a dial 0-9, in black bakelite case with handset attached. £2/10/-.
RELAYS. Type 3,000. 1,000 ohm coil, 2,000 ohm coil, 500 ohm coil, and 50 ohm coil. 7/6 each.
MILLIAMMETERS. 2in. dial. Reading 30-0-30, flush mounting. Ex-Govt. Not checked for accuracy. 6/-.
L.R. HEADPHONES. Lightweight. 7/6.
TUFNOL SHEETS. ¼in. thick, 47¼in. × 47¼in. £2. 23in. × 16in. 7/6. 16in. × 16in. 5/- per sheet.

All prices include carriage.

23 LISLE ST. (GER. 2969) **LONDON, W.C.2**
Closed Thursday 1 p.m. Open all day Saturday

NEW G.E.C., S.T.C. AND "WESTALITE" SELENIUM RECTIFIERS. Largest L.T. range in Gt. Britain. ONLY Makers' LATEST GOODS supplied NOT Surplus.

S.T. & C. E.H.T. K3/15, 5/ ; K3/45, 9/4; K3/50, 9/10; K3/100, 16/8; all post 4d extra.

BRIDGE CONNECTED FULLWAVE 17 v. 1 a., 13/4; 1.5 a. 26/6; 3 a., 30/6; 4 a., 38/-; 5 a., 38/6; all post 6d. 33 v. 1 a., 22/9; 1.5 a., 45/-; 3 a. 54/-; 5 a., 68/-; all post 1/6. 54 v. 1 a., 33/-; 1.5 a. 62/-; 2 a. 74/-; 3 a. 74/-; 5 a. 97/-; 72 v. 1 a. 42/-; 1.5 a. 78/-; 2 a. 95/-; 3 a. 95/-; 5 a. 124/-; 100 v. 1 a. 61/-; 1.5 a. 112/-; 2 a. 134/-; 3 a. 134/-; 5 a. 180/-, all post 2/-.

BRIDGE CONNECTED WITH 7½in. SQUARE COOLING FINS 17 v. 6 a. 53/7; 10 a. 61/-; post 2/6.

BRIDGE CONNECTED HEAVY DUTY FUNNEL COOLED or 7½in. SQUARE COOLING FINS. Both types, same price. 17 v. 20 a. 120/-; 30 a. 172/-; 50 a. 280/-; 33 v. 6 a. 89/-; 10 a. 102/-; 20 a. 202/6; 54 v. 6 a. 124/-; 10 a. 144/-; 72 v. 6 a. 160/-; 10 a. 186/-; 100 v. 6 a. 227/6; 10 a. 270/-; all post 3/-.

"WESTALITE" (BRIDGE) 12-15 v. D.C. 0.6 a. 12/-; 1.2 a. 30/-; 2 a. 32/6; 5 a. 37/6; 1.0 a. 64/6; 20 a. 117/6; 30 a. 171/-; 50 a. 278/-; 24 v. 1.2 a. 30/-; 5 a. 60/-; 10 a. 109/6; 20 a. 208/-; 36 v. 1.2 a. 47/6; 5 a. 82/6; 10 a. 154/6; 100 v. 1.2 a. 82/6; 2.5 a. 154/6; 5 a. 195/6; 10 a. 391/-; All post extra 1/6-3/6. E.H.T. Rects. 14D.134, 25/-; 36 E.H.T. 60 35/10, post 4d. 1 ma. AC/DC meter, rects. 14/6.

"G.E.C." (BRIDGE). 6 and 12 v. D.C. 1 a. 7/6; 1.5-2 a. 8/6; 2.5 a. 11/9; 3 a. 14/9; 4-5 a. 16/6; 6 a. 23/6; 10 a. 34/-; 14 a., 42/-; 24 v. 1 a. 12/6; 1.5 a. 14/3; 2 a. 15/6; 3 a. 26/-; 4 a. 29/6; 6 a. 36/6; 10 a. 75/-; other sizes. Post, under £1 add 1/- over £1 add 1/6.

Wholesale and Retail.

T. W. PEARCE
66 Great Percy Street, London, W.C.1
Off Pentonville Road. Between King's Cross and Angel

The FAMOUS R/T No. 22

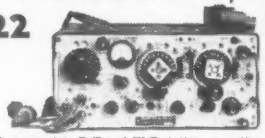

W/S No. 22 is a complete R/T and W/T station, operating from 2-8 Mc/s. (37.5-150 metres). Set may be used on C.W., M.C.W., and R/T, with Break-in working possible on C.W., and M.C.W., complete with 500 Micro-amp. meter and 13 valves: 2 of AR8, 1 ARDD5, 5 of ARP 12, 1 of Arp 34, 1 of CV65, 3 of VT52. In excellent condition £5/19/6. Carr. 15/-.
12 v. vibrator type Power Supply Unit for above set, 22/6. Carr. 5/6. For price list of additional 22 set accessories send stamped addressed envelope.

WALKIE-TALKIE No. 38 MK. II

RIGHT IN PRICE AND SIZE—9×6×3½in.

Ideal for search parties, fire brigades, civil defence, building contractors, etc. Range approximately 5 miles, 7.4-9 Mc/s. Brand new condition. Complete with 5 valves, headphones, throat mic., junction box, aerials, harness signal satchel, spare set of valves and instruction card with illustrations. Operated from dry batteries H.T. 120/150 v., and L.T. 3 v. (not supplied). In brand new condition, our price £2/17/6 each, p. & p. 7/6.

RECEIVER-TRANSMITTER No. 18 Mk III
6-9 Mc/s., Rec. can be detached from Trans. Unit, built-in micro-amp-meter, complete with headphone and mic., aerial etc. In excellent condition. Our price 75/-, p. & p. 7/6.

MIDGET ROTARY TRANSFORMER

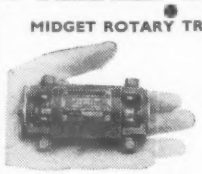

SIZE
Inp. 11.5 v. Output 365/310 v. at 30 mA. Brand new and Trop. packed, 17/6 ea. p. & p. 1/6.

EX G.P.O. ELECTRO MAGNETIC COUNTERS, 5 × 1½ × 1½in. 4 figures, various voltages D.C. 3/6 v. 18/24 v. 100/110 v. 200/230 v., 7/6 each, p. & p. 1/6.
INTERCOMMUNICATION HAND SETS, self-energised, similar to G.P.O. type, no electricity or batteries required, connect with 2-way bell wire, clear range of several hundred yards. Brand new, 32/6 per pair p. & p. 2/-.
HIGH SPEED RELAY. 2 bobbins, 1,000 ohms each 5/6, p. & p. 1/-.
U.S. HIGH SPEED RELAY, 300 ohms coil 2.05 v. adjustable contacts, 5/-, p. & p. 1/3.
HEADPHONES M/C, complete, 9/6 per set, p. & p. 1/6.
EX U.S. AERIAL, 9ft. spring loaded and fully collapsible, complete with cords and guys, ideal as aerial or fishing rod, brand new, 10/6, p. & p. 2/-.
AERIALS. 3 four foot "F" rods, bottom, centre and top (tapering) push-in-type sections, 10/6 per set, p. & p. 2/3. Matching aerial base 3/6, p. & p. 1/6.

BROADCASTER

for talking, singing or announcing over your own radio, simply connect to your Radio pick-up . . . 2 Broadcasters will make a 2 station intercom. house phone. No electricity or battery required, just connect with 2-way wire. 12/6 ea., p. & p. 2/-.
M/C METER. 0-15 and 0-600 v. D.C. 2in. flush mounting ex equipment, 8/6, p. & p. 1/3.
METER. 2½in., 0-1 amp., projecting type thermo-couple, new and boxed, 6/6, P. & P. 1/3.
U.S. MIDGET MOTORS. 2×1½in. Will operate from 6 v. to 24 v. D.C. 12/6 each, p. & p. 1/6.
DITTO. Will operate from 9 v. to 28 v. D.C., 12/6 each, p. & p. 1/6.

Special prices for bulk quantities. *Stockists of W/S No. 19 and spares.*
TERMS C.W.O.
We specialise in Telephone and Z.A. Equipment and spares as used by Govt. Depts. and the Services. Trade and manufacturers' enquiries invited.
Postage and Carriage quoted, British Isles only.

FINSBURY TRADING CO.
12 STOKE NEWINGTON HIGH ST., LONDON, N.16. *Tel.: CLissold 7342*

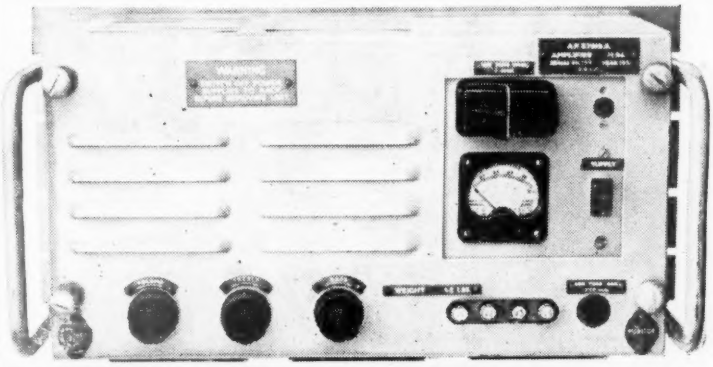

PUBLIC ADDRESS AMPLIFIERS

Two KT.66 giving 25 watts Push-Pull Output 110V-230V A.C. Mains. Ideal Factories, Fairgrounds, Sports Clubs etc. Built to most stringent Admiralty specification. Volume, Base and Treble Controls. Built in meter with switch for checking valves in operation. Paper block smoothing. Requires only 150 m-v high impedance input from gram or mike for full output. Tapped for 3.5-7-15 ohm Speakers and 600 ohm line.

BRAND NEW in original cases. **£12/17/6**. Carr. 12/6. Overall size approx. 17" × 17" × 8" Wt. 68lbs.

METERS BRAND NEW GUARANTEED PERFECT

Charging types.

2½ amp. D.C. M.I. 2in. fl. rnd.	7/6
5 amp. D.C. M.I. 2½in. fl. rnd.	11/6
7½ amp. D.C. M.I. 3½in. proj. rnd	12/6
9 amp. D.C. Hot Wire WR. 2½in. fl. rnd.	6/6

Voltmeters.

6 V. D.C. M.C. 2½in. proj. rnd.	8/6
12 V. D.C. M.C. 2½in. proj. rnd.	8/6
25 Volt D.C. M.C. 2in. fl. rnd.	7/6
30 Volt M.I. 3in. proj. rnd.	10/6
40 Volt M.C. 2in. fl. sq.	9/6
250 Volt A.C. rectified moving coil linear scale 3½in. fl. rnd.	35/-
300 Volt A.C. M.I. 2½in. fl. rnd.	22/-
400 Volt A.C. M.I. 4½in. fl. rnd.	35/-

Milliammeters

50 mA M.C. 2in. fl. sq.	7/6
30 mA M.C. 2½in. fl. rnd.	9/6
100 mA M.C. 2½in. fl. rnd.	9/6
500 mA M.C. 2½in. fl. rnd.	9/6
1 mA. M.C. 2½in. fl. rnd.	22/6
500 Microamp latest type Ernest Turner 2in. fl. rnd. with mounting ring and scaled 0-5	19/6
500 Microamp ex. equip. M.C. 2in. rnd. scaled 0-15 and 0-600 V.	14/6

Thermo-coupled

350 mA 2in. rnd. plug-in	2/6
500 mA 2in. rnd. plug-in	2/6
POSTAGE ON ALL METERS	1/-

U.S.A. PRECISION SERIES 834.S MULTIRANGE TESTERS for A.C. and D.C. volts, ohms and milliamps, basic movement 400 microamp., in wooden carrying case, complete with test prods, new batteries, guaranteed perfect. Price **£6/19/6**. P. & P. 2/6

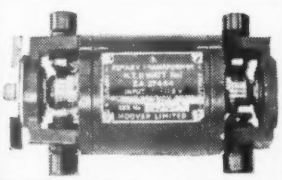

MIDGET ROTARY TRANSFORMERS 2½in. dia. x 4½in. Input 11.5 volt. Output 310/365 volt at 30 mA. Brand new. 17/6 each. P. & P. 1/6.

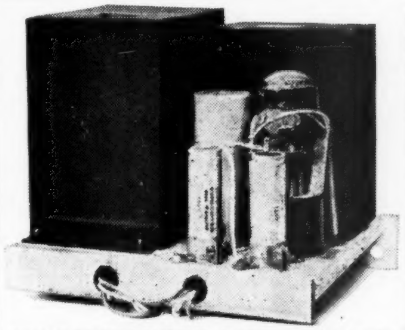

MAINS POWER SUPPLY UNITS, potted and sealed transformer and choke by famous maker. Mounted on metal chassis 6½ x 7½in. complete with 5Z4 rectifier valve and full smoothing. Input tapped 220-230-240 Volts. Output: 300 V D.C. at 100 mA.
6.3 V. A.C. at 4.5 amp.
6.3 V. A.C. at 2 amp.
Rectifier supply 5 V A.C. at 3 amp. Very conservatively rated. Price **42/6** plus P. & P. 3/6.

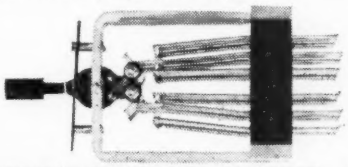

MUIRHEAD PRECISION KEY SWITCHES. Low capacitance, 6 single pole c/o each side. Brand new Chrome-plated bezel. Price **12/6** each. P. & P. 1/-.
MUIRHEAD VERNIER DRIVE. Scaled 0-180 degrees, ratio 31/1, dia. 3in., as fitted to R.F.26 units. Complete with lampholder. In manufacturers' original packing. New, **8/6** each. P. & P. 1/6.
AUTO TRANSFORMERS, step up, step down, 110-200-220-240 v. Fully shrouded. New. 300 watt type **£2/2/-** each. P. & P. 4/6. 500 watt type **£3/3/-** each. P. & P. 4/6, 1,000 watt type **£4/4/-** each. P. & P. 4/6. Also 60 mA., **19/6** each. Plus P. & P. 2/-.
Photo Multiplier. Type 931A, for Alfa counting, film scanning, spectography, etc., new. **£2/5/-** each. P. & P. 1/-.
AIRCRAFT CINE CAMERA G45B Mk. III, fully modified, fitted with f/3.5 triple anastigmatic lens, takes 25ft. of 16 mm. film, fitted with 24 v. motor. 16 exposures per sec. Mint condition, brand new, in maker's original packing. **£6/10/-** each. P. & P. paid.
MOVING COIL HEADSETS FINEST CANADIAN MAKE complete with moving coil No. 7 microphone, earpieces fitted with soft chamois leather. Ideal for No. 19 Sets and similar equipment. **BRAND NEW.** Price **12/6**. P. & P. 2/6.

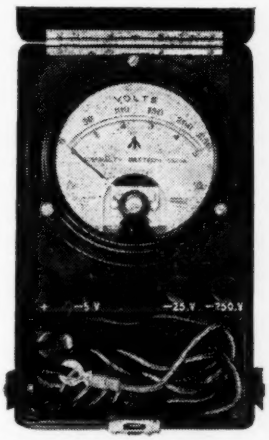

TRIPLE RANGE VOLTMETER, 0-5 25-250 V D.C. M/C 3½in. meter 3in. scale, mounted in bakelite carrying case 7½ x 4½ x 3in. complete with handle and test leads. **27/6** ea. P. & P. 2/-.

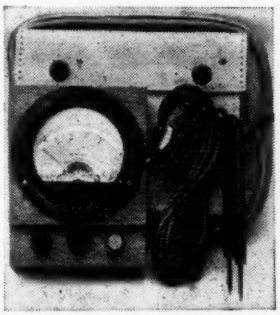

BRAND NEW BASIC 0-1 mA. MOVING COIL METERS. 3in. mirror scale 0-5 and 0-100 volt D.C., resistance 1,000 ohms per volt In wooden casing complete with test prods and beautiful leather case. **29/6** each. P & P. 2/-

U.S.A. 27-volt 4-Pole CHANGE-OVER RELAYS. Brand new and boxed. **5/6** each. P &. P. 6d.

VEEDER REVOLUTION COUNTER. 6 columns, fitted reduction drive, built inside small unit. New. **8/6** each. P. & P. 2/-.

ASK FOR EXPORT QUOTATIONS **WE ARE EXPERTS AT OVERSEAS PACKING & SHIPPING!**

SERVICE TRADING Co.

PERSONAL CALLERS ONLY: **9 Little Newport Street, London, W.C.2.** *Tel: GER 0576*
ALL MAIL ORDERS: *(Early Closing Thursday)*
47-49 High Street, Kingston-on-Thames.
Telephone: KINgston 4585

A TAPE PRE-AMP OF REMARKABLE QUALITY

Designed to produce the best from all good tape decks

THE TELE-RADIO (1943) LTD

MASTER-LINK M2A

★ ADJUSTABLE TO C.C.I.R. CHARACTERISTIC

★ ± 2DB FROM 30 C/S TO 8 KC/S AT 3¾ I.P.S.; 14 KC/S AT 7½ I.P.S.; 15 KC/S AT 15 I.P.S.

★ COMPLETE WITH SEPARATE POWER PACK & INSTRUCTIONS.

27 GNS. (P.P. 4/-)

An exclusive product of Tele-Radio (1943) Ltd., embodying the most advanced principles of tape recording techniques. Recordings may be taken direct from microphone, pick-up or radio, and it may be used with tape decks incorporating head switching. Includes playback speed equalisation, metering of signal and bias voltages, signal monitor output, oscillator cut-out, D.C. Solenoid supply and C.C.I.R. characteristic.

Full descriptive leaflet on request—

TELE-RADIO (1943) LTD., 189, EDGWARE RD., LONDON, W.2

Our only address • Few mins. from Marble Arch • Open all day Sat. • *Phone: PAD 4455/6*

OPPORTUNITIES IN RADIO

Get this FREE Book!

'ENGINEERING OPPORTUNITIES' reveals how you can become technically qualified at home for a highly paid key-appointment in the vast Radio and Television Industry. In 148 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study course in all branches of **TELEVISION and RADIO, A.M. Brit. I. R. E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency and General Wireless Courses.**

We definitely Guarantee

"NO PASS—NO FEE"

If you're earning less than £18 a week this enlightening book is for you. Write for your copy today. It will be sent **FREE** and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

388b COLLEGE HOUSE, 29-31 WRIGHT'S LANE, LONDON, W.8.

BIET

Fidelia

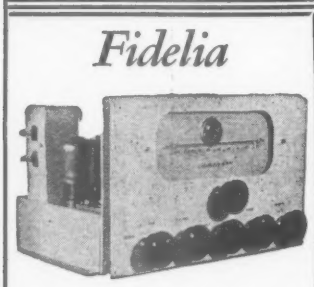

Demonstrations of Fidelia High Fidelity equipment can be arranged at any time including weekends by appointment. Occasionally we have ex demonstration or part exchanged models for sale at attractive prices.

Fidelia Imperial. V.H.F. reception, plus gramophone pre-amplifier for all types of pick-ups, full tone control circuit, tape jacks, etc. Price with our Major amplifier **£38.** As VHF tuner and Pre-amplifier/tone control unit **£20.**

Fidelia Major. Short, Medium and Long Wavebands, plus VHF/FM. Gram pre-amp. and full tone control. R.F. Stage on all bands, variable selectivity, etc. Price **£28/10/-**, or with our Major 10-watt amplifier **£44.**

Fidelia De Luxe. 11-valve chassis. VHF/FM plus Medium and Long wavebands, full tone control, 7-watt push-pull triode output stage **£34/10/-.**

Fidelia Junior. Our new 8-valve chassis, having many of the exclusive Fidelia features for **£25.**

Full details willingly on request. (6d. for postage is appreciated).

ELECTRO Acoustic DEVELOPMENTS

2 AMHURST ROAD, TELSCOMBE CLIFFS, Nr. Brighton. SUSSEX Tel. Peacehaven 3156

BARGAIN OFFERS

400 CYCLE ALTERNATORS. 1.5 kVA, 230 volts, 1 ph., 1500 r.p.m., by S.E.M., with 110 volt D.C. exciter and half coupling. 50 cycle 3-phase Alternator, 3 kVA, 230 volts, revolving field type by G.E.C. with half coupling. Few only, write for special leaflet.

200 WATT RADIO MARINE CRYSTAL CONTROL TRANSMITTER type E.T.8023, metered and complete with 5 crystals, valves fitted except two 813, no power supply. **£40.** Ex Battersea Stores.

TEMPERATURE CONTROL OVENS. Admiralty type, 230 volts A.C., give stability of 2 parts in a million with suitable crystals. Fitted thermostat and thermometer. Temp. adjustable 40/60 degrees Cent. Ideal for Quartz Crystals, Lab. tested. As new, **£9/10/-**, carr. 5/-.

YAGI AERIALS, tuning range adjustable to cover 120/150 Mc/s., 12 db gain over dipole, 2-stack array on revolving base, built-in Selsyn drive, 75 coax. input.

MOTOR PUMPS, 12 volt D.C. Stuart Turner type 10, capacity 100 g.p.h. New. **£4/10/-**, carr. 5/-. Ideal for caravans, etc.

A.C. MOTORS. ¼ H.P. 230 volts, 50 cycles S.P. by Crompton. 1400 r.p.m. 90/-, carr. 7/6.

RELAYS. G.P.O. type 3000 coil resistance, 1000 ohms with 3 sets contacts, 1 make, 1 break, 1 heavy contact make 8/6, post 1/-. Type 600 coil resistance, 1000 ohms 2-C.O. Contacts 8/6, post 1/-.

"S" METERS. 2in. square flush panel. New stock, suitable for A.R.88 or other receivers, 39/6, post 1/6.

METERS. A.C. Moving Iron 8/bd. mounting, 50 amps. 25/-; 150 amps. 55/-; 300 amps. 65/-; 400 amps. 75/-.

OVERLOAD INDICATOR VOLTMETERS. By Everett Edgcumbe, 20-30 volts or 45-55 volts D.C., 8in. 8/bd. **£4/10/-**, carr. 5/-.

Leslie Dixon & Co.

Dept. A, 214 Queenstown Road, London, S.W.8

Telephone : MACaulay 2159

SPECIAL OFFER

OF NEW EX W.D. EQUIPMENT

2,000 METERS, 0-100 M/A, 2½" Round Panel Mtg. (New/Boxed), 4/6 each. (Minimum Quantity 200.)

500 METERS, 0/30 M/A, as above.

400 RELAYS, STC Polarised, 1,500 + 1,500 Ohms (New/Boxed), 4/- each. (Minimum Quantity 100.)

5,000 AMERICAN VALVES, 1616 (New/Boxed), 1/- each. (Minimum Quantity 250.)

1,000 AMERICAN VALVES, 1625 (New/Boxed), 1/- each. (Minimum Quantity 250.)

4,000 TERMINAL BLOCKS, 2-Way, A.M. 5c/430, 70/- per Thousand.

200 Westinghouse Type 2 CONTACTORS (New/Boxed), 4/- each. To Clear.

1,000 PAINTON ATTENUATORS, 500 Ohm, 1" Spindle, 3/- each. To Clear. Brand New.

400 PAINTON ATTENUATORS, 3,000 Ohm, as above, 4/- each. To Clear. Brand New.

5,000 CONDENSERS (Block), B.I., 4 MFD., 400 v., Tropical, 9d. each. Brand New. (Minimum Quantity 500.)

1,000 SANTON SWITCHES, Heavy Duty, Various Types, 1/- each. To Clear.

600 H.D.W.W. POTENTIOMETERS, 3½" dia., 17,000 Ohms, 2/6 each. (Minimum Quantity 100.)

1,000 AIRCRAFT CAMERA MOTORS, Double Spindle, Ref. 5U/2705, 2/6 each. (Minimum Quantity 100.)

500 CAMERA CONTROL MOTORS, 24 v., Type B, Ref. 14A/988, 6/- each. (Minimum Quantity 50.)

250 B.T.H. STARTER MOTORS, 24 v., Type No. 5U/452, 17/6 each. Brand New. (Minimum Quantity 50.) Ref. 5U/452.

350 ROTARY TRANSFORMERS, Type 31 (Brand New), 5/- each. (Minimum Quantity 50.)

500 PUSH-BUTTON SWITCHES, 7-Way (Brand New), 1/- each. (Minimum Quantity 250.)

Large Stocks of A.M. COMPASSES, SANTON SWITCHES, RESISTORS, CONDENSERS, POTENTIOMETERS, etc., etc. To Be Cleared.

500 CONDENSERS (Paper), B.I., 4 MFD., 800 v. WKG. (Tropical) (Brand New), 1/6 each. (Minimum Quantity 100.)

All Goods Ex Warehouse Subject to being Unsold.

Enquiries to **MR. J. LECKIE**

169-171 EDGWARE ROAD, LONDON, W.2.

Telephone: PAD 7851 & AMB 5125

PROOPS BROTHERS LIMITED Walk-Around Shop

52 TOTTENHAM COURT ROAD, W.1. Phone: LANgham 0141. Hours 9—6, Thurs. 9—1. OPEN ALL DAY SATURDAY

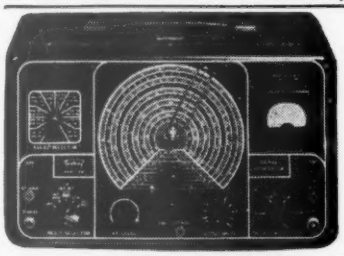

TRIPLETT 1632 SIGNAL GENERATOR AND CRYSTAL CALIBRATED FREQUENCY METER

100 kcs to 120 Mc/s IN 10 FUNDAMENTAL BANDS

Six valves, buffer amplifier, 100μA output meter. Variable carrier level, 5-step attenuator, dummy aerial. Audio output, external mod., 1,000 kc. Xtal marker, voltage regulated. Details by return for S.A.E. Demonstrated daily. See also July issue.

£13.10 Carriage paid.

ROOM THERMOSTATS
By a famous manufacturer. Voltage 0-250., maximum current 15 A. Temperature control range 50°F. to 80°F. Contemporary design in cream hammer finish, complete with wall fixing plate and full installation instructions. Brand new. 15/-, Carr. 2/-.

TRANSFORMERS, 230-250 volts, 50 c/s.
Heater 6.3 v., 1.5 A., 6/6, plus 1/- carr.
Miniature mains: 230 v. at 40 mA. and 6.3 v. at 1.5 A., 12/6, plus 1/- carr.
Charging: 9 v. and 17 v. at 3 A., 15/6, post free.
Mains isolating: 250 v./220 v. or 250 v./110-0-110 v. out OR double wound auto 250 v. in, 110 v. out, 5/-, carr. 1/6.

MINIATURE OUTPUT TRANSFORMERS
Plessey. Ratio 45 : 1 and 55 : 1, 4/6, post free. State ratio required.

FULL-WAVE CHARGING RECTIFIERS
24 volts 1.5 A., 12/6, post free.

HEADPHONES
High resistance balanced armature £1, post free.
Low resistance balanced armature, 8/6, post free.

MICROPHONES
Acos crystal inserts, 4/6, post free. American throat mic. switch socket, 3/-, post free.
Aircrew type electro magnetic microphones with switch, 2/-, post free.
Carbon type in black crackle case, 12/6, post free.

MINIATURE I.F. STRIP, 9.72 Mc/s.
Brand new with circuit, less valves, 12/-, post free.

MULTI-RANGE TEST METER
Ranges 0-1.5 v., 0.3 v.; 0-60 mA.; 0-500 and 0-5,000 ohms. 2½×3¾×3¼in. Brand new 8/6. Carr. 1/6.

GYRO UNIT AND INVERTER
Can be used as 12 v. D.C. motor. Inverter: 12 v. D.C. input, 3-phase 190 cycle output. Size 4×4×3in. 12/6 pair. Carr. 3/-.

DYNAMOTOR (U.S.A.)
28 v. D.C. input, 330 v. 170 mA. output. Fully smoothed by screened choke/condenser filter unit in base. Size 3¾×6in. Black crackle finish. Brand new in box 17/6, post free.

RADIO ALTIMETER
5 mA. panel mounting with 3in. dia. circular scale. Brand new in box, 7/6, post free.

BOLT CROPPERS
9in. long, 2/6, post free. Folding type 18in. long, 7/6, post free.

POCKET MARCHING COMPASS
In black plastic case with sighting reflector inside lid, luminous. Brand new, 12/6, carr. 1/-.

PRISMATIC TANK PERISCOPES
American type, 7/6, post free.

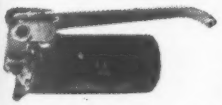

LOW VOLTAGE PRECISION RELAY 7/6

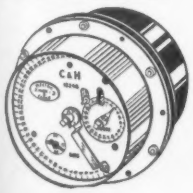

12 V. SOLENOID (½in. travel. 3½in. arm). 350 mA. 3 for 10/-.

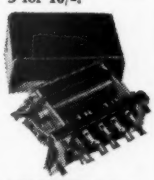

TIME SWITCH
4½-6 v. precision clock. Current negligible. Can be set to operate at any period between 15 minutes and 44 days. **12/6**

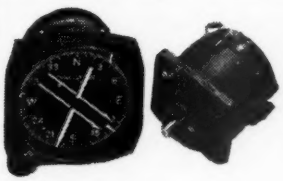

ANTENNA INDICATOR
Remote indication to within 1° on precision instrument type flush fitting black crackle indicator with 3in. dial calibrated in 2° steps plus the four cardinals. Simple D.C. wiring (6-30 volts) from specially wound potentiometer in sealed die-cast housing with ¼in. drilled spindle transmits accurate signal of horizontal or vertical bearing.
BRAND NEW POST FREE WITH INSTRUCTIONS **30/-**

POWER UNIT TYPE 234
For use with receiver 1392 on 250 volt 50 c/s. mains.
Double smoothed output 240 volts at 100 mA., 6.3 volts at 6 A.
Input and output fused, switched meter reads both in and out voltages.
Standard rack mounting, size 19×10×6¼in.
Carriage 10/-. **£4.10.0**

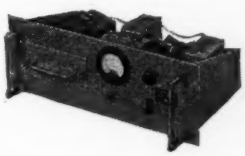

Tx POWER PACK AND MODULATOR BARGAIN
Superb, heavy-duty, power unit and modulator of "36 Sender." Fully-screened chassis housed in handsome oak cabinet with slide-out front; size 24½×16×15in. Weight 120 lb. Complete with built-in speech amplifier, push-pull 807 modulator (less trans) and separate power supplies for V.F.O., Bias and P.A. Valves: 3×FW4500, 3×6C5G, and 2×807. Input: 100/110 v. and 200/250 v. 50 c/s at 350 watts. Outputs: 200-0-200 v., 50 mA., 2×500-0-500 v., 200 mA., 6.5 v. 8 A. (c.t.) and 3×4 v., 4 A. Circuit diagram supplied.
£6.0.0 Carriage 15/-.

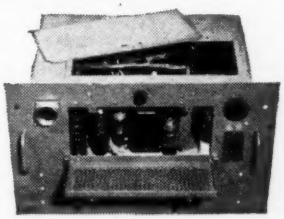

RECEIVER UNIT 1143A
Suitable for conversion to 2 metres or Wrotham. Valves 4×EF.50, 1×EL.32, 2×EF.39, 1×EBC.33, 1×EA.50. Complete Carriage 3/6. **25/-**

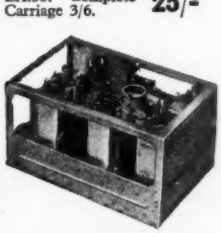

R.1392
95-150 Mc/s (2-3 Metres). 15 Valve Superhet. 1st and 2nd RF. EF54, 1st Local Oscillator SP61, 2 Oscillator Multipliers EF54, 3 IF's EF.39, AGC. 6Q7, Output 6J5. Muting EA.50, Noise Limiter EA.50, BFO.6J7, Mixer EF.54, Detector 6Q7. Normally Crystal Controlled, but can be tuned over 95 to 150 Mc/s. Power supply required = 240-250 volts at 80 mA. 6.3 volts at 4A. Standard Rack Mounting, 19×10in. Complete with valves and circuit diagram. Air tested. £6/19/6. Carriage 10/-.

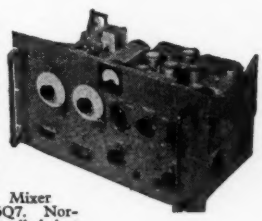

Low-voltage Halogen GEIGER-MUELLER TUBES 55/-
Straight from production, individually tested, fully guaranteed.

SERVO AND ELECTRONIC SALES LTD.

GEARED MAINS MOTORS. Drayton Type RQ 230 v. 50 c.p.s., 37 r.p.m. Torque 2 lb. in. **85/-** (P.P. 4/-). **VARIABLE SPEED MOTORS,** 1/6 h.p., 115 v. 50/60 c.p.s. with Graham variable speed gearbox. Output 0-166 r.p.m. **250/-** (carr. 15/-). **MOTOR ALTERNATOR SETS.** Newton Bros. Output 200 v. 1,100 c.p.s. 8 kVA, input 415 v. 50 c.p.s. 3 ph., driving motor 6 h.p. **£72/10/-** (c.p.). Another, output 80 v. 2,000 c.p.s., 620 W., input 80 v. D.C. **170/-** (carr. 20/-). Another, outputs 280 v. 400 c.p.s. 1680 W. and 200 v., 400 c.p.s., 1,200 W., input 230 v. 50 c.p.s., 1 ph., **980/-** (c.p.). Another, output 115 v. 400 c.p.s. 45 W., input 26 v. D.C., **120/-** (carr. 7/-). **RECTIFIER SMOOTHING UNITS.** Cat. L.176, gives two doubly choke/capacity smoothed outputs of 12 v. 3 A. or one of 24 v. 3A. With single stage smoothing 24 v. 6A. Standard 19in. rack mounting, **37/6** (carr. 7/6). **INTEGRATING HOUR METERS** for 200/260 v., 50 c.p.s. operation reading up to 10,000 hours accuracy 1 minute, 4½in. dia.. **39/6** (p.p. 3/6). **POWER UNITS TYPE 3,** input 200/250 v. 50 c.p.s., outputs 220 v. 100 mA. D.C. and 6.3 v. 4 A. A.C. with H.T. voltmeter and ammeter, **70/-** (carr. 10/-). **INDICATOR UNIT AFW9922A,** 1-VCR97, 2-VR91, 2-VR54, 1-CV1295, 1-VT61. Perspex shield, focus and brilliance controls, 8 pots, ideal for oscilloscope conversion or built-in C.R.T. display unit, new, **37/6** (carr. 5/-). **ADMIRALTY RESPONSER UNITS** complete with all valves and H.S. Relay, **25/-** (carr. 7/6). **NITROGOL CAPACITORS,** all 400 v. wkg. at 71°C. 1μF **2/3** (p.p. 9d.), 2 μF **2/9** (p.p. 1/-), 4 μF **3/6** (p.p. 1/3), 8 μF **4/9** (p.p. 1/9).

THIS MONTH'S SPECIAL OFFER!

HIGH STABILITY RESISTORS by Welwyn, Painton and Dubilier, all 5% tolerance, 50 different values or ratings in each 100 at **25/-** (p.p. 2/6). Quantities of 500 or over at the thousand rate of **£11/5/-** per 1,000. All are standard or sub-standard values. Enquiries invited for not less than 500 of any one value and rating. **TELCON TYPE 53C HIGH VOLTAGE SOCKETS,** polythene insulated, silver plated, in cartons, **10/-** per dozen, **100/-** per gross, **£30** per 1,000. **POTENTIOMETERS,** 500 ohm 5 watt, 2in. dia. × 1in. behind panel, complete with knob, **2/-** each. **17/-** per dozen, **£9** per gross. **£50** per 1,000. 50 ohm 6 watt, **2/9** each. Carr. on pots, sckts. and restrs. **7d.** ea., **3/6** per dozen, **12/6** per gross, paid per 1,000. **MINIATURE THYRATRON SET,** comprising 3-3D21 thyratrons and 1-VLS431 relay switch. **22/6** per set of four valves (P.P. 2/-). **MAGSLIP SUPPLY TRANSFORMERS,** input 10-0-220-240 v. 50 c.p.s., output 50 v. 30 vA., shrouded, **27/6** (p.p. 3/6). **MINIATURE RELAYS TYPE 4184GD.** 24 v. D.C. operation, d.p.c.o. contacts, **22/6** (p.p. 2/-).

General List on application (s.a.e. please).

1, HOPTON PARADE, STREATHAM HIGH ROAD, LONDON, S.W.16. STREATHAM 6165

Terms: c.w.o. Nett monthly approved A/Cs.

ELECTRICAL MEASURING INSTRUMENTS REPAIRED

1. *Considerable reductions in your overheads!*
2. *Prompt Quotations and Service!*
3. *Urgent orders given priority attention!*
4. *Guarantee of satisfaction!*

We specialise in the repair of all types and makes of Voltmeters, Ammeters, Microammeters Multirange Test Meters, Electrical Thermometers, etc.

As contractors to the Ministry of Supply, General Post Office and other Government Departments, we are the leading Electrical Instrument Repairers in the Industry. No enquiry is too big or too small. For prompt estimate and speedy delivery send defective instrument by registered post, or write to Dept WW

L. GLASER & CO., LTD.,

96-100, Aldersgate St., London E.C.1. Tel. MON 6822

The Northern Polytechnic

Holloway Road, London, N.7.

Principal: A. S. M. Symons, Ph.D., B.Sc., A.R.C.S., D.I.C., F.Inst.P.

Department of Telecommunications

Head of Department: J. C. G. Gilbert, M.Brit.I.R.E., Assoc.I.E.E., F.T.S.

Full-time, Part-time, Day and Evening Courses in Telecommunications Engineering in preparation for the Full Technological Certificate of the City and Guilds of London Institute, and Graduateship of the British Institution of Radio Engineers.

Evening classes in Industrial Electronics, Computors, Radar Principles and Practice, Electro-acoustics and Audio Frequency Engineering.

Full-time one-year course in Radio Servicing and full-time one-year course in Television Servicing, also part-time day release and evening classes are held in these subjects in preparation for the City and Guilds of London Institute and the Radio Trades Examination Board's Certificates.

Special evening course in the principles and practice of colour television with practical demonstrations.

All the above courses include practical laboratory and workshop experience.

London fees: £30 per year, or £11 per term, plus £2 registration fee, for full-time courses. (No fee for students under 18 years of age.) Evening class fees range from 40/- to 55/-. Enrolment for day classes by appointment. Enrolment for evening classes, 5.30-7.30 p.m. 16th and 17th September, 1958.

New term commences 22nd September, 1958.

PROSPECTUS FREE on application to the Secretary.

THE "ZEPHYR" (W) 200/250 volts. SHADED POLE MOTOR

Precision built. 2,600 R.P.M. 25 watts. 2¼in. wide (over fixing lugs). 2¼in. long. Shaft extension ½in. Die-cast rotor. Sturdy and SILENT. Ground and polished spindle (5/32in. diam.).

Suitable for Fans, Extractors, Fan Heaters, Projector cooling, cupboard airing and all purposes where reliability, silence and freedom from radio and T.V. interference is essential.

Price **37/6** post free (motor only)

ACCESSORIES

Bakelite fan. 8in. diam. **7/6. Metal fan.** 4in. diam. 5/-

THE BESTFREND ELECTRICAL CO., LTD.

BANSTEAD, SURREY.

F.H.P. motor manufacturers for 30 years.

Quantity enquiries invited.

PRECISION SHEET METALWORK

We specialise in manufacturing of Chassis in all metals, large or small quantities to your own specifications

V. W. BEAMISH

Shardloes Garage, Shardloes Rd., New Cross London, S.E.14

Telephone : TIDeway 4795

FM and HI-FI COMPONENTS

in stock for the

WIRELESS WORLD FM TUNER UNIT

DENCO EM TUNER	circuits	1s. 6d.
RADIO CONSTRUCTOR FM	,,	2s. 0d.
MULLARD AMPLIFIERS	,,	3s. 6d.
G.E.C. 912 PLUS AMPLIFIERS	,,	4s. 0d.
G.E.C. FM PLUS TUNER	,,	2s. 6d.

Separate price lists on request to

J. T. FILMER 82, DARTFORD ROAD, DARTFORD, KENT.

Tel: Dartford 4057

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE

3,000 STANDARD STOCK SIZES

No Quantity too Small. List on Application.

H. ROLLET & Co. Ltd.

6 Chesham Place, S.W.1. *SLOane* **3463**

ALSO AT LIVERPOOL, BIRMINGHAM, MANCHESTER, LEEDS.

Portable Record Player

CABINETS

With uncut motor boards and high-grade rexine finish.

Single Player Size, suitable most non-auto motor units, including transcription motors. Internal dimensions: 13½ × 16in. Height above motor board 3½in. Below 2½in. Colours: red or blue. **46/6** plus 5/6 carriage.

Single Player Size, with space for amplifier and speaker, suitable most non-auto motor units. Internal dimensions: 13 × 14½in. Height above motor board 3½in. Below 3in. Blue only. **55/-** plus 5/6 carriage.

Auto-change Type, with space for amplifier and speaker to house Monarch, Collaro 54, 456, Challenger or Conquest, Stear Galaxy or Garrard 120 Changers. Fitted catches and handles. Internal dimensions: 15½ × 14 × 7½in. Motor board 14 × 12½in. Height above motor board 5in. Below 2½in. **83/5/-** plus 5/6 carriage.

Printed Circuit Amplifiers using EL84 and 6X4 valves, complete with volume and tone controls, mounted on baffle board complete with 7 × 4in. speaker, and attractive grille cloth. Complete with all leads and requiring only four screws for installation in our £3/5/- cabinet. Price **24/19/6** plus 5/6 carriage.

Larger Type Auto-change Cabinet, suitable for Pleasey and early Collaro, etc. Will take 10 × 6in. speaker. Internal dimensions: 17 × 13 × 7½in. Motor board 15 × 12½in. Height above motor board 5½in. Below 2½in. Choice of red or blue. **£3/19/6** plus 5/6 carriage.

Send stamp for complete bargain list.

RONALD WILSON & CO.

DEPT. W.W.), 12 BRIDGE STEET WORCESTER

METERS

WE CAN SUPPLY WITHIN 7-14 DAYS

a complete range of moving coil—moving iron—electrostatic—thermocouple—also multirange meters—meggers—pyrometers and laboratory test instruments, etc.

All to B.S.89.

Instruments tested and standardised on your premises, and replacements supplied from our stock.

REPAIRS

Delivery 7-14 days

Our skilled craftsmen carry out repairs or convert any types and makes of single and multirange meters.

Where desired repairs are accepted on contract.

THE V.Z. ELECTRICAL SERVICE

9, NEWPORT PLACE, LONDON, W.C.2

Telephones; GERrard 4861 (Retail 2613)

59 GNS.—"17"

A full specification 17" Television Receiver to Spencer-West standards now available at your Dealers.

Remarkable performance and priced at 59 Gns. only complete.

For leaflet apply to :

SPENCER-WEST LTD.

GT. YARMOUTH, NORFOLK

Hours of Business:
9-6 Weekdays
9-1 Saturday

GEE Bros. RADIO Ltd.

ADJOINING
LEICESTER SQ.
TUBE STATION

15, LITTLE NEWPORT STREET, LONDON, W.C.2. Telephone : GERrard 6794/1453

SPECIAL TERMS FOR QUANTITIES—EXPORT ORDERS PROMPTLY EXECUTED

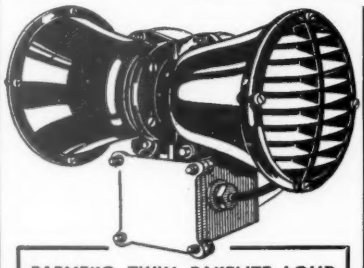

PARMEKO TWIN BAKELITE LOUD HAILERS (ex-Admiralty). Mounted on metal base. Complete with 600 ohm line transformer. 15 ohm voice-coil. Ideal for P.A. and all outside work. Length 15in., height 9in., dia. of horns 8½in. Price **45/-**. Carr. 7/6.

★ BAKERS SELHURST SPEAKERS ★

12in. P.M. 15 ohms 15 watts, 30–14,000 c.p.s., **£4/10/-**.

"HI-FI MASTER" 12in., 15 ohms, 12 watts, 20–16,000 c.p.s. Flux density approx. 14–15,000. OUR PRICE **£7/10/-**.

"SUPER HI-FI 25," 12in., 15 ohms, 25 watts, 25–20,000 c.p.s. Flux density 17,600. OUR PRICE **£9/9/-**.

All the above speakers are Brand New and full descriptive specification is available.

CONDENSERS. 2 mfd. 7.5 kv. wkg. at 15 kv. test. Good condition. **£2/10/-**. Carr. 10/-.

SELENIUM METAL RECTIFIERS.

	F/B		F/B
6 or 12 v. 1 amp.	7/6	24 v. 1 amp. ...	13/6
12 v. 2 amp ...	10/-	24 v. 2 amp ...	20/-
12 v. 2½ amp ...	15/-	24 v. 2½ amp ...	25/-
12 v. 4 amp ...	16/6	24 v. 4 amp ...	30/-
12 v. 6 amp. ...	23/6	24 v. 6 amp ...	35/-
12 v. 10 amp ...	40/-	24 v. 10 amp ...	80/-

AMPLIFIER. 12 v. D.C. For Mobile and Outdoor operation. Powered by Vibrator and Rectifier with 2 -EL35's or 6L6's in push pull. Output 18 watts approx., fitted for mike and gram inputs. A sound and practical unit in good condition for only **£12/19/6**. Carr. 5/-.

TRANSMITTER-RECEIVER No. 19. Mk. II complete with 15 valves. Frequency range A set 2–8 meg., B set 230–240 Mc/s., in good condition, **£2/19/6**. Carr. 10/6. 12 V. ROTARY POWER UNIT for above, **£1**. Carr. 7/6. All leads, headsets, variometers, etc., available.

18/24 v. 10 AMP. BATTERY CHARGERS for 200–250 v 50 cycles input, metered, switched and fused. As new, **£12/10/-**. Carr. 20/-.

A.C.-D.C. RECTIFIER POWER SUPPLY UNIT. 230 v. A.C. 50 cycles input 100 v. D.C. output max. 2½ amp. **£4/10/-**. Carr. 7/6.

C.M.G. 25 PHOTO CELLS (OSRAM). Brand new. 15/-. P. & P. 1/-.

MINIATURE 373 I.F. STRIPS for F.M. tuner as described in "Practical Wireless." Complete with all valves, conversion instructions and circuit. BRAND NEW. ONLY **42/6**, post paid.

TELEPHONE CABLE (Don 8). Twin one mile drums. **£5**. Carr. 20/-.

H.R.O. COILS. Frequency 50–100 kc/s. NEW. ONLY 15/-.

RECORDING WIRE. ¼ lb. spools, 3½in. dia. New and unused, 9/-. P. & P. 1/-.

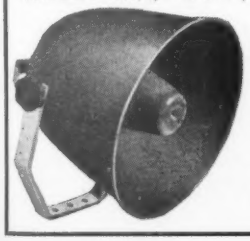

RE-ENTRANT LOUD HAILERS (Ex-Govt.)

Heavy duty 20 watts all-metal 15 ohms. Diameter 15in., length 15in., (approx.). Perfect condition. **£6/10/-**. Carr. 10/-.

BARGAINS IN ★ TEST EQUIPMENT ★

VALVE TESTER, TYPE 4. 200/230 v. A.C. input. Ex-Govt., in good condition, with descriptive book containing circuit diagram of instrument and how to test valves from 1.4 v. to 40 v. With valve holders for Brit., 4, 5, 7 pin and Octal, U.S., 5 and 7 pin, I/Octal, side contact large Brit., 4 and 9 pin. Acorn and diode. Housed in substantial wooden case with hinged lid. **£7/19/6**. Carr. 10/-.

PRECISION SERIES 834-S (U.S.A.). Multi range tester for A.C./D.C. volts, ohms and milliamps. Basic movement 400 microamps. Housed in wooden box with lid and carrying strap. Overall size 7½ × 7in. × 5in. Complete with test prods, batteries, etc. Ready to use. **£6/19/6**. Post 2/6.

EVERSHED & VIGNOLES MEGGER CIRCUIT TESTER (low reading ohm meter). 2 ranges. 0–3, 0–30 ohms. The perfect meter for continuity and polarity testing. Complete with test leads and ready to use. Brand new. Only **£4/17/6**. P.&P.3/-

EVERSHED & VIGNOLES. Series II 500 v. Megger Insulation Tester, with leather carrying case. As new. **£20**. Carr. Paid.

METERS. 0–1 mA. 2in. circular F/M, **17/6**. Ditto 2½in., **25/-**. 0–50 microamps. D.C. m/c., projecting 2½in. round, **49/6**. 0–10 m/A. A.C. m/c., rectifiers, F/M 3½in., round **49/6**. 0–300 v. A.C. 2½in. F/M, **25/-**. 0–200 v. A.C. 3½in. F/M. **25/-**. 0–300 v. A.C. 3½in F/M, **25/-** each.

RECORD MEGGERS. 500 v. insulation tester, 0–50 megohms. In leather case, good condition. **£8**.

TEST SET TS-26/TSM. This volt ohmmeter is the correct tester for EE8 telephones and all standard telephone equipment. Brand new and boxed, with full technical data and calibration charts. **£7/10/-**.

EVERSHED & VIGNOLES WEE MEGGER 500 v. New and unused. Only **£12/10/-**. Ditto 250 v. **£10/10/-**. P. & P. 3/- on each.

AVO TEST BRIDGE. A.C. mains operated from 200–250 v. Will test resistance from 5 ohms to 50 megohms and capacity from .00001 to 50 mfds. A most useful instrument for everyday uses. Our price ONLY **£7/19/6**. P. & P. 3/6.

★ ACCUMULATORS ★

BAKELITE-CASED 2 v. 100 ampere 75 actual. Ex-Govt. New and unused. Complete with carrying handle. Size 6½ × 6½in. × 3½in. **15/-** each. Carr. 3/6. 3 sent for **50/-**, or 6 for **£5** carr. paid. Ditto., 16 A.H., **5/-**. P. & P. 2/-. Ditto., 14 A.H. less handle **5/-**. P. & P. 2/-.

6 v. 20 A.H. comprising three 2 v. celluloid-cased cells in wooden case. Size 5 × 5 × 7½in. New and unused. **17/6**. P. & P. 3/6.

B.C.929A CRT INDICATOR UNIT. Containing 1–3PB1 3in. C.R.T., 3–6SN7s, 2–6H6s. 1–6G6, 1–6X5, 1–2X2; 8 valves in all. Ideal for 'scope conversion. New, in original sealed cartons. **70/-**. Carr. 5/-.

R109A RECEIVERS. Freq. range 2–12.0 megs. In good working order. **£4/7/6**. Carr. 10/-. A.C. mains 200–250 v., power packs available. **£4**. Carr. 5/6.

HEAVY DUTY—ALL STEEL

TRIPOD STANDS

Adjustable every 6in. to approx. 9ft. 6in. when fully extended. (Folds up to only 4ft. 6in. for storage.) Suitable for outdoor speakers, public address systems, floodlighting, etc., etc.

OUR PRICE **£3.10.0** Carr. 5/-.

These stands are ideal for our RE-ENTRANT LOUD HAILER as described below.

★ TRANSFORMERS ★

RCA PLATE TRANSFORMERS. 190 to 250 v. primary. 50–60 cycles. Secondary 1,500–0–1,500 or 2,000–0–2,000, at 1.75 kVA. Brand new and boxed. **£12/10/-**. Carr. 10/-.

VARIAC TRANSFORMER. 230 v. 50 cycles input, controlling 0–230 v. continuously at 9 amps. Perfect order. **£12/10/-**. Carr. 10/-.

DITTO, smaller type. 0–250 v. input controlling from 200–230 v. at 7 amps. **92/6**. Carr. 5/-.

E.H.T. TRANSFORMERS. 3,850 v. at 50 mA, with two additional 4 v. L.T. windings for 230 v. 50 cycles primary. New and boxed. **£3/15/-**. Carr. 5/-.

VARIABLE VOLTAGE REGULATOR TRANSFORMERS. Input 230 v. A.C. at 21 amps. Output 57.5 volts in 16 equal steps to 230 v. at 21 amps. Ex-Govt., in perfect condition. **£12/10/-**. Carr. 15/-.

TRANSFORMERS. 110–230 v. Pri. Sec. 26 v. tapped to 41 v. at 14 amps. New and boxed. **£3/10/-**. Carr. 5/-.

CAR RADIO VIB. TRANSPORMERS. 6 v. Input 280 v. at 80 mA. H.T. (ex-Philco). New, in perfect condition. **12/6**. P. & P. 2/-. Ditto., 12 v., same price.

E.H.T. TRANSFORMER. 20 kV at 140 mA. 230 v. 50 cycles primary. New and unused. Ex-Govt., Built to the highest specification. **£22**. Carr. 30/-.

TRANSFORMER. 1,800–0–1,800 at 1 kVA. 230 v. 50 cycles primary. Fully tropicalised. New and boxed. **£8/15/-**. Carr. 10/-.

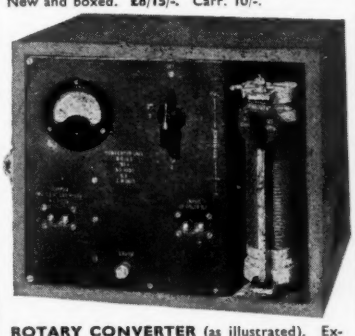

ROTARY CONVERTER (as illustrated). Ex-Govt. 12 v. D.C. input 230 v. A.C. Output 50 cycles at 135 watts. Complete in carrying case with lid, voltage control, sliding resistance, mains switch and 0–300 v. A.C. flush meter. In perfect working order, **£10**. Carr. 10/-.

ROTARY CONVERTER. 24 v. D.C. to 230 v. A.C. 50 cycles, 100 watts. Brand new and unused. **£6/9/6**. Carr. 7/6.

ROTARY CONVERTER. 110 v. D.C. to 230 v. A.C. 50 cycles, 300 watts. Fully smoothed and suppressed. Housed in strong steel cabinet complete with carrying handles. Absolutely brand new and unused, **£15**. Carr. 10/-.

English Electric Valve Company
CHELMSFORD
require

TECHNICAL ASSISTANTS

with education to H.N.C. (Electrical) standard for work in departments concerned with semi-conductors, travelling wave tubes and new developments in the field of vacuum physics. Age range 25-30. Applications should be submitted to **Dept. C.P.S., Marconi House, 336/7, Strand, London, W.C.2, quoting reference WW 1506N.**

COUNTY BOROUGH OF BOLTON

BOLTON TECHNICAL COLLEGE

Full-time Electronic Engineering Course

A three-year course in Electronic Engineering is now available. Candidates should be in the age range of 16 to 18, and have taken, or be taking, General Certificate of Education courses which include mathematics and physics at the Ordinary level, or equivalent courses in technical institutions.
This rapidly developing industry offers new and attractive openings to qualified men, and students who have passed through the course are readily absorbed in industry.
Further particulars may be obtained from the Principal.

W. T. SELLEY,
Chief Education Officer.

VACANCIES FOR CRAFTSMEN IN GOVERNMENT SERVICE AT CHELTENHAM

Experienced in the maintenance of:—
1. Radio Communication Receivers
or
2. Teleprinter, Cypher machines and associated telegraph equipment.

Basic pay: £9 2s. 4d. plus merit pay up to 70/- assessed at interview and based on ability and experience.
Opportunities for permanent and pensionable posts. Good working conditions. Single accommodation available.
Apply:
Personnel Officer (3/R.D.C.)
G.C.H.Q., 53 Clarence Street, Cheltenham.

BOROUGH POLYTECHNIC, Borough Road, S.E.1

Principal; JAMES E. GARSIDE, M.SC. TECH., PH.D., F.R.I.C., F.I.M., M. INST. F.

Applications are invited for the following posts available as from September next.

DEPARTMENT OF ELECTRICAL ENGINEERING AND PHYSICS

Assistant Lecturer (Grade B) in Electrical Engineering.

Applicants should be graduates in electrical engineering and/or graduate members of the Institution of Electrical Engineers with industrial or teaching experience, preferably in light current work. Duties will be mainly in connection with National Certificate courses.

SALARY SCALE
£650 x £25—£1,025 p.a. Plus allowances for degrees, training, teaching and industrial experience.
To all salaries the "London Allowance" (£36 or £48) is added.

Further particulars and Form of Application from the undersigned.

FREDK. J. PACKER,
Clerk to the Governing Body.

COMPUTER ENGINEERS

English Electric is considerably expanding its activities in the field of Digital Computers, and a number of qualified Engineers are required for their new Computer Laboratories, pleasantly located on the Staffordshire/Cheshire Border. Qualifications for these positions are normally a Degree or H.N.C., but consideration will be given to applicants with experience in Pulse Circuitry.

Unfurnished tenancies of recently built houses will be available after an initial period; the Company operates an attractive Staff Pension Scheme and Monthly Staff are entitled to three weeks' holiday from next year.

Please write giving full details to Dept., C.P.S., 336/7 The Strand, London, W.C.2, quoting reference WW306L.

THE TAPE RECORDER SPECIALISTS
STOCKISTS OF EVERY WELL-KNOWN MAKE INCLUDING
FERROGRAPH · SIMON · VORTEXION
TAPES, DECKS & ALL ACCESSORIES **SHERBOURNE** H.P. & CREDIT TERMS
50, TOPSFIELD PARADE
CROUCH END, LONDON, N.8
MOUntview 1987

LEEVERS RICH
PRECISION MAGNETIC RECORDERS
for
STUDIOS - INDUSTRY - RESEARCH
LEEVERS-RICH EQUIPMENT LTD.
138 Hampstead Rd. London, N.W.1. EUSton 1481

GALPINS

As announced in November we have taken over the Transformer Section of this business. For years we have wound all Galpin transformers and can promise you the same efficiency and quality as in the past.

JEFFERY TRANSFORMER CO.
199 Edward Street, New Cross, London, S.E.14
TIDeway 4458

REPANCO

HIGH GAIN TRANSISTOR COMPONENTS

MINIATURE RANGE—For pocket receivers. **Ferrite Slab Aerial Type FS3.** Medium Wave only. With fixing grommets. Size 3in. x ⅝in. x 5/32in., 7/6.
Oscillator Coil Type XO8. Medium Wave only. Overall size ¼in. dia. x 1in. Enclosed in Ferrite pots, 8/-.
I.F. Transformer Type XT6. Suitable for 1st and 2nd I.F. 455 Kc/s. Size ⅝in. sq. x 1⅛in., 10/-.
I.F. Transformer Type XT7. Designed for 3rd I.F.T. or detector I.F.T. 455 Kc/s. Size as XT6, 10/-.
Push Pull Interstage Transformer Type TT9. Ratio 1 : 1 C.T. Radiometal Core. Size ⅝in. x ⅝in. x 13/32in., 12/6.
Push Pull Output Transformer Type TT10. Ratio 8 : 1 C.T. Matched to 3 ohm. speaker. Size as TT9, 12/6.
Practical and Theoretical circuits enclosed with each Repanco Transistor Component.
"THE MINI-7" a new personal portable transistor receiver. Size 5¼in. x 3¼in. x 1⅝in. Send 1/9 P.O. for instructions.

Mail Order and Trade:
RADIO EXPERIMENTAL PRODUCTS, LTD.
53 Much Park St.
COVENTRY
Tel.: 62573

Wholesale Enquiries and Export:
REPANCO, LTD.
O'Brien's Buildings
203-209 Foleshill Rd.
COVENTRY
Tel.: 40594

NEW BOOKS ON RADIO and TELEVISION

The New A.R.R.L. Amateur Radio Handbook 1958. Postage 1/9	32/6
The HI-FI Year Book 1958. Postage 1/-	10/6
Beginners' Guide to Television, by Camm. Postage 9d.	7/6
An Approach to Audio Frequency Design, by G.E.C. Postage 1/-	10/6
Magnetic Tape Recording, by Spratt. Postage 1/6	55/-
Television Servicing Vol. 2, by Patchett. Postage 6d.	6/-
Radio Servicing Pocket Book, by Molloy. Postage 9d.	10/6
Tape Recorders and Tape Recording, by Weiler. Postage 1/-	23/-
High-Fidelity Loudspeaker Enclosures, by Babani. Postage 6d.	5/-
Electronic Novelties for the Constructor, by Bradley. Postage 6d.	5/-

A full range of Slide Rules and Drawing Instrument Sets in stock. Send for lists.

UNIVERSAL BOOK CO.
12 LITTLE NEWPORT STREET,
LONDON, W.C.2 (adjoining Lisle Street)

it's the
TA2B

TRANSISTOR AMPLIFIER

Max. Sens'ity 2 Microvolts RMS. Audio Range. Noise 3%. Portable. Internal switching to monitor either of two a.c. inputs. Built-in balance circuit for comparison of two anti-phase inputs, permitting measurements independent of source power variations. The 100 microamp meter may be used directly for d.c. measurements. Selective or wideband operation.
Write for leaflet A15.

MICROWAVE INSTRUMENTS LTD.
NORTH SHIELDS NORTHUMBERLAND

TERMS AVAILABLE

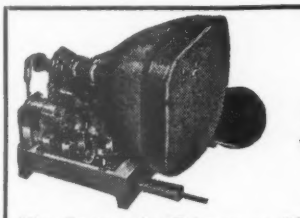

17" T.V. CHASSIS, TUBE & SPEAKER

£19 . 19 . 6

17in. Rectangular Tube on modified chassis. Supplied as single chassis covering B.B.C. channels 1-5, or incorporating Turret Tuner which can be added as an extra at our special price to chassis purchases **50/-**, giving choice of any 2 channels (B.B.C. and I.T.A.). Extra channels can be supplied at 7/6 each. I.F.'s 10.5-14 Mc/s. Chassis size: 12in. x 14½in. x 11in. Valve line up: 6SN7G, 6P25, EY51, 2—6D2's, EL38, EL41 and 7—6F1's.

With tube and speaker, **£19/19/6**. With all valves, **£25/19/6**. Complete and working with turret tuner, **£28/9/6**. 12 Months' guarantee on the tube, 3 months' guarantee on the valves and chassis. Ins. Carr. (incl. tube), **25/-**.

SUPER CHASSIS, 99/6

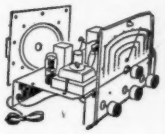

5-valve superhet chassis including 8in. P.M. Speaker and valves. Four control knobs (tone, volume, tuning, w/change, switch). Four w/bands with position for gram. P.U. and extension speaker A.C. Ins. Carr. 5/6.

14in. TV CHASSIS, TUBE AND SPEAKER, £13/19/6

As above with 14in. round tube. Chassis, valves and tube guaranteed for 3 months. With Tube and Speaker, **£13/19/6**. With all valves, **£19/19/6**. Complete and working with turret tuner, **£22/9/6**. Ins. Carr. (incl. tube), **25/-**.

HOME RADIO, 79/6

5-valve (octal) superhet, 3 waveband receiver. Can be adapted for your gram. P.U. at a little extra cost. A.C. Size: 9½in. x 20½in. x 11½in. Two A.C./D.C. sizes: 9½in. x 18½in. x 11½in.—9in. x 20½in. x 12in. Wooden cabinets. Ins. Carr. 4/6. Please state mains and size required when ordering.

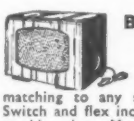

BEAUTIFUL EXTENSION SPEAKERS 29/9.

Fitted with 8in. P.M. Speaker "W.B." or "GOODMANS" of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Unrepeatable at this price. Money back if not completely satisfied. Ins. Carr. 3/6.

8" P.M. SPEAKERS 8/9

At this price you can have one in every room. With O.P. transformer fitted **10/-**. Postage 2/9.

TV MASKS

T.V. MASKS, 3/9. 12in. New White Rubber. Post 1/9. **17in. MASKS, 14/9.**

HEADPHONES, 1/9

Single earphone and band C.L.R. Ideal for crystal sets, extension on radio, etc. Post 1/3.

TRANSFORMERS

MAINS POWER TRANS., 350-0-350 v., **9/9**. 250 mA. 6 v. heater at 5 a. 4 v. at 5 a. centre tapped. Drop through type. Primary 200-250 v. (4½in. x 5in. x 5in.). Post 3/9.

MAINS TRANS., 3/9. 350-0-350 v. 80 mA., 4 v. 4 v. heaters, 200-250 v. Prim. Post 2/3.

MAINS TRANS., 5/9. 280-0-280 v. 80 mA., 6 v. 4 v. heaters, 200-250 v Prim. Post 2/3.

HEATER TRANS, 3/9. 1-2 Ratio Auto trans. 2 v. at 1.4 amp. Prim. 4 v secondary. Post 1/9.

O.P. TRANS., 1/3. Standard size, 2-5 ohms. Post 1/-. 20 for **£1**. P. & P. 5/6.

CO-AX CABLE, 6d. yard. Good quality. Cut to any length, 1/6 post on 20 yards. 45/- per 100 yards. Post 3/6.

INSULATION TAPE, 1/6. Finest quality 75ft. x ½in. wide. Post 9d.

RECTANGULAR T.V. TUBES (Reconditioned)

12 MONTHS GUARANTEE

17" £7.10.0 14" £5.10.0

6 months' full replacement, 6 months' progressive. Made possible by the high quality of our tubes. Ins. Carr. 15/6. 9in., 10in., 14in., 15in. and 16in. round tubes. Our special offer of these sizes, **£5**. **T.V. TUBES, £6.** Three months' guarantee on round tubes. Ins. Carr. 15/6.

SOLO SOLDERING TOOL, 19/6

110 v. or 6 v. (special adaptor for 200/240v. 10/- extra). Automatic solder feed. Including a 20ft. reel of ERSIN 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 2/9.

BARGAINS

CONSTRUCTURE T.V. CHASSIS

SOUND AND VISION STRIP, 10/6.
S/het. Complete vision strip, less valves. Free drawing. P. & P. 2/6.

TIMEBASE 4/9.
Including scanning coil, focus unit, etc., less valves. P. & P. 2/6.

POWER PACK AND AMPLIFIER, 29/6.
R.F. E.H.T. Not tested. Amplifier stage 6V6 with O.P. trans., 3 ohms matching. Smoothed H.T., 350 volt at 250 mA. 6.3 v. at 5 amp., 22 v. at 3 amp., 6.3 v. at 4 amp. and 4 volt centre tapped. Less valves. Drawings free. Size: 14½in. x 8in. x 7in. Ins. Carr. 5/6.

POWER PACK AND AMPLIFIER, 19/6.
Output stage PEN45 O.P. trans. choke. Smoothed H.T. 325 volt at 250 mA. 4 v. at 5 amp., 6.3 v. at 5 amp., 4 v. at 5 amp., centre tapped, valve base for rectifier. Octal or 4 pin. Output is taken from standard plugs. Less valves. Ins carr. 5/6.

POWER PACK & AMPLIFIER 19/6
Output stage 6V6 with O.P. trans. 3 ohms. Choke. Smoothed. H.T. 350 at 250 mA., 6.3 v. at 5 amp., 22 v. at 3 amp., 6.3 v. at 4 amp. and 4 v. centre tapped. Less valves. Not tested. Ins. Carr. 5/6.

TV CHASSIS, 25/6

Ideal only for spares. Although this chassis has a wealth of components, it is considered uneconomical to attempt rebuilding. This chassis is in three separate units. Power Pack, Time Base and S/Vision strip. I.F.'s 16-19.5 Mc/s. Drawings FREE. Ins. Carr. 10/6.

POPULAR RADIO OR RADIOGRAM CHASSIS, 39/6

3 w/band and gram. 5 valve s/het. International octal. Ideal table gram, but still giving high-quality output. 4 Knob control, 8in. P.M. Speaker, 7/9 extra. Set of Knobs, 2/-. Chassis size: 12in. x 6in. x 9in. Less valves. Ins. Carr. 4/6.

VALVE SALE. *3 MONTHS GUARANTEE*

2C22	2/9	12K7	8/9	ECH42	8/9	EF92	3/9
4D1	2/9	12BE6	6/9	EF39	3/9	EF36	5/9
6B8	3/9	451U	10/9	EF91	7/9	KTW61	5/9
6F12	5/9	77	1/9	EF37	4/9	PEN45	6/9
6H6M	1/9	CV188	1/9	ECH81	8/9	RL37	1/9
6P28	10/9	DF66	5/9	EF50	2/9	SP61	2/9
6SG7	2/9	EB34	1/9	EL32	4/9	TT11	4/9
8D2	3/9	ECC81	8/9	EL91	3/9	Z77	7/9

Closed Thus. 1 p.m. *Open ALL DAY SATURDAY* *Free 1958 Catalogue*

DUKE & Co. (Dept. 6), 621/3 ROMFORD ROAD, MANOR PARK, E.12. ILFord 6001/2/2.

3 essential books for students and technicians

Wireless Servicing Manual

By W. T. Cocking, M.I.E.E.

17s. 6d. net By post 18s. 8d.

This, the ninth edition of a standard work which has come to be recognised as a reliable and comprehensive guide for amateur and professional alike, has been thoroughly revised and set in a larger and handier format. Essential testing apparatus is described, and logical methods of deducing and remedying defects are explained. A completely new chapter on the servicing of frequency-modulated v.h.f. receivers has been added.

Television Receiving Equipment 4th Ed.

By W. T. Cocking, M.I.E.E.

454 pp. 30s. net By post 31s. 9d.

A practical book on television

This is the fourth edition of what may justly be claimed as one of the most important books on television. It deals comprehensively with television receiving equipment and gives many practical details and much design data.
Owing to the rapid development of television this new edition has been largely re-written and, with the addition of 169 pages of new matter, is virtually a new book.

Television Engineering

Principles and Practice
Vol. III: Waveform Generation

By S. W. Amos, B.Sc. (HONS), A.M.I.E.E., and D. C. Birkinshaw, M.B.E., M.A., M.I.E.E.

224 pp. 30s. net By post 31s.

A BBC Training Manual

Gives the application in television of sinusoidal, rectangular, sawtooth, and parabolic waves and shows the mathematical relationship between them. The main body of the text is devoted to the fundamental principles of the circuits commonly used to generate such signals. The treatment is largely descriptive and therefore less mathematical than that of the previous volume.

Published for "Wireless World"

ILIFFE technical books

from leading booksellers

ILIFFE & SONS LIMITED DORSET HOUSE STAMFORD STREET LONDON S.E.1

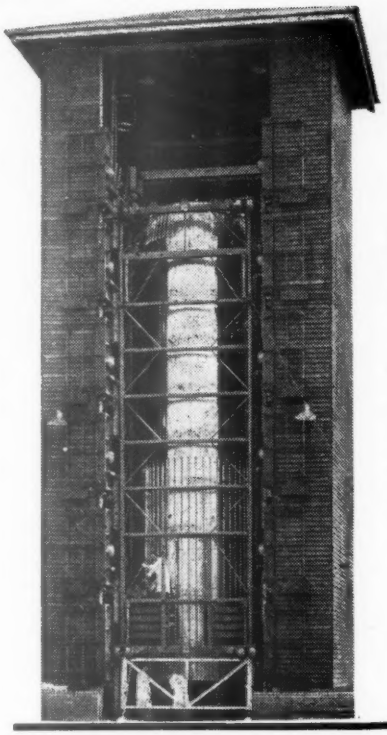

SPECIAL ANNOUNCEMENT

FOR

ELECTRONIC DRAUGHTSMEN

As prime Contractors for the British L.R.B.M. it is necessary for de Havilland Propellers Ltd. to form a new Drawing Office Team which offers opportunities for experienced Electronic Draughtsmen to take up established posts of National importance.

These posts provide the opportunity to work in amenable surroundings where housing will be available in appropriate cases within the New Town of Stevenage.

Special arrangements regarding interview can be made on written application stating details of age, experience, etc., quoting reference CTF3, to the

PERSONNEL MANAGER,
DE HAVILLAND PROPELLERS LIMITED,
STEVENAGE, HERTS.

All details will be treated in the strictest confidence.

ELECTRONIC ENGINEER

A Senior Project Engineer is required to handle electronic instrument design from conception to production. Used to working on own initiative. Degree or equivalent, five or more years' experience. Considerable drive and ability to overcome difficulties and to meet targets is essential.

Position offers real prospects in an active, growing company. Energy, interest and eagerness to tackle work necessitating periods of intense activity, will earn excellent rewards.

Apply at once,

CHIEF ENGINEER,
ADVANCE COMPONENTS LIMITED,
HAINAULT, ESSEX.

ELECTRONIC ENGINEERS

We are seeking electronic engineers to participate in original development and engineering work as members of a highly qualified team working on an extremely interesting range of projects. The essential qualification is an ability to devise and improve high grade circuitry, making full use of the latest known techniques in connection with both valves and transistors, and to follow this up by sound engineering design of pre-production prototype models.

The positions offered are permanent with a good commencing salary and excellent prospects of advancement. Attractive pension and life assurance cover is provided under a contributory scheme after a period of probationary service.

The Company is situated in pleasant country surroundings between Esher and Cobham in Surrey, and is well served by train, 'bus and Green Line routes. Working conditions are ideal with fully equipped laboratories and all the usual amenities of an established and progressive Company — good canteen, medical services, recreation and social club with sports facilities within the premises.

The Chief Engineer would be glad to see you for an exploratory chat in strictest confidence. Write or telephone for an appointment to:

COTTAGE LABORATORIES LTD.,
PORTSMOUTH RD., COBHAM, SURREY
Telephone : COBHAM 3191

S. SMITH & SONS (RADIOMOBILE) LTD.

(the marketing organisation for His Master's Voice & Radiomobile Car Radio)

Applications are invited for the following vacancies:—

1. **DEVELOPMENT ENGINEERS**—for car radio and low frequency amplifiers—recently qualified Design Engineers would be suitable.
2. **SERVICE ENGINEER** — for adjustment and repairs to car radios. Thorough knowledge of radio fault finding necessary.
3. **INSTALLATION ENGINEERS**—for car radio. Experience in radio and electrical installation work necessary.
4. **TECHNICAL SERVICE. CORRESPONDENTS** — to deal with customers' car radio technical enquiries and problems.

Excellent working conditions, generous salaries, pension and welfare schemes make employment with this Company an attractive proposition.

If you are interested address your application to:—

The Staff Manager,
S. Smith & Sons (England) Ltd.,
Cricklewood, N.W.2.
Quoting reference SM.119

Central Electricity Generating Board

INSTRUMENT ENGINEERS

INSTRUMENT ENGINEERS required in the Electronics and Instruments Section of the Research Laboratories, Leatherhead, Surrey. The Section provides an instrument service for all departments of the Laboratories and duties include the maintenance, calibration and repair of the wide variety of physical, chemical and electrical instruments.

Candidates should have the Higher National Certificate or equivalent qualification. Experience in electronic or nucleonic equipment will be an advantage.

Salaries within scales £820–£995 p.a. or £550–£725 p.a.

Applications stating age, qualifications, experience, present position and salary should be forwarded to S. S. Scott, Chief Personnel Officer, 24/30 Holborn, London, E.C.1. Envelopes should be marked "Confidential"—Ref.: WW/166.

"ALL your TV Components from one Source"

direct TV Replacements

BONA FIDE TRADE ONLY
Non-Trade Clients — see your dealer NOW!
138 LEWISHAM WAY, NEW CROSS, S.E.14
TIDeway 6666 *Grams: Flibak, London, S.E.14*

MIDDLESEX COUNTY COUNCIL
Education Committee

TWICKENHAM TECHNICAL COLLEGE,
Egerton Road, Twickenham, Middlesex.
(Tel: POPesgrove 7676)

PULSE CIRCUIT DESIGN

A course of twenty-two lectures will be given by specialist lecturers on Thursday evenings commencing 9th October, 1958, at 7 p.m.

Special consideration will be given to transistors in pulse circuits.

A brochure giving further particulars is available from the Principal.

C. E. GURR, M.Sc., Ph.D.,
Secretary to the Education Committee.

E.M.I.

CHIEF ENGINEER

E.M.I. ELECTRONICS invite applications for the post of Chief Engineer for their Broadcast Equipment Division. Applications are invited from qualified engineers with up-to-date experience of a wide range of Television Broadcasting equipment. The successful applicant should be able to play a large part in forming technical policy and be capable of directing the activities of various development teams.

Please apply:
Personnel Department,

E.M.I. ELECTRONICS LTD.,
Blyth Road, Hayes, Middlesex.

PLEASE QUOTE REFERENCE NO. EL/B74.

E.M.I.

ELECTRONIC ENGINEER

There is a vacancy in the Hayes Laboratories of the Company for an Electronic Engineer, trained to degree of H.N.C. standard and experienced in the design of test gear associated with Digital Computers. A knowledge of design techniques involving transistorised circuitry would be an advantage.

Please apply:
Personnel Department,

E.M.I. ELECTRONICS LTD.,
Blyth Road, Hayes, Middlesex.

PLEASE QUOTE REFERENCE NO. EL/B81.

ELECTRONICS RESEARCH LABORATORY STAFF

The following are required in the above department of large manufacturing company in North London:—

SENIOR QUALIFIED ELECTRONICS ENGINEERS of Degree or H.N.C. standard for work on the application of transistors to television and other electronic equipment.

JUNIOR ENGINEERS having O.N.C. or equivalent training to assist and work under the guidance of the above.

SECRETARY/TYPIST. This post offers a unique opportunity for a lady having training in Radio or Electronic theory (e.g. ex WRNS etc.) and secretarial experience, with ability to deal intelligently with technical correspondence and reports. To serve as secretary to chief engineer. If desired, an opportunity will be given to join in the practical work of the laboratory according to level of training attained. Box No. 6762, c/o "W.W."

TWO FIRST CLASS T/V ENGINEERS
REQUIRED

Good wages. Permanent position. Telephone appointment

T. A. BERRY (Lodge Radio) LTD.
EWELL 2317

OPPORTUNITIES IN

CANADA

A new division of a major electronics firm needs:—

ENGINEERS	electrical and mechanical.
PHYSICISTS	
ELECTRONICS	and electron tube specialists.
EXPERIENCE	in airborne electronics, radar or systems would be helpful.
LOCATIONS	Montreal, Toronto, some U.S. points.
INTERVIEWS	in the United Kingdom will be arranged at a later date.

Send full résumé in complete confidence to:-

DR. J. J. BROWN, Placement Division
INDUSTRIAL AUTOMATION LTD.
1121, Sherbrooke St. W., Montreal, Canada

SELENIUM RECTIFIERS

40 ma. to 10 amp., 6 v. to 100 v. Bridge, H. Wave or P.P.

WITH OR WITHOUT HIGH-GRADE TRANSFORMER TO SUIT. These are new goods, best makes, not reconstructed Government surplus. Popular types, 6 v. 1 a., 4/-, 2 a., 7/6, 12 v. 2 a., 8/6, 12 v. 1 a., 7/6, 12 v. 3 a., 15/-, 6 a. alloy-finned type, 27/6, 24 v. 0.3 a., 9/-, 0.6 a., 12/6, 24 v. 1 a., 13/6, 2 a., 15/6, 24 v. 3 a., 21/-, 50 v. 1 a., 24/-, 50 v. 2 a., 42/-, 130 v. 300 ma. h. wave, 38/-, 250 v. 300 ma. do., 65/-, 110 v. 1 a. bdge., 48/-, 130 v. 80 ma. bdge., 21/-. Postage 9d. extra each.

CHARGER KITS

No. 1, a kit for 2 v., 6 v., 12 v., 3 amp. transformer, rectifier, ammeter, all high-grade new parts, not rubbish, 52/6, unique convector housing for same, as illust., 12/6, p.p. 3/-, ditto, but 2 amp., 43/-, case 12/6, p.p. 3/-.

Economy 12 v. 3 amp. kit, no ammeter needed, 34/6, p.p. 2/6, all with 12 months' guarantee.

CHAMPION PRODUCTS
43 UPLANDS WAY, LONDON, N.21
Telephone LAB 4457

SOLDERING ?

HENLEY SOLON ELECTRIC SOLDERING IRONS

for 25 years the best

25 watt Instrument Model

A model for every purpose

Leaflets on request from:

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
Engineering Sales Department,
59-62, High Holborn, London, W.C.1
Telephone: CHAncery 4361
'Grams: "Henletel, Holb, London"

COPPER WIRE

ENAMELLED, TINNED, LITZ, COTTON AND SILK COVERED. RESISTANCE WIRES, 1 oz., 2 oz., and 4 oz. REELS All gauges available. B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets. EBONITE and BEKELITE PANELS. TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS. Latest Radio Publications. SEND STAMP FOR LIST. TRADE SUPPLIED.

G.E.C., B.T.H. & WESTINGHOUSE GERMANIUM CRYSTAL DIODES

1/- each. Postage 3d.

Diagrams and three Crystal Set Circuits Free with each diode.
A large purchase of these fully GUARANTEED diodes from the manufacturers enables us to make this attractive offer.

POST RADIO SUPPLIES
33, Bourne Gardens, London, E.4

CABINETS

for
Goodmans, G.E.C., Wharfedale, Jensen

STANDARD BASS REFLEX CABINETS
Walnut, Mahogany and Oak, as illustrated (34" high)
12" Speaker Model £10.0.0
10" Speaker Model £9.10.0
8" Speaker Model £9.0.0
Open till 5.30 Saturdays.

A. DAVIES & CO. (Cabinet Makers)
3 Parkhill Place, off Parkhill Road, London N.W.3. GULLIVER 5775

NEW METERS

(by well-known manufacturers)
to your requirements

7-14 DAYS DELIVERY

A.I.D. APPROVED

IEC METER REPAIRS by SPECIALISTS

Phone: HOP 1408

Prompt and Efficient Service

INSTRUMENTS ELECTRICAL CO.
107, Newington Causeway, London, S.E.1.

another amplifier circuit using KT 88's and MASSICORE SAVAGE transformers

Amplifier employing two KT 88's 50 watts as described by W. Ian Heath in "Design for a 50-watt Amplifier," and by G. R. Woodville in "Wireless World," April, 1957, and in "Audio," January, 1958.

OUTPUT TRANSFORMER TYPE 4N1

6,000 ohms centre tapped and tapped at 43% and 25%.
Secondary impedances: 0.45 ohms, 1.8 ohms, 4 ohms, 7 ohms, 11 ohms, 16 ohms, 22 ohms, and 30 ohms.
Primary inductance: 50 hys.
Primary D.C. resistance: 50 ohms + 50 ohms.
Leakage reactance: Primary to secondary 6 m/hys. Half primary to secondary 3 m/hys.
Power handling capacity: 50 watts at 25 c/s.
Size: 5½in. x 4½in. x 5½in. high. Weight: 14½ lbs.
Potted 4N1C. Size: 6in. x 5½in. x 6½in. high. Weight: 15 lbs.

MAINS TRANSFORMER TYPE 4W36A
Primary: 200/250v. 50 c/s single phase.
Secondary: 500-0-500v. 200mA. (D.C.), 6.3v. 5A., 6.3v. 2A., 5v. 3A.
Size: 5½in. x 4½in. x 5½in. high. Weight: 17½ lbs.
Potted 4W36C. Size: 6in. x 5½in. x 6½in. high. Weight: 19½ lbs.

CHOKE TYPE 4X83
5 hys. 200mA.
Size: 4½in. x 3½in. x 4½in. high. Weight: 6¾ lbs.
Potted 4X83C. Size 5in. x 3⅝in. x 4½in. high. Weight: 8½ lbs.

SAVAGE TRANSFORMERS LTD.

NURSTEED ROAD
DEVIZES, WILTSHIRE
ENGLAND.
Telephone: Devizes 932-3.

MARCONI TF-643 ABSORPTION WAVEMETER

20 to 300 mc/s. Complete with four pick-up coils and calibration charts. PRICE, unused, in perfect condition, in wooden transit case **£5/10** Carriage **15/-.**

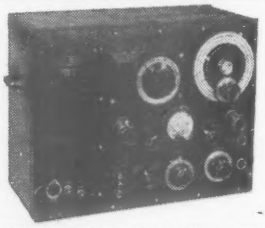

GENERAL RADIO TYPE 605B SIGNAL GENERATOR. Range 9.5 kc/s to 30 mc/s., giving a useful extension of the audio range. Accuracy ±1%. Power supplies 230 v. A.C. PRICE, fully overhauled and guaranteed, **£60.** Packing and carriage **£1/10/-.**

COSSOR MODEL 339 DOUBLE BEAM OSCILLOSCOPES FULLY OVERHAULED AND GUARANTEED £30. Packing and Carriage **£1.**

MARCONI TF-942 HIGH SPEED OSCILLOSCOPE, for pulse work; Trace Duration 0.1 to 0.55 musec; Calibration marks at 0.25-1.0-5.0-25 mc/s; "Y" Shift Voltmeter. Unused, as new condition.....**£180 0 0** Packing and carriage **£3.**

R-111/APR-5 RADAR SEARCH RECEIVER. Frequency range 1,000 to 6,250 mc/s; I.F. 30 mc/s; I.F. Bandwidth 10 mc/s. Power supplies 115 v. A.C. and 24 v. D.C. *Price and details on application.*

COLLARO 4-SPEED RECORD CHANGERS latest models "CHALLENGER" and "CONQUEST"; Crystal Turnover Pick-up. Brand new, **£8/15/-.**

TELEPHONE EQUIPMENT

American Field Telephones type EE8 and spares British UC 10-line Switchboards and spares American BD-71 6-line Switchboards. Also only few available: American BD-72 12-line Switchboards.

TRANSMITTING AND RECEIVING INSTALLATIONS SUITABLE FOR MARINE OR GROUND MOBILE USE

25 WATTS COLLINS TCS INSTALLATION, comprising Transmitter, Receiver, Antenna Loading Coil, Remote Control Unit with Loudspeaker, Power Supply Unit (state voltage required), Inter-connecting cables, Microphone, Headphones and Key. This installation can be used for VFO operation or as 4-channel crystal controlled equipment. Range 1.5-12 mc/s.

50 WATTS BC-375/BC-348 EQUIPMENT, comprising Transmitter BC-375, seven plug-in tuning units, Receiver BC-348, Aerial Tuning Unit, Power Supply Unit, Interconnecting cables, Headphone, Microphone and Key. Frequency Range: Transmitter 150 to 12,500 kc/s; Receiver 200-500 kc/s and 1.5-18 mc/s. Power Supply Unit for 24 v. supplied as standard. *Details and prices on application.*

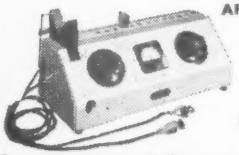

ARMATURE DROP TESTERS (Ex A.M. Ref. 5G/549)

For testing Motor and Generator Armatures, max. dia. of commutator approx. 4in.; max. overall dia. 7in.; max. length approx. 15in. PRICE **£5/10/-.** Packing and carriage 15/-.

INSULATION TESTERS

Record "Minor" 500 v. Insulation Tester, complete with leather case **£10 0 0**
Eversheds Series 1 Megger insulation Tester, 500 volts, 40 megohms **£25 0 0**
Eversheds Series 1 Megger Insulation Tester, 1,000 volts, 100 megohms, from... **£27 10 0**
Eversheds Series 1 Megger Insulation Tester, 1,000 volts, 100 megohms, complete with Decade Box, all brand new **£60 0 0**
Eversheds Series 2, 500 volt Megger Insulation Tester in leather carrying case ... **£25 0 0**
Eversheds Series 3 Megger Insulation Testers, 500 volt "Wee" Meggers)..... **£12 10 0**
Eversheds Bridge Megger, 500 v. ... **£45 0 0**
Eversheds Bridge Megger, 1,000 v.... **£50 0 0**
Leather cases for Eversheds "Wee" Meggers **15 0**

All above are fully guaranteed for six months.

RECORDERS

EVERSHED 12-PEN TIME RECORDER

Portable 12-channel instrument for simultaneous recording of eleven events with twelfth channel providing time markings. Pens and chart are operated by 28 v. D.C. supplies. Chart speed 2 inches per second. PRICE, unused, in original packing, complete with accessories, supply of charts, etc. **£30 0 0**
Packing and carriage **£1 0 0**

ELLIOTT SINGLE PEN PORTABLE RECORDING MILLIAMMETER

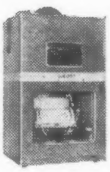

This is an A.C./D.C. instrument of the moving coil type, A.C. range being obtained through an internal metal rectifier. Separate terminals are brought out for A.C. and D.C. A.C. range 1 milliammeter; D.C. range approx. 0.9 mA. F.S.D. Clock driven chart 1 inch per hour.
PRICE, perfect condition and fully guaranteed **£35 0 0**
Packing and carriage **£1 0 0**
Other types available—please write for details.

PLEASE VISIT OUR RETAIL BRANCH AT 85, TOTTENHAM COURT ROAD, LONDON, W.1 (near Goodge Street Station). Telephone LANGHAM 8403. Open all day Saturday. Late closing on Wednesday (7 p.m.).

ARR-3 F.M. RECEIVERS, two RF Stages, two I.F. Stages, Automatic Frequency Control. Frequency range 62-70 mc/s. Simple Conversion to B.B.C. in 30 minutes. PRICE, complete with valves, modification instructions, circuit diagram and modification kit **£5 10 0**
packing and carriage **15 0**

R-1155B RECEIVERS, with super-slow motion drive, complete, air tested **£8 15 0**
Packing and carriage **15 0**

EDDYSTONE 358X COMMUNICATION RECEIVERS

40 kc/s to 31 mc/s covered continuously with ten plug-in coils. Perfect reception, unusually high sensitivity. PRICE, in perfect condition, with a set of ten plug-in coils and mains Power Pack, only **£15 0 0**
Packing and carriage **£1 10 0**

CR-150 MARCONI COMMUNICATION RECEIVER. Dual Superhet, 2 to 60 mc/s. "S" Meter. PRICE, fully overhauled and guaranteed **£50 0 0**
MARCONI Mains Power Pack for the above..... **£10 0 0**

P-104 RECEIVERS (R-1392) VHF Receivers, 95 to 150 mc/s, from **£3 10 0**

EDDYSTONE MAINS (230 v. A.C.) POWER PACKS

300 v. H.T. 200 mA. and 12 v. L.T., 3 amps..... **£2 8 6**
175 v. H.T. 65 mA. and 6.3 v. L.T. **£1 15 6**

ROTATING BEAM AERIALS. Tubular 2in. dia. x 6ft. high with rotating handle (worm-gear drive) and azimuth indicator **£1 15 0**
6ft. Extension Masts for the above (maximum of two per base), each **15 0**
Packing and carriage **12 6**

PETROL ENGINE

Single-cylinder 4-stroke air-cooled, 2.3 h.p. at 2,500 r.p.m.
BRAND NEW
PRICE, Engine only **£13 10 0**
Engine with Baseplate (to accommodate generator), Silencer with flexible exhaust pipe, and spares **£17 10 0**
Packing and carriage **£1 5 0**

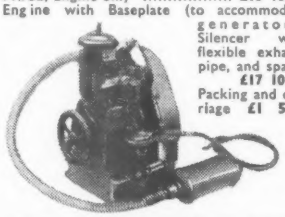

HEADSETS AND MICROPHONES

C.L.R. Low Impedance Headsets, each **5/6**
D.L.R. Low-Impedance Headsets, Balanced Armature, each **7/6**
C.H.R. High-Impedance Headsets, each **10/-**
D.H.R. High-Impedance Headsets, Balanced Armature, each **15/-**
R.A.F. Type Headgear Assembly: with Low Impedance Earphones, each **28/-**
Ditto with Electromagnetic Microphone, each **32/6**
Ditto with Throat Microphone, each... **35/-**
Headsets with High-Impedance Earphones, extra..... **2/-**
American HS-30/U Lightweight Headsets with miniature earplug type earpieces **12/-**
Electromagnetic type microphones, Type 48 **3/6**
American Throat Microphones Type T-30, each **1/6**
Carbon Hand Microphones, without Switches, each **4/-**

Please send s.a.e. for Valves and Meters Price Lists.

When ordering by post, please add (unless specified otherwise) 2/- in £ for packing and postage. Please send all Mail Orders and correspondence to our Head Office.

Z & I AERO SERVICES LTD.,

14, South Wharf Road, London, W.2

Telephone AMBassador 0151/2.

We buy high quality Test Equipment, Communication Receivers, Aircraft Transmitters and Receivers etc.

Wireless World Classified Advertisements

Rate 7/- for 2 lines or less and 3/6 for every additional one or part thereof, average lines 6 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 c/o "Wireless World" Dorset House, Stamford St., London, S.E.1.) Trade discount details available on application. Press Day September 1958 issue, Wednesday, July 30th. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components and valves which may be offered for sale through our displayed or classified columns carry no manufacturers' guarantee: Many of these items will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such items purchased.

NEW RECEIVERS AND AMPLIFIERS

SHIRLEY LABORATORIES, Ltd., 3, Prospect Place, Worthing, Sussex Tel. 30536. THE TWA/1515 stereoscnic tape recording and replay amplifier, separate meter monitoring on record and playback on both channels, 15watts O/P each channel, 96gns; TWA/15 tape recording and reproducing amplifier, 13watts O/P, for Wearite and Collaro decks, 45gns; TW/PA recording and replay pre-amplifier, 30gns; both with valve voltmeter monitoring; type SB/1-15E high-fidelity amplifier exceptionally wide tone-control system, 40mv sensitivity, 20gns; with two inputs and 3-position gram filter, 22gns; specialized amplifiers for the musical and scientific industries including the Mullard 20watt. [0095

RECEIVERS AND AMPLIFIERS—SURPLUS AND SECONDHAND

R1155 complete with speaker, power-pack working order; £9, carriage paid.—Hameed, 135, Knutsford Rd., Warrington. [7931

HRO Rx's and coils in stock, also AR88, BC348R, CR100, etc.—Requirements please to R. T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0053

TV RECEIVERS AND AMPLIFIERS—SURPLUS AND SECONDHAND

PROJECTOR television and screen, 5ft×4ft, fully maintained and in perfect condition, for sale, or part exchange for 21in television. —Apply Box 6793. [7954

PHILIPS 17in projection televisions available, as taken in part exchange, complete, but not guaranteed; £9/15, originally £92-£120 each.—Tomlins, 127, Brockley Rise, Forest Hill, S.E.23. [0343

TELEVISIONS needing attention, 9in-10in, nearly all makes, 45/- each, carriage paid; 12in televisions, needing attention, £5/10; 15in, £9/10; write for list.—Tomlins, 127, Brockley Rise, Forest Hill, S.E.23. [0344

NEW TEST EQUIPMENT

INSULATION testers by Wayne-Kerr Laboratories, brand new incorporating Variac transformer and large electrostatic voltmeter; highest quality throughout; output continuously variable 0-5KV AC or DC; price, ready for use, money back guarantee, £9/15 carr. paid. —R. Sankey, Picturedrome, Atherstone, Warwicks. Tel. Atherstone 3210/3202. [7962

TEST EQUIPMENT—SURPLUS AND SECONDHAND

SIGNAL generators, oscilloscopes, output meters, valve voltmeters, frequency meters, multi-range meters in stock; your enquiries are invited.—Requirements to R. T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986.

NEW COMPONENTS

A BANG up-to-date catalogue that will make your eyes pop! Free and post free to dealers: send your bill head; trade and export only supplied.—A.W.F., 10, Sackville St., Bradford, 1. [0132

CRYSTAL microphone inserts with exceptionally high output (Cosmocord Mic. 6), guaranteed newly made and boxed, 15/6 post free.—Radio-Aids, Ltd., 29, Market St., Watford, Herts. [0170

COMPONENTS—SURPLUS AND SECONDHAND

SOUTHERN RADIO SUPPLY, Ltd., 11, Little Newport St., London, W.C.2. See our displayed advertisement, page 153.

MAGSLIPS at low prices, fully guaranteed, 3 in Resolver No. 5 (AP 10861), 50v. 50c/s, unused each in tin, 35/-, post 2/1; large stocks of these and other types.—P. B. Crawshay, 94, Pixmore Way, Letchworth, Herts. Tel. 1851. [0087

CATHODE ray tubes used but in good working order with three months' written guarantee. 12in to 17in Mazda, Mullard and equivalent types only at £4/10 each plus 12/6 for carriage and insurance; enquiries and orders to BHP Distributors (London), Ltd., 379, Staines Rd., Hounslow, Middx. Tel. Hou. 5144. Our terms are C.W.O. or C.O.D. [0170

OF PARAMOUNT IMPORTANCE

to the Radio & Electronic Industry

the NEW PARTRIDGE PRICE LIST

Featuring all the popular lines from our last list with the addition of one or two **new lines, all available for immediate delivery—ex stock.**

In addition we have illustrated all the mounting styles referred to in this list for easier specification and ordering.

We are happy to say that our new price list shows a " trend " towards a general reduction in prices. A welcome feature in a field where " quality products " cannot be substituted by those of an inferior nature and price.

The finest possible materials; constant research and development keep Partridge Transformers in the lead. The first in the field, they have consistently proved to be the best. Inevitably, in any amplifier specification the words " Partridge Transformer recommended " will appear.

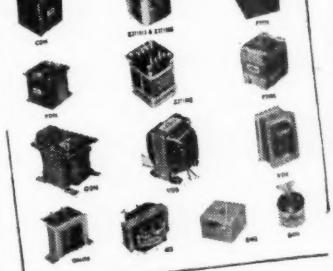

Write for your copy of the new Partridge Price List now to:

PARTRIDGE TRANSFORMERS LTD.

Roebuck Road, Chessington, Surrey.

Phone: ELMbridge 6737-8.

COMPONENTS—SURPLUS AND SECONDHAND

4½IN sq MC voltmeters basic 350μA, 300 or 250v, plain scale, 32/6, P/P 2/-; 100, 10 or 2v mirror scale 35/-, P/P 2/-; special scales extra to order.
TRANSFORMERS: TV type, 200-250v in, 350-0-350v 275 mA, 5v 3A, 6.3v 3AX2, 27/6, P/P 5/-; heater (a) 6.3v 3A X6, 6.3v 1.6A X8, 6.3v 0.3A X6, 12v 3A, 5v 3A X3, 230v in 22/6, carr. 5/-; Heater (b) 230v in, 6.3v 3A X4, 6.3v 1.6A X5, 6.3v 0.3A X6, 2v (ins 1500v), 20/-, carr. 5/-; HT 410-0-410v 100 mA, 330-0-330v 75 mA, 5v 3A X3, 230v in, 30/-, carr. 5/-; Advance Comps. CV type, input 190 to 260v output 230v constant 105W, £3/10, carr. 5/-; 250W £4/12/6, carr. 7/6; 500W £6/10, inc. carr.
PAPER caps: 8μF 1,000v 7/6, P/P 3/-; 8μF 750v 5/-, P/P 2/6; 4μF 750v 4/6, P/P 1/9; 4μF 500v 4/-, P/P 1/6. Plugs and skts., Jones 12-way, pair 3/6, P/P 9d; Cannon coax, pair 3/-, P/P 9d
VALVE bases: 10, 3/- doz., P/P 1/-; B7G 3/6 doz., P/P 1/-. Relays: 500ohm PO type fitted microswitch, 7/6, P/P 1/-; Elliott MC min. ¼/0/¼ mA, 2×350ohm, 15/-, P/P 9d.
NEUCLEX Co., Ltd., 44, Oak End Way, Gerrards Cross. Tel. 3296. [7974

ILLUSTRATED Catalogue No. 13 containing over 450 items of Government surplus and model radio control equipment, 2/2, refunded on purchase of goods. 2/6 overseas sea mail.—Arthur Sallis Radio Control, Ltd., Department W.W., 93, North Rd., Brighton. [0193

POWER units, ex-R.A.F., 12-volt input 200+ 13-volt output, ideal for car radio, electric shavers and many other uses, each power unit is brand new in maker's sealed boxes, all are fully smoothed and contain a rotary convetor, stabilizing valve and a heavy duty relay for remote control; cost over £20 each to manufacture, weight approx. 20lb each; our price 25/- each, plus 2/6 part carriage charge.—Waltons Wireless Stores, 46, 47, 48 & 49, Stafford St., Wolverhampton. [0147

NEW GRAMOPHONE AND SOUND EQUIPMENT

TAPE recorders, Ferrograph, Vortexion, Brenell, Telefunken, M.S.S., Truvox, and Reflectograph.
TAPE decks, Wearite, Brenell, Truvox, Dulci Harting, Sonomag Adaptatape (Collaro).
AMPLIFIERS and tuners, Leak, Quad, R.C.A., Dulci, Dynatron; microphones, Reslo, Acos, Philips, Labor, etc.
ALL tapes and accessories; audio service dept., and recording studio, hire-purchase facilities available.
LAMBDA RECORD Co., Ltd., 95, Liverpool Rd., Liverpool, 23. Great Crosby 4012. [7749

CINE-VOX disc recording mechanisms for L.P. or standard operation from 30gns.-56gns.; also complete tape/disc or direct channels from 50gns.-112gns.
DEMONSTRATIONS can be arranged in London.—For full details write to K.T.S., Ltd., " Coplow," Park Rd., Braunton, N. Devon. Callers by appointment only. [0210

GLASGOW.—Recorders bought, sold, exchanged, cameras, etc., exchanged for recorders or vice versa.—Victor Morris, 406, Argyle St., Glasgow, C.2. [0201

TAPE recorders for home and industry: Brenell, Mk. V, 68gns; Ferrograph recorders from 79gns; Standard and L.P. tapes; high quality mics, " Cadenza " Reslo, etc.; speakers tuners, etc.; tape/disc and complete recording service; also Chapman SE5 tuner unit VHF/AM self-powered, shop soiled, only £27.—" Eroica." Sound Recording Services (1949), 31, Peel St., Eccles, Manchester. Eccles 1624. Director: Thurlow Smith, A.R.M.C.M. [0122

GRAMOPHONE AND SOUND EQUIPMENT—SURPLUS AND SECONDHAND

FERROGRAPH 3A/N practically new, ten tapes; £80; accessories extra. (London).—Box 7001. [0232

M.S.S. disc cutter, 3 speed, hot-cut, matched playback/record amplifiers, speaker (all metal cased), cost £250; bargain £90, must sell. Box 7015. [7984

TAPE RECORDING, ETC.

TAPE to disc recording.—L.P. (30 mins.), 27/6; 78s, 15/6; 48-hour service, s.a.e. leaflet.—Marsh, Little Place, Moss Delph Lane, Aughton, Ormskirk, Lancs. Aug. 3102. [7782

FOR SALE AND WANTED ADVERTISEMENT FORM TURN TO PAGE No. 157

SOLDERING EQUIPMENT BY

LITESOLD

REGD. TRADE MARK

PRECISION SOLDERING INSTRUMENTS for the ELECTRONICS INDUSTRY

- Comprehensive range
- Robust & Reliable
- Light weight
- Rapid heating
- Bit sizes 3/32in to 3/8in
- All voltage ranges 6/7v to 230/250v
- Prices from 19/6

Illustrated is the 25w 3/16in replaceable bit model with safety shield.

British and Foreign Patents. Registered designs. Suppliers to H.M. and Foreign Governments. Agents throughout the world.

Brochure No. S.5 sent free on request.

Sole proprietors and manufacturers:

LIGHT SOLDERING DEVELOPMENTS LTD
106 George Street, Croydon, Surrey
Phone: CROydon 8589 Grams: Litesold Croydon

● **AERIAL EQUIPMENT.** Poles, Masts, Dipoles, Yagi, and Microwave arrays. 12in. Whips to 150ft. Masts.

● **CABINETS AND RACKS.** 36in. to 96in. high, standard 19in. wide.

● **CONDENSERS** up to 10,000 mfd. and 50 kV.

● **FUSES.** Cartridge and E.S. ¼ amp. to 600 amps.

● **INSULATORS.** 80 different patterns.

● **LOUDSPEAKERS** 3in. dia. to 50 watt Theatre Systems.

● **METERS** 2in. to 12in. dia. 120 different types.

● **POWER SUPPLIES.** Generators, Rectifiers, Vibrators, Inverters, Dynamotors from 2 volts 100 amps. to 36,000 v. ¼ amp.

● **RECEIVERS.** 80 types available from 15 kc/s to 600 mc/s. including portable, D.F., Table Rack and Pedestal.

● **TEST GEAR,** American, over 100 different types, Meters, Calibrators, Signal Generators, etc.

● **TELEPHONE AND TELEGRAPH EQUIPMENT.** Single- and multi-channel apparatus, filters, switchboards, power supplies, perforators, printers.

● **TRANSFORMERS** Audio and Power, 200 types from 2 volts to 18,000 volts and up to 15 kVA.

● **TRANSMITTERS.** 60 different types from UF-1 Handie Talkie to G-50, 2,500 watts.

FULL LISTS AVAILABLE

Send your requirements. All packing and shipping facilities

P. HARRIS
ORGANFORD, DORSET
Telephone: LYCHETT MINSTER 212

TAPE RECORDING, ETC.

TAPE to disc, Queensway Recording Studios, 123, Queensway, W.2. Bay. 4992. Recorders serviced and for hire. [7421

RENDEZVOUS RECORDS offer comprehensive 78/LP tape to disc recording facilities. —Leaflet from 19, Blackfriars St., Manchester, 3. [7402

TAPE/DISC/TAPE.—If quality and durability matter (especially with LPs) consult Britain's oldest full-time transfer service (1952 rates); limited quantity new 1,800ft LP tape 37/6, 1,200ft standard 25/-, post free; use our mixer units for improved tape recording.—Sound News, 10, Clifford St., London, W.1. [0192

VALVES WANTED

NEW valves wanted, any quantity, best cash price by return.—Stan Willetts, 43, Spon Lane, West Bromwich, Staffs. Tel. Wes. 2392. [7900

ALL types of valves British or American, transmitting and receiving; keenest cash prices paid. What have you to offer?—Write or call Lowe Bros., 9a, Diana Place, Euston Rd., N.W.1. Tel. Euston 1636-7. [7848

WANTED, EXCHANGE, ETC.

PROFESSIONAL disc recorder wanted, 3 or 4 speed, adaptable for stereo, capable of cutting masters.—Full particulars Box 6634. [7946

WANTED, HRO coils, Rxs., etc., A.R.88s, BS348s, S27s, etc.—Details to R. T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0163

WANTED, small quantity of transformers Metro Vickers Style 20033Z, VA 900, 230 volts tapped input, 13.0, 13.5, 14.0 and 15.0 volts output at 60 amps.—Box 6583. [7934

A BETTER cash offer for brand new valves, speakers, components, test instruments, etc., that are surplus to your needs.—R. H. S., 155, Swan Arcade, Bradford, 1. [0190

URGENTLY wanted, manuals or instruction books, data, etc., on American or British Army, Navy or Air Force radio and electrical equipment.—Harris, 93, Wardour St., W.1. Gerrard 2504. [7874

WANTED, BC610 Hallicrafters, E.T.4336 transmitters, BC312 receivers, BC221 frequency meters and spare parts for all above; best cash prices.—P.C.A. Radio, Beavor Lane, Hammersmith, W.6. [0079

WANTED, good quality communication RYS tape recorders, test equipment, domestic radios, record players, amplifiers, valves, components, etc., estb. 18 years.—Call, send or 'phone Ger. 4638, Miller's Radio, 38a, Newport Court, Leicester Sq., W.C.2. [7898

PROMPT cash for the purchase of surplus stocks of televisions, tape recorders, radios, amplifiers and domestic electrical appliances of every description; substantial funds available.—Spears, 14, Watling St., Shudehill, Manchester, Blackfriars 1916. Bankers: Midland Bank, Ltd. [0216

REPAIRS AND SERVICE

MAINS transformers rewound, new transformers to any specification.
MOTOR rewinds and complete overhauls; first-class workmanship; fully guaranteed.
F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate, Nottingham. Est. 1917. Tel. 54898. [0113

USE Jefco coil winder, cheapest machine on the market.—Details 170, London Rd., Southend-on-Sea. [0174

MAINS transformers, E.H.T.s, chokes, field coils, etc., promptly and efficiently rewound or manufactured to any specification; 12 months' guarantee.
LADBROKE REWIND SERVICE, Ltd., 820a, Harrow Rd., London, N.W.10. Tel. Ladbroke 0914. [0222

TRANSFORMERS to any specification, Singles, rewinds, small or large batches; quick and efficient service, competitive prices, estimates by return of post. From:
MESSRS. Newman & Son, 1, Grove Crescent, South Woodford, E.18. [0330

RENEW to stock your faulty speakers of all sizes, pressure units, microphones, coils, fields and cone assemblies in cartons.—D. C. Boulton, 134, Thornton Rd., Bradford, 1. Telephone 22838. [0171

ARMATURE rewinding service to the trade: vacuums, drills, grinders, hood driers, dental and washing machine motors; vacuum cleaner armatures replaced from stock; 24 hour service; every job guaranteed; all vacuum cleaner parts, bearings, etc. in stock for any make; complete overhauls our speciality.—Regam Electric, Ltd., 39a, Boar Lane, Leeds 1. [7708

MISCELLANEOUS

ETA wavefinder as new, extras; £25 o.n.o.—Dunstan, Chapel Terrace, Stithians, Truro. [7975

ENAMELLED copper wire 3.085lb. 44 s.w.g., 227lb 45 s.w.g., surplus due to design change.—Offers to Concentric Mfg. Co., Ltd., Priory Road, B'ham, 6. [7942

RELAYS Post Office type 250 ohms with 2 NO and 1 NC contacts, approximately 5,000 available for quick sale.—Hampson Industries, Ltd., West Bromwich. [7844

1958 EDITION

ELECTRONIC MUSICAL INSTRUMENTS

60/- By R. H. Dorf. Post 1/6

ELECTRONIC SEMICONDUCTORS by E. Spenke, 85/6. Postage 1/-.
RAPID TV REPAIR, by G. W. Heath, 23/-. Postage 1/-.
THE RADIO AMATEUR'S HANDBOOK 1958 Ed., 32/6. Postage 1/9.
MODERN OSCILLOSCOPES AND THEIR USES by J. H. Ruiter, Jr., 45/-. Postage 1/6.
TV FAULT FINDING a Data Pub., 5/-. Postage 6d.
PROBLEMS IN ELECTRONICS WITH SOLUTIONS by F. A. Benson, 36/-. Postage 1/-.
ELECTRONIC PUZZLES AND GAMES by M. Mandl, 15/-. Postage 8d.
ELECTRON-TUBE CIRCUITS by S. Seely, 81/6. Postage 1/-.
RADIO VALVE DATA. Compiled by "W.W." 5/-. Postage 8d.

THE MODERN BOOK CO.
19-23, PRAED STREET, LONDON, W.2
BRITAIN'S LARGEST STOCKISTS OF BRITISH AND AMERICAN TECHNICAL BOOKS
Complete Catalogue 6d.
PADdington 4185. Open 6 days 9-6 p.m.

COLLARO
MK IV TAPE TRANSCRIPTORS
£25 CARR. PAID

W.B. HF. 1016
Speaker
£8 carriage paid
AVO MULTIMINOR
£9.10s. carriage paid
COSSOR
3 Valve 3 Watt
AMPLIFIER KIT
complete with 2 SPEAKERS
£9.15s. carriage paid
COSSOR
6 VALVE
VHF/FM RECEIVER KIT
WITH SPEAKER
15 GNS. Carriage Paid.

COMPONENTS
still Available for ALL **OSRAM** AND **MULLARD** AMPLIFIER & F.M. CIRCUITS

WE ARE STOCKISTS FOR
Erie, Radiospares, T.C.C. Dubilier Condensers, Wearite, Osmor, Denco, REP (Repanco), Teletron, Elstone, Partridge W.B., Elac, J.B. Tuning Condensers, Emitape, Scotchboy, Bulgin, Westinghouse, Brimar, Mullard, etc., etc. **Viewmaster** and **Teleking** Spares.

Send 3d. stamp for Lists.

L. F. HANNEY
77, LOWER BRISTOL ROAD, BATH

BENSON'S BETTER BARGAINS

CRTs. VCR530 6½in. magnetic x/y., el. focus. Octal base; blue, 8 kV., **30/-**; CV951 (Cossor 32A), 5½in.; el. x/y, gas focus; green, 1.5 kV., **17/6**; CV954 (Cossor 20 K.) 5½in.; el. x/y and focus; white, 3 kV., **17/6**; CV952 2½in., **20/-**; **EF24** (new type), 20-25 Mc/s. (IF 15 Mc/s.), with 2/EF91, 1/EF93, motor tuned, new, **30/-** (p.p. 3/6).

POWER UNIT 358. Outputs: D.C. 200 v., 10 mA. and A.C. 12 v 2 A. on mains 200/250 v. input, *or* 12 v. D.C. input; dual purpose, **50/-** (rail 8/6). **BC929A** Indicator Unit, with 3BP1 CRT and all valves, new, **50/-** (rail 7/6).

BC906D Frequency Meters, 150/235 Mc/s. cavity tuned, new, **40/-** (rail 5/-). **INDICATORS.** Type 182, with use each, 6½in. and 3in. C.R.T.'s, etc., **50/-** (rail, 10/-).

DRIVES: slow-motion, Admiralty 200: 1 ratio, scaled 0-100, **5/6**. **CR100,** brand new; power transformers, **30/-**.

KIT OF SPARES, including 15 valves, **£3**. **POWER UNIT,** 301 input 200/250 v. Outputs: 250 v. 75 mA., 24 v. 1 A. D.C. and 6.3 v. 3 A. A.C. New, cased, with plugs, **45/-** (p.p. 3/6). **COMMAND RECEIVERS,** brand new, 6 valves, med. wave (3.52-1.5 Mc/s), **97/6**; used **52/6** (post 3/6). Conversion data and circ. to CAR RADIO, **1/6**. **I.F. STRIP 373,** new, with valves, **37/6**, less valves, **10/-**. **VIBRAPAKS** 6 v. D.C. to 250 v. 80 mA., smoothed, cased, **22/6**. HRO 6 v. to 180 v. 50 mA., **18/6**; Jefferson 12 v. to 150 v. 30 mA. **12/6**; 12 to 24 v. to 120 v. 30 mA. **12/6**. Above are smoothed, filtered and cased. Mallory 12 v. to 120 v. 35 mA. synch. **10/6** (p.p. 3/6). **VIBRATORS,** Mallory G629C 12 v., 4-pin, **7/6**. **BRAND NEW R.F.26, 20/-** (post 3/-); **RF37,** good cond., **18/-**. **DYNAMOTORS** (post 3/6); 12 v. to 250 v. 80 mA. **11/6**; 6 v. to 250 v. 80 mA., **12/6**; 11 v. to 200 v. 50 mA. and 13 v. smoothed, filtered, cased, **15/-**; "**Command**" type 28 v. to 250 v. 60 mA. (small), **7/6**. Input 11.5 v. to 350 v. 30 mA., cont.; 310 v. 60 mA., int., 4½ × 2½in. dia., **15/-**. **D.C. DYNAMOTORS,** 12 v. to 200 v. 50 mA., 5 × 3in. dia. **22/6**; 12 v. to 200 v. 80 mA. filtered, **15/-**; 24 v. to 350/475 v., 210/260 mA., **22/6**; 26 v. to 210 v., 140 mA., small, **12/6**; 24 v. to 300 v and 150 v. 100 mA., **12/6**. Rotary Convertors, 100 v. D.C. to 50 v A.C., 50 c. 4 amps. (rail 7/6), **60/-**; 24 v. D.C., **40/-**, 110 v. D.C. to 230 v. A.C. and 220 v. D.C. to 230 v. A.C. larger types. Prices on application. **R1155 S.M. DRIVES** "N" type new, **10/6**. **METERS,** contain 2 separate micro-amp. movements and 2 neons, new, **8/6**. Cross-over needle (L/R) 100μA each section; good condition, **8/6** or 1 mA. x 2, **8/6**. **ACCUMULATORS,** 2 v. 16 A.H., **7/6**; 2 v. 15 A.H., Dry, **10/6**. **AERIAL RODS,** 12in. × 4 dia., push-in, **3d.** **AERIAL ROD HOLDERS,** swivelling, **2/6**.

BOXES XTAL SELECTOR, 5×9×4in., with 2 relays 600 type and 24 v. miniature motor, etc., NEW, **10/6**. **BOX,** Metal, 6½in. cube. With toggle and two insulated terminals (Bel/Lee). Ideal for charger; train unit; new, **5/-**. **BOX,** Metal, with 10 mA. 3½in. M.C. meter, resistors, switch, etc. (p.p. 2/6), **8/6**. **BOX,** Metal, with 6.3 v. 3 A. C.T. trans., 4 fuses and 3 toggle switches, **10/6**. **BOX** with 6 key switches, etc., G.P.O., **15/-**. **BOX WITH BUZZER,** 4½/12 v. and press switch, **4/6**. **CONTROLS,** Camera Type 35. A timing device, 24 v. motor, **12/6**. **CHOKES**—LF Choke, 5 H. 50 mA., combined with Pentode output transformer, **5/6**; Potted 20 H. 80 mA., **8/6**; 12 H. 150 mA., **8/6**; 8 H. 250 mA., **9/6** (post 2/-); 8 H. 100 mA., Potted Collins, **8/6**. **CONDENSERS (Variable)**—Twin Variable Min. 15, 25 or 50 pfs., **4/-**; 100 pf. Twin, Ceramic base **3/6**, Single **2/-**; 150 pf. Standard, single **2/-**; 50 pf. TX double spaced, **3/-**. **CLIPS,** Bulldog, large, holding aerial (rod), insulator, with Pye outlet, **3/6**. **COILS,** Eddystone, TX type "P" and "Q" Ceramic on 5-pin hor. base, 2½in. dia., NEW, **4/-**.

KEYS, Brass, small (Morse), 8 amp., **3/6**. **KEYS,** Morse, large, covered, **10/6**. **MICS.,** breast, sound powered with toggle switch, **5/-**. **MIC.** inserts, carbon, G.P.O., **1/6**. **MIC.** inserts, bal. armature, **2/6**. **MOTORS,** Synchronous 3,000 r.p.m. 10 VA. 100 v. 50 cycles, Spur gear, new, **7/6**. Selsyn, 230 v., large, **25/-**. **LAMPS,** 200/250 v., 250 w. E.S. RD., **4/6**. **PROJECTOR,** 120 v., 750 w. Pre-focus base, S.C. or 50 v. 200 w., **15/-**. **PLUGS,** 2-pin 2 A. Bakelite, **6d.**; Socket, standoff, to fit, **6d.**; Plugs, 2-pin 2 A., 2-way adaptors, **9d.**; Plugs Co-AX. Pye chassis Mtg. (4/- doz.), **6d.**; Pye Elbows, **6d.** **TRANSFORMERS.** Input: 110/230 v. Output: 6 v. 2 A., Twice or Auto 25 watts, **10/6**. Input: 230 v. Outputs: 250-0-250 v. 30 mA., 6.3 v. 5 A., 5 v. 2 A., **10/-**. Input. 230 v. Outputs: 560-0-560 v., 120 mA., 6 v. 7 A.: 5 v., 3 A., **15/-**. "**C**" **CORE** Inputs 110/230 v. Outputs 315-0-315 v. 60 mA. 6.3 v. 1.5 A. and 5 v. 2 A., **25/-**. Input 230 v. Outputs: 565-0-565 v. 48 mA. 600 v.; 5 mA.; 4 v. 4 A.; 2 v. 1.5 A., **17/6**. Input 110/240 v. Outputs: HW 325 v. 20 mA. and 6.5 v. 1 A., **9/6**. Input 110/240 v. Output: 6.3 v. 3 A. and 6.3 v. 1 A., **8/6**. Potted Modulation 3.5 : 1 twin secs. (post 2/6), **4/-**. Open Modulation 1.5 : 1 C.T. sec., **4/-**. DLR5 with throat mic., **10/6**. **HEADSETS DLR3, 7/6**. **BLOCKS,** Grelco 10-way, **2/-**.

LF. AMPLIFIERS for R107, brand new, less valves, **22/6** (p.p. 3/6).

MORSE TRAINING BOARDS with buzzer and key, wired for 4½ v. battery operation, new, **8/6**.

VALVE CV16 (disc seal triode) in brass waveguide, **15/-**. **RELAYS** GPO 3000 type, 500Ω 8 pole changeover, **6/-**. Siemens hi-speed 145Ω **5/6**.

METAL RECTIFIERS H.W. 270 v., 80mA., **5/6**; 350 v. 80mA., **6/6**; 600 v. 20mA., **5/-**; 1kV., 30 mA., **7/6**; 240 v., 100mA., **4/-**; Bridge 6 : 12 v., 4A., **2/6**; 12 v., 1.5A., **7/6**; meter type 5mA., **5/6**; 120 v., 1A., **30/-**.

LIST AND ENQUIRIES: S.A.E. please! Terms. C.W.O. **Postage extra.** Immediate despatch.

Callers and Post:
W. A. BENSON (W.W.)
136 Rathbone Road, Liverpool, 15. *SEF 6853.*

Callers:
SUPERADIO (W'chapel) LTD.
116 Whitechapel, Liverpool, 2. *ROY 1130.*

MISCELLANEOUS

G.E. 805, 25/-; circuits, 2/- each: 19 (A), 21 (R), 21 (Tx), BC1206, BC624, CW4604SD, 941T, BC453.—Williams, 25, Glenmore Rd., Birkenhead. [7949

METALWORK, all types cabinets, chassis, racks, etc., to your own specification; capacity available for small milling and capstan work up to 1in bar.
PHILPOTT'S METAL WORKS, Ltd., Chapman St., Loughborough. [0208

VALVE cartons, plain white, from 12 to 100,000 "off the shelf"; miniatures 10/-, "G.T.s" 12/-, "G's" 14/- per 100, plus 2s postage; may we quote you for any type of printed carton, all kinds of printing, catalogues, lists, etc.; quotes and samples with pleasure.—J. & A Boxmakers, Ltd., 75a, Godwin St., Bradford, 1. [0034

PAINTS, CELLULOSE, ETC.

PANL, recognised for many years as the unique one-coat black crackle finish, brush applied, no baking; available by post in 1/8 pint cans at 3/9 from: G. A. Miller, 255, Nether St., London, N.3. [0260

AGENTS WANTED

MANUFACTURERS of electrical control equipment with works in Essex require experienced representatives in the Midlands and North England.—Apply in strict confidence to Box No. 6973. [7969

BUSINESS OPPORTUNITIES

ESTABLISHED and well known small company in radio components field seeks working arrangement with person or small company proposing to launch new product not necessarily in radio manufacturers, wholesalers, etc., strictest confidence assured and expected.—Box 6356. [7901

CANADIAN sales for you; we successfully represent to the Government of Canada, manufacturers in United States and Canada, covering electronics and allied industries; Department of Defence Production is our largest customer; we are an incorporated company with 25 years' experience in the electronic industry in Canada; references will be made available; we have an important sales story to tell British manufacturers at this time.—Box 6891. [7961

CAPACITY AVAILABLE

SMALL capacity avilable for electronic assembly and wiring.—Pakolor, Ltd., Epsom, Surrey. Tel. 1612. [7978

P.T.F.E. and plastics machining and moulding, A.I.D. approved.—Bel Sound Products, Marlborough Yard, London, N.19. Tel. Arc. 5078. [0165

CAPACITY available for electronic and electrical assembly and wiring; a development section available for experimental work if required.—Electronic Devices (Cheltenham), Ltd., Wellington Rd., Cheltenham. Tel. 4667. [7908

SITUATIONS VACANT

ANTARCTICA

THE Falkland Islands Dependencies Survey require (a) radio officer for the R.R.S. "John Biscoe" and (b) radio officer/purser for the R.R.S. "Shackleton" for two years in the first instance with prospect of further service. These vessels normally make an annual voyage to the Antarctic and return to the U.K. for a short period every summer. Salary £654 a year. Uniform allowance £30 a year and bonus of £50 on satisfactory completion of season. Free quarters and messing. Candidates must possess P.M.G. 2nd Class Certificate and preferably have experience as a Ship's Radio Officer.—Write to the Crown Agents, 4, Millbank, London, S.W.1. State age, name in block letters, full qualifications and experience and quote M2C/49951/WF for post (a) and M2C/49917/WF for post (b). [7980

NORTHAMPTON
COLLEGE of Advanced Technology
LONDON
ST. John St., E.C.1.
Grades I, II and III laboratory technicians required in electrical engineering department. In addition to holidays with pay totalling up to five weeks per year, part-time day release is granted for studies in approved National Certificate or Degree courses. Standard L.C.C. conditions; scales (from £245 to £815 p.a. according to age and qualifications) and superannuation.
LETTERS of application to Head of Electrical Engineering Department. [7979

GOVERNMENT OF JAMAICA.

ASSISTANT Superintendent of Police (Radio) required to assist the Police Radio Engineer in the installation, maintenance and operation of Police V.H.F. radio telephone apparatus and automatic repeater stations.
CANDIDATES should possess School Certificate or the equivalent and have good practical knowledge of radio engineering, particularly V.H.F. techniques; age limits 20 to 30 years. APPOINTMENT is on probation for permanent and pensionable employment with salary in the scale £720-£900 according to qualifications and experience; uniform allowance £60 p.a.; Government quarters at low rent; up to five free passages for officer, wife and children on appointment and on leave; free medical attendance; generous leave; income tax at low local rates.
SUMMARY of qualifications and experience to Director of Recruitment, Colonial Office, London, S.W.1, quoting BCD 55/32/010. [7941

Armstrong FM 61

the VHF tuner with the VERY HIGH PERFORMANCE

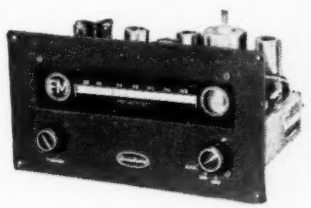

★ *Complete freedom from drift*
★ *Switched automatic frequency control*
★ *Full International FM Band*
★ *Exceptional sensitivity*
★ *Cathode follower output*
★ *Variable output matching control*
★ *Adjustable HT requirements*

This unit is designed to match the Armstrong A10 Mk II Control Unit and Armstrong AM44 Tuner in size and style. The A10 Mk II provides ample power supplies for the FM61, but a separate power pack (£4.18.0) is available if required.

The Tuner may be used with almost any amplifier, radio receiver or tape recorder. To facilitate its use with any of these having only a single audio input position, there is ingenious provision on the back of the FM61 to feed in an additional audio signal from either pickup, tape or AM radio. It may be left permanently connected and is automatically switched in when the FM61 is switched off.

Post this coupon or write for descriptive literature and details of Home Trial facilities and Guarantee to Armstrong Wireless & Television Co Ltd Warlters Road London N7 Tel: NORth 3213.

BLOCK CAPITALS PLEASE

NAME .....

ADDRESS .....

.....

..... WAT

Demonstrations at our Holloway Showrooms from 9 until 6 weekdays and Saturdays.

I WAS VERY THANKFUL TO GET HOME TO MY DUODE

"I heard every loudspeaker at the show and though some were very good none were so natural as my own."

That opinion came to us from a recent buyer of a new Duode 12B-C, who tried it at home first, then decided to keep it—as, indeed do nearly all who use our home test plan—and is now as happy as the many, many other people who enjoy Duode quality.

For clean, true string, brazen brass, husky wood-wind, deep hard drums—in fact, REAL—sound, you also need a Duode 12B-C Unit.

Incorporating dual drive with built-in crossover and feed-back.

Write for details to our temporary new postal address in London.

DUODE LTD.

BCM—DUODE, London, W.C.1

GILSON TRANSFORMERS——

are used in high reliability recording equipment by film studios and the B.B.C. Enquiries for prototypes and production runs are invited from electronic equipment makers.

R. F. GILSON LTD. Phone: Wimbledon 5695

St. George's Works, St. George's Road, Wimbledon, S.W.19

why not build your own

TAPE RECORDER

with the

'ASPDEN'

Tape Recorder Kits

TAPE DECK KITS

Two models, 5in. or 7in. spools, two speeds, twin track, ferroxcube heads, finest motor, and complete assembly instructions.

Compact model 582 kit £8 5 0

Standard model 782 kit..... £9 5 0

Assembled and tested 30/- extra.

And the

RECORD/REPLAY AMPLIFIER KIT, 2½ watt, neon indicator, without valves, £5/18/-.

POWER PACK KIT for above, less valve £2/18/6. Carr. extra.

You can get quality as Mr. S.B.S. of London who writes:—

". . . *on the high quality of your kits, and are comparable with recorders of twice the price.*"

At a very low price, as Mr. R.C.K. of Durham who writes:—

"*Many people who have heard it have been staggered that such quality can be obtained for such a low price.*"

Why not build one now.

Send STAMP for full particulars to:—

W. S. ASPDEN

Stanley Works, Clevedon Road, Blackpool, Lancs.

SITUATIONS VACANT

RADIO research with satellites.

D.S.I.R. Radio Research Stn., Slough, Bucks, requires scientific officers, experimental officers and assistant experimental officers for new programme of radio research using techniques provided by rockets and artificial satellites, including radio and visual observations on satellites, calculation and prediction of orbital information and collection, co-ordination and analysis of results; the work is located at Slough and Singapore; applications invited from mathematicians, physicists and electrical engineers, keen on being considered. Quals.: S.O. 1st or 2nd Hons. degree in approp. subject, E.O. Class (Minimum) G.C.E. (Advanced) in 2 science or a science and maths. subject but over age 22 pass degree, H.N.C. or equiv. generally expected. Salary: S.O. £595-£1,050. E.O. £920-£1,130. A.E.O. £370 (age 18)-£800 (men). Minimum age of 26 for E.O. Prospects of promotion and establishment. Additional allowances payable in Singapore.—Forms from M.L.N.S., Technical and Scientific Register (K), 26, King St., London, S.W.1 (quote A.201/8A/EW). [7932

EXPEDITION TO ANTARCTICA.

SCIENTIFIC assistant (ionospheric) required by the Falkland Islands Dependencies Survey for the operation and maintenance of special electronic ionospheric recording apparatus at an Antartic Base for two years; commencing salary according to age in scale £400 rising to £540 a year with all found including food, clothing and canteen stores; free passages, liberal leave on full salary. Candidates, preferably single and aged 21-28 years, must be of good education, of high physical standard and experienced in the servicing of radio or radar equipment. Genuine interest in life at an Antarctic Base essential.—Write to the Crown Agents, 4, Millbank, London, S.W.1. State age, name in block letters, full qualifications and experience and quote M3B/44628/WF. [7957

S. SMITH & SONS (RADIOMOBILE) Ltd.

RADIO TECHNICIANS of all grades are invited to apply for interesting and varied positions in car radio servicing, installation and development. Vacancies also occur from time to time for our dealers in all parts of the country. A high standard of practical and theoretical knowledge is required. Good wages, 5 day week and staff pension scheme.—Apply in writing to the Staff Manager at Cricklewood Works, London, N.W.2, quoting reference SM/116 [7916

W. H. ALLEN SONS & Co., Ltd., Bedford.

HAVE a vacancy in their laboratory; the successful applicant would be required to act as Assistant to the Head of the small but growing electronic section in the laboratory; the work involves acoustics, vibration, use of strain gauges and the development of special equipment for research work on steam and gas turbines, gears, centrifugal pumps, alternators, etc.

APPLICANTS should have a good theoretical training to at least H.N.C. standard and must give evidence of practical ability; some experience in engineering would be advantageous; this is an excellent opportunity for an enterprising young man on very interesting work, with opportunities to display initiative and originality.

GOOD staff pension scheme; assistance with moving, if necessary.

APPLICANTS should apply in writing, giving full details of age, qualifications, experience and salary required to the Personnel Manager. [7940

FULHAM and Kensington Hospital Management Committee.

TECHNICIAN required to assist in maintenance of electro-medical apparatus.

QUALIFICATION at least to ordinary National Certificate. Knowledge of mechanical engineering an advantage.

SALARY (at age 26+) £570 rising to £680.

APPLICATIONS, with full particulars, to Superintendent Engineer, Western Hospital, Seagrave Rd., Fulham, S.W.6, immediately. [7976

SOUTHAMPTON County Borough Education Committee.

TECHNICAL College.

REQUIRED for 1st September, 1958, full-time Assistant (Grade A for marine radio and radar courses; P.M.G. 1st class certificate and experience as radio officer, Merchant Navy, essential; M.O.T. certificate in radar maintenance desirable; main subjects morse and commercial procedure; salary scale £475×£25—£900.—Particulars and forms (to be returned within 10 days) from Chief Education Officer (57/66), Civic Centre, Southampton. [7950

TECHNICAL electronic sales engineer required by leading manufacturers and distributors for Yorkshire, County Durham, Northumberland and part of Nottinghamshire area.

SUCCESSFUL applicant will be required to commence employment in early August, if possible.

PENSION scheme. Good prospects.

WRITE, giving full details of past and present employment including present salary to Box 7014. [7983

ELECTRONICS technician required for biophysics dept., University College, London (Gower St., W.C.1), for construction and maintenance of specialised apparatus. Early twenties preferably. University scale. Application forms from Secretary, quoting Biophysics/4. [7977

The **VERDIK** QUALITY TEN

10 WATT PUSH-PULL ULTRA LINEAR FEEDBACK

20 GNS COMPLETE

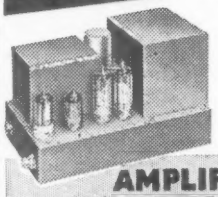

From Your Dealer

AMPLIFIER AND PRE-AMPLIFIER

For details write to

VERDIK SALES LTD.

139, 143 Sydenham Rd., Sydenham, S.E.26

SYDdenham 3118/9

LOCKWOOD

ENCLOSURES

Used by every Broadcasting & Television Authority in the British Isles, and Eire, for High Quality Monitoring

LOCKWOOD & CO. (Woodworkers) LTD., LOWLANDS ROAD, HARROW, MIDDX.

"DIPLOMA" HEADPHONES

Lightweight High Resistance (4,000 ohms). Complete with cord

17/6

Ideal for CRYSTAL SETS

The 'TYANA' Standard Soldering Iron

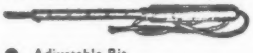

- Adjustable Bit
- Weight approx. 4 oz.
- Heating time 3 min.
- 40 Watt economy Consumption
- Standard Voltage Ranges

16/9

Replacement Elements and Bits always available

KENROY LIMITED

152/297 UPPER ST., ISLINGTON, LONDON, N.1

Telephone: CANonbury 4905-4663

SOUTHERN RADIO'S SPECIAL BARGAINS

SPECIAL OFFER

TRANSMITTER - RECEIVER

TYPE 38 MK 11

WALKIE - TALKIE

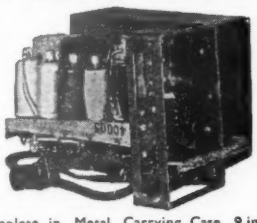

Complete in Metal Carrying Case. 9 in. x 6½in. x 4in. Weight 6lb. Frequency 7.3 to 9 Mc/s. Five valves. **£1/2/6.** Post paid.

These Tx-Rs are in NEW CONDITION, but owing to demand they are not tested by us and carry no guarantee, but should prove SERVICEABLE.

ATTACHMENTS for Type "38" Transreceivers. ALL BRAND NEW: Headphones **15/6**; Throat Microphones **4/6**; Junction Boxes **2/6**; Aerials, No. 1 **2/6**; No. 2 **5/-**; Webbing **4/-**; Haversacks **5/-**; Valves—A.R.P.12 **4/6**; A.T.P.4 **3/6**; Set of FIVE VALVES **19/-** the set.

OFFER No. 2:
"38," as above, complete with set of external attachments, **42/6**, post paid.

OFFER No. 3:
Transmitter-Receiver "38" Mk. II. Brand new with complete set of external attachments including Webbing, Haversacks and Valves, **57/6**, post paid. Fully guaranteed.

TRANSRECEIVERS. Type "18" Mark III, Two Units (Receiver and Sender). Six valves, Micro-ammeter, etc., in Metal Case, untested, without guarantee but COMPLETE, **£2/18/6.**

ATTACHMENTS for "18" Transreceivers ALL BRAND NEW. Headphones **15/6**; Hand Microphone **12/6**; Aerials **5/-**; Set of 6 Valves **30/-.**

R.109 RECEIVERS. S.W. Receiver in Case, eight valves. Speaker and 6-v. vib. Pack. Untested, no guarantee but COMPLETE, **£2/18/6.**

T1154 TRANSMITTERS. Complete in transit case. New condition. **£2.5.0.**

RESISTANCES. 100 assorted useful values. New wire end **12/6.**

CONDENSERS. 100 assorted Mica; Tubular, etc., **15/-.**

BOMBSIGHT COMPUTERS. Ex-R.A.F., NEW. Hundreds of components, gears, etc. Ideal for Experimenters. **£3.**

LUFBRA HOLE CUTTERS. Adjustable ⅜in. to 3½in. For Metal, Plastics, etc., **7/-.**

QUARTZ CRYSTALS. Types F.T.241 and F.T.243. 2-pin, ½in. spacing. Frequencies between 5,675 kc/s and 8,650 kc/s (F.T.243). 20 Mc/s and 38.8 Mc/s (F.T.241, 54th Harmonic), 4/- each. ALL BRAND NEW, TWELVE ASSORTED CRYSTALS, **45/-.** Holders for both types 1/- each. Customers ordering 12 crystals can be supplied with lists of frequencies available for their choice.

MORSE TAPPERS. Standard **3/6**; extra heavy on Base **5/6.**

TRANSPARENT MAP CASES. Plastic. 14in. x 10½in. Ideal for Maps, Display, etc., **5/6.**

STAR IDENTIFIERS. Type I A-N Covers both Hemispheres, **5/6.**

CONTACTOR TIME SWITCHES. 2 impulses per sec., in case, **11/6.**

Post or carr. extra. Full list Radio Books, etc., **3d.**

SOUTHERN RADIO SUPPLY, LTD.

11, LITTLE NEWPORT STREET,
LONDON, W.C.2. GERrard 6653

SITUATIONS VACANT

SALES manager required for an electrical wholesaling company in tropical Africa: handling radio, domestic appliances and installation materials.
WIDE experience in this field, with keen interest in selling, is essential; generous starting salary and attractive conditions of service. To a man with adequate background, this appointment offers unique opportunity for advancement in a company which is expanding rapidly.
PARTICULARS of experience, qualifications and age to Box 6983. [7972

RADIO service engineer required by firm distributing top quality F.M. sets.—Apply, giving full particulars of previous experience, salary required, etc., to Box 6588. [7936

VACANCIES occur in the design laboratories for engineers to assist in the development of radio and television receivers for home and export.
APPLICANTS should have a good knowledge of designing receivers for mass production, and should either have qualifications up to H.N.C. or degree standard, or practical experience in lieu.
THE work will cover a wide field, including transistors, stereo and V.H.F. Applicants mainly interested in television should be familiar with the problems associated with negative modulation.
SALARY will depend on experience and qualifications, but will not be less than £1K to the right man.
WRITE with full details of age, experience and qualifications to the Personnel Manager (R.14), Murphy Radio Ltd, Welwyn Garden City, Herts. [7884

THE Research Laboratories of the General Electric Co., Ltd., North Wembley, Middlesex, have several vacancies for technical assistants.—Please apply in writing to the Staff Manager (Ref. RLB/178). [7953

ENGINEERS required for repair and maintenance of all types of electronic measuring equipment.—Call or 'phone Aveley Electric, Ltd., 15-16, Ayron Rd., South Ockendon, Essex. Tel. South Ockendon 2021. [7952

A TECHNICAL copywriter is required in S.W. Lancs to assist with the creation of publicity material relating to certain radio and line transmission products of the telecommunication industry.
APPLICANTS should be about 25 years of age and be possessed of a good technical background and the ability to write clear, concise English; the work is congenial and a staff pension scheme is in operation.
PLEASE give full details and age and experience to Box 6825. [7955

JUNIOR engineer well grounded in electronics interested in audio-frequency engineering particularly in magnetic recording. A good technical background is required with ability and willingness to undertake practical work. Watford area. Salary £750-£1,000.—Box 6992. [7982

ELECTROCHEMIST required for small laboratory in Crawley, Sussex, engaged upon M.o.S. development contracts; the work consists of a study of electrode reactions in primary cells; housing available.—Write, stating age, experience and qualifications, to Box 6590. [7939

LABORATORY technician required for small laboratory in Crawley, Sussex, working on M.o.S. development contracts; duties will consist of making electrical test equipment and the testing of electrical components; housing available.—Write, stating age and experience, to Box 6589. [7937

ELECTRONICS division of West End company require capable girl assistant, must be efficient shorthand-typist with good knowledge of electronics, age late twenties-early thirties, able to drive car, must be unattached and preferably non-smoker; salary £12-£14 per week to start.—Write Box 6665. [7947

ELECTRONICS Engineer; a rapidly expanding Computer Group needs a capable and experienced Electronics Engineer, with H.N.C. or equivalent, to assist in the development of novel digital computing devices.—Applications to A. V. Roe & Co., Ltd., Hanworth Lane, Chertsey, Surrey. [7958

RADIO mechanic required for workshop overhaul/repair of modern aircraft radio apparatus and installations; paid holidays, sick benefit scheme and pension fund; permanent position for skilled men.—Write details to Labour Officer, Skyways, Ltd., Stansted Airport, Stansted, Essex. [7971

THE Research Company of a large group of textile machinery manufacturers require a young man to design and construct electronic apparatus, mainly in the low frequency range. Qualifications H.N.C in electronics or equivalent.—Apply: T.M.M. (Research), Ltd., Holcombe Rd., Helmshore, Rossendale, Lancs. [7914

TECHNICAL representative for ultrasonic flaw detection equipment. Applicants should have good technical qualifications in metallurgy, physics or electronic engineering, preferably to degree standard. Experience of ultrasonic testing would be an advantage. The post is for an expanding department and represents a good career for an engineer with initiative and drive.—Full details of age, exp., sal., to Ultrasonoscope Co., Sudbourne Rd., S.W.2. [7876

Smith's of EDGWARE ROAD

ELECTRONIC COMPONENTS DISTRIBUTORS FOR OVER 25 YEARS

FOUR-SIDED BLANK CHASSIS

Made in our own works from commercial quality half-hard aluminium of **16 s.w.g. thickness** these chassis will carry components of considerable weight and normally require no corner strengthening.
We are now able to supply **same day** any size of chassis in ½in. steps up to 17in. Depths ½", ¾", 1", 1½", 1¾", 2", 2½", 2¾", 3", at the following rates:—

48 sq. in*	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata.	

Post 1/3. Post 1/6. Post 1/9.
(*Length plus twice depth x width plus twice depth.)
½in. flanges on two sides (inside or outside) **1/6** extra.
Soldered corners (new process) **2/-** extra
Panels any size up to 3ft. at **4/6** sq. ft. (sq. in. × ⅛d.).
Full particulars on request.

Close Tolerance Wax-protected Silver Mica CAPACITORS

Values stock (pF):—

5	22	47	75	130	180	270	370	515	635	815	3000
10	25	50	80	135	200	280	386	533	670	820	3300
11	27	56	82	140	220	300	400	540	680	1000	3500
13	28	60	100	145	225	316	410	556	703	1500	4000
15	30	65	110	150	230	330	450	560	710	2000	4700
18	33	68	120	160	245	340	470	600	750	2200	5000
20	40	70	125	175	250	356	500	603	800	2500	

Tol. up to 33pF 1 pF., over 33pF 1 per cent.
PRICES: 5-300 pF **9d.**; 316-820 pF **10½d.**; 1,000-2,500 pF **1/3**; 3,000-5,000 pF **1/6.**
Special (limited number only), 0.1 mfd. 1%, **12/-.**

***DALY** guaranteed **ELECTROLYTICS**
Full range from **1/6** ea.

***HIGH STABILITY RESISTORS.** "T.S.L." ½-watt 10% tol., 5-year guarantee. Full "preferred value" range, 12Ω to 10MΩ, **6d.** each. Pairs matched to within 2% **3/-** pair.

***SURPLUS STOCKS,** various makes:—

	5%	2%	1%
½ watt	7½d.	10d.	1/3
¼ watt	9d.	1/-	1/6
1 watt	10½d.	1/3	1/9

***"ELECTROVOICE"** guaranteed **TRANSFORMERS AND CHOKES.** Individually tested. Fully shrouded. Used by leading laboratories. 66 types in stock.

The COOPER-SMITH HIGH FIDELITY AMPLIFIER

Model BP1 Main Amplifier, **£14/17/-.** Build-it-yourself **£12/12/-.** Mk. II Pre-amp. and Control Unit. **£11/3/-.** Build-it-yourself **£8/3/-.**

DIRECT FROM MAKER TO USER

A better 10 watt amplifier at lower cost. Send for illustrated booklet giving full constructional details of this remarkable outfit, **2/8** post free, or better still hear it in our demonstration room.

RELAYS 600 type **3/6** each.
2-make, 3000 Ω coil.
1-break, 1 c/o. 150 Ω coil.
1-break, 1 c/o 1 c/o (M before B) 150 Ω coil.

VISUAL INDICATORS, type 3 (10Q/4) containing two micro-amp movements. Brand new, **6/6** each. With neon lamps (two) **9/6.**

MANSBRIDGE CAPACITORS. 200 V. D.C. wkg. Suitable for crossover units, etc. .5 mF., **4d.** each; 1 mF., **6d.** each; 2 mF., **9d.** each; 4 mF., **9d.** each.

LIGHTWEIGHT HEADPHONES: 2,000 Ω, **12/6** pr. 4,000 Ω **17/6** pr.

MINIATURE MAINS TRANSFORMER. Pri. 0-200-220-240 v. Secs. 250 v. 40 mA., 6.3 v. 1.5 amp. Stack size 2½ × 1⅞ × 1¼in. **10/6.**

BELLING-LEE L430 PROTECTIVE SWITCHES. .3 amp. **1/3.**

T.C.C. VISCONOL CATHODE RAY CONDENSERS. .01 mfd. 12.5 kv. type CP57VO, **4/6.**

LOUDSPEAKER FABRIC. Brown with gold thread. **2/6** per sq. ft.

Please add approx. cost of postage.
*Lists available.

H. L. SMITH & CO. LTD

287/289 EDGWARE ROAD, LONDON, W.2
Telephone Paddington 5891

BAKER'S 'Selhurst' RADIO

The ULTRA DE LUXE

20-20000 c/s

12"

20W

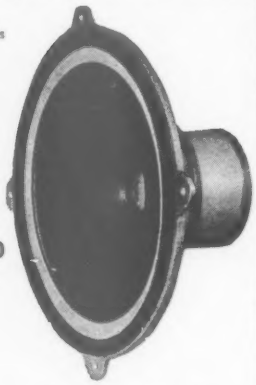

£15.15.0

For full range listening

Sales and Demonstration offices:

JOHN LIONNET & CO.

17, CHARING CROSS ROAD, LONDON, W.C.2. TRAfalgar 5575

MEGAOAKS FROM MICROACORNS GROW!

Many "Oaks" which today use our popular Type RXX-26 Benders, started as "Acorns" with our light Type RO-20.

No doubt it helped them to grow.

In June, we showed you our New Type RZ-26 tool, developed for the "Oaks."

NEXT MONTH, we will show you something new, specially for the "Acorns."

Be patient—a month soon passes.

For 6 page Folder write to:—

A. A. TOOLS (W)

197a Whiteacre Rd., Ashton-u-Lyne

TELETRON SUPER INDUCTOR COILS

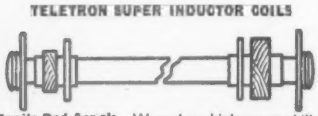

Ferrite Rod Aerials. Wound on high permeability Ferroxcube rod, Medium wave 8/9, Dual wave 12/9

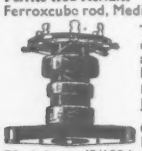

Type HAX. Selective crystal diode coil for tape and quality amplifiers, MW 3/-, LW 3/6. Dual wave TRF coils, matched pairs (as illustrated) 7/- pair. Type S.S.O. Supersonic Tape Osc. coil, provides 6.3 v. 3 a. RF for pre-amp heater. Eliminates induced 50 c/s hum, 40/100 kc, 15/- ea. Transistor coils, etc. Available from leading stockists. Stamp for complete data and circuits.

THE TELETRON CO. LTD.,
266, Nightingale Rd., London, N.9. How 2527

SITUATIONS VACANT

LABORATORY technician with experience of electronics required in the Electrical Engineering Department, University of Leeds; initial salary according to qualifications and experience.—Applications should be made in writing to Professor G. W. Carter, from whom further particulars may be obtained. [7939

COMPUTERS; in our expanding Computer Laboratory we have a vacancy for a Junior Engineer with O.N.C. or equivalent, who is keen to assist in the development of novel computing devices; some experience of analogue or digital computers and transistors would be an advantage.—Apply A. V. Roe & Co., Ltd., Hanworth Lane, Chertsey, Surrey. [7959

EXPANDING company specialising in electrical fire detectors and alarms seeks competent engineer with electronic or telephonic background to undertake development work. Must be able to work with minimum supervision. Good salary for right man.—Apply in writing, stating age, qualifications, experience and salary required, to Box No. 6974. [7970

TELEVISION Engineer required by old-established dealers with leading agencies; must be to R.T.E.B. and C. & G. standards; 44-hr week; accommodation available, new s/d house, summer holidays, with pay granted. —Write, stating experience and salary required, to: Wycombe Electrical Supplies, Ltd., 51-52, Oxford St., High Wycombe, Bucks. [7890

OVERSEAS.—Oil Exploration Company with world-wide seismic parties offers permanent career to electronic technicians; maintaining and operating field equipment; men prepared to accept responsibility and to live in camp conditions; academic qualifications to H.N.C. or equivalent or genuine practical experience to this standard; liberal home leave.—Box No. 6478. [0331

ELECTRONICS: Electronic Instruments, Ltd., of Lower Mortlake Rd., Richmond, have vacancies for junior and semi-senior engineers for instrument final testing. These are staff positions offering interesting and varied jobs with a bright future in this rapidly expanding Company. 5-day week, pension scheme. —Apply to the Company, giving qualifications and quoting reference TE/WW5M. [0126

RADIO Technicians required by International Aeradio Ltd. for overseas service. Permanent and pensionable posts. Normally tax-free, inclusive salary in local currency varying with location, and additional marriage and child differentials. U.K. leave, free air passages and insurance. Kit allowance. Qualified candidates to whom replies will be sent write to Personnel Officer, 40, Park St., W.1. [0262

DIGITAL computers.—A vacancy exists for an electronics engineer in a rapidly expanding computer group which is concerned with the development of novel computing devices; qualifications required are H.N.C. or equivalent, together with experience in the design of pulse circuitry, preferably using transistors.—Apply A. V. Roe & Co., Ltd., Hanworth Lane, Chertsey, Surrey. [7930

SENIOR laboratory technician required at Norwood Technical College, Knight's Hill, S.E.27, in telecommunications and electronics dept., for upkeep of laboratories, ordering stock, keeping inventories, repair and maintenance of equipment and supervision of six technical staff; salary £490 rising to £607; further increments to £727 for specified qualifications.—Partics. and application forms (returnable within 14 days) from Secretary. (1071) [7935

DEPUTY chief engineer required by large television and radio rental organisation on south coast, essential qualifications are a thorough knowledge of up-to-date television practice with sound theoretical background also ability to handle staff and deal with forward planning; familiarity with communal-aerial technique would be advantageous; commencing salary in region of £750 per annum according to age and experience with very real prospects ahead.—Box 6619. [7944

MEDICAL Research Council require an electronic engineer at their Molecular Biology Research Unit, Cavendish Laboratory, Free School Lane, Cambridge, to construct electronic instruments needed in a wide field of scientific research connected with fundamental biological problems; Higher National Certificate or university degree desirable; previous experience essential; age 25-35; salary at a point £535-£920 per annum according to age and experience; superannuation after probationary period. —Apply to Dr. M. F. Perutz at above address. [7933

KELVIN & HUGHES, Ltd., Winchester Road, Basingstoke, Hants have vacancies in their Systems Laboratory for senior and junior Development Engineers for work on the design of small electro mechanical control systems; applicants should have a degree or Higher National Certificate in electrical engineering and preferably several years experience in the design and development of transistor amplifiers and servo mechanisms; the laboratories are housed in a modern building on the outskirts of Basingstoke; the company has a staff pension scheme and housing accommodation will be made available to suitable applicants.—Applications should be made in writing, giving full details of qualifications, age, experience, etc., and addressed to The Personnel Manager. [7963

POST OFFICE TYPE LINE EQUIPMENT

POWER SUPPLY RECTIFIERS for Telegraph Systems, various types.
TELEPRINTERS: Perforators, Auto Transmitters.
SUPPRESSION FILTERS, Telegraph Relays, MC Capacitors and all manner of teleprinter spares.
LINE EQUALIZER UNITS: Attenuators, By-Pass Filters, Recording Bridges, Distortion Testers, Spark-Gap Protectors.
SWITCHBOARDS and spare parts, including Privacy Desk Tests.
CARRIER TERMINALS and Repeaters, Speech + Duplex, 1 + 1, 1 + 3 and 1 + 4, Diversity Combining Units and all manner of spares.
FREQUENCY FILTERS, Coils Inductance, Repeating, Retardation and Hybrid Transformers and close tolerance capacitors.

LOW POWER RADIO STATIONS (Ground Use)

COLLINS 18Q SERIES, 1½ to 12 Mc/s. RF Output 25 watts. Power Units for 12 v., 24 v., 115 v. D.C. and 115 v. and 230 v. A.C.
WIRELESS SET No. 19. 2-8 Mc/s. and 235 Mc/s., all ancillary equipment and RF Amplifier No. 2, Mk. 2.
WIRELESS SET No. 31. Manpack Walkie-Talkie, 40-48 Mc/s.
WIRELESS SET No. 62. Lightweight Communications Set, 1½-10 Mc/s.
WIRELESS SET No. 88. Manpack or Truck Walkie-Talkie 40/42 Mc/s., 4 channel.
AN/GRC SERIES. Sets and spares available.

LOW POWER RADIO STATIONS (Airborne Use)

SCR-522. 4-channel, 100/156 Mc/s., complete with all operating and test equipment.
AN/ARC-1. 20-channel, 100/156 Mc/s.
TR1934, 1935 AND 1936 Series Equipment, Sub-Units available.
RADIO COMPASS SCR-269G. All ancillaries and spares stocked in large quantities.
COMPONENTS: Capacitors, variable and fixed up to 2 mfd. at 10,000 volts. Transformers Heavy Duty, Rectifier various, Carbon brushes, Magslip Hunters, Ball races, Potentiometers, Test Meters.

R. GILFILLAN & CO. LTD.
7, High Street, WORTHING, Sussex.
Tel.: WORTHING 8719 and 30181.
Cables: "GILL WORTHING" Codes: "BENTLEY'S 2nd"

The NEW

EDDYSTONE '870' RECEIVER

PRICE — **£34.16.0** *(inc. P.Tax)*

Efficient broadcast reception on short, medium and long waves. A Semi-portable AC/DC set equally suitable for cabin or home use, offering Eddystone design and workmanship at a Reasonable Price.

In stock at :—

WEBB'S RADIO
14 SOHO STREET, LONDON, W.1
Telephone GERrard 2089

RADIO & ELECTRONIC ENGINEERS . . .

The MORSE CODE is still, and always will be, the basic Code for individual Signalling, whether on visual or telecommunication circuits. So add this simple and interesting subject to your qualifications. Apart from the pleasure derived from this extra knowledge, it counts for much when a step up the ladder is under consideration. *Write for the CANDLER BOOK OF FACTS and see for yourself how fascinating the Candler method of teaching the Morse Code will prove.*

CANDLER SYSTEM CO.
(56W) 52b ABINGDON ROAD, LONDON, W.8
Candler System Co., Denver, Colorado, U.S.A.

MICRO SWITCHES

BURGESS BRAND NEW MINISTRY RELEASE

MK. 4 BR METAL BODY UNIVERSAL CONTACT A.M. Ref. 5G/4098

78/- PER DOZ. **£25** PER 100 (min. quantity)

Compare this remarkable almost half-price offer with manufacturers' prices.

SPECIAL OFFER

AERIAL MASTS

R.A.F. TYPE 50

36ft. HIGH

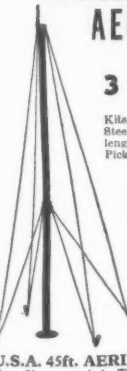

Kits comprise—9 2in. dia. Tubular Steel (Copper Plated) Sections of 4ft. length, top-section and base. Pickets, Guys and Fittings.

YOU can purchase this normally expensive MAST for a fraction of its cost, i.e.,

£8.10.0 ONLY (Carr. 15/6)

Please add £1 for (returnable) wooden carrying case.

The MAST is particularly suitable to take aerials for Tx., Rx., F.M. and T.V. (especially COMMERCIAL), and has many other uses. Extra 4ft. sections can be supplied at 11/6 per section.

U.S.A. 45ft. AERIAL MAST (10 sections 4ft. 6in. × 2in., guys etc.). This entirely new and complete set in canvas carrying bag £15/10/- each, carr. 17/6 or 2 sets with additional low and high frequency antenna £30 pair. Carr. extra.

ARMY TYPE 32FT. MASTS similar to above but 10 lin. screw-sections, suitable for permanent lightweight installation. Kit in canvas bag, £5/10/-, carriage 12/6.

TELEPHONE SETS

Ex-Govt. "DON Mk. V"

Currently used by Civil Defence

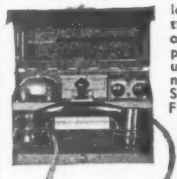

Ideal between 2 or more positions up to five miles. STORE, FACTORY AND OFFICE; FARM BUILDINGS; GARDEN SHED and HOUSE, 2 sets in individual carrying cases, complete with **long life batteries, bells, buzzer and 100 ft. telephone cable.**

£5.11.0 per pair. Carr. (G.B.) 9/6.

Magneto for use with above can be supplied at 15/6 extra.

D3 STRANDED TELEPHONE CABLE, NEW! mile drum, 85/-, carr. 17/6.

MINIATURE SEALED

RELAYS

SIEMENS TYPE High Speed Single change-over

96E, 1,700Ω + 1,700Ω	25/-
96D. 500Ω + 500Ω	22/6
96C. 145Ω + 145Ω	19/6
96B. 50Ω + 50Ω	17/6
96A. 2.2Ω + 2.2Ω	15/6
S.T.C. Types	
2,700Ω 2-pole change-over 4184 GE	21/6
700Ω 2-pole change-over 4184 GD	19/6
700Ω single heavy-duty make 4186 ED	18/6

SPECIAL QUOTATIONS FOR LARGER QUANTITIES

Quantity and Export enquiries invited.

HATTER & DAVIS (RELAYS) LTD.

2, IRONGATE WHARF ROAD, PRAED ST., LONDON, W.2

PAD 2231/2/3

SITUATIONS VACANT

SENIOR audio engineer required for development of high fidelity and stereophonic equipment, including the design of loudspeaker enclosures, applicants must be conversant with electro-acoustics and possess several years' experience in the design of audio amplifiers and associated equipment; the position is permanent and offers outstanding prospects for advancement.—Please write, quoting Ref. No. E.1646, giving full particulars of experience and qualifications to the Personnel Manager, Ferguson Radio Corporation, Ltd., Gt. Cambridge Rd., Enfield. [7943

COMPUTERS. A vacancy exists in an expanding and progressive Computer Group for a Senior Engineer to take charge of a circuit development section. The work is concerned with the application of transistors to new types of basic circuit elements which are required for use in novel types of computers at present under development. Qualifications required are a degree, H.N.C. or equivalent, with several years experience in digital, and preferably analogue, computing, together with a sound understanding of transistors and switching circuits.—Apply: A. V. Roe & Co. Ltd., Hanworth Lane, Chertsey, Surrey. [7966

AEON LABORATORIES have two interesting vacancies for technical assistants; one post will be concerned with the calibration of distributed delay cable; the other will include service of electron microscopes, construction of stabilised power supplies and work on vacuum systems; both posts call for men with considerable experience in experimental work; ability to use machine tools desirable; experience in the above specialised fields not essential; qualifications to O.N.C. standard; good working conditions, 5-day week; pension scheme.—Apply Aeon Laboratories, Beech Hill, Engiefield Green, Egham, Surrey. [7951

RANK CINTEL, Ltd., have a vacancy for a Junior Development Engineer to carry out development work on interesting projects in the electronics field; minimum qualification O.N.C. or C. & G. Inter. Cert. in Telecommunications; energetic and intelligent man capable of working with a minimum of supervision on electronic circuit development; laboratory experience essential; 5-day week; pension fund; canteen; 1 min. Bus and Train services.—Write, with full particulars of age, experience, qualifications and salary required, to Rank Cintel, Ltd., Worsley Bridge Road, Lower Sydenham, S.E.26. [7960

MINISTRY OF TRANSPORT & CIVIL AVIATION requires electrical engineers (Assistant Signals Officers) for aviation telecommunications and electronic navigational aids. Min. age 23, 1st or 2nd class degree in physics or engineering, or A.M.I.E.E. or A.F.R.Ae.S. (candidates with parts I, II and III of A.M.I.E.E. or parts I and II of A.F.R.Ae.S. or equivalent, or of very high professional attainment without these qualifications, considered). Salary £665 (age 23) to £1,085 (age 34). Max. £1,250. Slightly lower outside London and for women. 5-day week.—Further details and forms from M.L.N.S., Technical and Scientific Register (K), 26, King St., London, S.W.1, quoting D.129/8A. [7968

ASSISTANT engineer grade II required by East Africa High Commission Directorate of Civil Aviation on probation for pensionable employment. Gross salary according to age and qualifications up to £1,173 a year in scale £813 rising to £1,341 a year. Outfit allowance £30. Free passages. Liberal leave on full salary after each tour 30-36 months. Candidates, who should hold at least two second year and preferably one third year C. & G. Certs. in Telecoms. Principles or Radio, must have had at least three years' experience in erection and maintenance of ground station transmitters, radio and radar navigational aids and aerial systems. Up to date knowledge of workshop practice essential and a knowledge of teleprinter and perforator equipment or diesel electric power plant maintenance would be an advantage.—Write to the Crown Agents, 4, Millbank, London, S.W.1. State age, name in block letters, full qualifications and experience and quote M2C/49960/WF. [7981

SITUATIONS WANTED

SCIENTIFIC glass blower technician, age 34, 20 yrs. exp. in scientific, high vacuum, electronic and recon. cathode ray tube work.—Box 6923. [7965

TECHNICAL TRAINING

LEARN it as you do it—we provide practical equipment combined with instruction in radio, television, electricity, mechanics, chemistry, photography, etc.—Write for full details to E.M.I. Institutes, Dept. WW47, London, W.4. [0006

CITY and Guilds (Electrical, etc.) on "No Pass—No Fee" terms; over 95% successes; for full details of modern courses in all branches of electrical technology send for our 144-page handbook, free and post free.—B.I.E.T. (Dept. 388A) 29, Wright's Lane, London, W.8. [0017

TUITION

BATTERSEA COLLEGE OF TECHNOLOGY.

PHYSICS Department.

APPLICATIONS are invited for enrolment for the courses in Microwave Physics beginning on 29th September, 1958. Suitably qualified students may proceed to the M.Sc. degree of the University of London or the Post-graduate Diploma of the College. For further details apply Head of Department. [7975

CABINETS

FOR ANY EQUIPMENT—CABINETS TO YOUR—SPECIFICATION

THE BUREAU

This popular bureau cabinet is veneered with the finest selected Walnut and beautifully polished in a medium shade. Designed to accommodate almost any of the many units we have available and to give generous storage compartments.

WALNUT £16.16.0
NATURAL OAK £18.18.0

THE SERENADE

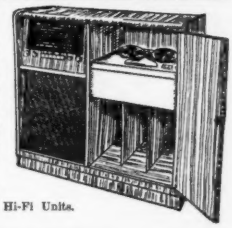

Veneered with finest selected walnut, beautifully polished to a medium shade; this attractive cabinet has generous storage space, with board sliding out smoothly on metal rollers. This cabinet can be fitted with any of the latest Hi-Fi Units.

£12.19.6

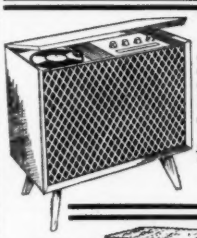

THE CONTEMPORARY

This beautifully designed Contemporary Cabinet can be supplied in Oak, Walnut or Mahogany Veneer and has a waxed semi-matt finish.

This cabinet can be fitted with any of the latest Hi-Fi Units.

£10.15.0

THE CONTINENTAL

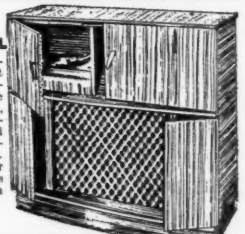

This elegant Cabinet is the latest in our range designed in the continental style, solidly constructed and finished in selected mahogany veneers. (Dark, medium or light, high gloss or satin finish available.)

£29.10.0

THE REGENT

This superb cabinet can accommodate almost any combination of Radio-Feeder Unit, Amplifier Control Unit, Motor Unit and Loudspeaker System. There is ample storage space. Available in finest selected walnut or mahogany veneer and polished. Has a pneumatic lid stay and ball-bearing castors.

£22.10.0

Send for the New illustrated equipment catalogue and booklet showing full range of cabinets etc., all available on easy terms.

LEWIS RADIO

120 GREEN LANES, (Dept. W88)
PALMERS GREEN LONDON N.13.
(Near the Cock Tavern)
Telephone: BOWes Park 1155/6

BAKERS 'Selhurst' RADIO

The ULTRA DE LUXE

20-20000 c/s

12"

20W

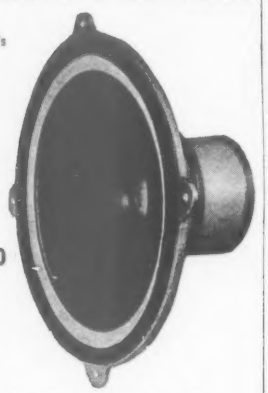

£15.15.0

For full range listening

Sales and Demonstration offices:

JOHN LIONNET & CO.

17, CHARING CROSS ROAD, LONDON, W.C.2. TRAfalgar 5575

MEGAOAKS FROM MICROACORNS GROW!

Many "Oaks" which today use our popular Type RXX-26 Benders, started as "Acorns" with our light Type RO-20.

No doubt it helped them to grow.

In June, we showed you our New Type RZ-26 tool, developed for the "Oaks."

NEXT MONTH, we will show you something new, specially for the "Acorns."

Be patient—a month soon passes.

For 6 page Folder write to:—

A. A. TOOLS (W)

197a Whiteacre Rd., Ashton-u-Lyne

TELETRON SUPER INDUCTOR COILS

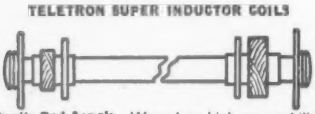

Ferrite Rod Aerials. Wound on high permeability Ferroxcube rod, Medium wave 8/9, Dual wave 12/9

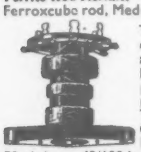

Type HAX. Selective crystal diode coil for tape and quality amplifiers, MW 3/-, LW 3/6. Dual wave TRF coils, matched pairs (as illustrated) 7/- pair. Type S.S.O. Supersonic Tape Osc. coil, provides 6.3 v. 3 a. RF for pre-amp heater. Eliminates induced 50 c/s hum, 40/100 kc, 15/- ea. Transistor coils, etc. Available from leading stockists. Stamp for complete data and circuits.

THE TELETRON CO. LTD.,
266, Nightingale Rd., London, N.9. How 2527

SITUATIONS VACANT

LABORATORY technician with experience of electronics required in the Electrical Engineering Department, University of Leeds; initial salary according to qualifications and experience.—Applications should be made in writing to Professor G. W. Carter, from whom further particulars may be obtained. [7939

COMPUTERS; in our expanding Computer Laboratory we have a vacancy for a Junior Engineer with O.N.C. or equivalent, who is keen to assist in the development of novel computing devices; some experience of analogue or digital computers and transistors would be an advantage.—Apply A. V. Roe & Co., Ltd., Hanworth Lane, Chertsey, Surrey. [7959

EXPANDING company specialising in electrical fire detectors and alarms seeks competent engineer with electronic or telephonic background to undertake development work. Must be able to work with minimum supervision. Good salary for right man.—Apply in writing, stating age, qualifications, experience and salary required, to Box No. 6974. [7970

TELEVISION Engineer required by old-established dealers with leading agencies; must be to R.T.E.B. and C. & G. standards; 44-hr week; accommodation available, new s/d house, summer holidays, with pay granted. —Write, stating experience and salary required, to: Wycombe Electrical Supplies, Ltd., 51-52, Oxford St., High Wycombe, Bucks. [7890

OVERSEAS.—Oil Exploration Company with world-wide seismic parties offers permanent career to electronic technicians; maintaining and operating field equipment; men prepared to accept responsibility and to live in camp conditions; academic qualifications to H.N.C. or equivalent or genuine practical experience to this standard; liberal home leave.—Box No. 6478. [0351

ELECTRONICS: Electronic Instruments, Ltd., of Lower Mortlake Rd., Richmond, have vacancies for junior and semi-senior engineers for instrument final testing. These are staff positions offering interesting and varied jobs with a bright future in this rapidly expanding Company. 5-day week, pension scheme. —Apply to the Company, giving qualifications and quoting reference TE/WW5M. [0126

RADIO Technicians required by International Aeradio Ltd. for overseas service. Permanent and pensionable posts. Normally tax-free, inclusive salary in local currency varying with location, and additional marriage and child differentials. U.K. leave, free air passages and insurance. Kit allowance. Qualified candidates to whom replies will be sent write to Personnel Officer, 40, Park St., W.1. [0262

DIGITAL computers.—A vacancy exists for an electronics engineer in a rapidly expanding computer group which is concerned with the development of novel computing devices; qualifications required are H.N.C. or equivalent, together with experience in the design of pulse circuitry, preferably using transistors.—Apply A. V. Roe & Co., Ltd., Hanworth Lane, Chertsey, Surrey. [7930

SENIOR laboratory technician required at Norwood Technical College, Knight's Hill, S.E.27, in telecommunications and electronics dept., for upkeep of laboratories, ordering stock, keeping inventories, repair and maintenance of equipment and supervision of six technical staff; salary £490 rising £607; further increments to £727 for specified qualifications.—Partics. and application forms (returnable within 14 days) from Secretary. (1071) [7935

DEPUTY chief engineer required by large television and radio rental organisation on south coast, essential qualifications are a thorough knowledge of up-to-date television practice with sound theoretical background also ability to handle staff and deal with forward planning; familiarity with communal-aerial technique would be advantageous; commencing salary in region of £750 per annum according to age and experience with very real prospects ahead.—Box 6619. [7944

MEDICAL Research Council require an electronic engineer at their Molecular Biology Research Unit, Cavendish Laboratory, Free School Lane, Cambridge, to construct electronic instruments needed in a wide field of scientific research connected with fundamental biological problems; Higher National Certificate or university degree desirable; previous experience essential; age 25-35; salary at a point £535-£920 per annum according to age and experience; superannuation after probationary period. —Apply to Dr. M. F. Perutz at above address. [7933

KELVIN & HUGHES, Ltd., Winchester Road, Basingstoke, Hants have vacancies in their Systems Laboratory for senior and junior Development Engineers for work on the design of small electro mechanical control systems; applicants should have a degree or Higher National Certificate in electrical engineering and preferably several years experience in the design and development of transistor amplifiers and servo mechanisms; the laboratories are housed in a modern building on the outskirts of Basingstoke; the company has a staff pension scheme and housing accommodation will be made available to suitable applicants.—Applications should be made in writing, giving full details of qualifications, age, experience, etc., and addressed to The Personnel Manager. [7963

POST OFFICE TYPE LINE EQUIPMENT

POWER SUPPLY RECTIFIERS for Telegraph Systems, various types.
TELEPRINTERS: Perforators, Auto Transmitters.
SUPPRESSION FILTERS, Telegraph Relays, MC Capacitors and all manner of teleprinter spares.
LINE EQUALIZER UNITS: Attenuators, By-Pass Filters, Recording Bridges, Distortion Testers, Spark-Gap Protectors.
SWITCHBOARDS and spare parts, including Privacy Desk Tests.
CARRIER TERMINALS and Repeaters, Speech + Duplex, 1 + 1, 1 + 3 and 1 + 4, Diversity Combining Units and all manner of spares.
FREQUENCY FILTERS, Coils Inductance, Repeating, Retardation and Hybrid Transformers and close tolerance capacitors.

LOW POWER RADIO STATIONS (Ground Use)

COLLINS 18Q SERIES, 1½ to 12 Mc/s. RF Output 25 watts. Power Units for 12 v., 24 v., 115 v. D.C. and 115 v. and 230 v. A.C.
WIRELESS SET No. 19. 2-8 Mc/s. and 235 Mc/s., all ancillary equipment and RF Amplifier No. 2, Mk. 2.
WIRELESS SET No. 31. Manpack Walkie-Talkie, 40-48 Mc/s.
WIRELESS SET No. 62. Lightweight Communications Set, 1½-10 Mc/s.
WIRELESS SET No. 83. Manpack or Truck Walkie-Talkie 40/42 Mc/s., 4 channel.
AN/GRC SERIES. Sets and spares available.

LOW POWER RADIO STATIONS (Airborne Use)

SCR-522. 4-channel, 100/156 Mc/s., complete with all operating and test equipment.
AN/ARC-1. 20-channel, 100/156 Mc/s.
TR1934, 1935 AND 1936 Series Equipment, Sub-Units available.
RADIO COMPASS SCR-269G. All ancillaries and spares stocked in large quantities.
COMPONENTS: Capacitors, variable and fixed up to 2 mfd. at 10,000 volts. Transformers Heavy Duty, Rectifier various, Carbon brushes, Magslip Hunters, Ball races, Potentiometers, Test Meters.

R. GILFILLAN & CO. LTD.
7, High Street, WORTHING, Sussex.
Tel.: WORTHING 8719 and 30181.
Cables: "GILL WORTHING" Codes: "BENTLEY'S 2nd"

The NEW

EDDYSTONE '870' RECEIVER

PRICE — **£34.16.0** *(inc. P.Tax)*

Efficient broadcast reception on short, medium and long waves. A Semi-portable AC/DC set equally suitable for cabin or home use, offering Eddystone design and workmanship at a Reasonable Price.

In stock at :—

WEBB'S RADIO
14 SOHO STREET, LONDON, W.1
Telephone GERrard 2089

RADIO & ELECTRONIC ENGINEERS . . .

The MORSE CODE is still, and always will be, the basic Code for individual Signalling, whether on visual or telecommunication circuits. So add this simple and interesting subject to your qualifications. Apart from the pleasure derived from this extra knowledge, it counts for much when a step up the ladder is under consideration. *Write for the CANDLER BOOK OF FACTS and see for yourself how fascinating the Candler method of teaching the Morse Code will prove.*

CANDLER SYSTEM CO.
(56W) 52b ABINGDON ROAD, LONDON, W.8
Candler System Co., Denver, Colorado, U.S.A.

MICRO SWITCHES

BURGESS BRAND NEW MINISTRY RELEASE

MK. 4 BR METAL BODY UNIVERSAL CONTACT A.M. Ref. 5C/4098

78/- PER DOZ. **£25** PER 100 (min. quantity)

Compare this remarkable almost half-price offer with manufacturers' prices.

SPECIAL OFFER

AERIAL MASTS

R.A.F. TYPE 50

36ft. HIGH

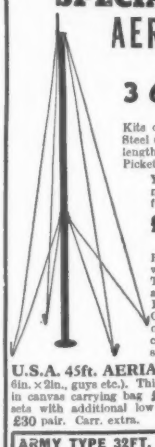

Kits comprise—9 2in. dia. Tubular Steel (Copper Plated) Sections of 4ft. length, top-section and base. Pickets, Guys and Fittings.

YOU can purchase this normally expensive MAST for a fraction of its cost, i.e.,

£8.10.0 ONLY (Carr. 15/6)

Please add £1 for (returnable) wooden carrying case.

The MAST is particularly suitable to take aerials for Tx., Rx., F.M. and T.V. (especially COMMERCIAL), and has many other uses. Extra 4ft. sections can be supplied at **11/6** per section.

U.S.A. 45ft. AERIAL MAST (10 sections 4ft. 6in. × 2in., guys etc.). This entirely new and complete set in canvas carrying bag **£15/10/-** each, carr. 17/6 or 2 sets with additional low and high frequency antenna **£30** pair. Carr. extra.

ARMY TYPE 32FT. MASTS similar to above but 10 lin. screw-sections, suitable for permanent lightweight installation. Kit in canvas bag, **£5/10/-**, carriage 12/6.

TELEPHONE SETS

Ex-Govt. "DON Mk. V"

Currently used by Civil Defence

Ideal between 2 or more positions up to five miles. STORE, FACTORY AND OFFICE; FARM BUILDINGS; GARDEN SHED and HOUSE. 2 sets in individual carrying cases, complete with **long life batteries, bells, buzzer and 100 ft. telephone cable.**

£5.11.0 per pair. Carr. (G.B.) 9/6.

Magneto for use with above can be supplied at **15/6** extra.

D3 STRANDED TELEPHONE CABLE, NEW 1 mile drum, 85/-, carr. 17/6.

MINIATURE SEALED

RELAYS

SIEMENS TYPE High Speed Single change-over

96E, 1,700Ω + 1,700Ω	25/-
96D. 500Ω + 500Ω	22/6
96C. 145Ω + 145Ω	19/6
96B. 50Ω + 50Ω	17/6
96A. 2.2Ω + 2.2Ω	15/6
S.T.C. Types	
2,700Ω 2-pole change-over 4184 GE	21/6
700Ω 2-pole change-over 4184 GD	19/6
700Ω single heavy-duty make 4186 ED	18/6

SPECIAL QUOTATIONS FOR LARGER QUANTITIES

Quantity and Export enquiries invited.

HATTER & DAVIS (RELAYS) LTD.

2, IRONGATE WHARF ROAD, PRAED ST., LONDON, W.2

PAD 2231/2/3

SITUATIONS VACANT

SENIOR audio engineer required for development of high fidelity and stereophonic equipment, including the design of loudspeaker enclosures, applicants must be conversant with electro-acoustics and possess several years' experience in the design of audio amplifiers and associated equipment; the position is permanent and offers outstanding prospects for advancement.—Please write, quoting Ref. No. E.1646, giving full particulars of experience and qualifications to the Personnel Manager, Ferguson Radio Corporation, Ltd., Gt. Cambridge Rd., Enfield. [7943

COMPUTERS. A vacancy exists in an expanding and progressive Computer Group for a Senior Engineer to take charge of a circuit development section. The work is concerned with the application of transistors to new types of basic circuit elements which are required for use in novel types of computers at present under development. Qualifications required are a degree, H.N.C. or equivalent, with several years experience in digital, and preferably analogue, computing, together with a sound understanding of transistors and switching circuits.—Apply: A. V. Roe & Co., Ltd., Hanworth Lane, Chertsey, Surrey. [7966

AEON LABORATORIES have two interesting vacancies for technical assistants; one post will be concerned with the calibration of distributed delay cable; the other will include service of electron microscopes, construction of stabilised power supplies and work on vacuum systems; both posts call for men with considerable experience in experimental work; ability to use machine tools desirable; experience in the above specialised fields not essential; qualifications to O.N.C. standard; good working conditions, 5-day week; pension scheme.—Apply Aeon Laboratories, Beech Hill, Englefield Green, Egham, Surrey. [7951

RANK CINTEL, Ltd., have a vacancy for a Junior Development Engineer to carry out development work on interesting projects in the electronics field; minimum qualification O.N.C. or C. & G. Inter. Cert. in Telecommunications; energetic and intelligent man capable of working with a minimum of supervision on electronic circuit development; laboratory experience essential; 5-day week; pension fund; canteen; 1 min. Bus and Train services.—Write, with full particulars of age, experience, qualifications and salary required, to Rank Cintel, Ltd., Worsley Bridge Road, Lower Sydenham, S.E.26. [7960

MINISTRY OF TRANSPORT & CIVIL AVIATION requires electrical engineers (Assistant Signals Officers) for aviation telecommunications and electronic navigational aids. Min. age 23, 1st or 2nd class degree in physics or engineering, or A.M.I.E.E. or A.F.R.Ae.S. (candidates with parts I, II and III of A.M.I.E.E. or parts I and II of A.F.R.Ae.S. or equivalent, or of very high professional attainment without these qualifications, considered). Salary £665 (age 23) to £1,085 (age 34). Max. £1,250. Slightly lower outside London and for women. 5-day week.—Further details and forms from M.L.N.S., Technical and Scientific Register (K), 26, King St., London, S.W.1, quoting D.129/8A. [7968

ASSISTANT engineer grade II required by East Africa High Commission Directorate of Civil Aviation on probation for pensionable employment. Gross salary according to age and qualifications up to £1,173 a year in scale £813 rising to £1,341 a year. Outfit allowance £30. Free passages. Liberal leave on full salary after each tour 30-36 months. Candidates, who should hold at least two second year and preferably one third year C. & G. Certs. in Telecoms. Principles or Radio, must have had at least three years' experience in erection and maintenance of ground station transmitters, radio and radar navigational aids and aerial systems. Up to date knowledge of workshop practice essential and a knowledge of teleprinter and perforator equipment or diesel electric power plant maintenance would be an advantage.—Write to the Crown Agents, 4, Millbank, London, S.W.1. State age, name in block letters, full qualifications and experience and quote M2C/49960/WF. [7981

SITUATIONS WANTED

SCIENTIFIC glass blower technician, age 34, 20 yrs. exp. in scientific, high vacuum, electronic and recon. cathode ray tube work.—Box 6923. [7965

TECHNICAL TRAINING

LEARN it as you do it—we provide practical equipment combined with instruction in radio, television, electricity, mechanics, chemistry, photography, etc.—Write for full details to E.M.I. Institutes, Dept. WW47, London, W.4. [0006

CITY and Guilds (Electrical, etc.) on "No Pass—No Fee" terms; over 95% successes; for full details of modern courses in all branches of electrical technology send for our 144-page handbook, free and post free.—B.I.E.T. (Dept. 388A) 29, Wright's Lane, London, W.8. [0017

TUITION

BATTERSEA COLLEGE OF TECHNOLOGY. PHYSICS Department.

APPLICATIONS are invited for enrolment for the courses in Microwave Physics beginning on 29th September, 1958. Suitably qualified students may proceed to the M.Sc. degree of the University of London or the Post-graduate Diploma of the College. For further details apply Head of Department. [7975

CABINETS

FOR ANY EQUIPMENT—CABINETS TO YOUR—SPECIFICATION

THE BUREAU

This popular bureau cabinet is veneered with the finest selected Walnut and beautifully polished in a medium shade. Designed to accommodate almost any of the many units we have available and to give generous storage compartments.

WALNUT £16.10.0
NATURAL OAK £18.18.0

THE SERENADE

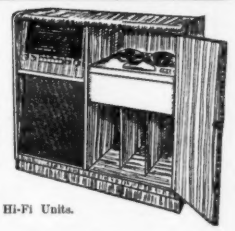

Veneered with finest selected walnut, beautifully polished to a medium shade; this attractive cabinet has generous storage space, with board sliding out smoothly on metal rollers. This cabinet can be fitted with any of the latest Hi-Fi Units.

£12.19.6

THE CONTEMPORARY

This beautifully designed Contemporary Cabinet can be supplied in Oak, Walnut or Mahogany Veneer and has a waxed semi-matt finish.

This cabinet can be fitted with any of the latest Hi-Fi Units.

£10.15.0

THE CONTINENTAL

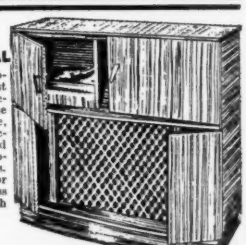

This elegant Cabinet is the latest in our range designed in the continental style, solidly constructed and finished in selected mahogany veneers. (Dark, medium or light, high gloss or satin finish available.)

£29.10.0

THE REGENT

This superb cabinet can accommodate almost any combination of Radio-Feeder Unit, Amplifier Control Unit, Motor Unit and Loudspeaker System. There is ample storage space. Available in finest selected walnut or mahogany veneer and polished. Has a pneumatic lid stay and ball-bearing castors.

£22.10.0

Send for the New illustrated equipment catalogue and booklet showing full range of cabinets etc., all available on easy terms.

LEWIS RADIO

120 GREEN LANES, (Dept. W88)
PALMERS GREEN LONDON N.13.
(Near the Cock Tavern)
Telephone: BOWes Park 1155/6

METERS

All types
Any make

Single and Multi-range repaired and recalibrated

Meters 2" to 6" supplied from stock.

Scaled to requirements.

E.I.R. INSTRUMENTS LTD.
329 Kilburn Lane, London, W.9
Tel.: LADbroke 4168

RADIO & TELEVISION COMPONENTS

We operate a prompt and efficient MAIL ORDER service.

3d. stamp (only) for catalogue.

James H. Martin & Co. Finsthwaite, Newby-Bridge, Ulverston, Lancashire.

NORTHERN RADIO SERVICES

are pleased to announce their new Symphony Stereophonic Amplifier, giving high quality results for only 19 gns. complete.

Also new Column Loudspeakers giving fantastic results on Stereo 20 gns. complete.

Complete Stereo Reproducer with Transcription Unit and two speakers, completely cabinetted, ready to play, £85.

11 Kings College Road, London, N.W.3
PRImrose 3314.

TANNOY
SOUND EQUIPMENT

Tells you what's going on clearly

WEST NORWOOD · S.E.27
Telephone: GIPsy Hill 1131 (7 lines)

Q.C.C.

LOW FREQUENCY QUARTZ CRYSTALS

Increased manufacturing facilities have enabled us to extend the frequency range of Q.C.C. Quartz Crystal Units in the low frequency direction. Units are now available in the frequency range from 1 kc. to 40 kc/s.

Bimorph, NT Cut, or 5 X Cut Flexural elements are used according to frequency, and prices are fully competitive.

Low frequency units for frequencies higher than 40 kc/s are covered by our standard range of 5 X Longitudinal Mode, CT Cut, and DT Cut crystals.

We can offer prompt deliveries, and a technical advisory service on circuitry and other problems is always at your service.

● *WHEN IT'S QUARTZ CRYSTALS THINK OF Q.C.C. FIRST.*

The QUARTZ CRYSTAL Co. Ltd.

Q.C.C. Works, Wellington Crescent, New Malden, Surrey.

Telephones: MALden 0334 & 2988

TUITION

PLYMOUTH AND DEVONPORT TECHNICAL COLLEGE, Tavistock Rd., Plymouth. RADIO Officers' Course.
THE next full-time course leading to the P.M.G. Certificates will commence in September, 1958.
APPLICATION for entry should be made as early as possible to the Principal, giving particulars of previous education.
ANDREW SCOTLAND,
CLERK to the Governors. [7945

FULL-TIME courses for P.M.G. Certificates. C.G.L.I. Telecommunications and Radar Maintenance Certificates.—Information from College of Technology, Hull. [0111

WIRELESS.—See the world as a radio officer in the Merchant Navy; short training period; low fees, scholarships, etc., available; boarding and day students; stamp for prospectus.—Wireless College, Colwyn Bay. [0018

T/V and Radio.—A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc., on "No Pass—No Fee" terms; over 95% successes; details of exams and home training courses in all branches of radio and T/V, write for 144-page handbook—free.—B.I.E.T. (Dept. 397A), 29, Wright's Lane, London, W.8. [0116

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, etc., on "No Pass—No Fee" terms, over 95% successes—or details of Exams and courses in all branches of Engineering, Building, etc., write for 144-page Handbook—Free: B.I.E.T. (Dept. 387B), 29, Wright's Lane, London, W.8. [0118

ALL examinations easier to pass by I.C.S. home-study methods. A.M.Brit.I.R.E., C. & G. Telecoms., P.M.G. Cert. in Wireless, Telegraphy, Radio and TV Servicing, etc.—Write for free prospectus: International Correspondence Schools, 71, Kingsway (Dept. CL. 42A), London, W.C.2. [0033

LEARN-AS-YOU-BUILD course in basic radio, electronic and electrical theory, with practical training, building a 4-valve receiver and superhet signal generator and multi-tester.—Write for free book: International Correspondence Schools, 71, Kingsway (Dept. CL42), London, W.C.2. [0350

TRAIN at home for a better position or a new hobby.—We offer comprehensive modern home tuition courses covering over 100 careers and hobbies; practical equipment supplied with many courses.—Write for free brochure, stating subject of interest, to E.M.I. Institutes, Dept. WW39, London, W.4. (Associated with H.M.V.) [0180

FREE!—Brochure giving details of home study training in radio, television and all branches of electronics; courses for the hobby enthusiast, or for those aiming at the A.M.Brit.I.R.E., City and Guilds, R.T.E.B., and other professional examinations; train with the college operated by Britain's largest electronics organisation; moderate fees.—Write to E.M.I. Institutes, Dept. WW28, London, W.4.

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative; moderate fees to a limited number of students only; syllabus of instructional text is free; the Practical Radio Engineer journal, sample copy 2/-; 6.000 alignment peaks for superhets, 5/9; membership and entry conditions booklet 1/-, all post free, from the Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8. [0088

BUSINESS & PROPERTY

RADIO and television business, S.W.20, turnover £8,000 p.a., leading agencies, good service trade; price £1,500 s.a.v.—Apply Marcus Leaver & Co., 36, Bruton St., W.1. Mayfair 4266. [7967

HOTELS AND ACCOMMODATION

RADIO SHOW. When visiting London for the Radio Show, or at any other time, stay at Hans House. Private suites comprising bedroom, sitting-room, bathroom and telephone, from 2½ gns. daily, 15 gns. weekly, for apartments and breakfasts.—Write Hans House, 16, Hans Road, London, S.W.3. Tel. Kensington 3764. [7845

BOOKS, INSTRUCTIONS, ETC.

"RADIO Interference Supression: As Applied to Radio and Television Reception." By G. L. Stephens, A.M.I.E.E. 2nd Ed. An up-to-date guide to the various methods of suppressing electrical interference with radio and television reception. Many practical applications are given, particular attention being paid to the problem of interference at television frequencies. Other chapters deal with the design and choice of suppressor components, methods of locating the source of interference, and suppression at the receiver itself. 10/6 net from all booksellers. By post 11/4 from Iliffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1.

"RADIO Laboratory Handbook." By M. G. Scroggie, B.Sc., M.I.E.E. This well-known practical work describing laboratory equipment and methods of operation has been entirely re-written and greatly enlarged. Among the subjects considered are layout and furnishing of premises, methods of measurements, sources of power and signal measurements. There is a comprehensive reference section and many photographs, diagrams, graphs and tables: 25/- net from all booksellers. By post 26/9 from Iliffe & Sons Ltd., Dorset House, Stamford Street, S.E.1.

TRANSFORMERS for MULLARD 510 AMPLIFIER

Fully Shrouded Upright Mounting. Fully Guaranteed, interleaved and Impregnated. T.56 300-0-300 v. 100 mA., 6.3 v. 2-a ct., 6.3 v. 1 a. 27/- P/P 2/6. T55 for 510 Amp. and Tuner 300-0-300 v. 120 mA., 6.3 v. 2.5 a. ct., 6.3 v. 2.5 a., 6.3 v. 1 a. 32/-. P/P 2/6. Primaries for above 240-220-200; 0-10 v 50 c/s. T44 Ultra-Linear Output Transformer 8,000 ohm. with 42% tappings for 510 Amp. 30/-. P/P 2/-
SPECIAL OFFER T44 and T55 59/-. P/P 3/6.
All carefully made to conform to specifications.
SOUTHERN TECHNICAL SUPPLIES
13 NORTH STREET, PORTSLADE SUSSEX
Tel.: HOVE 47223

Instrumentation at its best . . .

SIFAM ELECTRICAL INSTRUMENT CO. LTD.
LEIGH COURT - TORQUAY - Telephone 4547/8

Research Development Work Undertaken

Design and Prototype Development of Audio-Electro Devices and Equipment. Box No. 2336 *c/o "W. World"*

"Easco" INTER-COM & SOUND Advisors

BRIGHTON TERRACE. LONDON. S.W.9
'Phone: BRixton 4961
EASCO ELECTRICAL

ODDIE FASTENERS

Pat. 507249

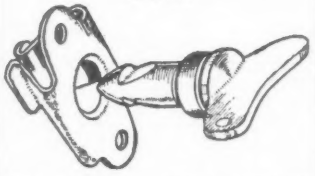

THE FASTENER WITH ENDLESS APPLICATIONS—SIMPLE—POSITIVE SELF-LOCKING. MADE IN A VARIETY OF TYPES AND SIZES. SPECIAL FASTENERS TO SUIT CUSTOMERS' REQUIREMENTS. WIDELY USED IN THE RADIO INDUSTRY.

Illustrated brochure and other information will gladly be sent on request.
DEPT. "W.W."

Oddie, Bradbury & Cull Ltd., Southampton
Tel.: 55883 Cables: Fasteners, Southampton

BOOKS, INSTRUCTIONS, ETC.

"THE Williamson Amplifier." This 15-watt amplifier has gained world-wide recognition on account of its remarkably low distortion. The issues of WIRELESS WORLD in which it was originally described have long since been out of print, and the present booklet, which reprints all the relevant articles from 1947 onwards, gives full details not only of the basic circuit and layout, but also of the ancillary circuits recommended by the designer for high-quality reproduction of record and radio programme; 3/6 net from all booksellers. By post 3/10 from Iliffe & Sons Ltd., Dorset House, Stamford St., S.E.1.

BOOKS, INSTRUCTIONS, ETC.

"WIRELESS Servicing Manual." By W. T. Cocking, M.I.E.E. This, the ninth edition of a standard work, which has come to be recognised as a reliable and comprehensive guide for amateur and professional alike, has been thoroughly revised and set in a larger and handier format. Essential testing apparatus is described and logical methods of deducing and remedying defects are explained. A completely new chapter on the servicing of frequency modulated V.H.F. receivers has been added: 17/6 from all booksellers. By post 18/8 from Iliffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1.

BOOKS, INSTRUCTIONS, ETC.

"RADIO Designer's Handbook." Editor: F. Langford-Smith, B.Sc., B.E., Senior Member I.R.E. (U.S.A.), A.M.I.E. (Aust.). A comprehensive reference book, the work of 10 authors and 23 collaborating engineers, containing a vast amount of data in a readily accessible form; the book is intended especially for those interested in the design and application of radio receivers or audio amplifiers. Television, radio transmission and industrial electronics have been excluded in order to limit the work to a reasonable size; 42/- net from all booksellers. By post 44/3 from Iliffe & Sons Ltd., Dorset House, Stamford St., S.E.1.

10 WATT TRANSISTOR AMPLIFIERS

Type 1MAI - For any type of input - £30
Type 2MAI - For mic input only - - £18

Also

TRANSISTOR TESTERS

THE LAVENTA SOUND CO.,
24 Arden Rd., Birchfields, Birmingham, 6.

WANTED

SPEECH AMPLIFIERS

BC614D £10.0.0
BC614E £15.0.0

Must be in good condition

P.C.A. RADIO
BEAVOR LANE
HAMMERSMITH, W.6
RIV 8006

NEUCLEX CO. LTD.
for your Prototype Units. Designed and manufactured to specification.
INFRA RED DEVICES and **TRANSISTORISATION** our speciality.
44 Oak End Way, Gerrards Cross, Bucks
Tel. 3296

STEREO AMPLIFIERS (Gram. or Tape)
Stereo pick-ups, Tape Recording Amplifiers, Transistor Mixers, Pre-amps, etc.
HARDING ELECTRONICS
120A, Mora Rd, Cricklewood, London, N.W.2
Phone: GLA 1770.

NEST OF DRAWERS
Overall: 6¼in. wide × 5in. deep × 10¼in. high. 12 drawers, each 3in. wide × 4¼in. deep × 1¼in. high. Useful storage for radio components, nuts, bolts and other small parts. Sheet steel 20/-. P. & P. 3/-.

HARMSWORTH, TOWNLEY & CO.
2 JORDAN STREET, MANCHESTER 15

A MAST PROBLEM? WRITE TO **Skymasts**
BEADON GARAGE BEADON ROAD LONDON W6 Telephone RIVerside 1124 and 7878

CLASSIFIED ADVERTISEMENTS

Use this Form for your Sales and Wants

To "Wireless World" Classified Advertisement Dept., Dorset House, Stamford Street, London, S.E.1

PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW

- **RATE: 7/- for TWO LINES. 3/6 every Additional Line. Average six words per line.**
- **Name and address to be included in charge if used in advertisement.**
- **Box No. Allow two words, plus 1/-.**
- **Cheques, etc., payable to Iliffe & Sons Ltd., and crossed "& Co."**
- **Press Day, Wednesday July 30th for September 1958 issue.**

NAME .....

ADDRESS .....

.....

			REMITTANCE VALUE.....ENCLOSED		

Please write in block letters with ball pen or pencil.

NUMBER OF INSERTIONS .....

INDEX TO ADVERTISERS

	Page
A.A. Tools	154
Abix (Metal Industries), Ltd.	54
Acoustical Mfg. Co., Ltd.	27
Adcola Products, Ltd.	36
Adler, B., & Sons (Radio), Ltd.	130
A.D.S. Relays, Ltd.	40
Advance Components, Ltd.	11, 145
Allan, Richard, Radio, Ltd.	44
Alpha Radio Supply Co., The	133
Amalgamated Wireless (Australasia), Ltd.	46
Amphenol, Ltd.	83
Amplex Appliances (Kent), Ltd.	126
Andec, Ltd.	88
Anders Electronics, Ltd.	81
Antiference, Ltd.	6
Appointments Vacant	142, 145, 146
Arcolectric Switches, Ltd.	78
Arden Eng. Co.	72
Ardente Acoustic Laboratories, Ltd.	80
Armstrong Wireless & Television Co., Ltd.	38, 151
Aspden, W.	152
Automatic Telephone & Electric Co., Ltd.	63
Aveley Electric, Ltd.	85
Avo, Ltd.	1
Baker's "Selhurst" Radio	154
Beamish, V.	140
Belclere Co.	66
Belling & Lee, Ltd.	101
Benson, W. A.	151
Berry, T. A. (Lodge Radio), Ltd.	146
Berry's (Short-Wave), Ltd.	68
Bestfriend Electrical Co., Ltd.	140
Birmingham Sound Reproducers, Ltd.	9, 106
Borough Polytechnic	142
Bradmatic, Ltd.	76
Britbond, Ltd.	43
Britain, Chas. (Radio), Ltd.	127
British Communications Corporation, Ltd.	17
British Institute of Engineering Technology	132, 138
British Insulated Callender's Cables, Ltd.	Cover ii
British Thomson-Houston Co., Ltd.	77
Brookes Crystals, Ltd.	62
Brown, S. G., Ltd.	72
Bulgin, A. F., & Co., Ltd.	Edit. 401
Bullers, Ltd.	50
Candler System Co.	154
Capital Radio	67
Central Electricity Board	146
Champion Products	147
Channel Electronic Industries, Ltd.	82
Chapman, C. T. (Reproducers), Ltd.	62
Ciba (A.R.L.), Ltd.	21
City Sale & Exchange, Ltd.	52
Clyne Radio, Ltd.	114, 115
Cossor Instruments, Ltd.	102
Cottage Laboratories, Ltd.	145
County Borough of Bolton	142
Coventry Radio	132
Daly (Condensers), Ltd.	44
Davies, A., & Co.	147
Davis, Jack (Relays), Ltd.	76
De Havilland Propellers, Ltd.	145
Delaney Gallay & Co., Ltd.	71
Denco (Clacton), Ltd.	60
Dependable Radio Supplies, Ltd.	132
Dependable Relay Co.	66
Direct T.V. Replacements	146
Dixon, L., & Co.	138
Dubilier Condenser Co. (1925), Ltd.	33
Duke & Co.	143
Dulci Co., Ltd., The	42
Duode Natural Reproducers	152
Dynatron Radio, Ltd.	81
Easco Electrical, Ltd.	156
Eddy's (N'tham), Ltd.	126
E.I.R. Instruments, Ltd.	156
E.K. Electronics	132
Electrical Instruments (H'ton), Ltd.	82
Electro-Acoustic Developments	138
Electro-Acoustic Industries, Ltd.	24
Electronic Precision Equipment	112, 113
Electronics (Fleet Street), Ltd.	135
Electronic Technical Service	75
Electronic Tubes, Ltd.	18
Electro-Winds, Ltd.	84
E.M.G. Handmade Gramophones, Ltd.	82
E.M.I. College	83, 110
E.M.I. Electronics, Ltd.	105
E.M.I. Institutes	65, 103, 108, 146
E.M.I. Sales & Service, Ltd.	49
English Electric Co., Ltd.	19, 142
English Electric Valve Co., Ltd.	6, 142
Enthoven Solders, Ltd.	42
Farnell Instruments Ltd.	73
Ferranti, Ltd.	16
Filmer, J. T.	140
Finsbury Trading Co.	136
Foyle, W. & G., Ltd	86
Fringevision, Ltd.	84
Garrard Eng. & Mfg. Co., Ltd., The	69
Gee Bros., Radio, Ltd.	141
General Electric Co., Ltd.	12, 39
Gilfillan, R., & Co., Ltd.	154
Gilson, R. F., Ltd.	152
Glaser, L., & Co.	140
Goodmans Industries, Ltd.	53
Govt. H.Q.	142
Grampian Reproducers, Ltd.	87
Gray, Arthur, Ltd.	78
Grayshaw Instruments	91
Hall Electric, Ltd.	29
Harney, L.	150
Harding Electronics	157
Harmsworth, Townley & Co.	89, 157
Harringay Photographic & Electrical Supplies, Ltd.	89
Harris Electronics (London), Ltd.	128
Harris, P.	150
Hatter & Davis, Ltd.	155
Henley's, W. T., Telegraph Works Co., Ltd.	147
Henry's (Radio), Ltd.	124, 125
Hewlett-Packard Co.	41
Hinchley Engineering Co., Ltd.	37
Hivac, Ltd.	85
Home Radio, Ltd.	89
H.P. Radio Services, Ltd.	60
Hunt, A. H. (Capacitators), Ltd	25
Hunton, Ltd.	40
Iliffe & Sons, Ltd.	32, 70, 86, 88, 90, 93, 144
Industrial Automation, Ltd.	146
Instruments Electrical Co.	147
International Correspondence Schools	91
Jackson Bros. (London), Ltd.	52
Jason Motor & Electronic Co.	92
Jeffery Transformer Co.	142
Kenroy, Ltd.	152
Keyswitch Co., The	80
Kimberley Eng. Co., Ltd	64
Kolectric, Ltd.	79
Lasky's Radio, Ltd.	118, 119
Laventa Sound Co.	157
Leak, H. J., & Co., Ltd.	111
Leevers-Rich Equipment, Ltd.	142
Lewis Radio Co.	72, 155
Light Soldering Developments, Ltd.	150
Linear Products, Ltd.	14
Lionnet, J., & Co.	154
Lockwood & Co. (Woodworkers), Ltd.	152
London Central Radio Stores	136
Long Playing Record Library	93
Lyons Radio, Ltd	126
Magnetic Devices, Ltd.	45
Mail Order Supply Co.	86
Marconi Instruments, Ltd.	51
Marconi's Wireless Telegraph Co., Ltd.	57, 104
Martin, J. E.	156
McMurdo Instruments Co., Ltd.	13, 54, 77
Microwave Instruments	142
Midland Instrument Co.	92
Mills, W.	91
Modern Book Co.	150
Modern Electrics, Ltd.	74
Modern Techniques	68
M.R. Supplies, Ltd.	60
M.S.S. Recording Co., Ltd.	84
Mullard, Ltd.	3, 15, 22, 23, 98
Multicore Solders, Ltd.	Cover iv
Multitone Electric Co., Ltd.	10
Murex, Ltd.	46
Neuclex Co., Ltd.	157
Newmarket Transistors, Ltd.	26
Northern Polytechnic	92, 140
Northern Radio Services	156
Oddie, Bradbury & Cull, Ltd.	156
Oryx Electrical Laboratories, Ltd.	38
Osmor Radio Products, Ltd.	88
Painton & Co., Ltd.	48
Partridge Transformers, Ltd.	149
P.C.A. Radio	58, 157
P.C. Radio	58
Peace, T. W.	136
Piezo Limited	90
Plasticable Ltd.	88
Post Radio Supplies	147
Premier Radio Co.	94, 95
Preston, A., & Sons	86
Proops Bros., Ltd.	139
Pye, Ltd.	47
Pye Telecommunications, Ltd.	96
Quartz Crystal Co., Ltd.	156
Radio & T.V. Components (Acton), Ltd.	128
Radio Clearance, Ltd.	130
Radio Component Specialists	131
Radio Exchange Co., The	90
Radio Experimental Products Co.	142
Radio Ham Shack, Ltd.	84
Radio Resistor, Ltd.	7
Radio Servicing Co.	62
Radio Supply Co. (Leeds), Ltd.	122, 123, 124
Radio Traders, Ltd.	134
Radiospares, Ltd.	83
Rank Cintel, Ltd.	5
Record Housing	64
Relda Radio, Ltd.	129
Reliance Manufacturing Co., Ltd.	75
Reproducers & Amplifiers, Ltd.	4
Rogers Development (Electronics), Ltd.	68
Rola-Celestion, Ltd.	59
Rollett, H., & Co., Ltd.	140
Runbaken	86
Salford Electrical Instruments, Ltd.	20
Samsons Surplus Stores	91
Sangamo-Weston, Ltd.	110
Savage Transformers, Ltd.	147
Service Trading Co.	137
Servo & Electronic Sales, Ltd.	140
Sherbourne Television Service	142
Siemens Edison-Swan, Ltd.	34, 35, 100, 107
Sifam Electrical Instrument Co., Ltd.	156
Simmonds, L. E., Ltd.	78
Skymasts	157
Smith, G. W. (Radio), Ltd.	116, 117
Smith, H. L., & Co., Ltd.	153
Smith, S., & Sons, Ltd.	146
Solartron Electronic Group, Ltd.	2
Sonomag, Ltd.	80
Southern Radio Supply, Ltd.	153
Southern Technical Supplies	156
Specialist Switches	74
Spencer-West, Ltd.	140
Stamford, A. L.	136
Standard Telephones & Cables, Ltd.	28, 99
Stern Radio, Ltd.	120, 121
Stewart Transformers, Ltd.	74
Sugden, A. R., & Co. (Engineers), Ltd.	36
Tannoy Products, Ltd.	156
Taylor Electrical, Ltd.	76
Technical Trading Co.	132
Telefusion (Eng.), Ltd.	56
Telegraph Condenser Co., Ltd.	Cover iii
Telequipment, Ltd	31
Tele-Radio (1943), Ltd.	138
Telerion Co., The	154
Trix Electrical Co., Ltd.	Edit. 399
T.R.S. Radio	134
Twickenham Technical College	146
Ultra Electric, Ltd.	30
Universal Book Co.	142
Vacwell Engineering Co., Ltd.	64
Valradio, Ltd.	70
Verdik Sales, Ltd.	152
V.E.S. Wholesale Services, Ltd.	86
Vitavox, Ltd.	55
Vortexion, Ltd.	109
V.Z. Electrical Service	140
Walmore Electronics Ltd.	70
Watts, Cecil E.	132
Wayne-Kerr Laboratories, Ltd., The	61
Webber, R. A., Ltd.	90
Webb's Radio	154
Westwood, L.	90
Weymouth Radio Mfg. Co., Ltd., The	64
Wharfedale Wireless Works	50
White, S. S., Co. of Gt. Britain, Ltd., The	48, 79
Wilkinson, L. (Croydon), Ltd.	126
Willesden Technical College	92
Wilson, Ronald & Co., Ltd.	140
Wright & Weaire, Ltd.	56
Wolsey Electronics, Ltd.	87
Young, C. H.	92
Z. & I. Aero Services, Ltd	148

Printed in Great Britain for the Publishers, ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1, by CORNWALL PRESS LTD., Paris Garden, London, S.E.1. *Wireless World* can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service, Ltd.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd., William Dawson & Sons (S.A.), Ltd. UNITED STATES: Eastern News Co., 306 West 11th Street, New York 14.

TCC FLUSH-BONDED PRINTED CIRCUITS

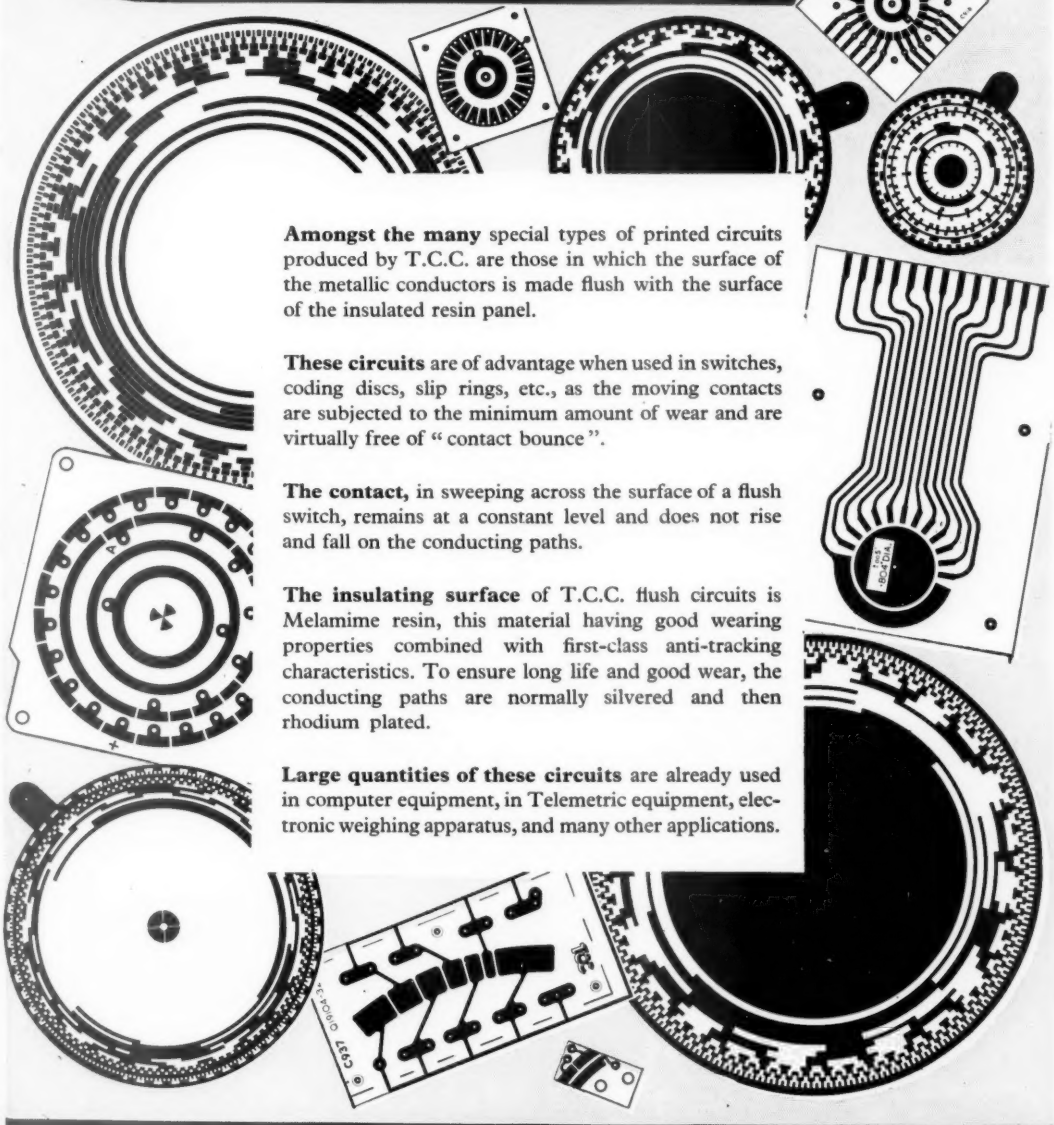

Amongst the many special types of printed circuits produced by T.C.C. are those in which the surface of the metallic conductors is made flush with the surface of the insulated resin panel.

These circuits are of advantage when used in switches, coding discs, slip rings, etc., as the moving contacts are subjected to the minimum amount of wear and are virtually free of "contact bounce".

The contact, in sweeping across the surface of a flush switch, remains at a constant level and does not rise and fall on the conducting paths.

The insulating surface of T.C.C. flush circuits is Melamime resin, this material having good wearing properties combined with first-class anti-tracking characteristics. To ensure long life and good wear, the conducting paths are normally silvered and then rhodium plated.

Large quantities of these circuits are already used in computer equipment, in Telemetric equipment, electronic weighing apparatus, and many other applications.

THE TELEGRAPH CONDENSER CO. LTD.
PRINTED CIRCUITS DIVISION · NORTH ACTON · LONDON · W.3 · ACOrn 0061

ERSIN

Multicore

5-CORE SOLDER

TYPE 1 ALLOY

CONTAINING TYPE 362 FLUX

REDUCES BIT WEAR AND *INCREASES* STRENGTH OF JOINTS

SAVBIT FOR FACTORIES

Savbit Type 1 Alloy is supplied to factories at bulk prices on 7 lb. reels. 16 and 18 s.w.g. are the diameters most suitable for the majority of soldering processes. Supplies are also available on 1 lb. reels in all gauges.

SAVBIT FOR THE SERVICE ENGINEER

Approx. 170 ft. of 18 s.w.g. SAVBIT is supplied on a 1 lb. reel individually packed in a carton and is available from trade stockists under reference R18SAV. Price 15/- (subject).

SAVBIT FOR THE SMALL USER

The popular Size 1 Carton is now supplied in 3 specifications: 53 ft. of 18 s.w.g., 30 ft. of 16 s.w.g. or 20 ft. of 14 s.w.g. 5/- each (subject).

Leading manufacturers of electronic equipment throughout the country find that by using Ersin Multicore Savbit Type 1 Alloy the cost of maintaining and replacing soldering iron bits is drastically cut. The inclusion of a small percentage of copper in Savbit Alloy prevents copper absorption by the solder alloy from the soldering bits — *increasing their useful life by up to 10 times.* At the same time, the presence of this extra copper increases the creep properties and strength of joints in all soldering processes.

More and more Electronics manufacturers are using Ersin Multicore SAVBIT Type 1 Alloy.

MULTICORE SOLDERS LIMITED, MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)

hroughout
re Savbit
soldering
a small
ts copper
ng bits —
ame time,
the creep
processes.

Alloy.

OR 3636)